
贝封记

April 1953 40 Cents

45c in Canada

TO TO THE STATE OF THE PARTY OF

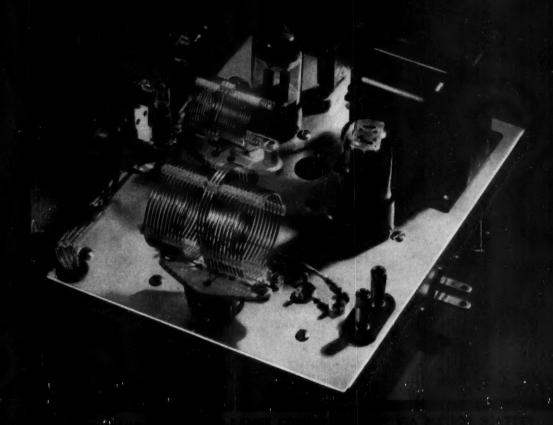

ULTRA COMPACT UNITS...OUNCER UNITS

HIGH FIDELITY SMALL SIZE FROM STOCK

UTC Ultra compact audio units are small and light in weight, ideally suited to remote amplifier and similar compact equipment. High fidelity is obtainable in all individual units, the frequency response being \pm 2 DB from 30 to 20,000 cycles.

True hum balancing coil structure combined with a high conductivity die cast outer case, effects good inductive shielding.





TYPE A CASE 11/2" x 11/2" x 2" high

UTC OUNCER components represent the acme in compact quality transformers. These units, which weigh one ounce, are fully impregnated and sealed in a drawn aluminum housing 7%" diameter...mounting opposite terminal board. High fidelity characteristics are provided, uniform from 40 to 15,000 cycles, except for 0-14, 0-15, and units carrying DC which are intended for voice frequencies from 150 to 4,000 cycles. Maximum level 0 DB.



CASE
%" Dia. x 11/6" high

Type He.	Application	Pri. Imp.	Sec. Imp.	List
0-1	Mike, pickup or line to 1 grid	50, 200/250 500/600	50,000	\$14.00
0-2	Mike, pickup or line to 2 grids	50, 200/250 500/600	50,000	14.00
0-3	Dynamic mike to 1 grid	7.5/30	50,000	_13.00
0-4	Single plate to 1 grid	15,000	60,000	11.0
0-5	Plate to grid, D.C. in Pri.	15,000	60,000	11.0
0-8	Single plate to 2 grids	15,000	95,000	13.0
0-7	Plate to 2 grids, D.C. in Pri.	15,000	95,000	13.0
0-8	Single plate to line	15,000	50, 200/250, 500/600	
0-9	Plate to line, D.C. in Pri.	15,000	50, 200/250, 500/600	
0-10	Push pull plates to line	30,000 ohms plate to plate	50, 200/250, 500/600	14.0
0-11	Crystal mike to line	50,000	50, 200/250, 500/600	14.0
0-12	Mixing and matching	50, 200/250	50, 200/250, 500/600	13.0
0-13	Reactor, 300 Hysno D.C.;	50 Hys 3 MA. D.C.,	6000 ohms	10.0
0-14	50:1 mike or line to grid	200	1/2 megohm	14.0
0-15	10:1 single plate to grid	15,000	1 megohm	14.0



Save space ...

• Increase rectifier life . . .

• Get top dollar value! G-E GERMANIUM DIODES

THINK OF THE SPACE SAVED when you use diode rectifiers approximately 1/4" long, 1/4" diameter! Think of that worry-free feeling that comes from knowing these tiny marvels can give you 10,000 hours and more of reliable service!

DIODES ARE SELF-HEALING when temporary overvoltage occurs. They stand up under shock and vibration. They have no filaments to heat, so power drain is less. You get no filament hum!

YOUR G-I TUBE DISTRIBUTOR is your best source for germanium diodes, for General Electric makes and markets more diodes than any other manufacturer. Huge G-E production by the most modern methods assures dependable performance-packs extra value into thrifty G-E prices.

CHECK THE LIST BELOW for popular G-E types. There are many more available. Then see your distributor for further information, including descriptive diode Bulletin ECG-3B. Or write Tube Department, General Electric Company, Schenectady 5, New York.





TYPE			INVERSE VOLTAGE		RECTIFIED CURRENT (IN MA)			
RTMA	Q-E	USE	PEAK	CONTINUOUS	OPERATING	PEAK	SURGE, 1 SEC.	MAX INV. AT -50 V
1N48	G5	General	85	70	50	150	400	.833
1N52	G5D	General	85	70	50	150	400	.15
1N63	G5E	General	125	100	50	150	400	.05
1N64	G5F	*Video Det.	20	-	0705-0110	7	-	.25 at-1.3 v
1N65	G5G	General	85	70	50	150	400	.20
1169	G5K	General	75	60	40	125	400	.85
1N70	G5L	General	125	100	30	90	350	.30
1N72	G7	**U-h-f	2	-	25	75	_	-
1N81	G5P	General	50	40	30	90	350	.01 at-10 v

other G-E "first"—Diffused-junction Germanium Rectifiers! Hermetically sealed against humidity and dust . . . extremely small and compact . . . with high output ratings, low leakage loss. Your G-E tube distributor has them!

	General	100	30	150	470	25 amp	-
1N92 4JA1A2		200	65	100	310	25 amp	-
1N93 4JA1A3	General	300	100	75	230	25 amp	-
1N94 4JA2A4	Line voit. rect	r 400	185	500	1570	25 amp	-


*Tested at 44 mc for rectifying efficiency.

**Tested at 500 mc as a low-noise mixer.

GENERAL



A MICHANICAL FILTER FOR YOUR 75A-2!

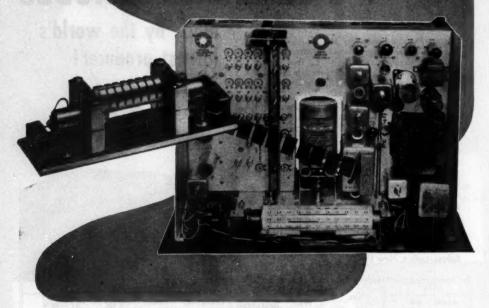

Your Collins distributor has a kit that will enable you to convert your 75A-2 into a 75A-2A.— the equivalent of our new 75A-3!! Or, if you prefer, your distributor will make arrangements for you to return your receiver to Collins. We will make minor repairs and completely realign your 75A-2 in addition to converting it into a 75A-2A.

The type number "75A-2A" indicates that the receiver was once a 75A-2 but has been converted and is now the same as the new 75A-3 — including mechanical filter!

Whether your 75A-2 is brand new or several

years old, it can share honors with the 75A-3 as the world's most advanced ham receiver.

Conversion kit, complete with a 3 kc plug-in mechanical filter and instructions
Net domestic price \$100.00

Factory modification, including minor repairs, complete realignment, and installation of a mechanical filter conversion kit complete with a 3 kc filter

Net domestic price \$125.00 Type F455B-08 — 800 cycle mechanical filter

plug-in unit
Net domestic price \$ 75.00

COLLINS EQUIPMENT IS A GOOD BUY — FOR THE PRESENT AND FOR THE FUTURE. SEE YOUR COLLINS DISTRIBUTOR TODAY.

For the best in amateur radio, it's . . .



COLLINS RADIO COMPANY, Cedar Rapids, Iowa

11 W. 42nd St., NEW YORK 36

1930 Hi-Line Drive, DALLAS 2

2700 W. Olive Ave., BURBANK



APRIL 1953

VOLUME XXXVII · NUMBER 4

PUBLISHED, MONTHLY, AS ITS OFFICIAL ORGAN, BY THE AMERICAN RADIO RELAY LEAGUE, INC., AT WEST HARTFORD, CONN., U. S. A.; OFFICIAL ORGAN OF THE INTERNATIONAL AMATEUR RADIO UNION

STAFF

Editorial

A. L. BUDLONG, WIBUD

Editor

HAROLD M. McKEAN, WICEG Managing Editor

GEORGE GRAMMER, WIDF

DONALD H. MIX, WITS BYRON GOODMAN, WIDX Assistant Technical Editors

EDWARD P. TILTON, WIHDQ V.H.F. Editor

C. VERNON CHAMBERS, WITEQ LEWIS G. McCOY, WITCP Technical Assistants

ROD NEWKIRK, WIVMW DX Editor

ELEANOR WILSON, WIQON YL Editor ANN B. FURR Production Assistant

WALTER E. BRADLEY, WIFWH Technical Information Service

Advertising
LORENTZ A. MORROW, WIVG
Advertising Manager
EDGAR D. COLLINS
Advertising Assistant
Circulation
DAVID H. HOUGHTON
Circulation Manager
HAROLD K. ISHAM, WIMFA
Assistant Circulation Manager

OFFICES

36 La Salle Road

West Hartford 7, Connecticut TEL.: 3-6268 TWX: HF 88

Subscription rate in United States and Possessions, \$4.00 per year, postpaid, \$4.25 in the Dominion of Canada, \$5.00 in all other countries. Single copies, 40 cents. Foreign remittance should be by international postal or express money order or bank draft negotiable in the U. S. and for an equivalent amount in U. S. funds.

equivaient amount in C. 8, funds.

Entered as second-class matter May 29, 1919, at the post office at Hartford.
Connecticut, under the continuation of the second special rate of postage provided for in section 1102. Act of October 3, 1917, authorized September 9, 1922. Authorized September 9, 1922 and 1916 in the formation of February 21, 1929, under the Act Convight 1953 by the American Park

Copyright 1953 by the American Radio Relay League, Inc. Title registered at 1. S. Patent Office. International copyright secured. All rights reserved. Quedian reservados 10d0s 10s derechos. Printed In U.S.A.

INDEXED BY INDUSTRIAL ARTS INDEX

INDUSTRIAL ARTS INDEA

-CONTENTS-

TECHNICAL—			
		d G. Villard, jr., W6QYT, llen M. Peterson, W6POH	
TVI Hints for the V.H.F.			
		dward P. Tilton, WIHDQ	10
Folded and Loaded Ante		liam B. Wrigley, W4UCW	2
Improving the Series No.	ise L	imiter H. O. Lorenzen, W3BLC	30
Design Notes on a Speci		The state of the s	3
Technical Topics — Diode Modulators		Byron Goodman, WIDX	39
		ARRL Lightning Calculator Donald H. Mix, WITS	
The Antenna Coupler He			
		John J. Glauber, W3GQD	4
Wide-Band Re-Entrant N			*
	Wil	burn D. Fingers, WK4ZY	48
Suitable Relays for the U	Iltim	atic Key	45
MOBILE-			
A Different Approach to	High	-Power Mobile	
	J.	Emmett Jennings, W6EI	28
NOVICE—			
A Sweep-Tube C.W. Rig	for 3	S and 7 Ma	
A Sweep-Tube C.W. Mig		ernon Chambers, WIJEQ	38
OPERATING-			
The 1953 Governors-to-F	resid	lent Relay	43
		akes	84
Simulated Emergency Te			
Diministra amongoney 10	-	George Hart, WINJM	62
Fourth 10-Meter WAS Co	ntes	Results	64
GENERAL-			
	Eme	rgency Service — Part II	88
Bules and Bemilations of	41-	•	0
Communications Depart	rtmer	at	74
"It Seems to Us"	9	In OST 28 Years Age	51
Our Cover	10	Silent Keys	6
Hamfest Calendar	10	United States Naval Reserve Military Affiliate Radio System	61
Coming ARRL Conventions	10	How's DX?	6
Quist Quiz		Hints & Kinks	7
Happenings of the Month	46	Correspondence from Members.	7
On the Air with Single Sideband	50	Operating News	
YL News and Views	52	With the AREC	71


QRK?*

ALWAYS TOPS WITH A hallicrafters

You'll have the best QRK 100 watts can give with Hallicrafters HT20 transmitter—and you'll *listen* to more and hear it better on a Hallicrafters receiver. You be the judge—you hear the difference!

It's value like this—and more of it dotlar-for-dollar in every price class that has made Hallicrafters equipment the unchallenged first choice of the world's most critical expert, the American amateur operator for 19 years.

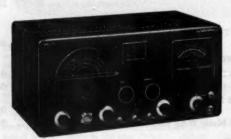Hallicrafters equipment is designed specifically for the ham operator—planned to meet his problems—planned to fit his pocketbook. The measure of Hallicrafters success is in the reputation this group of experts extends to this equipment. And that reputation is unchallenged in the field. You can hear the answer every night of the year on the air—just listen!



◆ Top Selectivity — Low Price I Model \$76 — Dual Conversion Super with 50 kc amplifier for tops in selectivity, 500 C.P.S. at 6 db down — 3.5 kc at 60 db down. Giant 4-in. "S" meter. 540-1580 kc, 1.72-32 Mc in 4 bands. 1 r-f, 2 conversion, 2 i-f stages. 5pos. selectivity. Phono input jack. 3 watt output. \$179.50

A Ham's Dream! Model \$X71—Com.

Rcvr. especially designed for top ham performance. Double conversion, built-in NBFM limiter stage. 538 kc to 35 Mc, 46-56 Mc in 5 bands. Temp. Comp., voltage reg. 1 r-f, 2 conversion, w i-f stages.

Xtal. filter, w-pos. selectivity, 18½" x 8½" x 12" deep. Ship. wt. 51 lbs. 115V,

A.C. 11 tubes reg. tact. \$224.50









Model S-40B-Covers Broadcast Band 540-1700 kc and three short-wave bands. 1.7-43 Mc. One r-f, two i-f stages. Electrical bandspread tuning. Switches for automatic noise limiter, code reception and three-position tone control. Code pitch control. Built-in PM speaker. 115 V, A.C. Only \$119.95

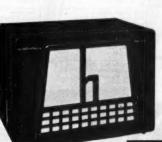TVI Suppressed 100 Watter—Model HT20 Here's the transmitter you've been waiting for! Continuous coverage from 1.7 Mc to 30 Mc. Full band switching, no more plugin coils; choice of 10 crystals. Shielded, filtered r-f compartments plus low-pass 52 ohm co-axial line output filter assures at least 90 db suppression of all harmonics above 40 Mc. Only \$449.50



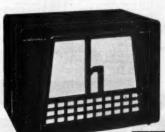Matched Speaker, Model R46-The perfect speaker for SW. Includes transformer of 500/600-ohm input. Voice coil impedance 3.2 ohms. 10" cone. Black finish. 15" x 101/8" x 101/8" deep. Only \$19.95



QRK-International "Q" Signal for-"What is my readability?"

hallicrafters

Chicago 24, Illinois

World's Leading Exclusive Manufacturer of Communications, High-Fidelity, Precision Radio and Television

Section Communications Managers of the ARRL Communications Department


Reports Invited. All amateurs, especially League members, are invited to report station activities on the first of each month (for preceding month) direct to the SCM, the administrative ARRL official elected by members in each Section. Radio Club reports are also desired by SCMs for inclusion in QST. All ARRL Field Organization appointments are now available to League members. These include ORS, OES, OPS, OO and OBS. Also, where vacancies exist SCMs desire applications for SEC, EC, RM, and PAM. In addition to estation and leadership appointments for Members, all amateurs in the United States and Canada are invited to join the Amateur Radio Emergency Corps (ask for Form 7).

		ATLANTIC DIVIS	ION	
Eastern Pennsylvania Maryland-Delaware-D. C. Southern New Jersey Western New York Western Pennsylvania	W3BXE W3EOK W2UCV W2SJV W3NCD	ATLANTIC DIVISI ARTHUR W. Plummer Lloyd L. Gainey Edward Graf R. M. Heck L. Lund H. F. Lund H. F. Lund C. McGuyer Reno W. Goetach DAKOTA DIVISIC Everett E. Hill	2219 Rhawn St. 3804 Rexmere Road Hoffman Ave. & Mariton Pike 81 King St. RFD 1	Philadelphia 15 Baltimore 18, Md, Merchantville Tonawanda Sharpaville
Illinois Indiana Wisconsin	W9KQL W9DGA W9RQM	H. F. Lund Clifford C. McGuyer Reno W. Goetsch	3135 S. 5th St. 1321 South Governor St. 929 S. 7th Ave.	Springfield Evansville 13 Wausau
North Dakota South Dakota Minnesota	WØVKP WØRRN WØMXC	I. W. Sikorski	1527 Fifth Ave., So. 1900 South Menlo Ave. 1611½ E. Lake St.	Fargo Sioux Falls Minneapolis 7
Arkansas Louisiana Mississippio Tennessee	W5LUX W5GHF W5JHS W4CXY/WLG	Charles M. Bove DELTA DIVISIO Fred Ward Robert E. Barr Norman B. Feehan Mark M. Bowelle GREAT LAKES DIVI Ivan C. Kelly Fabian T. McAllister John E. Skringer HUDSON DIVISIO Stephen. Neason	ON	Harrison Springhill Gulfport Oak Ridge
Kentucky Michigan Ohio	W4TUT W8HKT W8AJW	Ivan C. Kelly Fabian T. McAllister John E. Siringer	415 E. Mt. Vernon St. RFD 1, Box 368 2972 Clague Rd.	Somerset Bridgman Cleveland 16
Eastern New York N. V. C. & Long Island Northern New Jersey	W2ILI W2OBU W2VQR	Stephen J. Neason George V. Cooke Lloyd H. Manamon	794 River St. 88-31 239th St. 410½ Fifth Ave.	Troy Bellerose 26, L. I. Asbury Park
Iowa Kansas Missouri Nebraska	WØPP WØICV WØGBJ WØCBH	William G. Davia Earl N. Johnston Clarence L. Arundale Floyd B. Campbell	ON. 3rd St. 624 Roosevelt 1048 South Jefferson Ave. 203 W, 8th St. 1810N.	Mitchellville Topeka Springfield 4 North Platte
Connecticut Maine Eastern Massachusetts Western Massachusetts New Hampshire Rhode Island Vermont	WIHYF WIPTL WIALP WIJYH WIGMH WIJBB WIFPS	John E. Shringer John E. Shringer John E. Shringer John K. Sander John J. Sandel	RFD 4 Goodrich St. 91 Atlantic St. 67 West Allen Ridge Road 1426 Belmont St. 22 Annandale Road 2 Annandale Road VISION	Ridgefield Bingham North Quincy 71 Springfield Manchester Newport Brattleboro
Alaska Idahu Montana Oregon Washington	KL7NT W71WU W7KGJ W7BUS W7CZY	Edward G. Brown John M. Carroll Laurence Sebring	421 Yellowstone Ave. P. O. Box 706 Route 2, Box 384	Anchorage Boise Billings Pendleton Everett
Hawaii Nevada Santa Clara Valley East Bay San Francisco Sacramento Valley* San Joaquin Valley	WHORU WILL WOLZL WOJZ WOATO WOCKV WOFYM	John R. Sanders Ray T. Warner Roy I. Cousin Ray H. Cornell R. F. Cselkowits Willie van de Kamp E. Howard Hale ROANOKE DIVISI	c/o Mackay Radio & Telegraph	Honolulu Boulder City Los Gatos Albany 6 San Francisco 12 Chico Turlock
North Carolina South Carolina Virginia West Virginia		T. Hunter Wood H. Edgar Lindauer John T. Steele	1702 North Rhett Ave. Route 1, Box 431	Charlotte North Charleston Annandale Decota
Colorado* Utah Wyoming	W#CDX W7UTM W7JDB	Karl Brueggeman Floyd L. Hinshaw L. L. Daily	1945 Kearny St. 165 East 4th, North 1205 Lewis	Denver Bountiful Laramie
Alabama Eastern Florida Western Florida Georgia West Indies (Cuba-P.RV.I.) Canal Zone KZ5NM.	W4GJW W4FWZ W4MS W4ZD) KP4DJ	ROCKY MOUNTAIN D Karl Bruegeman Floyd L. Hinshaw L. Daily SOUTHEASTERN DIV Dr. Arthur W. Woods John W. Hollieter Edward J. Collins James P. Born, jr. William Werner	Day 171	Birmingham Jacksonville Pensacola Atlanta Urb. Truman, Rio Fiedras, P. R. Margarita, C. Z.
Los Angeles ^e Arizona San Diego Santa Barbara	W6YVJ W7LVR W6FJH W6IOX	Nelson W. Magner SOUTHWESTERN DIV Howard C. Bellman Albert Steinbrecher Edgar M. Cameron, jr. Vincent J. Haggerty	973 Mayo St. 973 Mayo St. Maple Road, RFD 5, Box 237 1430 So, Escondido Blvd. 1017 Indio Muerto St.	Los Angeles 42 1 ueson Escondido Santa Barbara
Northern Texas Oklahoma Southern Texas New Mexico*	W5GF W5GVV W5FJF W5BIW	William J. Gentry Jesse M. Langford Dr. Charles Fermaglich Dick Matthias	1509 Avenue Q 2005 W. Oklaboma Ct. 618 Medical Arts Bldg. P. O. Box 548	Lubbock Enid Houston 2 State College
Maritime	VEIDQ	A. M. Crowell	69 Dublin St.	Halifax, N. S.
Ontario	VEJIA	QUEBEC DIVISIO	0N	Burlington, Ont.
Quebec	VE2GL	Gordon A. Lynn	R.R. No. 1	Ste. Genevieve de Pierrefonds, P. Q.
Atberta British Columbia Yukon	VE6MJ VE7US	Sydney T. Jones Wilf Moorhouse	10706-57th Ave. 808 Victoria Rd.	Edmonton, Alta. Nanaimo, B. C.
Manitoba* Saskatchewan	VE4LC VE5HR	Leonard E. Cuff Harold R. Horn	DN 286 Rutland St 1044 King St.	St. James Saskatoon

Standard of Excellence



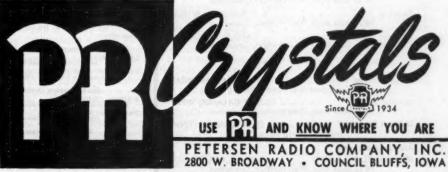20 METERS, Type Z-3, \$3.75 • 40, 80 AND 160 METERS, Type Z-2, \$2.75



EXPORT SALES ONLY: Royal National Company, Inc., 75 West Street, New York 6, N. Y., U. S. A.

THE AMERICAN RADIO RELAY LEAGUE, INC.,

is a noncommercial association of radio amateurs, bonded for the promotion of interest in amateur radio communication and experimentation, for the relaying of messages by radio, for the advancement of the radio art and of the public welfare, for the representation of the radio amateur in legislative matters, and for the maintenance of fraternalism and a high standard of conduct.

It is an incorporated association without capital stock, chartered under the laws of Connecticut. Its affairs are governed by a Board of Directors, elected every two years by the general membership. The officers are elected or appointed by the Directors. The League is noncommercial and no one commercially engaged in the manufacture, sale or rental of radio apparatus is eligible to membership on its board.

"Of, by and for the amateur," it numbers within its ranks practically every worth-while amateur in the nation and has a history of glorious achievement as the standard-bearer in amateur affairs.

Inquiries regarding membership are solicited. A bona fide interest in amateur radio is the only essential qualification; ownership of a transmitting station and knowledge of the code are not prerequisite, although full voting membership is granted only to licensed amateurs.

All general correspondence should be addressed to the administrative headquarters at West Hartford, Connecticut.



Past Presidents

HIRAM PERCY MAXIM, WIAW, 1914-1936 EUGENE C. WOODRUFF, W8CMP, 1936-1940 GEORGE W. BAILEY, W2KH, 1940-1952

Officers

President GOODWIN L DOSLAND, WØTSN Moorhead, Minn.

First Vice-President WAYLAND M. GROVES, W5NW

P.O. Box 586, Odessa, Texas
Vice-President FRANCIS E. HANDY, W18DI

38 La Salle Road, West Hartford, Connecticut

Secretary A. L. BUDLONG, W1BUD 38 La Saile Road, West Hartford, Connecticut

Treasurer DAVID H. HOUGHTON 38 La Salle Road, West Hartford, Connecticut

General Counsel PAUL M. SEGAL 816 Connecticut Ave., Washington 6, D.C.

Technical Director GEORGE GRAMMER, W1DF 38 La Salle Road, West Hartford, Connecticut

Technical Consultant PHILIP S. RAND, W1DBM Route 58, Redding Ridge, Conn.

Assistant Secretaries:

JOHN HUNTOON, WILVO JOHN E. CANN, WIRWS
38 La Salle Road, West Hartford, Connecticut

DIRECTORS

Canada

ALEX REID. VI2BE 240 Logan Ave., St. Lambert, P. Q. Vice-Director, William W. Butchart. VE8LQ 10740 107 St., Edmonton, Alta.

Atlantic Division

ALFRED C. HECK W3GEG 515 Cedar Ave., Sharon, Pa. Vice-Director: Charles O. Badgett. W3LVF 725 Garden Road, Glenside, Pa.

Central Division

WESLEY E. MARRINER. W9AND 844 N. Galena Ave., Dixon 7, Ili. Vice-Director: Harry M. Matthews. W9UQT Box 1195, Springfield, Ill.

Dakota Division

Delta Division

JAMES W. WATKINS. W4FLS 220 N. Howell Ave., Chattanooga, Tenn. Vtce-Director: George S. Acton. W5BMM Plain Dealing, La.

Great Lakes Division

JOHN H. BRABB 417 Ford Bidg., Detroit 26, Mich. V4cs-Dtrector: Harold E. Stricker 247 W. 5th St., Marysville, Ohio

Hudson Division

Midwest Division

WILLIAM J. SCHMIDT ... W#OZN 306 S. Vassar, Wichita, Kansas Vice-Director: James E. McKim ... W#MVG 1404 S. Tenth, Salina, Kansas

New England Division

PERCY C. NOBLE. WiBVR 37 Broad St., Westfield, Mass. WIALP Vtcs-Director: Frank L. Baker, jr. WIALP 91 Atlantie St. . North Quincy 71, Mass.

Northwestern Division

R. REX ROBERTS W7CPY 837 Park Hill Drive, Billings, Mont. Vice-Director: Karl W. Weingarten W7BG 3219 N. 24th St., Tacoma 7, Wash.

Pacific Division

KENNETH E. HUGHES. W6CI8 3105 Crest Haven Drive, Sacramento, Calif. Vtco-Director: Richard F. Czeikowits. . . W6ATO 243 Colon Ave., San Francisco 12, Calif.

Roanoke Division

P. LANIER ANDERSON, JR. W4MWH 428 Maple Lane, Danville, Va. Vice-Director: Gus M. Browning. W4BPD 135 Broughton St., S. E., Orangeburg, S. C.

Rocky Mountain Division

Southeastern Division

LAMAR HILL. W4BOL
104 Myrtie, Cochran, Ga.
W4ce-Director: Ernest W. Barr. W4GOR
911 Rosemary Ave., 5W, Atlants, Ga.

Southwestern Division

JOHN R. GRIGGS

3502 Chesapeake Ave., Les Angeles 16, Calif
Vico-Director: Walter R. Joos.
1315 N. Overhill Drive, Inglewood 3, Calif.

West Gulf Division

A. DAVID MIDDELTON

Ø Kay Road, Tijeras, N. M.

Vice-Director: Carl C. Drumeller. W5EHC
5824 N.W. 58th 88., Oklaboma City 12, Okla.



CONELRAD FOR AMATEURS

One of the problems of a nation tightening its defenses is radio security, which among other things includes insurance against the use of domestic radio stations as "homing" objectives to aid the navigation of enemy aircraft. Such stations are beacon lights pointing the way to the hearts of our industrial cities. A way must be found to extinguish these "lights," or otherwise render them useless, in

time of emergency.

The Communications Act of 1934, as amended, provides the President (in time of declared national emergency, as now) with broad authority to control or even close radio stations. By an Executive Order in December, 1951, the President delegated much of this power to the Federal Communications Commission, along with instructions to set up a security system for all civilian radio services. The term "Conelrad" was derived from the phrase, "control of electromagnetic radiations." Broadcast stations were the first on the list, and it has taken these many months to set up the measures now being put into effect. Briefly, in the event of an aircraft warning, all f.m. and TV stations would go off the air, and all a.m. stations would either do likewise or shift to one of two spot frequencies, 640 or 1240 kc., and operate in what is known as cluster patterns with precautions designed to thoroughly confuse any direction-finding equipment.

In their own way, amateur stations might be beacons, too. For that reason some reasonable procedure is needed to provide suitable warning for amateurs so that they may leave the air in the event of impending enemy attack. So, early in February another step in the implementation plan was taken with the holding, by FCC, of an informal engineering conference in Washington to discuss a Conelrad system for the amateur service. The discussion on this and related subjects occupied a full day, at the end of which it appeared a common viewpoint that such a warning procedure could best make use of the established system for broadcasters. One form it might take would be that before an amateur went on the air, he would check the local b.c. band. If stations were

operating normally, he would be free to proceed. But if the usual local stations were off the air, or were abserved to go off the air while ham operating was in progress, and all local b.c. entriers on 640 or 1240 kc., he would be alerted to stay of, or go off the air at the time the general Conelrad condition went in effect. A continuous clerck would be the obvious aim. Monitoring the broadcast band aurally is the simplest system, but there are more practical ones and several technical approaches suggest themselves. For example, an amateur might build himself an automatic device by tying a relay-operated indicator into the a.v.c. line of an a.c.-d.c. set, to show whether a local b.c. station were on the air. Gadgets of this nature have appeared in radio magazines off and on for a number of months now, and QST will undoubtedly carry similar data tailored to ham needs when the rules are made final and the actual requirements known.

It is expected that the Commission will now move toward issuing proposed rule-making for amendment of our regulations to require observance, and therefore we shall then have the opportunity to file comment if desirable. It is, at present at least, contemplated that FCC rules would not require any specific equipment or systems, but simply obligate the amateur to have some means of knowing of attack warnings or alerts when issued.

We should here underscore that what we have been talking about is a procedure strictly for the amateur service in the present condition of national emergency. Participants operating in the Radio Amateur Civil Emergency Service are subject to control by their radio officers, who separately will establish such silencing procedures as are found necessary

for security.

No one, FCC included, looks forward with any eagerness to the obligation which will be imposed on amateurs' operations. It is simply a necessary evil required for our common interest by the complexities of the world situation. We know that amateurs will tackle this new job with full understanding that it is in the public interest and that, as always, the thoroughness with which we do the job will further reflect credit upon the amateur service.

OUR COVER

Novice and old-timer alike will find much appeal in this completely-contained low-power crystal-controlled transmitter built by WIJEQ. Vern makes use of one of the new 6BL7 dual triodes developed for TV sweep circuits, resulting in a compact two-stage rig. Full constructional details appear in this issue starting on page 35.

Strays 3

What is believed to be the first transistor-totransistor communication by amateurs was held on February 13, 1953. The contact was between W2JEP and W2YTH at a distance of half a mile.

Two single-stage transistor transmitters were operated c.w. on 40 meters with a power input of 60 milliwatts. The signal reports were R5 and 88/9 and would probably have been readable much farther. The oscillator at W2YTH was crystal-stabilized and showed better frequency stability than the one used by W2JEP which had no crystal.

We believe that this contact is a "first" in amateur communications on any band and if this is disproved we limit the claim to the 40-meter band. Are there any challengers?

- W2JEP and W2YTH

W1FWH was disturbed by an implication contained in the description of W6WZD's "Tree-Top Beam" on page 46 of February QST. Walt assures us that anyone the least bit familiar with tree-ology knows that the array can't possibly grow up around it!

Roy D. Jordan, W2KUD, and Neal F. Harmon were recently honored by the presentation of the Charles A. Coffin Award, highest honor given by the General Electric Company to its employes. Mr. Jordan, advertising and sales promotion manager for the GE Commercial and Government Equipment Department at Syracuse, has had 25 years of continuous service with the company.

W2KUD is active in civil defense and emergency work, has held OPS, OBS, ORS and EC appointments, is a member of the Old Timers Club and was first licensed in 1923.



During a discussion of antennas, A makes the statement that "Any Twin-Lead feed line will radiate unless the standing-wave ratio is brought down to a very low value — something below 1.2 or so." B takes exception to this remark, claiming that the s.w.r. has very little to do with the radiation from a line of this type. Who is right?

(Please term to page 140 for the answer)

HAMFEST CALENDAR

ARKANSAS — Saturday and Sunday, April 11th and 12th, at the Creecent Hotel, Eureka Springs — a non-profit hamfest. On the agends for Saturday are a buffer supper, hayride, square and round dancing, and a midnight weiner roast. A banquet will be held at noon on Sunday. The fee of \$3.75 per person covers the above-listed activities, plus room and board with the exception of Sunday breakfast. Write WSMED for further information.

KANSAS—Sunday, April 12th, at the City Building, Coldwater—the Coldwater Amateur Radio Club will sponsor its bamfest. Those who attended last year's hamfest will be pleased to know that another auction will be held. Registration to be handled at the door. WθDOZ, president of the club will answer inouries.

KANSAS — Sunday, May 3rd, at the American Legion Hall, Satanta — the Fourth Annual Hamfest of the Hi Plains Amateur Radio Club will be held. This will be an all-day meeting with entertainment for all, including the XYLs and children. Everyone is requested to bring a covered dish contribution for the luncheon at noon. For further information, write to W#GID.

NEW JERSEY — Saturday, April 25th, in the Grand Ball Room of the Hotel Stacy-Trent, Trenton — the Ninth Annual Old Timers' Nite Round-up and Banquet will be held, sponsored by the Delaware Valley Radio Association, to honor the early living pioneers of wireless and to remissee on their experiences of yesteryear. Turkey dinner will be served promptly at 6:30, after which the program will include personalities prominent in early wireless history. Bring along your oldest amateur and commercial tickets, as awards will be made to those holding the earliest dated licenses. A special award will go to the "Grand OM" whose radio operating experiences can be traced back to the earliest days of wireless. W2Z1's famous collection of old-time gear will be on display. Tickets are by reservation only, and may be obtained prior to April 21st from General Chairman Ed Raser, W2ZI, 315 Beechwood Ave., Trenton 8, at \$5.00 per person. Late comers without tickets will pay \$6.00 at the door. Guesta are welcome, regardless of age or amateur experience. As in the past, the party will be stag.

NEW YORK — Saturday, April 25th, at the Elks Club, Rochester — the Rochester Amateur Radio Association will hold a Western New York Hamfest. The afternoon program will consist of a number of technical and group seasions, with exhibits and amusements of various types. Following the dinner at 6:30 p.m. the evening program will feature speakers. Special plans have been made for the XYLs, with several sessions of particular interest to them. Registration begins at 2:00 p.m., with tickets selling for \$3.75.

PENNSYLVANIA — Saturday, April 18th, at the Stock Yards Inn, Lancaster — the Annual Banquet of the Lancaster Radio Transmitting Society. Festivities will begin at 6:30 r.m., and entertainment has been planned for OMs, YLs and XYLs. Registrations are in advance, \$2.50 per person, and may be obtained through A. C. Jacoby, W3OY, 589 N. Plum St., Lancaster.

WISCONSIN—Saturday, April 18th, at the Youth Building, Wausau—Annual Hamfest and Banquet of the Wisconsin Valley Radio Association. Scheduled for the afternoon is a meeting of the Wisconsin Council of Radio Clubs delegates at 1 r.m., followed by a Section meeting of appointees and net members at 3 r.m. Beginning at 6 r.m. a well-rounded program has been arranged featuring an excellent banquet, entertainment and hamfesting galore. Transmitters on 3950 and 29,620 kc. will be on the lookout for incoming mobiles. Please make reservations in advance to assist with meal plans. Tickets available for \$3.00 from Lawrence Lapinske, WOEWM, P. O. Box 179, Wausau.

COMING A.R.R.L. CONVENTIONS

June 20th-21st — Rocky Mountain Division, Estes Park, Colo. July 10th-12th — National Convention, Houston, Texas

Meteor Scatter

A Newly-Discovered Means for Extended-Range Communication in the 15- and 20-Meter Bands

BY OSWALD G. VILLARD, JR., * W6QYT, AND ALLEN M. PETERSON, ** W6POH

• Although you might not suspect it, in view of this past winter's experience, the 14-Mc. band is never completely "dead." This article describes a newly-discovered type of propagation that is always present, for which the optimum communication distance is of the order of 800 miles. It has gone undetected for many years because it is usually masked by other forms of propagation and requires first-rate equipment for its exploitation — equipment which, however, is not at all unusual.

Want to keep a schedule with someone seven or eight hundred miles away after the 20-meter band has "gone dead" at night? Thanks to a recent discovery in which amateurs have played a part, it is now possible to do this without shifting down to a lower frequency and battling the usual QRM. By taking advantage of a new type of radio propagation known as "meteor scatter," two stations can communicate far beyond ground-wave range all night long and have the band essentially to themselves.

Furthermore, QSOs can be carried on by this means all day long too, even though the station at the other end is well inside the skip zone at all times. And best of all, here is one type of reasonably long-distance radio transmission which promises not to be subject to fadeouts, ionospheric storms, and all the other uncertainties which plague the regular ionospheric layers.

* Trustee, W6YX; Dept. of Electrical Engineering, Stan-

ford University, Stanford, Calif.


** Radio Propagation Laboratory, Stanford University,
Stanford, Calif.

Schedules using this type of propagation should be 100 per cent successful.

The catch? Yes, there is one, for new types of propagation such as this don't keep themselves hidden all these years without good reason. The disadvantage is that at amateur power levels, it is necessary to be content with a fairly weak signal, and one which fades fairly rapidly between very wide limits. The signal is on the average too weak for satisfactory telephony, but is adequate for c.w. It makes occasional brief dips into the noise, but promptly comes back again. It will often rise twenty or thirty decibels above the noise, for as much as five or ten seconds at a time. The astonishing part of the matter is that the signal - at least some signal is there substantially all of the time, even when the band, by every normal criterion, should be completely dead!

What does one need to take advantage of this form of transmission? Nothing more than an efficient station, and some knowledge of what to expect. Briefly, the explanation of the signal—at least in the vicinity of 20 meters—is forward scattering from ionization trails left behind by the myriads of tiny meteors which pepper the E region of the ionosphere at all times. Hence the maximum range for this form of transmission is essentially that for normal one-hop E-layer transmission, or 1500 miles. For reasons which will be brought out later, a good transmission distance in practice is about half this value, or around 800 miles.

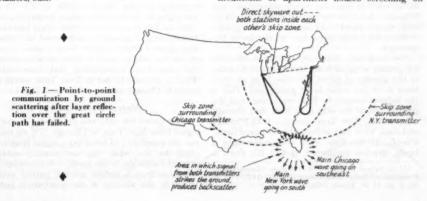In view of the low height of the E region—roughly 70 miles—the vertical angle of take-off even for the shorter distance is quite low—of the order of 5 or 6 degrees. Thus a good site is a requirement: one which does not have nearby mountains or apartment houses screening off





Visible meteors during a shower: a two-second exposure during the great Draconid display of October, 1946. Lines drawn through individual meteor trails (inside circles) intersect at a common point known as the shower radiant. Thousands of meteors too small to be seen — but producing radio reflections — strike the E region of the ionosphere at all times.

low-angle radiation in the desired direction of communication. An antenna well up in the air, a sensitive receiver, and a location reasonably free of man-made QRN are also important. If this sounds formidable, remember that these are no more than the requirements for reasonably good DX results. A "full gallon" is not essential—two or three hundred watts will do, although the more the merrier. It follows that many thousands of operators throughout the country should be able to take advantage of this new type of extended-range transmission.

Ground-Scatter Transmission

How does this type differ from those to which we are already accustomed? The story, briefly, is as follows. Consider two cities, say New York and Chicago, spaced roughly 800 miles apart. (Any other two cities, spaced the same distance, would do equally well.) Until fairly recently, it was thought that communication between these two communities at frequencies below 30 megacycles could only be conducted when the "regular" layers — F, E and sporadic-E — were sufficiently ionized to reflect a signal from one city to another. The distance involved is much too great for ground- or space-wave communication, and it is also too great for the extension of groundwave range caused by tropospheric bending, even if that effect were important at the lower fre-

Not long ago, however, another mechanism for getting a signal from New York to Chicago in the absence of direct reflection from an overhead layer has come to be understood. This is the indirect bounce by back-scattering from the ground. When the skip is so long that Chicago cannot hear New York directly, both Chicago and New York may still be able to hear Miami, Florida. If the New York transmitter uses a beam directed southward, it will lay down a

strong signal all over the state of Florida and the Atlantic Ocean on one side, and the Gulf of Mexico on the other. A small but detectable part of this signal will be scattered in all directions by water waves in the Gulf and the Atlantic, by houses and trees on the land, and so forth. If the Chicago station also uses a beam directed at Florida, it will be able to pick up scattered components of the signal originating in New York, and the two stations will be able to communicate via Florida, as in Fig. 1. The indirect signal will be much weaker than a direct bounce over the great circle path, and will have a hollow, fluttery sound not unlike that of a DX station, but it will be well above the noise level and perfectly readable for both voice and code. (See description on page 74 of the 1953 ARRL Handbook.)

This type of scattering has been observed quite regularly by amateurs interested in 50-megacycle DX, and has been given a variety of names including "rebound scattering" and "reflected skip." The authors, who prefer to call it "ground scattering" since this seems to be the more descriptive term, have shown some photographs illustrating it in their article on scatter-sounding in the March, 1952, QST. Those photographs show scatter echoes received at the same spot from which the initial signal had been transmitted; it should be understood, of course, that ground scatter echoes from a given transmitter can also be heard at other locations inside the skip zone surrounding that transmitter. Thus a scatter-sounder in New York would be

heard in Chicago under conditions of Fig. 1. Meteor Reflections

Now about the only remaining way to get a signal from New York to Chicago — if we leave out the possibility of bouncing a signal from one place to the other via exceptionally strong auroral ionization to the north — is by means of reflection from a meteor column formed somewhere in the vicinity of the great-circle path.

¹ O. G. Villard, jr., and A. M. Peterson, "Instantaneous Prediction of Radio Transmission Paths," QST, Vol. 36, No. 3, pp. 11-20, March, 1952.

It has been thought until recently that these meteor reflections were always of short duration, and of no practical value for communication except perhaps during an exceptionally strong meteor shower such as the great one of October, 1946. This impression has stemmed from the fact that most observations of meteors have been conducted with transmitter and receiver at one location, which is clearly the most convenient experimental arrangement. Under these conditions relatively isolated reflections, or signal bursts, are obtained.

Recent advances in understanding the nature of these reflections, however, have led to some interesting conclusions.² It is now known that there are in general two types of meteor echoes. About 10 per cent of the total detected under ordinary conditions have very long durations (ten seconds to ten minutes), strong fading fluctuations, and an irregular and unpredictable "life history." Their behavior is not yet well understood. The other 90 per cent of the echoes

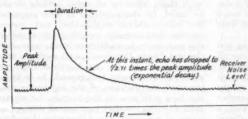


Fig. 2 — "Life history" of the most commonly-encountered type of radio echo from a meteor trail. Shape is the same for either backward or forward reflection (see Fig. 3)

have a surprisingly regular behavior, being characterized by a rapid rise to peak amplitude, followed by a decay of exponential form as shown in Fig. 2. Since the decay is exponential, it is convenient to define duration as the time interval between the peak and the time at which the echo strength has dropped to roughly one-third the peak strength. Thus this "duration" is analogous to the time constant of a condenser discharging through a resistor.

Now it turns out that the height of the peak can be predicted quite accurately for this type of echo, and varies inversely as the three-halves power of frequency, assuming all other factors to be held constant. Thus, an echo having a peak of unit strength at 14 megacycles will be less than one-third as strong at 28 megacycles. Furthermore, the duration of this type of echo has been found to vary inversely as the frequency squared. Thus if an echo lasts for one second

² Von R. Eshleman, "The Mechanism of Radio Reflections from Meteoric Ionization," Technical Report

nections from Meteoric Ionization," Technical Report No. 49, Electronica Research Laboratory, Stanford University, Stanford, Calif., July 15, 1952.

³ L. A. Manning, O. G. Villard, ir., and A. M. Peterson, 'Radio Doppler Investigation of Meteoric Heights and Velocities," Journal of Applied Physics, Vol. 20, No. 5, pp. 475–479, May, 1949.

⁴ O. G. Villard, ir., "Meteor Detection by Amateur Radio," QST, Vol. 31, No. 7, pp. 13–18, July, 1947.

at 14 megacycles, the same echo would last only one-fourth of a second at 28 megacycles.

Lastly - and here is the payoff - it has been discovered that the duration of a meteor echo at any given frequency, increases very rapidly when transmitter and receiver are separated by several hundred miles. This increase factor is proportional to the square of the secant of the forward-scattering angle 2\$\phi\$ in Fig. 3. It works out that for a transmitter-to-receiver distance of 800 miles, the remote reflection produced by a meteor column formed over the midpoint of the path will have a duration more than twenty times that which it would have if the receiver were adjacent to the transmitter.

Thus, by going to a relatively low frequency, such as 14 megacycles, we get stronger echoes, and ones which have longer duration. Then, by changing from a backward to a forward path, we get another increase in echo duration - and quite a large one at that.

For some years, back-reflection experiments have shown that a truly astonishing number of meteor echoes can be received even with relatively low-power equipment. Measurements at Stanford University 3 using equipment and power levels substantially equivalent to that employed in a 1947 amateur experiment 4 have shown that at a frequency of 23.1 megacycles, during the early morning hours, several thousand meteor reflections per hour can be detected. This is at a rate of nearly one per second. The average duration of each echo at this frequency may be taken (conservatively) to be one-quarter of a second. This implies that on the average, meteor echoes are

present for nearly one-quarter of the total time. If now the frequency is lowered to 14 megacycles, and an 800-mile forward bounce is considered, the average duration of the meteor reflections is multiplied by a factor of roughly 50 times! Thus, if one echo occurs each second, and each echo lasts on the average twelve seconds, there will clearly be more than enough meteors present to guarantee a continuous signal by meteor reflections alone.

This picture is, of course, greatly oversimplified, although it does represent a fair approximation. For example, the area of the sky from which meteor echoes are obtained for overhead reflection is not the same as it is for distant reflection. However, when all the details are worked out, to the best of present knowledge, there

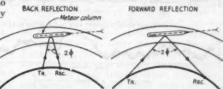



Fig. 3 — Illustrating backward and forward reflection (or "scattering") from a meteor trail.

will be at 14 megacycles enough meteor reflections on the average at all times of the day and year to guarantee a continuous signal between two amateur stations separated by 800 miles and having moderate transmitter powers, good locations, and simple beam antennas.

Accidental Discovery

This effect was turned up accidentally by the authors during the course of the W6YX scatter-sounding experiment, which consisted of a demonstration that when echoes from a particular area appear on the scatter-sounder, strong signals can actually be heard from amateur stations located in that area. The converse, of course, was also investigated at the same time. In other words, the authors were just as eager to be able to show that when no echoes appeared from a given area, amateur signals could not be received from that area, either. This proved to be a tricky proposition, as was pointed out, because as long as any echoes appear anywhere on the indicator, it is always possible for a sta-tion in a supposedly "dead" region to be heard weakly by ground scattering via the area from which the echoes are coming.

It was decided that the most convincing test would be to wait until late on a night after all F, E, and sporadic-E activity had disappeared, and the indicator showed no echoes at all. Such nights are actually few and far between on the West Coast during the months of November and December. When one was at last found, a phone call was put through to Rod Beaudette, W7FXI, at Spokane, Washington, about 750 miles airline from Palo Alto. Rod, a Stanford graduate who had participated in the early meteor experiments at W6YX, has 500 watts on the air feeding a 3-element beam perched 30 feet above the roof of his house in suburban Spokane. At his location the ground slopes off toward the south (the direction to Palo Alto), and there are no intervening mountains to block off the horizon. Aside from this, Rod's location might be termed average, having the usual number of impedimenta in the form of light lines, neighboring houses, etc. W6YX's location (at least for the north and south directions) is better than average; the station is located atop a small hill one or two hundred feet above the

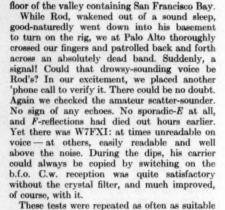

conditions could be found, with similar results on each occasion. The signal was definitely always there, when by all rights nothing should be heard. Its characteristics at once suggested the meteor-scatter explanation, and instantaneous field-intensity recordings strengthened this impression. In addition to bursts, nose whistles and "body Dopplers" could easily be seen superimposed on the continually-fading, but almost-always-present background. As is to be expected, the duration of the big bursts over this long path was, on the average, far greater than anything we had experienced during the course of local tests. Fig. 4 illustrates this effect by showing the comparison between a recording of backward-reflected meteor echoes obtained

determination of individual echo durations but the increased average duration is clear.

Other Paths

locally, and a similar recording of forward-re-

flected meteor echoes over a 750-mile path. Echo

overlapping in the latter case prevents accurate

In the thought that there might be something magic about the path to Spokane, similar tests were carried out with W7PZ in Tucson, Arizona - about 750 miles away in a southeasterly direction. Ben has a three-element beam, about 300 watts, and a location outside Tucson on flat land not far from the airport. His signals

were heard just as consistently as

W7FXI's in Palo Alto.

In addition, W6HJT in San Marino only 300 miles away and nearly south from Palo Alto - also put in a very strong signal with a steady background underlying the meteor bursts.

Attempts to increase the frequency or the distance met with less success, however. Transmissions to and from Tucson on 10 meters resulted in a signal audible only during well separated bursts, with no sign of a background between.

On one occasion, WØPRZ in Aberdeen, South Dakota, was asked to listen for the 20-meter W6YX signal. His dis-

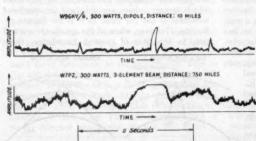


Fig. 4. — Forward and back-reflected meteor ecnoes at a range-cycles. When these records were made (late at night), no layer propagation of any kind could be shown to be present.

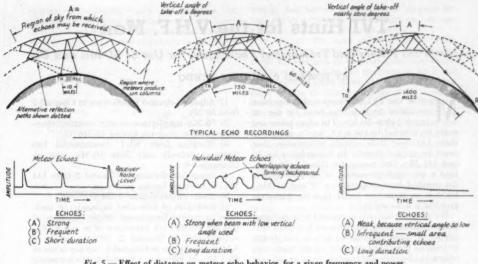


Fig. 5 - Effect of distance on meteor echo behavior, for a given frequency and power.

tance is near the maximum for one-hop E-layer reflection: about 1400 miles. During the course of a 15-minute transmission, only one or two distinct bursts were heard. His antenna, location and equipment are top-flight, as his DX record shows, so the conclusion seems to be that at extreme range the number of meteors which can produce a signal over the path (they have to be just about exactly over the midpoint) becomes so small that a continuous background is not supported. Also, the angle of take-off becomes so low (down around one degree) that antennas of practicable height are quite inefficient. The effect of varying transmitter-receiver distance, with frequency and power constant, is shown in Fig. 5.

Relationship to 50-Mc. Scattering

The theoretical investigations which followed these ham experiments confirm the expectation that meteors alone can support the entire signal.5,6 However, the possibility that other factors may be involved can by no means be ruled out. There has recently been published an account of another new form of propagation, in many respects resembling that discussed in this article, which is effective at frequencies of the order of 50 megacycles and at very high power levels.7 It is suggested that this propagation may be explained as forward-scattering from irregularities such as might be caused by turbulence in the E region of the ionosphere. Meteors are cited as playing an important part. The observed signal, however, has certain characteristics for which meteors would almost certainly not be responsible.

These characteristics, unhappily, are not easy to study at 15 megacycles. It is not yet known to what extent, if any, the 15- and 50megacycle signals are caused by the same agency. The situation as of December, 1952, may be summarized in the following way. At the lower frequency, theory indicates that meteors alone should easily account for the observed signal. Nothing in the experimental evidence thus far disagrees with this conclusion. At 50 megacycles, however, the theory - based on present knowledge of meteor echo behavior predicts that they alone will not be sufficient to account for what is observed. It appears that other factors must be sought.

The unscrambling of the several factors which may contribute to the signal observed at the two frequencies will be an exciting and challenging job. One of the first tasks will be to gain as much experience with these new types of propagation as possible. Here the amateurs, with their wide geographical distribution, and their willingness to experiment at all hours of the day and night, are in a position to make a real contribution. It is obvious that any means for making the 20-meter band work around the clock (at least for 800-mile QSOs!) is going to be important as crowding on the lower frequencies increases. Furthermore, the invulnerability of meteors to ionospheric storms is another important point: a weak, but really reliable circuit may, during emergencies, be worth much more than one which could fade out at the crucial moment.

(Continued on page 124)

⁵ O. G. Villard, jr., A. M. Peterson, et al., "Extended-Range Radio Transmission by Oblique Reflection from Meteoric Ionization," Journal of Geophysical Research, March, 1953 (in press).

⁶ Von R. Eshleman and L. A. Manning, "Radio Com munication by Scattering from Meteoric Ionization," Technical Report No. 57, Electronics Research Laboratory, Stanford University, Stanford, Calif., December 1, 1952.

⁷ D. K. Bailey, et al., "A New Kind of Radio Propaga-tion at Very High Frequencies Observable over Long Distances," *Physical Review*, Vol. 86, pp. 141-145, April 15, 1952.

TVI Hints for the V.H.F. Man

Low-Pass Filters and Transmitter Techniques for Use at 50 Mc. and Up

BY EDWARD P. TILTON.* WIHDO

Most of the TVI information that has been published to date has been for use on bands below 50 Mc. The ideas presented could be adapted to the v.h.f. man's needs, but there has been little specific information that could be applied directly to transmitters for 50 and 144 Mc. One reason for this is, of course, that a very high percentage of all TVI to date has resulted from operation on 28 and 14 Mc., for it is on these two bands that the harmonic problem is most severe.

We've been primarily concerned with reducing the amount of energy radiated on low-order harmonics of these frequencies, too, so the design techniques have been directed toward harmonics falling in Channels 2 through 6. Even in the case of 28-Mc. operation, the lowest harmonic that could cause trouble in the high channels is the seventh, so shielding and filtering methods that cut out the more troublesome low-band harmonics are almost always effective in the high band, too. With v.h.f. operation, however, the problems may be quite different. The 50-Me. operator has a 4th-harmonic possibility in Channels 11, 12 or 13, and tripler stages multiplying to 144 Mc. can create quite a rumpus in Channels 9 and 10. Though the amount of TVI thus far resulting from use of the v.h.f. bands is relatively small, there is certain to be more before long as more TV stations begin using the high-band assignments. U.h.f. TV now bursting forth on a commercial scale cannot be expected to make life any easier for the v.h.f. operator.

Sources of V.H.F. TVI

Just as with our lower bands, before we can do anything about reducing v.h.f.-caused TVI we must be sure of the nature of the problem. Unless we know what is causing the interference we will be very lucky if we happen onto a solution. Experience has shown that the principal sources of TVI from v.h.f. rigs are as follows:

* V.H.F. Editor, QST.

 Adjacent-channel interference in Channel 2 from 50 Mc.

 50-Mc. interference on any occupied channel in certain receivers having 45-Mc. i.f.

 Blocking from v.h.f. fundamental frequency, normally only from 50-Mc., and on Channels 2-6.

 Image interference in Channel 2 from 144 Mc., in receivers having 45-Mc. i.f.

5) Audio effects similar to BCI.

6) Radiation of unwanted harmonics of oscillator or exciter frequencies. Some examples of this are 9th and 7th harmonics of 6- and 8-Mc., respectively, in Channel 2, 10th harmonic of 8.4-Mc. oscillators in Channel 6, 3rd harmonic of 25-Mc. or higher in Channel 3, 7th harmonic of 25-Mc. stages in Channel 7, and 4th harmonic of 48-Mc. triplers in Channels 9 or 10. These are just examples; there may be other combinations.

7) 4th harmonic of 50-Mc. operating frequency, in Channels 11, 12 or 13.

8) Various harmonies of 50 or 144 Mc. falling in the u.h.f. range, Channels 14 through 83.

The first five categories are receiver faults. Nothing can be done at the transmitter to correct the first four items, other than to reduce power or increase the separation between the transmitting and TV receiving antennas. Corrective measures that can be applied to the receiver will be discussed later; what we are concerned with for the present is the transmitter, and steps we can take to reduce its TVI potentiality. Item 5 is a receiver condition, too, but it can be eliminated at the transmitter end by avoiding the use of amplitude modulation. Frequency modulation or c.w. will do the trick ordinarily.

The radiation of unwanted harmonics of exciter frequencies (Item 6) is a common cause of TVI, particularly where the transmitter is operated in close proximity to TV receivers. In an open layout there is little that can be done to correct this, so the first step is thorough shielding, if the exciter frequencies cannot be shifted to avoid



A low-pass filter for use with a high-powered 50-Mc. transmitter. Though variable condensers are used, they are not adjusted in normal operation, and shafts should be anchored in place with lacquer to prevent their being moved accidentally.

having harmonics in locally-used channels. An example of the latter approach is the avoidance of 8-Mc. crystals in 50-Mc. work where Channel 6 is used. Crystal or other oscillators in the 8-Mc. range may produce sufficient 10th harmonic to

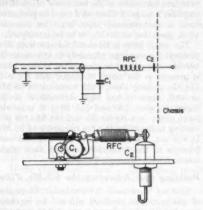


Fig. 1 -- Filter method for suppressing high-band harmonics that might otherwise be radiated from power cabling. A typical physical arrangement is shown in the sketch.

C₁ — 0.001-µfd. miniature disk ceramic. C₂ — 0.001-µfd. feed-through by-pass (Erie Style 326). (For 500-2000-volt lead, substitute Plasticon Glass mike, LSG — 251, for C₁ and C₂.)

14 inches No. 26 enamel close-wound on 3/16-

inch diam. form or resistor.

interfere in Channel 6, but shifting to a 6-Mc. oscillator moves the harmonics to other channels that may not be used locally.

Often the interfering harmonics will be passed on through succeeding stages, particularly with the capacity-coupled circuits so often used in frequency multipliers, so shielding alone may not effect a cure. But just as with other forms of harmonic trouble, shielding is the first step in a corrective program. You have to have it before other measures will work.

The More Stubborn Cases

What to do from here on depends on the severity of the problem. If your harmonic TVI (either from exciter stages or the final operating frequency) is just a matter of faint cross-hatching, it is quite possible that shielding the rig and installing an antenna coupler fed with coaxial line may clear it up, as these simple steps are capable of holding down radiation of the harmonic by the antenna system to quite low levels.

If these measures make little or no change in the intensity of the interference, filtering of the power cables is next in order. As simple a matter as by-passing power leads where they are brought out of the transmitter enclosure may help, though use of shielded wire for interior power

wiring, and the addition of small ceramic bypasses where the leads are brought out, as suggested by Grammer,2 is much better.

In all but the more difficult cases, trouble will have been corrected by now, and in any event the strength of the harmonic interference will have been reduced to the point where it will be possible to track down the source. The simplest way to do this is to have a TV receiver running in close proximity to the transmitter, and use it as a visual indication of the effectiveness of suppression measures. A probing lead can be clipped to the TV antenna lead (no electrical connection; just the capacity coupling will suffice) to check for harmonic leaks in the transmitter and its associated cabling. Couple the transmitter to a lamp or other dummy load and see if harmonic energy is present in the antenna line. If the power cabling shows appreciable harmonic energy, more effective filtering of the individual leads will be required.

The use of shielded wire and ceramic by-passes will take care of most low-band harmonic radiation from power leads, but where Channels 7 through 13 are involved, something better may be needed. The exciter and amplifier described by the writer in QST for September and December serve as a good example. This combination was substantially free of harmonic TVI in the low channels, but when it was operated on 50 Mc. in the presence of a weak signal on Channel 11 it wiped the picture completely out with its fourth harmonic. Furthermore, it did it with only the exciter running.

The probe test showed that the power cable was hot with 200-Mc. energy, so the filter circuit of Fig. 1 was installed in each power lead. Even the smallest by-pass condensers of conventional construction have sufficient lead inductance to make them relatively ineffective at 200 Mc., so feed-through capacitors were used at C_2 . Then small v.h.f. chokes were inserted in series with the leads, and the ceramic by-passes left as they were originally, connected as shown in Fig. 1 and the photograph on page 17 of April, 1951, QST. These methods are not applicable to leads carrying more than about 400 volts, so we had to settle for something a bit less effective on the feedthrough terminal for the 4-250A plate voltage. Here a high-voltage by-pass of the most compact construction we could find was mounted as close as possible to the feed-through bushing, and the connection made to it with copper strap to hold down lead inductance. There was still a faint trace of harmonic left on the terminal and cable, but it did not interfere seriously except when the probe was held near the lead or terminal. These Channel 11 tests were made with a very snowy signal, with the 50-Mc. transmitter only six feet away from the receiver, running inputs up to 750 watts.

Shielding requirements were more stringent for the 200-Mc. harmonic than for lower frequencies. The covers on both units had to be screwed down tightly all the way around, as the slightest crack leaked enough 200-Mc. r.f. to

Antenna couplers for 50 and 144 Mc. were described in QST for October, 1952, p. 58, and January, 1952, p. 50.
 Grammer, "By-Passing for Harmonic Reduction," QST, April, 1951, p. 17.

cause trouble. A hole in the side of the chassis for the ventilating fan, a source of no troublesome harmonic radiation at 54 to 86 Mc., had to be covered with screening to contain the 200-Mc. harmonic.

Low-Pass Filters for 50 and 144 Mc.

Having gotten the level of the harmonic radiation on Channels 2 through 13 down to the point where very little could be found other than in the transmitter output load, we were ready to go to work on low-pass filters designed especially for the v.h.f. man. The filters shown in the photographs were designed according to information presented about two years ago in QST.3 They

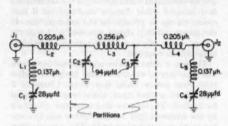


Fig. 2—Schematic diagram of the 50- and 144-Mc. filters. No partitions are built into the 144-Mc. unit. Values on the drawing are for the 50-Mc. filter.

C1, C4 - 50 Mc.: 50-µµfd. variable, shaft-mounted, set to middle of tuning range (Johnson 50L15). 144 Mc.: 11-µµfd. fixed ceramic (10-µµfd. use-

able) 50 Mc.: 100-μμfd. variable, shaft-mounted, set with rotor ¾ inch out of stator (Bud MC-905). C2, C3 -

144 Mc.: 38-μμfd. stand-off by-pass (Erie Style

721A). 50-Mc. coil data:

-- 3½ turns ½ inch long. Top leads ¾ inch, bottom leads ¼ inch long.
-- 4½ turns ¾ inch long. Leads ½ inch long L1, L5

each end, -5½ turns ½ inch long. Leads 1 inch long each. All 50-Mc. coils No. 12 tinned, ½-inch diam., coil length measured between right-angle bends where leads begin.

144-Mc. coil data:

L1, L5 - 3 turns 1/4 inch long. Leads 1/4 inch long each end.

-2 turns 1/8 inch long. Leads 1 inch long each end.

5 turns ¼ inch long. Leads ¼ inch long each end. All 144-Mc. coils No. 18 tinned, ¼-inch diam., lengths measured as for 50-Mc. coils.

- Coaxial fitting.

use standard parts, and the adjustment procedure is simple enough if one has access to a grid-dip meter. Even without adjustment it is quite possible to achieve satisfactory results with these filters if the physical and electrical specifications given are followed closely.

The larger of the two is suitable for use with the high-powered amplifier for 50, 28 and 21 Mc., described in December QST, providing protection of Channels 3 through 13. Appreciable attenuation across the whole of Channel 2 is not practical for a filter that will also pass the 50-Mc. band without insertion loss. Any of the commercial filters, or the various designs that have appeared in QST and the Handbook, can be used to reduce harmonics of the two lower bands in the amplifier's range, if Channel 2 must be protected. Such a conventional filter must be removed when operation on 50 Mc. is to be attempted.

The small filter is intended for use with lowpowered 2-meter rigs, primarily to attenuate the 192-Mc. component in the output that so often is present as the result of stages that triple to 144 Mc. passing along a 4th harmonic of 48 Mc. as well. Since it has high attenuation in the region between 190 and 215 Mc., it may also serve nicely in a rig for 50 and 144 Mc., in preventing radiation of the 4th harmonic of 50 Mc. It will not, however, remove any spurious components in the transmitter output that might interfere with Channels 2 through 6.

Building and Adjusting the 50-Mc. Filter

This is a "how-to-do-it" treatment, Discussion of the principles involved will not be repeated here, but it is strongly recommended that anyone unfamiliar with filter fundaments read basic information on this subject that has already been presented.³ The material to follow will concern itself only with the practical application of earlier design ideas to the needs of the v.h.f. operator, giving only the practical information that will be necessary to insure duplication of the results achieved with the two filters shown.

The circuit used in both filters is shown in Fig. 2, with values of inductance and capacitance for the 50-Mc. job given on the diagram. If means for arriving at these precise values are available, the components can be preset and the filter assembled and used without further adjustment. A method of using a grid-dip meter and simple standards for measurement of both C and L was outlined recently in QST.4 If the builder is in doubt of his ability to do this, or if he does not have access to a grid-dip meter, a satisfactory job can be done by using exact duplicates of the parts and layout, and setting the condenser plates at the positions shown in the interior photograph.

The 50-Mc. filter case is a standard ICA box (Slip Cover, No. 29100), though a suitable container can be made from the dimensions given in the layout drawing, Fig. 3. Physical layout of parts is important, if results obtained with the original are to be duplicated without extensive adjustments. It is suggested that the drawing and photographs be studied carefully with this in mind.

Looking at the interior view, it will be seen that the two end condensers, C1 and C4, are mounted with their two stator posts toward the ends of the filter. The two larger units are mounted in the center compartment with their rotor shafts toward the middle. The top leads from coils L1 and L5 are wrapped around the stator terminals of C1 and C4, and the bottom

³ Grammer, "Eliminating TVI with Low-Pass Filters," QST, Feb., March, April, 1950.

Grammer, "Inexpensive L and C Standards," QST, Jan., 1953, p. 48.

leads fit directly into the coaxial input and output fittings. The outer ends of coils L2 and L4 are soldered to the coaxial fitting terminals, and their inner ends are soldered to lugs supported on one-inch ceramic stand-off insulators. Leads from the standoffs go through holes in the partitions to the bottom stator lugs on C2 and C3. L3 is soldered to the two upper lugs on these two capacitors, thus completing the filter circuit. Note that in addition to turns data, lead lengths for the coils are given in the parts list. These are the total lengths to be left when the winding is completed, including the portions

that will be used in soldering operations. If the components used in the original model are duplicated exactly it should be possible to set up the filter without the use of instruments and obtain usable results, though following through on the recommended adjustment procedure is a much more satisfactory approach. Using standard coils and condensers and a grid-dip meter in the manner outlined by Grammer,4 the coils and condensers in the filter assembly were adjusted to the values given in the schematic diagram. The value of 28 $\mu\mu$ fd. for C_1 and C_4 came at almost exactly the middle of their adjustment range. C_2 and C_3 reached 94 $\mu\mu$ fd. with their rotors extending out of the stators about 1/4 inch on the side of the condensers nearest the wall of the filter case.

With these settings the filter attenuation curve begins to rise at about 55 Mc., reaching its peak in Channel 6 but providing a useful degree of attenuation in all channels from 3 up. The rejection is high all across the high band, 175 to 220 Mc. This range takes care of most of the spurious

No.24 Drill, 6 Holes

No.27 Drill, 8 Holes

13"

Fig. 3 — Layout drawing for drilling the 50-Ma, filter case and partitions.


frequencies that are likely to be generated in a 50-Mc. transmitter, and it will handle all harmonics in the TV range from lower amateur frequencies as well, except those falling in Channel 2.


The 2-Meter Filter

Values of inductance needed in a 2-meter filter are too small to be very readily obtained by the methods outlined for the 50-Mc. job, so a somewhat different approach is used. The filter was made in sections, using capacity values determined in advance and then adjusting the inductances to achieve resonance at the desired frequencies.

The case for the small filter was made of flashing copper. Dimensions are not particularly critical, but in this instance the box is 1½ inches square and 7½ inches long. The main portion of the case is cut from a single piece of copper, with the end tabs folded down and soldered to the sides. Flanges are folded over at the bottom, and a cover is made to slip over these. Details of the

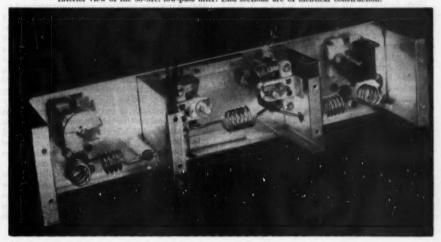Interior view of the 50-Mc. low-pass filter. End sections are of identical construction.



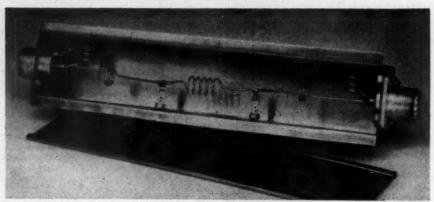

Low-pass filter for use with low-powered 144-Mc. transmitters. Maximum attenuation is in the region of 190 to 215 Mc., but good from 170 Mc. up.

construction are visible in the photograph. Coaxial fittings are mounted in the middle of

Optimum capacitance values figured out to be 11 µµfd. for the end sections and 38 µµfd. for the middle ones. If a device for measuring capacity values accurately is available, standard 10- and 35- or 39-μμfd. units can be measured and those coming nearest the desired values used. Stand-off type by-passes are ideal for this sort of work because of their minimum lead inductance, but suitable values of that kind of unit were not available for the end sections, so ordinary "dog bone" ceramics were used for C_1 and C_4 . Several of these were measured and two nearest to 11 µµfd. were selected. The center capacitors, C2 and C3, were stand-off units marked for 35 μμfd., though the actual value was slightly higher. Values as much as 10 per cent away from the optimum given under Fig. 2 should not make a large difference in results, if the adjustment procedure outlined below is followed.

The filter is assembled and adjusted in sections. First, L_1 and C_1 are mounted in place. A direct short is made across the input connector, J_1 , and the inductance of L₁ is adjusted so that it and C_1 resonate at 200 Mc. Then, connect in L_2 and C_2 , removing the short from J_1 . The circuit including C_1 , L_2 , L_2 and C_2 should be adjusted (by adjusting the turn spacing of L_2) to resonate at 144 Mc. Now disconnect L₂ from C₂ and mount L₃ between C2 and C3. Adjust the turns of this winding until it resonates at 112 Mc. Mount Ls and C4 and adjust, as for the opposite end, with the coax terminal, J_2 , shorted. Add L_4 and C_3 , as for the other end. Now connect all parts and check resonance with the grid-dip meter. The dip, all through the filter, should now be at about 160 Mc., the approximate cut-off frequency.

How About U.H.F. TV?

Tests conducted in the ARRL lab and elsewhere, and results so far obtained in Portland and Bridgeport, the only two areas where u.h.f. TV has been in operation for extended periods, indicate that the advent of u.h.f. TV generally will alleviate rather than increase our TVI problems. Certainly this is true for the user of the frequencies below 30 Mc. The order of harmonic, even from 28 Mc., that will appear in the u.h.f. TV range is so high that there should not be much trouble ordinarily. The 4-250A rig on 28 Mc. made no TVI in a lab u.h.f. check.

The v.h.f. man is more likely to run into TVI trouble, however, as the order of his harmonics in the u.h.f. range is not so high. No means were available for checking the attenuation of the filters described at frequencies higher than 250 Mc., but indications obtained with various u.h.f. TV receiving set-ups are that the filters help materially when harmonics do show up.

The crystal diodes commonly used as mixers in u.h.f. TV receivers have the unhappy faculty of generating harmonics on their own, when strong r.f. fields are present. Preliminary checks indicate that harmonics up to the 10th or higher may be generated in this way. Like the first five items listed on page 16, this is a receiver fault. As such it will be dealt with in a subsequent article.

There is one aspect of u.h.f. TV that should make our problems somewhat simpler than those we've learned to live with in our experience with Channels 2-13: Where high-order harmonics are involved, a small change of transmitter frequency shifts the offending harmonic out of a locally-used channel. The 10th harmonic of 50 Mc. is the first one to appear in the u.h.f. range, so a change of 200 kc. in the operating frequency should be enough to move the interference out of the critical spot in the channel. Even the 4th harmonic of a 144-Mc. rig, the lowest that could interfere directly with a TV signal, could be moved out of trouble in Channel 31 without too great a change at the operating frequency.

We will run into some new problems when u.h.f. TV gets going in high gear, but after the progress we've made in the last few years, who can doubt that any troublesome circumstances arising from u.h.f. expansion will be solved in

short order?

Folded and Loaded Antennas

Suggestions for Mobile and Restricted-Space Radiators

BY WILLIAM B. WRIGLEY,* W4UCW

 Using a simplified method of calculation, the author develops values for the radiation resistance of various folded and loaded forms of short antennas.
 Several interesting possibilities for small radiating systems are discussed.

While we are all quite familiar with the half-wave folded dipole, its radiation pattern, input or radiation impedance, and application to amateur installations, it seems that there are many more folded configurations which are not well known and which may prove quite surprising in their usefulness. Most of us are also reasonably familiar with the basic methods of loading mobile antennas, but we may be surprised at what a few simple calculations can tell us about the effects of various methods of loading.

First let us consider the basic half-wave thin dipole 1 with a theoretical balanced center-feed impedance of about 72 ohms. Fig. 1A shows such an antenna with its current distribution (dashed line) and charge distribution (solid line). While these distributions are not exactly sinusoidal as shown, the assumption that they are so introduces negligible error in impedance and field-pattern calculations, and at the same time reduces these calculations from formidable complexity to fairly simple operations. Now Fig. 1B shows what happens if we attempt to operate this antenna at the second harmonic. We now have a condition of antiresonance. The input resistance is much higher and the reactance variation with frequency is much greater than in the original resonant case at the fundamental frequency. Fig. 1C shows the current distribution at the third harmonic, where we once again have a reasonably broad resonant condition. Fig. 2 shows qualitatively this same information as resistance and reactance plotted against antenna length in wavelengths.

We might conclude from all this toat, at least in the symmetrical case, an antenna will be reasonably broad-band only at frequencies where

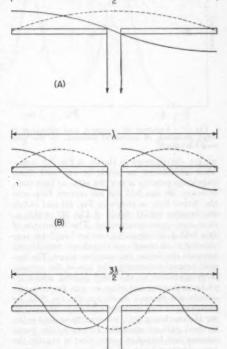


Fig. 1 — Current and voltage distribution on half-, one-, and one and one-half wavelength antennas, fed at the center.

* Asst. Prof. Research, Georgia Institute of Technology; home address, Route 3, Marietta, Ga.

1 Editon's Note: As some readers may not be familiar

with the terms used here, the following may be helpful:

A "thin" antenna is one having a very large ratio of length to conductor diameter, approaching infinitely-small diameter; practically, a wire antenna at low frequencies is "thin" but a 10-meter beam element is fairly "thick."

The thickness affects the resonant length, radiation resistance, and sharpness of tuning.

ance, and sharpness of tuning.

"Antiresonance" is the same as parallel resonance; in the antenna case, it is the condition that exists when a resonant antenna is viewed at a voltage loop.

resonant antenna is viewed at a voltage loop.
"Charge" and "charge distribution" are equivalent
to "voltage" and "voltage distribution."

The "far field" is the radiation field at a large distance from the antenna—so far that the waves may be considered to be plane waves, and, of course, far beyond the region where the induction field is of any consequence.

A "monopole" is one-half of a dipole; e.g., a grounded antenna or one in which a ground plane is substituted for actual ground. the length is an odd number of half-wavelengths or such that the feed point is at a current maximum.

Why can we not simply move the feed point to a current maximum in the second-harmonic case of Fig. 1B? We can, in fact, but then things change somewhat since the now-continuous center cannot support a discontinuity in charge. So

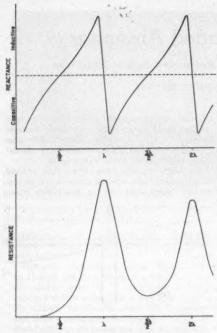



Fig. 2 — Variation of reactance and resistance at input terminals of center-fed antennas as the total length is varied.

we get distributions as shown in Fig. 3A, somewhat unbalanced, as would be expected. Since the charge polarity is now the same at both ends, however, we can fold the left current loop over the driven loop as shown in Fig. 3B and obtain the familiar folded dipole of Fig. 3C, which is, of course, quite symmetrical. The impedance of this folded arrangement can be found by considering it as merely an impedance transformer between the feeder line and free space. The farfield intensity normal to the axis of the antenna is proportional to the total current added up along both wires and, since we now have exactly double the current producing the far field, as compared to that in either wire alone (in particular the one being fed), we must have double the far-field pattern strength. However, the transmission line furnishes power that is exactly the same as in a simple dipole, hence the input or radiation resistance must be directly proportional to the square of the total far-field intensity as compared to that of the fed wire only $(W = E^2/R)$. In this case $2^3 = 4$ and 4×72 is 288 ohms, which is the approximate theoretical radiation resistance of a thin folded half-wave dipole. It is well known that the reactance-frequency variation of the antenna is, in this particular case, partially cancelled out by the opposite variation of the two transmission line stubs in series seen from the feed point such that the

² Lindenblad, "Television Transmitting Antenna for Empire State Building," RCA Review, 3, p. 400, April, 1939. folded dipole has, in fact, broader bandwidth than the single thin dipole.

Other Folded and Loaded Systems

Since this folding operation has proved so attractive, let us now investigate the possibility of folding the configuration of Fig. 1A. Because of the mobile antenna application we shall consider half the antenna of Fig. 1A against a ground plane and fed with a coaxial cable as shown in Fig. 4A. We can fold the antenna as in Fig. 4B and obtain the eighth-wave folded monopole of Fig. 4C.2 Since the opposite ends of the original dipole were at opposite charge polarity (Fig. 1A), we must leave these ends unconnected upon folding; or, in the ground plane case, the folded-over section must not be allowed to contact the ground plane. For radiation purposes, the current in the folded section is opposite in direction

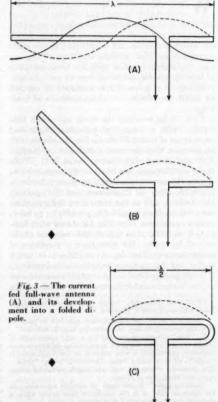

to that of the unfolded half and one must be subtracted from the other, resulting in the radiation current distribution shown in Fig. 4D.

Now in the folded dipole case we found the impedance by adding (mathematically integrating) the current distribution along the wire to obtain a figure proportional to far-field strength.

Actually, these figures of proportionality are only valid comparisons of two antennas if the far-field patterns or current distributions are identical. However, in all the cases we shall consider here, there will be only one combined radiating current loop and hence only one far-field pattern lobe. These lobes will not be exactly the same shape, but to assume them so is a reasonable approximation as evidenced by the fact that the far-field radiation pattern of a halfwave dipole with sinusoidal current distribution is only slightly more directive (78 degrees between half-power points) than that of a minutely short dipole with uniform current distribution (90 degrees between half-power points).


As shown by the calculations in the Appendix, the approximate radiation impedance of the folded eighth-wave monopole of Fig. 4D is 6.2 ohms. A similar analysis of a bottom-loaded eighthwave monopole, Fig. 4E, shows that its radiation resistance also is 6.2 ohms,

which is the same as for the folded case! This identity holds for a quarter-wave monopole which is folded into any even number of elements as compared to a bottom-loaded single element of the same actual height.


Fig. 4F shows the current distribution of a top-loaded eighth-wave monopole.8 The approximate radiation resistance, as shown in the Appendix, is 18 ohms. For the center-loaded eighthwave monopole of Fig. 4G the approximate method of calculation still applies and leads to a theoretical radiation resistance of 11.5 ohms.


Folded Mobiles

Fig. 4D could be interpreted as a 20-meter mobile antenna made up of two adjacent eightfoot whips. One significant advantage of this arrangement is that there is no loading-coil loss to contend with. A further advantage is in the realization that a shorted stub of appropriate length ($\frac{\lambda}{4}$ at 20 meters) connected to the mounting point of the folded or second whip will be an open

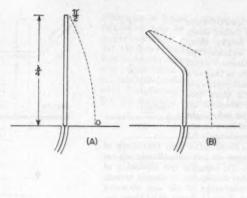


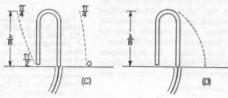4 - Coaxial-fed quarter wave antenna and ground plane (A); effect of folding (B, C and D); bottomloaded eighth-wave (E), top-loaded eighth-wave (F), and center-loaded eighth wave (G).



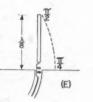



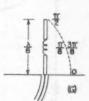

circuit at 20 meters and a closed circuit at 10 meters. At 10 meters the system becomes a quarter-wave folded monopole (half a folded dipole) with an input impedance of a little over 100 ohms, while at 20 meters, with no mechanical change, it becomes an eighth-wave folded monopole with an impedance of about 5 ohms. (Five ohms is probably closer than the theoretical 6.2 ohms since mobile quarter-wave whips look more like 30 than 36 ohms. They are not "thin.") The rather severe difference in impedance between the fundamental and second-harmonic case can be taken care of by feeding the pair of whips with another quarter-wavelength of cable at 20 meters. Being a half-wave at 10 meters, this would give a load impedance at the transmitter of somewhat

over 100 ohms at 10 meters and $\frac{Z_0^2}{5}$ ohms at 20

meters, where $Z_{\rm o}$ is the characteristic impedance of the cable used. This double whip 10–20 system will be slightly more selective, however, than either of the plain folded monopoles, since the reactance deviation with frequency of the shorted stub is opposite in sign from that required to counteract the reactance deviation of the antenna.


³ Terman, Radio Engineers' Handbook, McGraw-Hill Book Co., Inc., New York, 1943, par. 11, sec. 11.

If a 40-meter quarter-wave monopole were folded down to eight-foot height there would be four sections. The resulting impedance, which again is the same as that of a bottom-loaded sixteenth-wave monopole, is 1.2 ohms (see Appendix). An 80-meter arrangement would take eight whips and would have an impedance of approximately 0.3

RESSA.

ohm. However, these latter two extensions of the folding process do not immediately appear very attractive. To complete our discussion of folded and loaded monopoles we should include the radiation resistances of 40- and 80-meter loaded antennas. Table I shows all of these figures calculated by the far-field factor method and based on a nominal quarter-wave monopole impedance of 30 ohms, more realistic than the theoretical "thin" monopole value of 36 ohms.

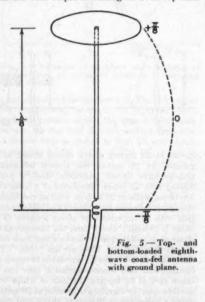
It is interesting to investigate the impedances of short monopoles with optimum current distributions. This requires loading at both top and




bottom so as to center the current loop on the antenna as shown in Fig. 5. The values of radiation resistance for 40 and 80 meters are also included in Table I.

A top- and bottom-loaded (current loop centered) 10-meter quarter-wave monopole has the very attractive impedance of 120 ohms, calculated by this method. The ground current losses in it would be considerably less than the losses in the unloaded case for the same radiated power.

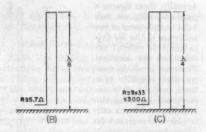⁴ Jordan, Electromagnetic Weres and Radiating Systems, Prentice Hall, Inc., New York, 1950, pp. 510-517.



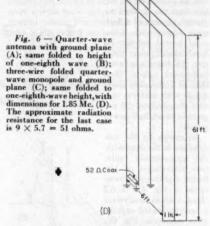

Comparisons

We can now draw some very definite conclusions regarding the merits of various loading schemes. Since the principal loss in a vertical radiator (outside of the loading-coil loss) is due to ground currents, the efficiency rapidly decreases with decreasing radiation resistance. For constant radiated power, the current must be greater for smaller values of radiation resistance. Greater current means greater loss and consequent reduc-

	TABLE I					
Approximate radiation resistance of various loaded and folded monopole antennas based on a quarter-wave value of 30 ohms						
	λ	λ	λ			
Electrical height	8	16	32			
Wavelength for mobile 8-foot whip	20 meters	40 meters	80 meters			
Radiation resistance, top-and bottom-loaded	21 ohms	4.7 ohms	1.2 ohms			
Radiation resistance, top-loaded	15 ohms	4.4 ohms	1.1 ohms			
Radiation resistance.	111	INSTANTAL STATE	5 3 110			

bottom-loaded or

5.2 ohms 1.2 ohms 0.29 ohm


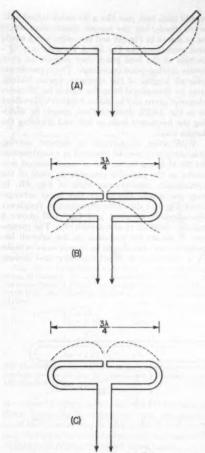


Fig. 7 — Center-fed antenna one and one-half wavelengths long (A) folded into a three-quarter-wave folded dipole (B and C).

tion in efficiency; therefore, the power loss in a center-loaded eighth-wave monopole is more than that of a top-loaded equivalent antenna and the loss in the bottom-loaded case is more than that of the center-loaded case. A combination of both top and bottom loading, however, gives a radiation impedance which in some cases reduces the loss to an exceptionally low value compared to that of the bottom-only loaded, folded, or unloaded case. Sufficient top loading is usually impractical, however, particularly in the case of very short monopoles.

The main conclusion we can draw from all these calculations is that short antennas (monopoles less than one-tenth wavelength) have uncomfortably low radiation resistances and practically nothing can be done to improve their efficiencies to a reasonable value, except possibly by using a multiwire system to raise the impedance as described earlier. On the other hand, the

efficiencies of longer (quarter- or eighth-wave) monopoles may be increased considerably by proper loading, or folding. A practical example is the 160-meter folded eighth-wavelength three-wire monopole shown in Fig. 6B. Adding a third wire to the folded quarter-wave monopole, Fig. 6C, raises the resistance to about 300 ohms, and when this antenna is folded over as shown in Fig. 6D, the radiation resistance becomes about 50

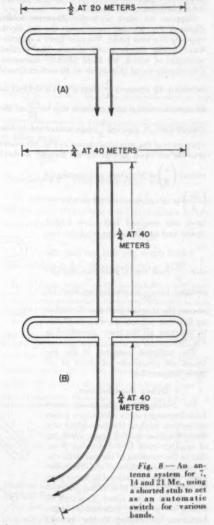

ohms, a good match for coaxial cable. Suggested dimensions for 1850 kc. are given in the sketch.

 $\frac{3\lambda}{4}$ Folded Dipole

Now, since we have pretty well folded and loaded Fig. 1A, let us investigate the results of

folding Fig. 1C. This process and the resulting current distribution is shown in Fig. 7 where the center line represents a ground plane for the vertical analogue of the system. Calculation leads to an impedance for this three-quarter wave folded dipole of about 420 ohms. J. D. Kraus 5,8 (W8JK) has measured one of these to be about 450 ohms. The new 21-Mc. band makes this arrangement quite useful as can be seen in the following scheme:

Suppose we start with the 20-meter folded dipole of Fig. 8A and open-circuit the top dipole opposite the feed point. We now have a quarterwave folded dipole at 40 meters, the vertical analogue of which we have already discussed. The impedance of this dipole at 40 meters should be about 12 ohms. A $\frac{\lambda}{4}$ length of Twin-Lead at 40 meters would then transform this to $\frac{Z_0^3}{12}$ at the transmitter. A shorted $\frac{\lambda}{A}$ stub connected to the open ends of the dipole as shown in Fig. 8B would provide an open circuit at 40 meters, a short

 $\left(\frac{3\lambda}{4}\right)$ at 15 meters. At 20 meters we have our original half-wave folded dipole and at 15 meters we have our folded dipole. In this last case the now $\frac{3\lambda}{4}$ feed line transforms the impedance to $\frac{Z_0^3}{420}$ at the transmitter. Of

circuit $\binom{\lambda}{2}$ at 20 meters, and open again

course, the shorted stub may be folded up in some convenient way so as not to consume all the space indicated in

The radiation patterns of the antenna are practically identical at all three frequencies.

Other Possibilities

No doubt there are many more folded arrangements which may prove attractive, such as the possibility of a 40-meter close-spaced beam made up of quarter-wave folded dipoles. Now, due to the coupling of the parasitic elements, the impedance of the driven element would be considerably lower than the 10 to 12 ohms of a folded quarterwave dipole in free space. This may be raised to a more reasonable value, however, by feeding at the current node (voltage feed) rather than at the current loop.2 The driven element


would then look just like a 20-meter folded halfwave dipole, but the current distribution would be as shown in Fig. 9A and the entire array would look something like Fig. 9B. A T-match or a "Q"section at the feed point may provide an even better driving-point impedance. The approximate over-all lengths of the elements, before folding, may be determined from the curves for 20-meter elements given in The Radio Amateur's Handbook or in the ARRL Antenna Book, simply by dividing the frequency scale in half and doubling the length scale.

With some compromise in element spacing this array may even be operated as a combination 40-20-15 beam by the use of small lumped networks in the parasitic elements in place of the rotationally cumbersome stubs of Fig. 8B. In case you would like to try this latter arrangement, Fig. 10A shows the impedance vs. frequency characteristic required and Fig. 10B shows a suitable network to accomplish this. The parameter K allows for variation in the over-all impedance level, but should be chosen so as to make C₁ a conveniently small capacitor and include

(A) Fig. 9 -A possible 40-meter beam arrangement using quar-ter-wave folded elements. (A)

⁵ Kraus, Antennas, McGraw-Hill Book Co. Inc., New York, 1950; particularly Chapter 5 and par. 13 of Chapter 14. 6 Kraus, "Multiwire Dipole Antennas," Flec-

tronics, 13, pp. 26-27, Jan., 1940.

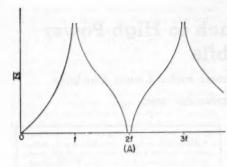

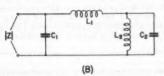


Fig. 10 — Impedance variations in the frequency range of interest (A) and a lumped-circuit equivalent of the stub shown in Fig. 8. Component values can be calculated from the following formulas, where f is in megacycles:

$$\begin{array}{ll} C_1 = K & \mu\mu fd. \\ C_2 = 2.4K & \mu\mu fd. \\ L_1 = \frac{4220}{Kf^2} & \mu h. \\ L_2 = 1.67 \; L_1 & \mu h. \end{array}$$

The factor K may be chosen to make the inductances and capacitances come out to convenient or constructionally-feasible values.

the capacity between the two ends of the element. Since harmonic antennas are not, in general, exact multiples of length, all the network elements may require some adjustment after final assembly to approach resonance on all three bands.

Appendix

$\frac{\lambda}{\rho}$ Folded Monopole (Fig. 4C)

To find the radiation impedance of the eighth-wave folded monopole we must find the far-field figure of proportionality normal to the axis of the antenna by subtracting the integrated current of the folded-over half from the integrated current of the unfolded half. The total length is $\frac{\lambda}{2}$ or $\frac{\pi}{4}$ radians so:

$$E_{\frac{1}{8}} \text{ Folded } \int_{0}^{\frac{\pi}{4}} \frac{1}{\cos\theta \, d\theta} - \int_{\frac{\pi}{4}}^{\frac{\pi}{2}} \cos\theta \, d\theta = \sin\theta \int_{\frac{\pi}{4}}^{\frac{\pi}{4}} - \sin\theta \int_{\frac{\pi}{4}}^{\frac{\pi}{2}} (1) \\ = 0.707 - 0 - 1.00 + 0.707 = 0.414.$$

This is the far-field proportionality constant whose square must be compared with that of a known antenna to give the impedance. The known standard is, of course, the thin quarter-wave monopole whose figure is

$$E_{\frac{\lambda}{2}} \propto \int_{0}^{\frac{\pi}{2}} \cos \theta d\theta = \sin \theta \int_{0}^{\frac{\pi}{2}} -1.0 - 0 = 1.0 \quad (2)$$

and whose theoretical input impedance is about 36 ohms.

Therefore, the approximate radiation impedance of the thin folded eighth-wave monopole is

$$R_{\frac{\lambda}{8}}F = 36(0.414)^2 = 6.2 \text{ ohms.}$$
 (3)

Bottom-Loaded $\frac{\lambda}{B}$ Monopole (Fig. 4E)

The current distribution on a bottom-loaded eighth-wave monopole, Fig. 4E, is identical with the top half of the quarter-wave monopole which we folded over in the previous case, since the loading coil merely replaces the missing half. We can calculate the radiation resistance of the remaining half as follows:

$$E_{\frac{\lambda}{8}} \text{ Bottom Loaded } \text{ or } \int_{\frac{\pi}{4}}^{\frac{\pi}{2}} \cos \theta d\theta = \sin \theta \prod_{\frac{\pi}{4}}^{\frac{\pi}{2}}$$

$$= 1.00 - 0.707 = 0.293.$$

This far-field figure, however, concerns the impedance referred to a current maximum point and since we are feeding at the $\frac{\pi}{4}$ or 45-degree point we must divide by the square of the cosine of 45 degrees (constant power impedance is inversely proportional to the square of the current). So finally we get

$$R_{\frac{\lambda}{6}\text{BL}} = 36(0.293)^2 \left(\frac{1}{0.707}\right)^2 = 6.2 \text{ ohms.}$$
 (5)

Top-Loaded $\frac{\lambda}{R}$ Monopole (Fig. 4F)

The approximate radiation resistance can be calculated from the cosine integral from 0 to $\frac{\pi}{4}$ which gives a far-field factor of 0.707.

$$R_{\frac{\lambda}{2}}$$
 TL = 36(0.707)² = 18 ohms. (6)

Center-Loaded $\frac{\lambda}{8}$ Monopole (Fig. 4G)

For the center-loaded case the calculation is a little more complicated, but our approximate method still applies. The far-field factor includes two additive components, the first of which comes from the bottom section of the antenna and is merely the cosine integral from 0 to $\frac{\pi}{8}$. The loading ceil effectively replaces the missing center half of the antenna so that the current distribution along the top section is essentially the cosine curve from $\frac{3\pi}{8}$ to $\frac{\pi}{2}$. Since the current is continuous through the coil, however, this second integral must be multiplied by the ratio of the cosines of $\frac{\pi}{8}$ and $\frac{3\pi}{8}$. The approximate theoretical radiation resistance of a

conter-loaded eighth-wave monopole is then $\int_{0}^{\pi} \int_{0}^{\pi} dx dx = \int_{0}^{\pi} dx dx$

 $R_{\frac{\lambda}{8} \text{ CL}} = 36 \left(\int_{0}^{\frac{\pi}{8}} \cos \theta d\theta + \frac{0.924}{0.383} \int_{\frac{3\pi}{8}}^{\frac{\pi}{2}} \cos \theta d\theta \right)$

Bottom-Loaded $\frac{\lambda}{16}$ Monopole or $\frac{\lambda}{4}$ Monopole Folded Twice

The cosine integral is broken down into four equal parts between 0 and $\frac{\pi}{2}$ or 90 degrees. Two alternate parts are added and the other two are subtracted. The resulting impedance, which is the same as that of a bottom-loaded sixteenth-wavelength monopole, is

$$\frac{R}{16} = \frac{\lambda}{16} = \frac{\lambda}{16} \text{BL} \qquad (8)$$

(Continued on page 188)

A Different Approach to High-Power Mobile

Power Economy and Compactness with a Linear Amplifier

BY J. EMMETT JENNINGS,* W6EI

FTER examining various mobile installations for 75-meter operation and feeling dissatisfied with existing equipment, we decided to build a new mobile transmitter. Before the design could be crystallized, it was necessary to examine existing modulation systems and methods of portable power generation. We established requirements which we felt should be met in our new design. They were:

1) The power for satisfactory communication should be in the range of a 200- to 250-watt

2) The size of the transmitter should be as small as possible. 3) The weight should be kept to a minimum.

4) The equipment should not require stabilized voltages.

5) Dynamotors and batteries should be avoided because of over-all efficiency and unsuitability for high power.

6) High-quality voice, considered a must, should be as good as the best fixed station. Dis-

* 1098 East William St., San Jose 12, Calif.


• Although a ¼-kw. mobile rig is definitely in the luxury class, we think you will be interested to see how W6EI solved some of the problems of high-powered mobile operation. And the small size of the finished product may give you reason to consider the possibility of using a linear amplifier in your home rig, instead of the prevalent high-level modulation.

tortion, usually caused by overloaded modulators, should be kept low to prevent interference.

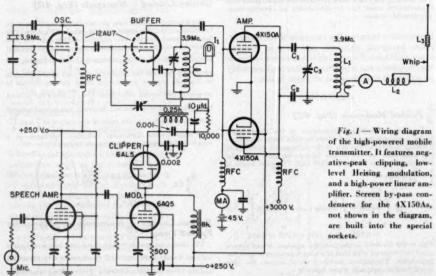7) To clear bridges and overhead obstructions, the antenna would have to be limited to a height of 13 feet 6 inches above ground.

Power Supplies

We had heard of using a d.c. generator driven from the fan belt, and also of using a gasolinedriven generator either under the hood or in the rear compartment. The Leece-Neville alternator



0.001-µfd. 5000-volt mica.

250-µµfd. 5000-volt vacuum (Jennings JCS-L-250). 5000-volt variable vacuum (Jennings UCS-L-250).

18 turns %-inch copper tubing, 2½-inch diameter, 4-turn link winding.

L4 - 18-turn adjustable coil (with roller taken from

surplus gear). Center loading coil.

6-ampere r.f. ammeter.
 2-volt 60-ma. flashlight bulb, modulation indicator and r.f. load.

was suggested, but frequency variation was thought to be a reason why the alternator could not work into a transformer load. However, tests were made in a car with a Leece-Neville threephase generator connected to a double-delta step-up transformer bank. With a load on each phase of approximately 250 watts of light bulbs, we were surprised to learn that excellent regulation took place just above the idling speeds. Later, a three-phase bridge rectifier that produced 3000 volts at 220 ma. was tested. No input filter choke was necessary, and only a 2-µfd. condenser was used to filter the output. The 250 volts d.c. for the exciter was obtained from a power supply connected to one phase. Another phase supplied the power for the high-voltagerectifier filament transformers. The a.e. from the alternator could not be used to operate relays

because, while normal operation was obtained at low engine speeds, at higher speeds the higher frequency caused the relays to unlatch. However, 6-volt d.c. relays give satisfactory results.

The present power supply (not shown in the photographs) is smaller and lighter than the original. It measures only 12 inches long, 8 inches wide and 7 inches high, and weighs less than 40 pounds. This new power supply also delivers 3000 volts at 220 ma., as well as filling the low-voltage requirements, and it was made possible by a special design of 3-phase transformer.

The Transmitter

The transmitter departs from usual amateur practice, in that it uses a low-level modulation

(Continued on page 130)


This transmitter and power supply, tucked away in one corner of W6EI's station wagon, looks too small to put out a 250-watt carrier, but that's what it does. The secret lies in using low-level modulation followed by a linear amplifier, and compact tubes and condensers in the final. The linear is run at high voltage from a three-phase power supply, which cuts down the size of the power-supply filter components.

supply, which cuts down the size of the power-supply filter components.

The transmitter proper is small enough to be held easily in one hand, but the use of 4X150As in the output

stage requires the use of forced cooling, which accounts for the blower mounted under the rig.

One problem with high-powered mobile operation on 75 is the possibility of corona at the tip of the antenna whip, but this is solved by using a small wire cage at the tip of the whip.

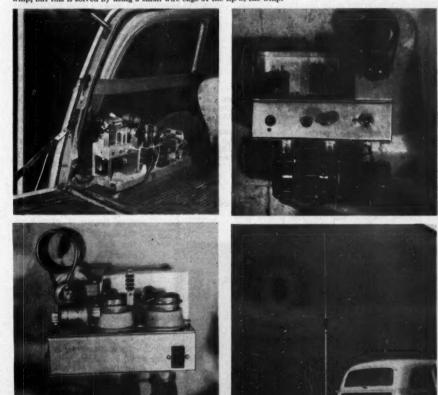

April 1953

Improving the Series Noise Limiter

Simple Circuit Changes for Better Performance

BY H. O. LORENZEN, * W3BLC

SEVERAL years ago I became interested in putting a noise limiter in my BC-348. Friendly amateurs and engineers were only too happy to disclose their pet circuits, and each scheme was duly installed and evaluated. The results with all of them were pretty much the same, with one exception. In operation this particular circuit not only limits the noise peaks but seems to remove the remaining "stumps." After using it for a couple of years and recommending its use to all my friends, I felt ashamed at not having taken time to pass it along to the remainder of the amateur fraternity, so that anyone who wanted to might enjoy its use.

The circuit is shown in Fig. 1, and it can be seen that it closely resembles one of the series-limiter circuits carried in the Handbook. Actually, it differs only in the feed-back path of the cathode of V_1 to the cathode of V_2 , and this change calls only for one additional component. But it is this feed-back path that seems to do the trick of changing it from a conventional limiter to a real limiter. Several of my friends had expensive

 Any amateur plagued by automobileignition interference will welcome an improved noise-limiter circuit. Here W3BLC shows a simple modification of a widely-used series-limiter circuit that is well worth the slight effort involved. It should be particularly interesting to anyone operating mobile.

6H6 or 6AL5, or any other type that has cathodes brought out separately. Crystals were tried in the circuit but do not operate successfully. In the original circuit, as passed along to me, R₃ was shown as a 50,000-ohm potentiometer, but after weeks of adjustment I decided there was little or no improvement with changes in the value, and a 6800-ohm fixed resistor was substituted. This value is not critical, and anything from six to nine thousand ohms works satisfactorily. The audio volume control should be one megohm or higher. It is obvious that considerable loss in

audio voltage is inherent with this circuit, but most receivers have twice as much as they normally need, so this is no serious drawback. To eliminate "tweets" at multiples of the intermediate frequency, it is advisable to shield the "hot" i.f. leads, keeping C_1 , R_1 and R_4 enclosed by a small metallic cover and the leads short. This is just good receiverdesign practice. If the switch S₁ is located remotely from the last i.f. transformer can, the leads to and from it should be shielded to cut down hum pick-up in the receiver. In my BC-348 I put this switch in one of the

'phone-jack holes, thus necessitating a long run around the chassis, but the hum pick-up from heater leads was completely eliminated by the shielding. I mounted the 6AL5 under the chassis on a little bracket near the terminals of the last i.f. transformer. For my money, the limiter could be permanently wired in the circuit. The only time I use S_1 is to demonstrate the limiter.

For the record, this limiter, like all series limiters, does not show any appreciable improvement when operating on c.w. with a heavy b.f.o. signal swamping the second detector. However, when you use it on 'phone it's a "honey."

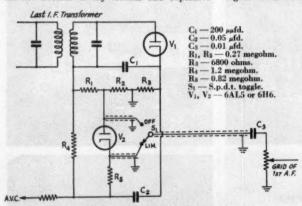


Fig. 1 - Circuit of the improved series limiter.

commercial receivers with conventional series limiters in them and, after changing over to this circuit, reported the receivers sounded like new sets. The boys operating on 10-meter 'phone will find this circuit excellent for eliminating ignition interference. One of my friends operating near the end of a bus line reported 99 per cent operating capability after installing the new limiter circuit. Previously, each QSO was interrupted by idling busses, while the drivers went out for their smokes.

The dual diode used in the circuit can be a *3713 Bangor Street, S. E., Washington 20, D. C.

Design Notes on a Specialized **Phone Receiver**

Circuit Tricks for Improving Performance and Enjoyment

BY ROBERT W. EHRLICH.* W2NJR

If a communications receiver means anything more to you than a box with a knob on the front, you will find a wealth of ideas in this article. It isn't intended for the amateur who has no idea how his receiver functions, but we guarantee that anyone else will read every word of it without stopping. W2NJR's trick for selectable-sideband reception without double conversion is particularly ingenious.

HILE for years it has been customary for amateurs to buy their receivers rather than make them, it is becoming increasingly apparent that the modern commercial receiver, expensive as it is, falls short of furnishing the best in reception of amateur signals. When, as often as not, the owner of a brand-new receiver finds it necessary to augment its performance with a collection of adapters, selectors, preamplifiers and so on, a re-exemination of the old custom appears to be indicated.

Most of the complexity and expense of the standard communications receivers is attributable to the features of broad coverage: bandswitching and gang tuning. These features require engineering compromises all along the line, and precision craftsmanship is needed to get even fair performance. Fortunately, the amateur who builds his own receiver is in a unique position to by-pass all these problems by designing his receiver just to cover his favorite ham band, relying on crystal-controlled converters to pick up any other bands that may be wanted. In this way, the construction job can revert to the standard chassis-and-panel technique, leaving the builder free to concentrate on the circuit design features he wants to incorporate.

The amateur who builds his own receiver has several other advantages over the commercial designer. He can incorporate the exact combination of features to handle his particular needs. He can also avail himself of high-grade surplus components that would be out of the question commercially. And he can take advantage of the latest available techniques that usually take years to find their way into commercial products. As an example of this last item, the now familiar Q5-er was first described in QST in 1947, yet it is only within the last year or so that receivers incorporating this degree of selectivity have appeared on the market. Meanwhile, still better selective systems have been devised.


A receiver is described here that illustrates the principles just mentioned. No elaborate machine work was involved in making it, and its cost was moderate, yet for its specific job it will completely outperform anything on the market.2 A detailed discussion of how to make this particular receiver would not be appropriate, because very few amateurs would want to copy it exactly, but it is hoped that a description of the significant features might offer some helpful ideas to the amateur who is seriously interested in getting the most out of his favorite band.

* 21 Glen View Drive, West Orange, N. J.

Rand, "The Q5-er," QST, December, 1947.

This article was written before it was announced that the Collins 75A-3 includes extreme skirt selectivity for 'phone. See Roberts, "Mechanical Bandpasa Filters," QST, February, 1953.— Eb.

> Front view of the home-made receiver. Panel layout problems are minimized by the absence of bandswitching or gang tuning.

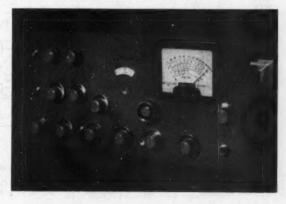

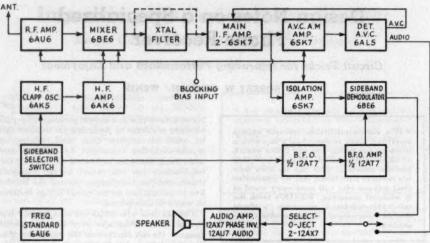


Fig. 1 - Block diagram of the homemade receiver.

The Circuit


A block diagram of the receiver is shown in Fig. 1. The circuit was designed for 75-80 meters, with primary emphasis on the reception of singlesideband signals. Here, stability is the first requirement - the receiver should be exceptionally stable and capable of being tuned just a few cycles at a time. To take full advantage of s.s.b. communication, the selectivity should be highhigh enough to accommodate just one sideband and reject strong adjacent-channel signals without intermodulation effects. Such other features as image ratio and noise limiting, which would be important in a 10-meter receiver, for example, seem to require only secondary consideration.

To start with the front end, its circuit is perfeetly ordinary, but the mechanical arrangements for tuning are a departure from the usual 3 Mix, "Bullding a Series-Tuned VFO Unit," QST, December, 1948.

complex assembly of gears and shafts. The two r.f. circuits are gang-tuned with an ordinary two-section 50-µµfd. variable, with 100-µµfd. condensers added across each section to establish the right ratio of minimum to maximum capacitance for tuning the band.

The tuning circuits have slug-tuned coils, making it easy to set them to tune together. This condenser is brought out to a panel knob that works about like the old antenna trimmer; it is only necessary to peak up the front end occasionally.

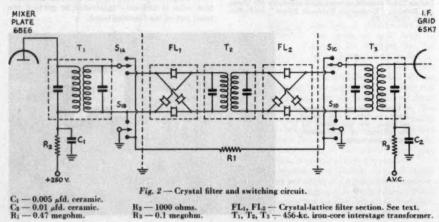The high-frequency oscillator was designed by pretending it was a transmitter VFO. Construction followed that of a high-stability Clapp VFO described in QST, in which a separate box houses just the coil and condenser forming the tuned circuit. In this case, the tuning box was made by cutting down a surplus BC-458 transmitter chassis, which provided an excellent main tuning



 $R_3 - 0.1$ megohm.

32

condenser and a geared dial to go with it. In addition to the usual bandsetting fixed condensers, a 5-μμfd. variable was also added to provide a ± 2 kc. vernier adjustment on the front panel. This has proved to be very helpful in actual receiver operation.

Following the oscillator, an amplifier was found necessary to get enough drive for the 6BE6 mixer. This amplifier is fixed-tuned and peaked near the high-frequency end of the band, to compensate for the tendency of the Clapp

oscillator to lose output at that end.

The crystal filter is, of course, the heart of the receiver's selectivity. The filter circuit is just as described by Weaver and Brown in QST, using eight crystals of the 2-digit series. A switching circuit, shown in Fig. 2, enables the filter to be cut out when desired but still leaves two i.f. transformers in the circuit to retain moderate selectivity. The coupling resistor, R_1 , is selected to make the over-all level of transmission through the i.f. system about the same whether the filter is in or out. The switching circuit and its shielding

⁴ Weaver and Brown, "Crystal Lattice Filters for Transmitting and Receiving," QST, June and August, 1951.

had to be designed to contribute no stray capacitance paths around the filter when it is being used.

It is significant that the filter is the first thing in the i.f. system. This follows the principle usedin producing high adjacent-channel selectivity in commercial mobile receivers, the idea being to eliminate all unwanted signals at the lowest possible power level before they are amplified. There was some apprehension that the attenuation of the filter might degrade the over-all signal-tonoise ratio, but it was found that the front end had enough gain so that the first r.f. grid circuit still is the controlling noise source.

After two stages of amplification, the i.f. system splits into two branches. One branch feeds a carrier-type demodulator, using a 6BE6 tube, for detection of c.w. and s.s.b. signals. With this kind of detector, shown in the upper portion of Fig. 3, no intermodulation products are developed as long as the signal input is held below about one volt. The i.f. stage feeding this detector does not provide any additional gain; its main function is to isolate the main i.f. and a.v.c. systems from the effects of the strong b.f.o. signal (about 20 volts) injected into the 6BE6.

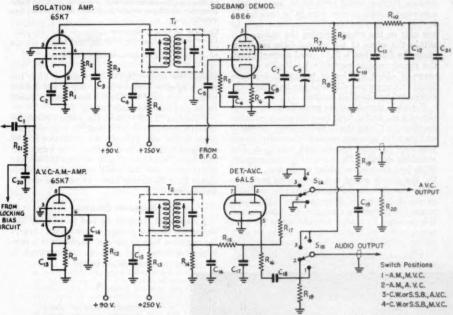


Fig. 3 - The i.f. branch amplifiers, detectors, a.v.c. and switching circuits.

C1 - 100 µµfd. C2, C3, C4, C6, C7, C12, C14, C15, C18, C20, C21 - 0.01-µfd. ceramic. Ca. C11 --470 µµfd. - 10-µfd. 50-volt electrolytic. Co, C10 -- 8-µfd. 450-volt electrolytic.

C12, C16, C17 - 270 µµfd. C19 - 1 µfd., oil-filled.

R1, R5--20,000 ohms. R2, R10, R15 - 47,000 ohms.

R₃, R₄, R₁₂, R₁₃ — 1000 ohms.

R₁₁ — 220 ohms. — 10,000 ohms, 1 watt. Ro, R11 R7

Rs - 2700 ohms. Ro 33,000 ohms.

R₁₆, R₂₀ — 10 megohms. R₁₇ — 2.2 megohms.

R₁₉ — 1 megohm.

– 0.47 megohm.

2-circuit 4-position wafer switch. R18, R19 -R21

456-kc. iron-core interstage transformer. 456-ke. iron-core output transformer.

The second branch feeds a combination a.m. detector and a.v.c. system, using a 6AL5 double diode. This circuit, together with the switching arrangement for the two detectors, is shown in the lower part of Fig. 3. Of particular interest is the diode section that is cut in series with the a.v.e. line on switch position No. 3, for a.v.c. reception of c.w. or s.s.b. signals. This diode causes the a.v.c. to charge up quickly but discharge slowly, so that in effect the a.v.c. bias "hangs up" and rides with the peaks of the received c.w. or s.s.b. signal. Discharge time is about 2 seconds.

The i.f. stage feeding the a.v.c. detector operates at a fixed gain of about 40. With this arrangement, there can be 40 volts of a.v.c. bias for every 1 volt of signal at the 6BE6 demodulator grid. Since 40 volts is enough to cut off the main i.f. amplifiers, it follows that, with the a.v.c. operating, no signal can possibly overload the 6BE6 demodulator.

Coming to the matter of sideband selection, nothing further would need to be done if only a.m. signals, with carrier, were to be received. It is only necessary to tune the receiver a little to one side or the other, keeping the carrier just within the edges of the crystal filter response. Since the filter has a flat-topped characteristic, the signal remains perfectly intelligible over a range of about 21/2 kc. of tuning. Heterodyne QRM falling on one sideband can be completely eliminated by judicious tuning.

For s.s.b. signals, or for exalted-carrier reception of a.m., tuning from one sideband to another requires that both the high-frequency oscillator and the b.f.o. injection oscillator be moved simultaneously in order to maintain zero beat. The switching circuit of Fig. 4 is used for this purpose. With just the two switching condensers, C1 and C2, the circuit would not perform properly because the shift in the high-frequency oscillator would be different at different parts of its tuning range. Compensating capacitor, C3, takes care of this problem. Its shaft is brought out to the front panel, and a calibration mark is made for each 100 kc. across the band. The setting need only be

⁸ Villard and Weaver, "The Select-o-ject," QST, November, 1949.

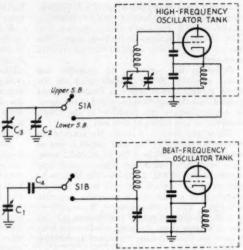


Fig. 4 - The sideband-switching circuit. The connections are shown for use with a receiver with the high-frequency oscillator on the high side of the signal frequency.

 C_1 , $C_2 - 7$ -45 $\mu\mu$ fd. trimmer. $C_3 - 15$ - $\mu\mu$ fd. midget variable with shaft. $C_4 - 10$ $\mu\mu$ fd.

- 2-circuit 2-position ceramic wafer switch.

within the proper 100-kc. segment to keep the switching error within a few cycles. If one desired to go to the trouble, this condenser might easily be ganged with the main tuning.

Following the detectors, the audio system includes a standard Select-o-ject 5 to help with the heterodynes, etc., that are not eliminated by the sideband filter. Following this, it is important that there be plenty of gain, so that neither the Select-o-ject nor the 6BE6 stage need operate above their distortion limits to produce enough audio output.

Receiver Quieting

A somewhat unusual method is used for disabling the receiver during transmissions. Applying negative bias to various amplifiers is a convenient scheme, but such an arrangement is (Continued on page 128)



Ordinary chassis and panel Construction can be used. The large box at the center houses the coil and tuning condenser for the high-frequency oscillator. The crystal-filter network elements are mounted in the group of shield cans at the left.

A Sweep-Tube C.W. Rig for 3.5 and 7 Mc.

Low-Power Transmitter Complete with Power Supply and Antenna Coupler

BY C. VERNON CHAMBERS,* WIJEQ

*Although this rig is suitable for the Novice making his start on 3.5 and 7 Mc., it is also one of those jobs that should be popular with every type of licensee. Therefore, if you have need for a small package that can be put on the air in jig time, don't pass up this description just because the Novice has been mentioned.

This complete crystal-controlled 15-watt transmitter has features which should appeal to every type of amateur. It has a commercial appearance that was obtained without any difficult constructional tricks and it employs simple circuits that discriminate against inadvertent out-of-the-band operation. The layout employs an oscillator-amplifier r.f. section and includes the antenna coupler and the power supply as integral parts of the assembly.

As we have indicated, the transmitter is so practical because of its completeness as to make it useful for many applications. For instance, it is ideal for emergency work requiring a rig that can be installed quickly and easily. It will take up less than one third of a cubic foot of car trunk space when you're packing up for that next vacation, and it is small enough to keep around the shack as a spare until such time as failure, revamping or de-TVIing disables the big rig for an extended period. There is also the possibility of adding an auxiliary power plug to the unit so that it may be used for field day or mobile operation. The output—approximately 10 watts

* Technical Assistant, QST.


1 Chambers, "A 30-Watt Transmitter for 50 Mc.," QST,
August, 1952.

— is not only enough to provide many an enjoyable contact but also will drive a sizable amplifier. The power-supply components used in the transmitter are of the inexpensive b.c. replacement type and may therefore be used with converter, VFO, etc., circuits if and when the r.f. section has outlived its usefulness.

Selection of a Type 6BL7GT as the r.f. tube and the use of a triode oscillator-neutralized amplifier combination resulted in simplicity all along the line. The 6BL7 is a rugged TV-type twin triode that had already proven itself at frequencies as high as 50 Mc.1 and the triode circuits usually call for less parts and handle more easily than their pentode or tetrode counterparts. Old-timers may shudder a little at the thought of going back to a triode oscillator, but the circuit can be made to do a job without blowing the crystal right out of the holder and it delivers practically no output at harmonic frequencies. This last feature is of particular interest to anyone who has gone through the battle against TVI. As for the triode final, it also features simplicity inasmuch as there is no screen circuit to worry about, and it is easily stabilized, once and for all, by a simple neutralizing adjustment. In addition, the tuning range of the amplifier plate circuit prevents inadvertent doubling in the output stage. In other words, you will not accidentally end up one band higher than intended as long as the tank coil has been properly selected

The appearance of the transmitter is made appealing by housing the chassis in a metal cabinet and by marking the panel with decals. Constructional chores are reduced to a minimum by circuitry already mentioned and by mounting

This interior view of the low-power transmitter shows the antenna coil centered at the left edge of the $2 \times 7 \times 9$ -inch aluminum chassis. Five feed-through bushings for the antenna circuit are located to the right of the coil and the feeder terminals are at the rear of the base. L_3 , the oscillator tube, and the crystal are at the front right-hand section of the chassis and the 5Y3GT is on the center line just to the left of the power transformer. A 7/n-inch hole, equipped with a rubber grommet, to the front of T_1 , provides through-chassis clearance for a neutralizing tool. The a.e. input connector is located on the rear wall of the chassis.

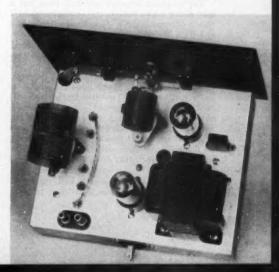



all components on a compact but not overcrowded chassis Having the r.f., power and output coupling circuits arranged as a single assembly eliminates the need for cables and individual enclosures and greatly increases the portability of the transmitter. The cost of the rig—including cabinet, tubes, two crystals and two sets of commercial coils—is about \$47.

The Circuits

As shown by Fig. 1, the crystal oscillator utilizes one section of the 6BL7. J_1 of this circuit is the keying jack for the complete transmitter and also serves as the oscillator metering jack during tune-up time. The plate tank, C_2L_1 , is a 2-band affair that works with both crystals. The frequency range (3.75 to 9.2 Mc.) of the tank has been adjusted so that by observing a simple precaution it is possible to obtain adequate drive for the amplifier without endangering the crystal. (More about this later on.)

Plate voltage for the oscillator is held to a safe value (approximately 200 volts) by a series-dropping resistor, R_2 , and output from the stage is capacity-coupled to the final through C_6 . Although the oscillator has a 2-band plate circuit, the circuit is never used as a frequency doubler.

The amplifier employs grid-leak bias, has a split-stator plate circuit, and is neutralized by means of capacitor C_7 . J_2 is the metering jack and S₁ is the plate-voltage on-off switch. With excitation available and with S1 open, a meter plugged into J_2 will register amplifier grid current. When the switch is closed, the meter will indicate the combined plate and grid currents. J_2 is insulated from ground (so far as d.c. is concerned) except for a return through J_1 of the oscillator. This arrangement allows both stages of the transmitter to be keyed at J_1 . Because the amplifier jack is insulated from ground, it is extremely important that capacitors C_{10} and C_{11} be included in the circuit. Otherwise, there is sufficient r.f. radiation from the plug-in-meter leads to cause TVI in a weak-signal area.

Output from the amplifier is link-coupled to the antenna tuner, $C_{13}L_4$. The tuner uses an

The two-band transmitter is boused in a hinged cover metal cabinet. The knobs across the bottom of the 7×10 -inch panel, from left to right, control the oscillator, amplifier and the antenna coupler. S_1 is located directly above J_1 and to the left of the panel indicator. S_2 is mounted above the amplifier metering jack, J_2 .

inductor that is physically larger than that of the amplifier only because of the desirability of employing variable coupling at one end of the circuit. Unfortunately, the MCL series of coils does not include a swinging-link model and they are not easily modified to include this feature. The tuner components have been wired to feed-through bushings and the antenna feeder terminals in a manner which permits adjustment of the LC ratio for either series or parallel tuning. An accompanying chart lists the jumper connections which should be used for setting up the tuner circuit.

The power supply employs a condenser-input filter and delivers approximately 330 volts when loaded by the transmitter. S_2 is the on-off switch for the supply and the a.c. input must be controlled by the power switch for the station. Incidentally, if the supply is used for some other purpose at a later date, and if the new application calls for less voltage, the output under full load can be reduced to approximately 260 volts by removing the input filter capacitor, C_{14} .

Construction

Three photographs of the transmitter show how the components are laid out on the chassis and the panel. The jacks, switches, and the panel indicator are the only parts actually mounted on the panel of the Bud type C-993 cabinet. Tuning capacitors for the oscillator and the amplifier are mounted on the front wall of the chassis and C_{13} of the coupler is mounted on small pillars at the right side (rear view) of the base. C13 must be insulated from ground and this is taken care of by the physical construction of the Bud type LC-1663 capacitor and by employing an insulated shaft coupling between the capacitor and a panel bearing assembly that is in turn mounted on the front wall of the chassis. A space must be left between the chassis and the panel to accommodate the flange of the bearing assembly and this is provided by using 1/4-inch metal pillars between panel and base at either end of the unit. Three-eighths-inch holes are drilled in the panel for the tuning shafts of the three capacitors, and 11/2-inch openings are punched in the front wall of the chassis to provide clearance for the panel-mounted jacks.

The rear view of the transmitter shows the coil sockets mounted on $\frac{1}{2}$ -inch metal pillars. The socket for L_2 should be oriented with prong No. 3 facing toward the 6BL7 and the socket for L_4 should have prong No. 3 pointing in the opposite direction. This allows a short length of 75-ohm

Twin-Lead to be connected most directly between the coupling links of the two circuits. Wiring and layout of small components will be further simplified if the key of the 6BL7 socket faces the rear of the chassis and if the heater pins

of the 5Y3GT face the panel.


The bottom view of the transmitter identifies the components which require somewhat special placement. No. 16 tinned is used for the r.f. wiring, and Belden shielded wire No. 8885 is used for the leads running to the switches and the pilot lamp. The strip of flashing copper that supports C_7 is $\frac{1}{2}$ -inch wide at one end and tapers down to 1/8 inch at the tube socket end. C7 is mounted in a 1/4-inch hole, drilled at the wide end of the strip for that purpose.

The oscillator plate dropping resistor, R_2 , must normally dissipate slightly over 2 watts. Inasmuch as a 5- or 10-watt unit was not on hand at the time of construction, the required resistance and dissipation ratings were obtained by connecting three 33,000-ohm 1-watt resistors in parallel. The three jumpers for the antenna circuit are 2, 31/2 and 41/2 inches long, respectively, and are made with ordinary hook-up wire and Millen type 36021 grid connectors. The holes in the connectors must be enlarged by reaming so that they will fit over the National type TPB bushings that serve as Terminals 1 through 5 of Fig. 1. Small battery or Fahnestock clips may be used with the jumpers if the Millen connectors are not readily obtainable.

Testing

A 15-watt lamp bulb equipped with short wire leads, a 0-100-ma. meter, a key and a voltmeter should be available for testing the transmitter. The first test is made with the key (make sure the contacts are open) plugged into J_1 , with S_1 set at the open position and with the voltmeter connected across R_4 . Under these conditions, and with 115 volts a.c. applied to T_1 , the supply output should exceed 400 volts when S_2 is closed.

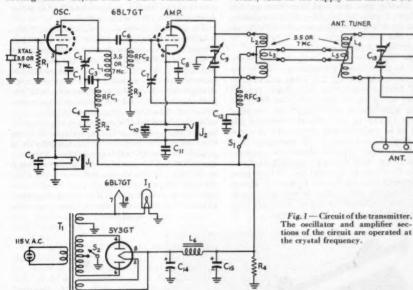Next, turn off the supply and insert a 3.5-Mc.



C1, C3, C4, C8, C12 - 0.005-µfd. disk ceramic C₂ — 140-µµfd. variable (Hammarlund HF-140). C₅, C₁₀, C₁₁ — 0.001-µfd. disk ceramic.

 15-μμfd. mica or ceramic.
 1-8-μfd. tubular trimmer (Erie 532-10). C₀, C₁₈ — 100-μμfd.-per-section variable (Bud LC-1663). C₁₄, C₁₈ — 8-μfd. 450-volt electrolytic (Sprague TVA-C14, C18 -1704).

68,000 ohms, ½ watt. 10,000 or 11,000 ohms; see text. 10,000 ohms, ½ watt. 50,000 ohms, 10 watts. Ra

33 turns No. 24, ¾-inch diam., 1½; inches long (B & W Miniductor No. 3012). 3.5 Me. — 40 µh. — 46 turns No. 24, 1¼-inch diam., 1½ inches long, center-tapped (B & W

80MCL).

Mc. — 14 μh. — 26 turns No. 22, 1¼-inch diam., 1½ inches long, center-tapped (B & W

-3.5 and 7 Mc. - Each 3 turns No. 18, wound

with turns spaced wire diam., over center of L₂.

3.5 Me. — 37 μh. — 38 turns No. 16, 1¾ inch diam., 23/4 inches long. Wound in 2 sections with diam., 23/a inches long. wound in 2 sections with 7(4-inch space at center for Ls (B & W 80) YL).

Me. — 12.8 µh. — 22 turns No. 16, 13/4-inch diam., 23/a inches long. 2 sections with 7/4-inch space at center for Ls (B & W 40) YL).

5 and 7 Mc. — Each 3 turns No. 16, 13/4-inch direct terms are selected with d

Ls - 3.5

diam., turns spaced wire diam. 8-henry 75-ma. filter choke (Stancor C1355).

I₁ - 6.3-volt panel-indicator assembly.

J₁, J₂ — Closed-circuit jacks.

RFC1, RFC2 - 1-mh. r.f. choke (National R-50).

RFC₃ - 2.5-mh. r.f. choke (National R-1008).

S₁, S₂ - S.p.s.t. toggle switch.

T₁ — Power transformer: 340 volts r.m.s. each side of center tap, 70 ma.; 5 volts, 2 amp.; 6.3 volts, 2.5 amp. (Stancor PC8408).

05

03

01

crystal in the holder and a 3.5-Mc. coil in the amplifier. The meter should be plugged into J_2 and S_1 must be open for the time being. Now, turn on the power, close the key and tune the oscillator plate capacitor, C_2 , for an amplifier grid current of approximately 10 ma. If the crystal kicks out as the maximum capacitance of C_2 is reached, the plate tank is tuned too close to the crystal frequency and it is necessary to retune to the high frequency side of resonance. With the original circuit, we pruned L_1 until the lowfrequency limit of the circuit was approximately 3.75 Mc. with the result that it is impossible to knock any of our pet 3.5- to 3.6-Mc. crystals out of oscillation by improper tuning of the plate tank. In any event, make certain that the oscillator is not tuned for maximum output inasmuch as this type of adjustment results in excessive crystal current. If the meter is transferred to J_1 , it should show a cathode current of 30 ma.

The next step is that of neutralizing the amplifier. Start with C_7 set for minimum capacitance (slug all the way out) and then increase the capacitance until the amplifier plate condenser, C_9 , can be swung through resonance without affecting the amplifier grid current. S_1 must be

open during this adjustment.


If the lamp is to be used as the test load, connect it to the antenna terminals and insert the 7-Me. coil in the coupler. The 7-Mc. coil and the high-C jumper connections (see chart) provide the best match for the bulb at 3.5 Mc. Start the loading adjustments with very loose coupling between L4 and L5 and with the oscillator adjusted for an amplifier grid current of 5 or 6 ma. Now, close S_1 and tune C_9 for resonance. The amplifier cathode current should be approximately 25 ma. with the stage lightly loaded and may be increased to 55 or 60 ma. by increasing the coupling between L4 and L5 and by adjustment of C_{13} . As the loading is increased, make certain that the amplifier and the tuner are kept at resonance by retuning both C_0 and C_{13} .

Anter	ana-Coupler C	Connection Ch	art
	Ja	imper Connection	one
Tuning	Low-C	MedC	High-C
Parallel	1-5 2-3	1-5 3-4	1-5 2-5 3-4
Series	1-2	1-4	1-4 2-5

With the amplifier fully loaded, the power supply output voltage will drop to approximately 325 volts and, as a result, the cathode current for the oscillator section of the 6BL7 will be lower than that recorded earlier. About 15 ma. is correct for the oscillator and this current may be checked by inserting the meter plug into J_1 . Of course, with the amplifier in operation, it is necessary to subtract the amplifier cathode current from the reading registered at J_1 in order to determine the true oscillator drain.

The set-up for testing the transmitter at 7 Mc. is identical to that used at the lower frequency except for the antenna coupler connections. At 7 Mc., the bulb loads best with the coupler circuit adjusted for low-C operation. One precaution must be observed with the 7-Mc. crystal in use. Always start the oscillator adjustment with the tank capacitor, C2, set for minimum capacitance and then tune for a maximum amplifier grid current of 5 or 6 ma. There is always a temptation to continue increasing the capacitance of C2 as this results in more drive for the amplifier (it is possible to drive the grid current up to 10 ma. or more) but please remember that the crystal may be damaged by this abuse. And even if the crystal does stay in the holder, you can be very certain that it won't key well if the circuit has been adjusted for maximum output. Just keep that

(Continued on page 138)

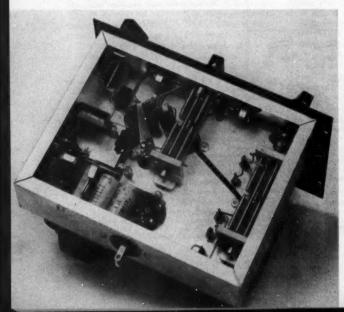

Bottom view showing L_1 and RFC_2 mounted on tie-point strips to the left and the rear of the 6BL7 tube socket, respectively. RFC_1 is parallel with the left wall of the chassis and RFC_2 stands up to the left of C_0 . R_2 and R_4 are in front of L_5 and the filter capacitors at the rear of the chassis. The neutralizing capacitor, C_7 , is supported by the rear stator terminal of C_9 and by a strip of flashing copper which also serves as the capacitor-to-grid lead. Holes, $1/\epsilon_8$ inches in diameter, punched in the chassis just below the centers of C_9 and C_{15} , provide clearance for the coil-socket wiring.

• Jechnical Jopics -


Diode Modulators


Until the current interest in single-sideband transmitting techniques, amateurs had little or no contact with diodes used as modulators. While it is true that we have been using them for years as demodulators—"detectors" is the common word—there was never any reason to consider their use in the allied function of modulator. Their use as modulators is old hat to the commercials, however, particularly in the field of carrier telephony, and if you work for the telephone company you have probably run into them hundreds of times.

But before we get into a discussion of diodes, let's review some of our basic concepts and terminology, because it will help us to understand a few things later on. You are all familiar with the plot of an alternating current or voltage with respect to time. This is shown in Fig. 1A, where the time is represented along the horizontal axis and the amplitude is shown on the vertical. An alternating current or voltage of a single frequency is called a "sine" (or "cosine") wave, from the trigonometric function that defines the instantaneous values. It is symmetrical about the zero-amplitude axis, the positive peaks extending as far above as the negative peaks do below. Along the time axis, the distance between similar parts of the wave is a time equal to 1/f, where fis the frequency. If the wave in Fig. 1A is to represent a 1000-cycle wave, 1/f is 0.001 second, but if it were a 100-kc. wave, 1/f is 0.00001 second. Drawn to the same scale, the 1000-cycle and 100-kc. waves might look as in Fig. 1B. But remember that the shape is always the same, and that only the scale changes. It's something like those trick mirrors in a penny arcade they change the scale in one or the other dimension.

One very important thing to remember from the preceding paragraph is that a single-frequency a.c. wave is always symmetrical about the zero axis. If it isn't symmetrical, it isn't a singlefrequency affair. Take, for example, the job shown in Fig. 1C. At first glance it looks exactly the same as that in Fig. 1A, with the zeroamplitude axis displaced. (That's just what it is.) But it no longer represents a pure a.c. wave, because it doesn't satisfy our definition of being symmetrical about the zero-amplitude axis. Instead, it is now a representation of the a.c. wave of Fig. 1A plus a d.c. (zero-frequency) component. It is obtained by adding the a.c. wave to a steady d.e. value, as shown. The polarity never goes negative, in contrast to the pure a.c. wave where the polarity is negative half the time. (Of course, the d.c. component could be negative, in which case the polarity would never go positive; or the d.c. component could be less than the peak value of the a.c., in which case the wave would fall on both sides of the zero-amplitude axis, but not symmetrically.)

This a.c. wave with a d.c. component is easy to come by, and exists in many places throughout radio equipment. The current in an audio amplifier is of this type, where the d.c. component is the steady value of plate current and the a.c. component is the audio signal. But there is one more thing we should know — and remember — about it. If the d.c.-plus-a.c. signal is coupled to anything, like a load or another stage, through a condenser or a transformer, only the a.c. component appears at the load. This should be obvious, of course — the condenser or transformer cannot pass the d.c., and anything passing through the condenser or transformer must swing equally about the zero-amplitude axis. Thus the signal of Fig. 1C passing through a condenser or

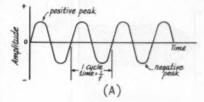

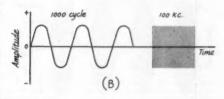

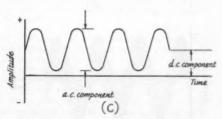


Fig. 1.— The old sine wave, familiar to one and all, is shown at (A). It is a plot of amplitude vs. time of a single-frequency a.c. wave.

single-frequency a.e. wave.
Two different frequencies drawn to the same timebase scale look entirely different, because the higherfrequency cycles are necessarily crowded (B). The shape is the same, however — only the scale is different.

A pure single-frequency a.c. wave must swing equally above and below the axis — if it doesn't, it has a "d.c. component" (C).

transformer - or "a.c. coupler" - will appear as Fig. 1A.

Envelopes

Before we settle down to the main business at hand, there is one more aspect of a.c. that we should review. The signals in Fig. 1 were drawn for only a few cycles, for convenience and ease of studying, but we should worry a little about how they start and stop. Suppose we examine a 100ke. signal that builds up slowly (instead of instantaneously as in Fig. 1B) and then decays slowly. It might look as in Fig. 2A. The first few (and the last few) cycles do not have the same peak-to-peak amplitude that the main bulk of the cycles do. The outline of the 100-kc. wave is represented by the dashed line and is called the "envelope." Notice particularly that this dashed line (envelope) does not represent the instantaneous value of the wave, but only the limits of its peak-to-peak excursions. It is, however, symmetrical about the axis, and must always be so if no d.c. component is present.

Fig. 2B should be a familiar picture. It represents this 100-kc. signal we have been using

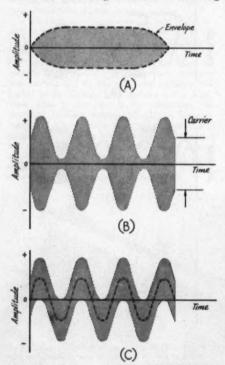


Fig. 2—High-frequency waves don't start and stop instantaneously, and the outline of their rise and fall is called the "envelope" (A). Each cycle swings equally above and below the axis, however.

The familiar envelope of a "modulated" wave is shown at (B), with the less-familiar pattern of "superimposed"

"modulated" by our 1000-cycle signal. Actually, the only a.c. signal drawn here is the 100-kc. "carrier," although we immediately recognize that the envelope has the form of our 1000-cycle signal. The amplitudes of the 100-kc. cycles are changing from time to time. Notice also that, looking at the half r.f. cycles above the zeroamplitude axis, the outline bears a strong resemblance to Fig. 1C, except that in Fig. 2B the envelope replaces the signal, and the (half) carrier amplitude replaces the d.c. component. The same picture, flopped over, appears below the zeroamplitude axis, and the envelope is symmetrical about this axis, as it was in Fig. 2A. Remember that the only a.c. existing here has a frequency of 100 kc. (and some 99- and 101-kc. side frequencies that we won't discuss), and that there is no 1000-cycle component that we could find with a wave analyzer.

But consider the signal in Fig. 2C. Here a 1000-cycle signal and a 100-kc. signal exist in the same circuit. It is no longer symmetrical about the zero-amplitude axis. Instead, one signal is "superimposed" on the other, and a wave analyzer or tuned circuit could select one or the other quite easily. This is the basic difference between this "superimposed" wave and the "modulated" wave of Fig. 2B. In the superimposed waves, the peak-to-peak amplitude of each 100-kc. cycle is the same as that of the previous cycle, even though the excursion above and below the zeroamplitude axis is not always the same. And the envelope is not symmetrical about the zeroamplitude axis - it is as though the 1000-cycle signal had become the axis (dashed line)

Now that you can recognize the difference between superimposed signals and modulated signals, and know the effects of a.c. couplings, we are ready to talk about the mechanics of modulation in a diode.

Modulation

If we feed the superimposed signals of Fig. 2C into a resistor (or into a good Class A or Class B amplifier of such bandwidth as to pass 1000 cycles and 100 kc.), they will come out looking exactly the same as they did at the input. But suppose we use the circuit of Fig. 3A, and feed them into a diode? The action can be analyzed by plotting the effect in the diode, as in Fig. 3B. Whenever the 100-kc. applied voltage swings to the right (is positive), the diode conducts and a half cycle of r.f. passes through R₁. Plotted against time, they would appear as the "output current" shown to the right of the diode characteristic. When the applied voltage swings negative, the diode will not conduct and no output current appears.

So far we have only half cycles of 100-kc. r.f., all swinging up from zero to an amplitude determined by the 1000-cycle signal that was superimposed on the original signal. You know that half cycles of any frequency contain harmonics of that frequency, so we can expect that the current through R_1 is made up of a 1000-cycle component, a 100-ke. component, and some harmonics of 100 kc. (There are also those side frequencies we mentioned earlier, but they are close to 100 kc. and its harmonics, and we will again ignore them in this discussion.) If now we connect a parallel circuit tuned to 100 kc. on the other side of C_2 (as shown by the dotted lines), only the 100-kc. energy will appear across it, the other components being rejected by the selectivity of the circuit. The voltage across this tuned circuit will appear as in Fig. 3C, since the a.c. coupling (through C_2) has made it necessary that each 100-kc. cycle swing as much below the axis as above. This figure we recognize as a modulated wave.

The diode characteristic shown in Fig. 3B is much too good to be true, and in practice it isn't a straight line from zero on up. A practical characteristic has some curvature, and so the usual practice in diode modulators is to use a large r.f. signal and a small audio signal. This has the effect of doing the actual work of modulating on a small relatively-straight portion of the diode characteristic, and simply means that you can't use a high percentage of modulation without running into distortion of the envelope. The same thing is true, of course, in plate-modulated Class C stages - you can't run high percentages of modulation without distortion - but there we don't worry about it so much. In the applications where diode modulators are used, we try to hold the distortion down as low as possible.


Balanced Modulators


A balanced modulator is a device for obtaining the side-frequency components of modulation without passing the carrier. In single-sideband transmitters, this is done prior to removing one of the sidebands with highly-selective circuits. While balanced modulators may take several different forms, they all serve the same basic purpose, and the various circuits involving diodes differ only in the frequency components (harmonics) that appear in the output.

The most common circuits are those shown in Fig. 4.1 It is apparent in both that the carrier frequency cannot appear in the output because the net effect of the carrier across the output is zero, when there is no audio signal.

Now suppose that we disconnect the audio transformer and connect a small battery across points B and D in Fig. 4A, the positive terminal to B. Diodes AB and CD will be "biased back" by the amount of the battery voltage, and they will not conduct r.f. (of the proper polarity) until the r.f. voltage exceeds this bias value. The other two diodes, BC and AD, will conduct readily, however, and over more than half the r.f. cycle, because they are biased "forward." Since the one set of diodes is conducting better than the other, the circuit is no longer balanced, and r.f. will appear across the output. The fact that these are approximately half cycles of r.f. flowing through the diodes shouldn't bother you - remember that this is an a.c.-coupled affair and the

1 A third type, the "series" modulator, is described by Berry in the Sept., 1952, QST.

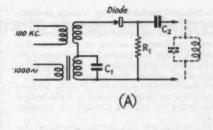

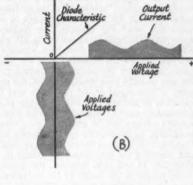

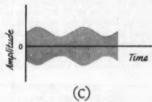



Fig. 3 — A basic diode-modulator circuit is shown in (A). C₁ and C₂ are by-passes for the 100-kc. signal. The modulator action is shown at (B), where the envelope of the superimposed signals becomes a modulated envelope in the output. The a.c. coupling in the output of the modulator, and the tuned circuit, convert the "output current" envelope of (B) to the modulated-wave envelope of (B) wave envelope of (C).

r.f. will be normal full cycles in the output. The more voltage applied, the more the unbalance, and the more r.f. there is in the output. When the polarity of the bias is reversed, the diodes BC and AD will be biased "back," and diodes AB and CD will be the easier paths.

Since the output depends upon the voltage across points B and D, if we reconnect our audio transformer and apply a single audio frequency, the r.f. output will appear in proportion to the audio voltage and regardless of its instantaneous polarity. Thus we will obtain an output like that of Fig. 5B when an audio voltage like that of Fig. 5A is applied. Anyone who has followed s.s.b. testing techniques will recognize this pattern as that of the "two-tone" test signal, but it should be apparent to all how it is the envelope pattern of a balanced modulator when a single modulating frequency is used. It will also occur to the reader that the balanced-modulator action could have been described simply on the basis of a balanced bridge being upset by the action of the audio, without any introduction explaining something about normal modulators and a.c. However, the difference in envelope patterns between carrier and no-carrier signals is brought home a little better by running through the complete

story

Except that this isn't the complete story. One thing these envelope patterns can't show is the resultant frequency "spectrum" of the modulated wave, although the Handbook attempts to correlate the two.3 For example, the frequency spectrum of the envelope shown in Fig. 5B, when generated in a balanced modulator, consists of two side frequencies, separated from the (eliminated) carrier by the modulation frequency. In the case we have been speaking about, the spectrum of this signal would show two side frequencies, 99 and 101 kc., with no energy at the (eliminated) carrier frequency of 100 kc. Such an envelope pattern can be generated in a normal modulator, by modulating with a complex wave that could be obtained from a full-wave rectifier and adjusting the modulation percentage to exactly 100. In this case, however, the spectrum would consist of the carrier at 100 kc. and sidefrequency components spaced at 1000-cycle intervals out to 10 or 15 kc. either side of 100 kc. Hence, although the envelopes could look the same, the spectrums could differ greatly - the difference is in the phase of the r.f. cycles and the lack or presence of a carrier. In the balanced

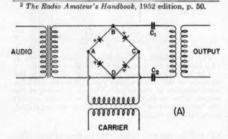


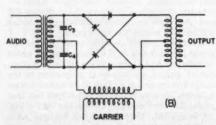


Fig. 4 — The two common diode balanced-modulator circuits are (A) the bridge and (B) the ring. Condensers C_1 , C_3 , C_3 and C_4 are r.f. by-pass condensers, used to complete r.f. paths without short-circuiting the audio.

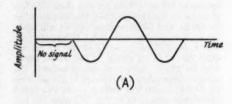

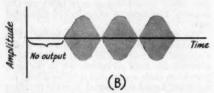


Fig. 5 — A modulating signal as in (A) gives an r.f. output from a balanced modulator as in (B).

modulator, the phase of the r.f. in the output is reversed as the modulating signal passes through zero value, because the one pair of diodes takes over the job from the other, and routes the r.f. differently from its source to the output transformer.

Practical Considerations

It has already been mentioned that the ratio of modulating voltage to carrier voltage should be low in a diode modulator, if the distortion products are to be held to a low value, and this is equally true in the balanced-modulator application. Normal practice is to make the carrier voltage at least 10 to 20 times the peak modulating voltage. For germanium crystals and copper-oxide rectifiers, the r.f. voltage is usually on the order of 2 to 6 volts. The inherent carrier balance will sometimes run as high as 30 db. without any balancing adjustments, and with balancing (through circuits shown in any practical description) it will run to 60 or 70 db. Sideband energy is equal to the modulator power delivered, minus the resistance losses in the diodes, and these losses will run from 2 to 10 db. depending upon the carrier frequency. The rectifiers are in common use up to 4 Mc., and will be usable at higher frequencies with careful construction. A bugaboo at the higher frequencies is the variation in internal capacity of the rectifiers, and consequently they must be operated at lower impedance levels as the operating frequency is increased. From 600 to 1000 ohms is a practical level at 500 kc., but 50 to 100 ohms is recommended at 4 Mc. - B. G.

Strays 3

W2KG, W4HB and W4JQ, who recently together shot rounds of 79, 77 and 76, respectively, on the West Palm Beach, Fla., Country Club course, challenge local or visiting amateurs to take them on individually or collectively.

The 1953 Governors-to-President Relay

In the year 1925, prior to the inaugural of President Coolidge, the first ARRL Governors-to-President Relay was held. At each presidential inauguration since that time, amateurs throughout the country and in all territorial possessions have taken part in the GPR, exhibiting the operating skills and achievements which have helped make this an outstanding event. In 1949, during the last GPR, the greatest number of states to date was heard from. At that time, a total of 41 states and 4 territories was reported as being active in the relay.

This year, upon occasion of the 7th Governors-to-President Relay, participating amateurs have established relay records which will be the standard to meet in years to come. Every one of the 48 states made report of its activity in the GPR; 47 states were heard from by radio. The actual number of originations of messages from state governors to the President-elect was 46. Two other states, Washington and New York, made repeated attempts to obtain messages from their Governors, but to no avail. Additional congratulatory messages were received from 3 territorial governors and several military commands. This outstanding showing reflects great credit upon the amateurs who participated in originating and relaying the messages and to the splendid cooperation of the Washington-area amateurs.

Coördinated under the able direction of their SCM, Jim John, W3OMN, amateurs in the Capitol area began a 24-hour alert at 5:00 p.m. EST on the evening of January 19th. Through intensive monitoring by the master station, W3PZA, the section net MDD, and individual amateurs throughout the area, all GPR messages were received and accounted for within 18 hours. The call of the hour, "CQ Washington de . . . GPR," brought results!

Eppa Darne, W3BWT, net manager of MDD and faithful GPR participant, reported MDD operating shifts manned by W3AKB, W3COK, W3ECP, W3MCG, W3NOE and W3QZC. Other MDD stations such as W3HC, W3JHW, W3JZY and W3TRN combed the bands for GPR traffic. The master station, W3PZA, staffed by W3CDQ, W3MSU, W3OMN and W3RNA, accounted for a large number of messages received. In addition to their air activity, the W3PZA operators took all incoming landwire messages, typing copies for the President and ARRL. The numbers of

messages accredited to the individual amateur stations on the receiving end of the GPR (messages) were K4USA (13), W3QZC (5), W3FQB (4), W3ECP (3), W4NF (3), W3OMN (3), W3PZA (3), W3CVE (2), W3NOE (2), W3MCG (2), and one each by W3AKB, W3BHV, W3CIC, W3CLY, W3FPT, W3HVL, W3IL, W3JQN, W3PFO, W3QQS, W3TNA and W4KFC.

Most of the traffic was handled on the 3.5-Mc. band with considerable additional activity on 75-meter 'phone and on forty and twenty meters. In spite of poor conditions, the quality of the operating personnel resulted in an unusually large number of state messages arriving in the key area without intermediary relays. Out of 46 congratulatory messages originated by 46 different states, 28 were received in Washington directly from the stations of origin! This impressive 61 per cent speaks for itself.

The unprecedented success of the 1953 relay was due not only to the individual amateurs who actually did the operation, but also to the SCMs and the amateurs in their sections who worked at cutting the red tape in the state capitols and who solicited the messages, to all the nets who participated, from section to transcontinental level, to the ARRL National Traffic System and its trunk line stations, to the splendid cooperation of the MARS operators and to the many non-amateur hands who so enthusiastically lent their support to help make the 1953 Governors-to-President Relay the most active to date. It was a job well done.

Message Routings

All relay routes reported to ARRL are listed below. Unless otherwise noted the first call listed is that of the station of origin. A question mark indicates that no information is available on how the message got from one station to the next, whether through additional relay stations or direct.

Alabama: W4AUP-W4PW8-W4PL-K4USA.
Arisona: W7QZH via W7LVR-W4ZD-W4CAK-W6CIW/9-W2BTB-1-W3FPT.

Arkansas: W5AY-K4USA.
California: W6CIS/6-W4KFC.
Colorado: W6CW3ECP.
Connecticut: W1TIA/W1LKF-W3MCD-W3NOE.
Delaware: W3HC-W3AKB.

Texas, the biggest state in the Union, arranging to send congratulations to their first native-son President via the Governors-to-President Relay. L. to r.: W5GQ, originator of the Texas message, W5NZE past-president of the Austin Amateur Radio Club, and Governor Allan Shivers of Texas.



Getting Acquainted with the ARRL Lightning Calculator

Tuned-Circuit Problems Made Easy

BY DONALD H. MIX,* WITS

The ARRL Lightning Calculator, Type A, was devised by a ham who, like everyone else, found tank-coil calculations too complicated and time-consuming, and decided to do something about it. A very frequent problem in building a receiver or transmitter is the one of determining the dimensions of a coil to resonate at some desired frequency with some selected value of condenser capacitance. (For transmiters, there is a chart in the *Handbook* that tells you what tank capacitance you ought to use.) The first formula you have to use is the one that tells you what inductance is required to resonate with your condenser at the frequency you want to hit.

$$L=\frac{25{,}330}{f^{\sharp}C}$$

The units are in microhenrys, micromicrofarads and megacycles. It isn't a very complicated formula, but choose some values and see how long it takes to get the answer.

Now, let's see how it's done on the Calculator. On one of the scales (a portion is shown in Fig. 1) you will see an F. Immediately below is a rotating scale of frequency. Set the frequency you want to the F mark. Then below (Fig. 2), you will find, automatically lined up opposite each other, the numerous combinations of inductance and capacitance that will resonate at your frequency. You don't even have to find the decimal place.

Coil Dimensions

Doing it the hard way, you now would have to calculate the coil dimensions that give you the required inductance. The formula is

$$N = \sqrt{\frac{3a + 9b}{0.2a^2} \times L}$$

• Although the Type A Lightning Calculator has been available for nearly two decades, our Technical Information Service correspondence indicates that there are still many — old-timers as well as Novices — who either are not aware of its existence or have no idea what it is. It's really too bad, because perhaps next to a milliammeter, it is just about the most useful (as well as the cheapest) gadget a ham can have around the shack. If you don't believe it, read on.

where N is the number of turns, a the diameter and b the length of the coil. This turns out to be a lulu. The fact that most hams will consider it complicated is only the beginning. There are three unknowns. You have to decide the diameter and length before you know the number of turns. And then, when you find the number of turns, you'll probably discover that, with the size wire you want to use, the turns won't fit into the required length. So you pick another length and try again.

Here is where the Calculator really saves time and head-scratching. You have previously found the inductance you want. Below the inductance scale, you will find three wire-size scales (see Fig. 2), depending on the kind of insulation, i.e., enameled, silk, cotton, etc. Set the desired inductance value opposite the size wire you want to use. (We'll talk about wire size a little later.) Then, at the top of the Calculator (Fig. 1), you'll find, automatically lined up, all of the practical combinations of length and diameter that will give your inductance. Opposite each wire size on the scales below, you'll find a scale of turns per inch for each size of wire. To determine


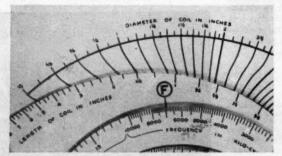


Fig. 1— Frequency, diameter and length scales. The frequency set here is 7000 kc. For a capacitance of 50 µµfd. and a coil wound with 19 turns per inch (see Fig. 2) the various coil lengths and diameters are shown above. Examples: 1½-inches diameter, ½ inch long; 1-inch diameter, 1½ inches long, etc.

^{*} Assistant Technical Editor, QST.

Fig. 2—Inductance, capacitance and wire-size scales. For the 7-Me. setting of Fig. 1, the Calculator shows various combinations of capacitance and inductance that will resonate. Examples: 50 μμβα, 10.5 μh; 100 μμβα, 2.25 μh; 35 μμβα, 15 μh, etc. Below each of these will be found the largest size wire that can be used to fit the sizes of Fig. 1. This information, as well as that of Fig. 1, is obtained with one setting of the Calculator. By shifting the inductance line to line up with a different number of turns per inch, a whole new set of coil dimensions is obtained. The transparent celluloid indicator facilitates lining up the scales.

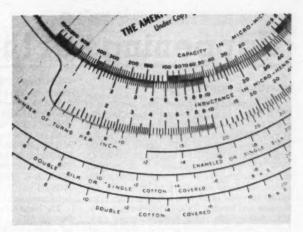

the number of turns for a close-wound coil, all you have to do is multiply your chosen coil length by the number of turns per inch. It's as easy as that! If you want a space-wound coil, set the inductance line opposite the line for half the number of turns per inch instead of the wire-size line. For example, the Calculator shows that a close-wound coil of No. 14 enameled runs 15 turns per inch. Set the inductance line opposite 7½ turns per inch for a double-spaced coil, etc.

Sometimes you have a coil form you want to use for a certain inductance and want to know what size wire you can use to get the needed inductance without running off the coil form. This is easy, too. On the top scales, set your form length opposite its diameter and at the bottom, opposite the inductance, read the maximum wire size that will fit. Similarly, you can measure the diameter and length of a coil and the turns per inch and find its inductance in about 15 seconds.

Tuning Range

Another annoying bit of formula juggling that the Calculator makes light work of is the business of determining what range of frequencies a variable condenser will tune over with a given coil. Simply set the inductance value opposite the minimum capacitance and, under the F mark, read the maximum frequency. Then, move the inductance line opposite the maximum capacitance line and under the F index read the minimum frequency. You can, of course, just as easily reverse the process and find out how much capacitance variation you will need to cover a desired range of frequencies.

The scales cover frequencies from 150 Mc. to 400 kc., inductances from 1 μh. to 1500 μh., capacitances from 3 μμfd. to 1000 μμfd., wire sizes from No. 0 to No. 36, coil lengths from ½ inch to 10 inches and diameters from ½ inch to 6 inches.

Accuracy

The accuracy of the Calculator is well within

the limits that it is possible to approach in winding a coil. The only catch is that the actual capacitance across the coil is seldom known precisely. The capacitances-to-ground of the tube, socket, wiring, coil, coupling condenser, r.f. choke, and, most of all, the capacitance of the tuning-condenser stator to ground, all add to the value of capacitance marked on the tuning condenser by the manufacturer. Nevertheless, the important point is that if you use the values of tuning-condenser capacitance, minimum and maximum, specified by the maker, you will never end up with a coil that hasn't enough turns. You can always adjust the coil by removing turns instead of winding the whole coil over again. However, it is pretty safe to say that in a circuit of conventional design, using standard components, you will have to add at least 20 µµfd. to the minimum and maximum values specified for the tuning condenser if you use inductive coupling, and 30 µµfd. in the case of capacitance coupling with screen-grid tubes.

Coil and Wire Size

Of course, the Calculator won't show you optimum coil dimensions nor the best wire size to use. In practice, the considerations of form and wire size for minimum loss often are less of a determining factor than the coil size that will fit into available space or will handle the required power without burning up. This is especially true in these days of screen-grid tubes where the relatively small driving power for the final amplifier can be obtained easily even if losses in the exciter are quite large. It may be considered preferable to take the power loss if the size of the exciter can be kept down by making the coils small.

The accompanying table shows typical conductor sizes that are usually found to be adequate for various power levels. For powers under 75 watts and for receivers, the minimum wire sizes shown are largely a matter of obtaining a coil of reasonable Q. So far as power is concerned,

(Continued on page 138)

Happenings of the Month

NATIONAL CONVENTION

The sponsoring committee and members of the Houston Amateur Radio Club are buckling down to work even harder as they come into the stretch of planning the Seventh ARRL National Convention, to be held in the largest city in the largest state of the Nation on July 10, 11 and 12, 1953. Although arrangements for the program and its participants are of course not yet completed, the hosts assure you of interesting and varied coverage of all ham subjects - technical lectures and forums, TVI, civil defense, mobile, DX, transmitter hunts, radioteletype, s.s.b., traffic nets, emergency communications, contests, v.h.f.-u.h.f., and even ham TV. An initia-tion of the Royal Order of the Wouff Hong will be held. There'll be a delegation from ARRL Hq., and it is expected that Phil Rand, W1DBM, will present his famous TVI demonstration. For the ladies, social functions including luncheons, teas,

entertainment. A formal dance and banquet will climax the affair.

The Shamrock Hotel will be convention headquarters, though the banquet and some other activities will be held at the Rice. Room reservations are to be made directly with hotels or motorcourts; get yours in early! Some of the hotels are, in addition to the Shamrock and Rice, the Lamar, Texas State, Ben Milam, and the Montague. Houston is called the most thoroughly air-conditioned city in America, with 3860 conditioned hotel rooms and 370 motor court units.

The registration fee is \$13.50 per person, and includes all the convention activities. There will be a pre-convention party the evening of July 9th, \$2 per person. Send your check or money order now, payable to the Houston Amateur Radio Club, to P. O. Box 10173, Garden Oaks Station, Houston 18, Texas.

May QST will have a complete story on convention plans.

Seventeen persons — nearly one-third the total of Hq. employees — have completed ten years or more of ARRL staff service. Shown at a recent gathering to commemorate the 25th anniversary of Circulation Supervisor Cecilia C. Hatch, and the 10th of Advertising Assistant Edgar D. Collins, are, l. to r., seated: Communications Department Administrative Aide Lillian M. Salter (22 years); Treasurer David H. Houghton (31); Mrs. Hatch; General Manager A. L. Budlong, W1BUD (29); Communications Manager F. E. Handy, W1BDI (28); Chief Accountant Alice V. Scanlan (24). Standing: Walter E. Bradley, W1FWH (11), Technical Information Service; Asst. Technical Editors Donald H. Mix, W1TS (19), and Byron Goo-lman, W1DX (17); Asst. Circulation Mgr. Harold K. Isham W1MFA (16); Mr. Collins; Technical Director Geor e Grammer, W1DF (23); Circulation Supervisor Marion E. Bayrer (15); Technical Assistant C. Vernon Chambers, W1EQ (23); Deputy Communications Manager Joseph A. Moskey, W1JMY (14); Asst. Secretary John Huntoon, W1LVQ (14). Absent, on a civil defense mission: Nat'l Emergency Coördinator George Hart, W1NJM (14). Total service represented: 335 years!



BOARD MEETING

A special meeting of the Board of Directors of the ARRL has been called for May 8th in Hartford, Conn. At press time we have notice of several proposals which will be presented by Director Middelton, West Gulf Division. The Board will of course make its usual examination of ARRL and amateur affairs. In this connection amateurs and clubs are invited, as always, to express themselves to their directors concerning topics of the day, or to originate new proposals. The list is on page 8.

The May meeting is termed "special" because under the new charter the regular annual meeting is normally scheduled for sometime in the first quarter. Such a meeting was held, as required, but it was no surprise when no directors appeared inasmuch as they had all earlier indicated inability to attend a meeting so early in the year.

Director Middelton's proposals are to establish a committee to investigate relationships between the staffs of FCC and ARRL; to provide verbatim transcripts of proceedings of Board meetings; to instruct Headquarters (or a qualified testing laboratory) to evaluate TV receivers, high- and low-pass filters, and TVI-treated transmitters advertised in QST as to their performance; to make space available in QST to any elected ARRL official; to sponsor an ARRL Technical Scholarship, leading to a year's paid employment in the Hq. lab., for which all amateurs under 21 would be eligible; and to establish an ARRL yearly Merit Award for outstanding technical contributions by an amateur.

The Antenna Coupler Helps the Receiver. Too!

BY JOHN J. GLAUBER,* W3GQD

ANY amateurs do not give adequate attention to the most efficient means of coupling the receiver to the antenna. Where an antenna coupler is used, the antenna feeders are usually connected to the receiver by means of a single-pole double-throw relay in each feeder line, if balanced feeders are employed, or by a singlepole double-throw relay if coax is used. Sometimes an untuned pick-up coil is coupled to the tuner tank coil.

After completing a wide-range coupler with B& W type TVL coils, various means of coupling the receiver coax input to it were tried. The pick-up coil was tried because it offered flexibility for all-band operation with the possibility of eliminating costly relays. Because of the lowimpedance coax input to the receiver, the pick-up coil, which was loosely coupled to the tank coil, required series tuning by a variable condenser. A 100-μμfd. tuning condenser was incorporated in the coupler, mounting it beneath the main chassis so as to be out of the direct field of the tank inductance and yet be adjustable from the front panel of the coupler by means of a knob.

A small d.p.s.t. normally-closed relay opens the receiver antenna and B+ during transmitting periods. A small coax relay is preferable for the antenna switching.

The advantages of this means of coupling the receiver to the antenna are obvious. The proper impedance match between antenna and receiver is readily obtained. The coupler tank is, as usual, tuned to the desired frequency. By adjusting the series variable condenser, the receiver input circuit is tuned to the same frequency. The condenser tuning is not critical and need not be varied over any one band.

ing as indicated in Fig. 1. This is desirable as no supply lines enter the coupler housing and thus no r.f. is induced in the relay-solenoid windings and possibly the supply lines. The appropriate receiver pick-up coil is

The relay is mounted outside the coupler hous-

plugged in place with the tank coil for the desired

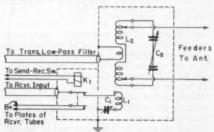


Fig. 1 - A separate link and coax line is provided for receiver input.

receiver input.

C1 — 100-µµfd. variable.

L1 — 3.5 Me. — 35 turns, 1½ inches long.

— 7 Me. — 19 turns, 1 inch long.

— 14 Me. — 8 turns, ½ inch long.

— 28 Me. — 4 turns ¾ inch long.

All coils wound with No. 26 enameled wire, 1½-inches diam. (National XR-6 forms).

L2C2 — Usual transmitter antenna-coupler coil and condenser.

condenser.

K₁ — D.p.s.t. normally-closed relay (coax type preferable),

band. A combination arrangement can be constructed in which the pick-up coil and tank inductance are integral so that both may be plugged in as a unit.

With C1 tuned to resonance, a gain of six S units has been observed over the nonresonant condition, or with the condenser shorted.

^{* 1014} Lansdale Ave., Lansdale, Penna.

Wide-Band Re-Entrant Networks

A Solution to the Problem of Amateur Antenna Loading

BY WILBURN D. FINGERS,* WK4ZY

Many times in amateur activities, it is taken for granted that a job can be finished. At this writing, it is by no means certain that the study to be described has been brought to any degree of conclusion.

Like many others, we have often been faced with the problem of loading the final properly. Many methods have been tried, and we have had

some measure of success.

A New Circuit

About one year ago, a new output circuit was evolved from a series of experiments. It is shown in Fig. 1. It became immediately evident that this circuit has great flexibility. Adjustments

Fig. 1 — The "pi-ip" antenna-coupler circuit uses a few more components than usual, but results in a much wider range of possible adjustments.

were found to be quite critical with regard to the type of antenna in use, but at the same time almost any variation of loading could be had.

It will be noted by some that the combination L_1 , C_1 , C_2 resembles the familiar pi network. Reference to the Handbook and other articles will show that this circuit has great versatility of itself. The added elements, L_2 , L_3 , C_3 and C_4 , develop an imaginary impedance that can be considered to be the reverse of that of the "pi" network. It has therefore been aptly named the "ip" network, to distinguish its function from the more usual parts of the circuit. Referring now to Fig. 1, we see that, without leaving any critical component values, at least five variable elements have been introduced into the over-all adjustment procedure. Assume that the setting of C_3 is at some arbitrary value, then L_2 , C_3 and the lower part of L4 up to the ground tap becomes a series-resonant circuit, which can absorb considerable power and pass it to ground at the particular frequency. This has proved to be a rather mixed blessing at times as the curves to be given later will show. Thus, the setting of C3 has considerable effect.

* Canyall, Ga.

 Antenna coupling and transmitter loading have always been confusing to many amateurs, and this article is intended to help in that direction. The mathematics has been edited out, in an effort to make this a "non-technical" article in every sense of the expression.

At the same time, the coil L_2 , together with C_4 , and the upper portion of L_3 down to the antenna tap, must be considered a series-resonant circuit capable of conveying some power to the antenna. This is considered desirable. However, it has been found that we must be careful to tune to the proper frequency.

Looking at the "ip" network as a whole, C_3 ,

Looking at the "ip" network as a whole, C_3 , C_4 and L_3 form a network having paralleiresonant characteristics. Its tuning will be affected by C_3 and C_4 and also the setting of the taps on L_2 and the loading presented by the antenna system. One begins now to see the flexibility built into the combination as it has evolved. Since L_3 can be made plug-in, its value can be any reasonable one, and the taps can be placed anywhere on the coil.

Applications

Let us now come to the application of this circuit and evaluate results in practical terms. It was found, at first, that most of the possible-adjustment combinations resulted in curves such as shown in Fig. 2. The point where resonance

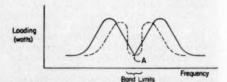


Fig. 2 — Improper tuning of the "pi-ip" coupler will result in a "V" (solid line) or "M" (dashed line) characteristic. The point of minimum loading, marked "A," is called the "trap" or "suck-out" point, and is to be avoided.

was obtained for the final resulted in very light loading in the desired band. Some adjustments, of course, were found that gave very high loading. Most of these, however, gave very poor results and, after much testing and measurement, it was found that the trouble was an overly large fraction of the available r.f. flowing into L_2 , C_3 , and L_3 and going to ground. As this trouble had occurred often before with many types of output circuits, no special blame was put on the "ip"

¹ Strictly speaking, an imaginary of this type calls for a j factor, and should therefore be written "jip." However, the j is omitted here in the interests of simplicity. — Ep.

network, but precautionary procedures to guard against this condition must be used.

At the present time, some experience has been gained in the adjustment of the "pi-ip" net to permit very useful operation. Fig. 3 is representative of the best results obtained so far.

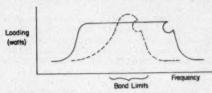


Fig. 3 — Proper tuning gives a broad coupling characteristic or a narrow one (dashed line), either of which can be adjusted to fit the band.

If the adjustment gives too flat a "top" to the curve, the best results will fall outside the band. However, because of the interacting nature of tuning C_3 and C_4 , the width of this flat top can be controlled.

Results

When we began to get good reports using our newly-developed system, we then took several very exact plots on the frequency response using an ancient-but-accurate R-meter in combination with a Quite Stable Amplifier No. 5 built by a noted amateur manufacturer many years ago. S-meter readings could be expected to give comparable results.

All conditions of tuning that gave good reports turned out to conform with the curve shown in Fig. 4, the ideal of Fig. 3. The peculiar shaping of this curve and the unusual means of accomplishing it resulted in its being called the "S9"

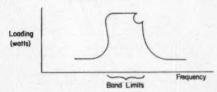


Fig. 4 — Perfect tuning of the coupler gives uniform loading across the entire band, with the exception of a residual suck-out point at the high-frequency end. In practice this is not too important,

curve. In achieving this we believe we have found what many amateurs are seeking.

This article has been hastily prepared so that as many as possible could take advantage of the experience gained so far. It is to be hoped that, in the near future, we can present a few more exact figures on performance and on the components to be used. In the meantime, we hope that every amateur station will report on its results with this loading method.

Full credit is given those amateurs in daily association with the author for the inspiration necessary for this article.

Suitable Relays for the Ultimatic Key

M any inquiries have been received asking about the feasibility of substituting relays other than those specified for the "Ultimatic" key (QST, February, 1953). Virtually any relay of 5000 ohms resistance or higher that can be adjusted to reasonable sensitivity and travel time will perform any of the functions in the Ultimatic. For example, the Potter-Brumfield LM11 10,000-ohm d.p.d.t. relay is satisfactory for K_1 - K_2 and K_3 - K_4 , and the Potter-Brumfield LM5 5000- or 10,000-ohm s.p.d.t. is suitable for K_5 , K_6 and K_7 . When relays are adjusted for other than 2-ma. operate/1-ma. release, R_9 , R_{14} , R_{20} , R_{32} and R_{25} must be modified to give a holding current halfway between the operate and release values.

When using relays of less sensitivity than the Sigma 4F, C_6 , C_7 and C_8 should be increased slightly for successful trip and release of the memories. R_{23} and R_{26} approximate the relay's resistance, although their values can be reduced somewhat to increase the relay pull-in current, if C_6 is increased. R_{24} must then be modified to prevent reverse-current hang-up of the memory relays on clearance. R_{21} must provide adequate current for the snappy closure of K_6 .

If high-current (3- to 6-ms. operate) relays are used, it may be necessary to increase the power-supply voltage to 200 or 250. Under these conditions, the cathode voltage dividers must be reproportioned, to give slightly more than cut-off bias for V_5 and V_6 with the bus grounded and a V_3 cathode potential equal to a bit more than V_4 plate potential plus cut-off for V_3 . With a higher supply voltage, the tube heaters should be tied to one-half the source voltage, and the time-base section should be fed 150 volts, regulated.

In the QST design, the time-base parameters were tailored so that the mark-space ratio of the multivibrator varies with speed to compensate for the mark-space ratio change with speed introduced by the finite armature travel time of the Sigma 4F relay (0.008-inch spacing, 2-ma. operate, 1-ma. release). Other relays, adjusted differently, would require modification of C_3 , R_5 and possibly R_1 . These changes should be checked with an ohmmeter connected across the output, watching the effect of speed changes on the mark-space ratio.

By splitting the wiring, removing the weight, and running the dot contact in to block the damper spring, a bug key can be used as an external control without any mechanical butchering.

— John Kaue, W6SRY




On the Air with SINGLE SIDEBAND

In the January issue this column reported that the then-current (September) roster of 75-meter s.s.b. stations showed a total of 237 stations. A new list, again compiled by W2SHN, W3ASW, W3KPP and W9DYV, and dated February 1st, shows 308 Ws, with 17 VEs and one KH6. The current group has W2 leading with 62, followed by 42 W9s and 41 W6s. The cellar honors still go to W5, with 10 representatives.

If Dick Long, W3ASW, hasn't worked the most s.s.b. stations it isn't from lack of trying. Since starting back in 1948, Dick has worked 300 different s.s.b. stations, which is probably the record at this time. But the actual number doesn't mean anything — what is noteworthy is the hours spent by pioneer stations like W3ASW in proving to the fraternity the worth and effectiveness of the mode, and the helping hands they offered to less-experienced operators.

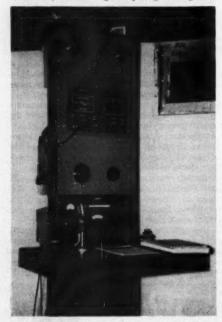Of course, everyone knows you have to be a radio engineer to use s.s.b. Granting that is a true statement, it's amazing how young the engineers



This is all there is to the s.s.b. station of Harold Gibson, W9PQO, at South Bend, Ind. A Multiphase Exciter drives a single 811-A amplifier to about 200 watts on peaks—the receiver is a 75A-2. Neat, compact, and effective.

are these days. For example, there is Tom Blakeslee, W9TAP, in Winnetka, 17. Latest reports had him active on 160 with a Multiphase Exciter and a TZ40 linear, when his daily work as a sophomore at New Trier High School will permit it. Tom is 14 years old — too young to know how tough s.s.b. is.

The Atlantic on 75 s.s.b. was a tougher nut to crack than was generally realized, but it has finally been crushed to smithereens. Possibly the first two-way was between W2PEO and OZ7BO on February 5th at 2245 GCT—at least it was almost certain to be the first OZ-W on 75 s.s.b. Dates are lacking on other contacts, but the Europeans getting across have included G3COJ, G3CWC, G3FHL, G3IMW and DL6WL. This side has been represented by W1IZY, W2JN, W2MTJ, W2SBI, W3BOL, W3QCM, W4IZL, W4MCL, W4NJG, W9UIT and VE1DZ, that we know of. The activity centers around 3800 kc, but the Europeans might be received a little better if they never went higher than 3790.

W2PEO has his sights set on working a VK or two on 75, but with no luck at this time of writing. Eric checks conditions by working VKs 5KO and 5JE on c.w. at 3510 kc., and he mentions that JJY, a 1-kw. Japanese frequency-standard station on 4000 kc., is a good indicator of band conditions. JJY must have fair strength before you hear anything but his carrier—when he comes up you can detect the 1000-cycle dash every second.

Bandpass Crystal Filter for Receiving

KP4HF, Braulio Dueão, of Mayagues, P. R., operates a.s.b. in the 14-Mc. band with a crystal-exciter rig. He uses a slick receiving stunt, shown in Fig. 1. It simply consists of

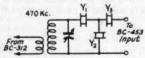


Fig. 1 — KP4HF adds selectivity between his BC-312 receiver and the BC-453 "Q5-er" by using this crystal filter.

Y₁, Y₃ — Channel 339 (470.833 kc.) surplus crystal. Y₂ — Channel 338 (469.44 kc.) surplus crystal.

adjacent-channel crystals used as a filter connection between his BC-312 receiver and the BC-453 "Q5-er." The crystals must be near or on the nominal i.f. of the receiver they are working out of, and the Q5-er is then set on them. The circuit tightens up the bandpass to about 1.3 kc., according to KP4HF.

A Different Balanced Modulator and Crystal Filter

The s.s.b. rig used by Ken Stone, W7BMF, has several novel features in the exciter. For example, the balanced-modulator circuit (swiped from Motorola) doesn't require push-pull inputs of any kind, an advantage or convenience in many cases. As can be seen from Fig. 2, the carrier voltage is applied to the cathodes in parallel, and the modulating voltage is fed to one grid. A similar circuit is also used to convert the 450-kc. output of this unit to the operating frequency — VFO output is fed to the two cathodes and the 450-kc. s.s.b. signal goes to one grid.

The crystal filter uses adjacent-channel crystals (Y1 and

The crystal filter uses adjacent-channel crystals (Y_1 and Y_2). Tests on a single section of the filter show about 35-db. rejection, and the two cascaded sections measure up around

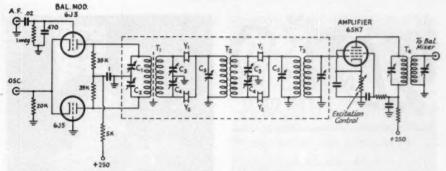


Fig. 2 — The balanced-modulator and crystal-filter circuit used by W7BMF. All transformers (T_1, T_2, T_3) and T_3 are standard types, with the phase-splitting condensers (C_1-C_3) added. These condensers are made of good quality mice in parallel with 50- μ_0 fd. air trimmers. The Faraday shield between the windings of T_1 is made by winding several turns of No. 18 d.c.c. between primary and secondary and grounding one end.

55 db. The filter was aligned with a signal generator, introduced at the audio-input terminal (oscillator turned off). The first step was to align all circuits to the mid-frequency between Y₁ and Y₂. The signal generator is then set to a frequency about 3 kc. higher (or lower), and C₃ and C₄ are adjusted simultaneously until a very sharp null is obtained. C₃ should be adjusted to the center of the passband, since improper adjustment will cause a large dip in response between the two crystal frequencies. It has been found that a 6-db. sag causes no impairment of voice quality, however, and it does improve the skirt selectivity. The adjustments may require several go-rounds, because they interlock slightly.

The final at W7BMF uses p.p. 807s, triode-connected with the grids and screens connected together and operated at zero bias. Plate voltage is 750.

A High-Powered Grounded-Grid Linear Amplifier

Ed Brown, W9ROQ, has a pair of 304TLs in his 14-Mc. output amplifier driven by the p.p. 811A rig in the Handbook. The 304s are in the grounded-grid circuit shown in

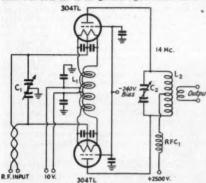


Fig. 3 — The 14-Mc. grounded-grid linear at W9ROQ uses a pair of $304 \mathrm{TLs}$.

C₁ — 100-µµfd.-per-section variable.

C₂ — 50-µµfd.-per-section variable.

All other condensers are 0.004-µfd. 600-volt mica.

All other condensers are 0.004-µfd. 600-volt mica. L₁ — 20 double turns No. 12 enam., wound on 1-inch

diam. form. L₂ — B & W HDVL-20. RFC₁ — R.f. choke (National R-175).

Fig. 3, and Brownie says it is about the most foolproof amplifier he ever tried. The 240 volts bias is obtained from a VR-150 and a VR-90 in series, and this holds the idling ourrent to around 100 ms. On peaks, the indicated plate current is around 300 ms. Parasitic suppressors were originally included in the plate leads but they were found to be unnecessary.

A Simple Audio Oscillator for Tune-Up

The trend certainly seems to be to build an audio oscillator into your speech amplifier, for quick testing and tune-up of the s.s.b. rig. Curt Smith, W6VCM, sends along the dope on the audio-oscillator circuit be built into the speech amplifier and voice-control circuit given in the s.s.b.

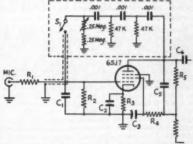


Fig. 4 — W6VCM added this audio test oscillator to the speech amplifier and voice-control circuit shown in the s.s.b. chapter of the current Handbook. It is turned on by S₁, mounted on the 0.25-megohm variable (pitch) control. Values not given are the same as in the original circuit.

chapter of the last several editions of the Handbook. As shown in Fig. 4, the only components needed to make this addition are a few resistors and condensers. The switch S₁ is mounted on the 0.25-megohm variable pitch control. With these constants, the frequency range is approximately 450 to 600 cycles, and different frequencies can be obtained with a different set of constants. The output is not constant over the range of adjustment of the 0.25-megohm variable, dropping off as the resistance is made lower.

Shifting Filter-Crystal Frequencies

Brian Bower, G3COJ, passes along a method for shifting crystal frequencies in the 450-kc. range (so-called "surplus" crystals — plated, in F7241-A holders). The scheme was given to him by GM3BEA, whose instructions are: "Make a dilute solution of copper sulphate in water—about ½ teaspoonful in a pint of water (½ teaspoonful inch in diameter). For small frequency shifts (a few hundred cycles), merely dip the crystal in the solution for 10 to 15 seconds (longer if necessary), take it outs, wash it and dry carefully in a current of warm air (e.g., over an electric fire).

(Continued on page 138)



BY ELEANOR WILSON, WIQON

Can We Interest You?

While preparing a little "sales talk" in the hope of interesting more YLs in working the very high frequencies, the thought occurred that it would be best to let some of the YLs well known in y.h.f. circles try to "sell" the idea themselves.

in v.h.f. circles try to "sell" the idea themselves.

Margaret Roberts, W8BFQ, winner of nine section awards in ten v.h.f. contests entered (national high scorer in the June, '52, affair), who has worked 41 states on Six and 21 states on Two, and who broke the world's 220-Mc. record last September by working W1HDQ (record since broken), seemed to sum up in one letter most of the thoughts of all of the girls contacted for the project, so we'll let Margaret do the first "commercial":

Remember 'way back, when everything "from 200 meters and down" was amateur territory? Well, perhaps it's very hard to sell an article until it's scarce, but I do hope you can help sell v.h.f. while there is plenty to go 'round. As for my story, all I can claim is enthusiasm, with maybe a little persistence [A little? — Eo.] thrown in. I'm neither a good rag-chewer nor an experimenter, and I have no scientific interest in radio, but I do have ful on v.h.f. I had fun on the lower frequencies also, but there's something about the very-highs — the friendly contacts, the exciting unpredictability, the freedom from QRM, the challenging ARRL v.h.f. contests. I've found the v.h.f. gang in general the most enthusiastic of all hams, and the good-fellow-

*YL Editor, QST. Please send all contributions to WIQON's home QTH: 318 Fisher St., Walpole, Mass.



W4UDQ uses an SCR-522 at 15 watts, a crystalcontrolled converter into an HRO and a "5-over-5" Yagi on 144 Mc. On 220 Mc. Dorothy has an 832 running at 20 watts, a 616 r.f. HFS-HRO receiving combination and a 32-element array.



W8BFQ operates 50, 144, 200, 420, 1215 and 2400 Mc. with inputs of 300, 800, 300, 50, 80 and 0.5 watts respectively. Margaret has worked seven states on 144-Mc. radioteletype and has earned DXCC, WAC and WAS on 28 Mc.

ship among them almost unbelievable. The v.h.f. contests furnish a lot of competition, but a lot more cofteration. Six-meter F-layer openings provided DX hunting as thrilling as any lower-frequency DX; sporadic-E openings were as exciting, and by reporting these openings to the Air Force through RASO I felt I was helping in a small way in the amateur tradition. I've watched the working groundwave range on two meters grow, stayed up all night during tropospheric openings, strained my ears over weak signals and raised my blood pressure to the danger point when "impossible" signals were arriving by auroral reflection. Working W1HDQ for the 220-Mc. DX record was a greater thrill than my marest DX on lower frequencies; and when W2QED's 420-Mc. signal came over the Alleghenies and he couldn't hear mine, I felt worse than if I'd missed AC4YN.

And so Margaret could go on and easily write several articles of her own filled with her experiences and reasons why she has been sold on v.h.f. Thoughts expressed in other letters received reinforce what Margaret has already said or implied.

Well-known W9DXX, Alice R. Bourke, who has worked some 325 different stations on two meters, writes that she likes v.h.f. "because of the high concentration of fine, friendly people who populate those frequencies."

WN9RUJ, Mary Meyer, a newcomer to v.h.f., is happy about the warm welcome the v.h.f. gang gives to new stations.

W4UDQ, Dorothy B. Wilson, knows that it's still possible to get excited over working a station only 75 miles away — if you're on 220 Mc.!

W8FMW, Ann Hughes, sums up the challenging surprise element in v.h.f. when she says that "you never know just what you are going to be able to do. Like fishing, you never know what you're going to hook. There is something about it (two meters) that you can't give up after you once get acquainted with the band."

Intrigued with the higher frequencies since 1933, W2FHJ, Viola Kapp, finds that "it is looking forward to the unexpected and freak conditions which holds the interest of the v.h.f. 'diehards'." Although Viola has worked 44 states on Six and 13 on Two and has regularly won v.h.f. contest awards, she uses low power and crystal control, using only one frequency on either two or six meters, thus proving what a simple, efficient rig along with a measure of stick-to-it-iveness can do on the higher frequencies.

And Marvel Sines, WSHUX, writes that she "has worked twelve states and many stations in Canada on Two. Of course, to those not having experience with v.h.f. that would not sound like very many. But when we work a new state on v.h.f. it is as much of a thrill as working a new country on some of the other bands. I wish more YLs and XYLs would get on. . . ."

Yes—we do too, Marvel. Sounds as if there's room, fun, and new experiences for all. See you in "the world above 50 Mc.!"

Keeping Up With the Girls

There are now some thirty Z86 YLs. . . . W3CDQ, Lis, has been Asst. Atlantic Division Director for better than twelve years. . . Ex-W\$CCK is now W5YRT. Maxine writes that there is one other YL at her new QTH (Tyler, Texas) and that her name is Maxine also (W5VSN). . . . W3AKB, Fran, and W3MSU, Ethel, are members of the Washington chapter of the newly formed Society of Women Engineers. . . OM W\$GMZ calls attention to the fact that the early call of the late May Smith was IBAE and not prefixed by a "W" as given in the Jan., '53, column. . . W9MGT, Lenore, reports more new very young YLs in her radio classes at the Browning School, Granville, Wisconsin (see Nov., '52, column) — WNS UCU, VAE and VCM, all age 9, and WN9VAP, age 14. . . And 14-year-old sister Helen is WN1WYT. . . VESDF, Mary, of Whitehorse in the Yukon Territory, enjoyed a visit with



W8FMW runs 250 watts to a home-built 2-meter transmitter and receives with a crystal-controlled converter ahead of a Super Pro. Ann's antenna is a 32element array.



W2FHJ has separate 829B rigs on Two and Six, 50 and 90 watts respectively. Viola uses a 6-element beam on 144 Me, and a 4-element affair on 50 Mc.

KL7CY, Flo, at Anchorage, Alaska... W4ITR is at present living in Baguio City in the Philippines. Ida, who worked 123 countries when in the States, is unhappy about a new ruling there which prohibits amateur operation by "aliene"... WN4WXF, Clars, is an enthusiastic new Novice from Antioch, Tenn... New officers of the Long Island Unit of YLRL are Pres. W2KDP; V. P. W2BXT; Sec.-Treas. W2JZX; Board, W2s KEB and GRQ.... The day after OM WN2IQW worked his first YL, WN3-URU, Sara, of Norristown, Ph., Doc answered a CQ put out by WN3URT, June, who turned out to be Sara's twin sister!... WSGJX's (Helen Cloutier, Escanaba, Mich.) new novel Sim Barton, Girl Radio Operator, has recently been released. The story of a girl's determination to achieve success as a commercial radio operator on a Great Lakes' ship, the book should be of interest to young girls who aspire to be radio operators.

Miscellany

The LARK (Ladies Amateur Radio Klub) of Chicago announces that a certificate will be awarded to any amateur (Continued on page 196)



The 2-meter equipment at W9DXX includes an SCR-522 transmitter, an AR-88 with VHF-152A converter and a 5-element Yagi skywire. Alice also has worked her share of DX on the lower frequencies.

Results-6th V.H.F. Sweepstakes

As it has in the five previous runnings of this popular event, the club award incentive brought out a large number of contestants. The tabulation of scores at the end of this department shows 385 reports, 20 more than in 1952, and an all-time high for a v.h.f. activity. This keeps the V.H.F. SS firmly established as one of the major ARRL operating activities, being topped in number of reporting contestants only by the Field Day, the regular Sweepstakes and the DX Contest.

Scores, the country over, were indicative of good activity, though there were no spectacular firsts or all-time highs in any particular field of endeavor. The country's top score was turned in by W2PAU, with 188 contacts on 6 and 2 meters, for a total of 3384 points. Just across the Delaware River, W3KKN was able to make 197 contacts, but he fell one section short of Brownie's 9, and so came up in second place, with 3152 points. The best single-band score was turned in by W3IBH, Philadelphia, who worked 183 different stations on 144 Mc. for 2928 points. Not many contestants reported work on 50 Mc. only, but of those who did, W1DJ, Winthrop, Mass., was top man, with 51 stations worked.

Scores are usually higher in the East, where large population centers and geographically small ARRL sections combine to make the numbers of stations and multipliers exceed those attainable in other sections. It is for this reason that competition is not carried out on a national scale. You compete only with others in your own section, and many scoring inequities are ironed out in this way. A glance through the tabulation will show that the top man in each ARRL section did an outstanding job in almost every case. Look at 120 contacts for W6TFZ in the Santa Clara Valley Section, or 107 for W6AJF in East Bay. One hundred and four contacts for 2496 points for W1RFU, 97 in Rhode Island by W1SGA, 78 and 90, respectively, in Western New York, for W2ORI and W2RUI, and many others with 50 or more stations worked show how well this party brings out the v.h.f. operators.

Among the clubs, it is usually a battle to the very end between the two giants of the Philadelphia area, the South Jersey Radio Association and the York Road Radio Club. This year the South Jersey gang pulled out in front by a substantial margin to win the silver-banded gavel for the highest club aggregate. A new club to place in the top three is the Nassau Radio Club of Long Island.

Though the club award guarantees a large turnout, there are many potentially strong clubs that never seem to participate. There should be at least twice as many entries in that column of club scores. It takes planning and coördination, but it's great fun — how about beginning now to have your club membership out in force for the next V.H.F. SS?

CLUB SCORES

Club	Aggregats	Certificate Winner
South Jersey Radio Association	. 30,493	W2PAU
York Road Radio Club	25,835	W3KKN
Nassau Radio Club	6721	W2GLU
Hartford County Amateur Radio Assn		W1PHR
Hampden County Radio Club	. 3426	WIRFU
Lake Success Radio Club	3154	W2BNX/2
Providence Radio Association	2908	W18GA
Waltham Amateur Radio Association		W2BVU
El Ray Radio Club	1526	WIAQE
San Mateo County Amateur Radio Club		W6TFZ
Northeast Radio Club	. 1190	WN3TYU
Old Colony Amateur Radio Association		-
Dayton Amateur Radio Association		W8LUZ
Rochester V.H.F. Group	. 782	W2OWF
West Side Radio Club	. 666	VE3AIB
Lakeland Amateur Radio Association	648	W2RQI
Philadelphia High Frequency Club	600	W3QAS
Sonoma County Radio Amateurs	204	-

In the tabulation to follow, the columns give the total score, the number of contacts made, the section multiplier, and the bands used, A being for 50 Mc., B 144 Mc., C 220 Mc. and D 420 Mc. No contacts were reported for any higher band. The club listing gives the combined club total and the call of the winner of the certificate for the highest individual score in the club. The first call in each section listing is the winner of a certificate award unless otherwise noted.

ATLANTIC DIVISION	W3IND 212- 53- 3-B
Eastern Pennsulvania	WN3UMI 212- 53- 2-B
	WN3ULC 204- 51- 2-B
W3KKN 3152-107- 8-A-B	W3GKW 200- 50- 2-B
W3UKI 3141-176- 9-A-B	W3QB 192- 48- 2-B
W3IBH 2928-183- 8-B	W3KD 160- 40- 2-B
W3PKJ 1230-123- 5-B	W3RAA 160- 40- 2-A-B
W3BQY 1060-106- 5-B	W3SON 120- 30- 2-B
W3GRY 1056- 88- 6-A-B	W3BX 116- 29- 2-B
WN3TYX 1030-103- 5-B	W3SBD 104- 26- 2-B
W3RZU 960-120- 4-B	W3AYG 100- 25- 2-B
W3NXT 910- 91- 5-B	W3PNL 96-24-2-B
W3SAO 880-110- 4-B	W3KIY 76- 19- 2-B
W3IAU 816-102- 4-B	W3QV 60- 15- 2-R
W3QVK 714-119- 3-A-B	W31HF 28- 7- 2-B
W3SOB 688- 86- 4-B	W3BWQ1 1356-113- 6-B
W3MQU/3 678-113- 3-A-B	WN3TYK1 252-63-2-B
W3RFI 666-111- 3-A-B	
W3ANK 656- 82- 4-B	MdDelD. C.
W3NKD 630-105- 3-B	W3LMC 774-65-6-8
W3CLT 828-67-4-A-B	W3CGV 444- 57- 4-A-B
WN3TYU 492- 82- 3-B	W3RUA 336- 42- 4-B
W3KIW 486 81 3-A-B	W3RKQ 93- 16- 3-B-D
W3QXV 486- 81- 3-B	W3PZK 76- 19- 2-B
W3OCU 468- 78- 3-B	W3RAH 54- 9-3-B
W3AJF 432- 72- 3-A-B	W3BNC 54- 9-3-B
W3UMT 372-93-2-B	W3MIR 40- 10- 2-B
W3DJ 372-62-3-B	W3NH 32- 8- 2-B
W3SMK 344- 86- 2-B	W3VAM 16- 4- 2-B
W3NLL 340- 85- 2-B	W2PTM/M 2- 1-1-B
W3F8C 316- 79- 2-B	
W3A'-B 288-48-3-A-B	Southern New Jersey
W3QAS 230- 70- 2-B	W2PAU 3384-188- 9-A-B
W3DHH 268- 67- 2-B	W2QED 2080-130- 8-A-B-D
W3LVF 264- 44- 3-A-B	W2BV 1890-135- 7-B
W3HWV 232- 58- 2-B	W2JAV 1620-135- 6-B

W3WW

Wathe

Wakdh

220- 55- 2-B 216- 55- 2-B

216- 54- 2-A-B

1320-132- 3-B-D 1110-111- 3-B 944-118- 4-B

W2BLV

W2GLV

W2NFL

W2EWN	928-116- 4-B	W9USI	102-33- 3-B	W2EWI	462- 77- 3-B	W1TXM1	76- 19- 3-B
W2HMP	850- 85- 5-B	W9MBI	176- 21- 4-B-D	W2KQC	390- 65- 3-B		ern Massachusetts
W2SPV	750- 75- 5-B	W9ADO	96- 24- 2-B	W2DLO/2	366 61 3-B	WIAHB	1548-129- 6-A-B
W2REB	720-90-4-B	WN988I	96-24-2-B	W2ODB	300- 50- 3-B	WIAQE	1080- 10- 6-A-B
W2TJX	702-117- 3-B	W9PK	32- 8- 2-B	W2JXX	294- 49- 3-B	WiBJN	900- 90- 5-A-B
W2YT	696- 87- 4-B		Indiana	W2KIR	288- 49- 3-B	WIRUU	630- 63- 5-A-B
W2DAJ	618-103- 3-B	W0NJ8	610- 62- 5-B	W2IBQ	279- 47- 3-B	WICPB	560- 70- 4-B
W2KHW	612-102- 3-B	W9ORZ	156- 26- 3-B	W2AOD	276- 46- 3-B	WIQMN	544- 69- 4-A-B
W2CNI	582- 97- 3-B	W9BUM	56- 14- 2-B	W2CBQ	270- 45- 3-В	WIDJ	510- 51- 5-A
W2JRO	552- 92- 3-B		Wisconsin	W2FI	246- 41- 3-B	WIHIL	450- 45- 5-A-B
W2GQO	540- 90- 3-B	W9BTI	332- 42- 4-B	W2IFM	246 41 3-B	W1MCR	300- 50- 3-B
W2ADA	504- 84- 3-A-B	W9TQ	304- 38- 4-B	W2KAC	234- 39- 3-В	W1PYM	276- 46- 3-B
W2LBX	450- 75- 3-B	W9LJV	272- 34- 4-B	W2WCR	224 28 4-B	W1TQF	246- 41- 3-B
W2OQN	438- 73- 3-A-B	W9UJM	168- 21- 4-B	W2KEB	216- 54- 2-B	WIJSM	204- 30- 3-B
W2ZUL	438- 73- 3-B	WN9UEK	162- 27- 3-B	KN2BIC	216- 54- 2-B	W1RO	210- 21- 5-A
W2DMU	432- 67- 3-A-B	.W9YEG	138- 23- 3-B	W2JBQ	204- 51- 2-B	WIDPI	200- 20- 5-A
W2EXB	408- 51- 4-B	W9FAN	132- 17- 4-B	W2KAE	192- 48- 2-B	WILHV	192- 32- 3-B
W2UCV	372- 93- 2-B	W9LJV/AM		W2IN	186- 31- 3-B	WIOTH	128- 32- 2-B
W3LTC/2	362- 91- 2-B	W9NVK	76- 19- 2-B	W2IHQ	126- 21- 3-B	WIQQW	84- 14- 3-B
W2AUA	360-36-5-B	W9D8P	48-12-2-B	W2JCI	120- 30- 2-B 80- 20- 2-B	WILUW	46- 23- 1-B
W2HEK	318- 53- 3-B-D	W9WTL	30- 15- 1-B	W2TUK		WICTR	38- 19- 1-B
W2ABQ W2VX	300- 50- 3-B 300- 75- 2-B		as pungon	W2ZPG	80- 20- 2-B	WITVK	15- 8- 1-B
	288- 72- 2-B	DAKC	TA DIVISION	W2IQR	72- 9- 4-B	W1MGP/M	6- 3- 1-A
K2ANW W2FXT	280- 70- 2-B		Minnacela	W2BVL ² W2SOB	66- 33- 1-B 60- 15- 2-B	West	ern Massachusette
K2AFJ	260- 65- 2-B	WøQIN	208- 26- 4-A-B	W2CB	56- 28- 1-B	W1RFU	2496-104-12-A-B
W2PFQ	260- 65- 2-B	WøJHS	168- 21- 4-A-B	W2QBR	48- 24- 1-B	WiGJO	1368-114- 6-A-B
W2FGP	244- 61- 2-B	WØOAC	168 21 4-B	W2QBR W2LGK	48- 12- 2-B	WNIVNH	882- 49- 9-B
W2SDO	224- 56- 2-B	WøTKX	126- 21- 3-A-B	W2BZZ	46- 23- 1-B	WIESA	36- 9- 2-B
W2BGF	200- 50- 2-B	WØTJF	114- 19- 3-A-B	W2OGA	46- 23- 1-B	W1RVW	48- 8-3-A
W2PEN	196- 98- 2-B	WØHXY	96- 12- 4-B	W2ZWB	44- 11- 2-B		Rhode Island
W2KBR	184- 46- 2-B	-		W2ZWB W2TNI	42- 21- 1-B	W18GA	970- 97- 5-A-B
KN2AIS	180- 45- 2-B		EAT LAKES	W2VL	42- 21- 1-B	WIKCS	870- 87- 5-A-B
W2BAY	180- 18- 5-A		DIVISION	W2FDM	40- 20- 1-B	WIBIL	336- 56- 3-B
WN2OGZ	176- 44- 2-B		Kentucky	W2SPI	38- 19- 1-B	WIGBQ	270- 45- 3-B
W2080	172- 43- 2-B	W4PCT	228- 38- 3-B	W2UXY	36-18-1-B	WIVDI	188- 47- 2-B
W2TM	150- 15- 5-B	***********	Michigan	W2MFP	30- 15- 1-B	WIKKE	156- 39- 2-B
W2EET	140- 35- 2-A-B	W8GNN	232- 29- 4-B	W2HPH/M		WIUEF	135- 29- 3-B
W2OWA	132- 33- 2-B	W8UMI	192- 24- 4-B	W2EBY	20- 10- 1-B	WIVEM	128- 32- 2-B
W2ORA	120- 20- 3-A	W8DDO	153- 26- 3-B	W2OKX	18- 9- 1-B	WIQLD	92-23-2-B
K2BQW	108- 27- 2-B	WSDIV	120- 20- 3-B	W2JRL	14- 7- 1-B	WICN	64- 16- 2-B
W2AKI	72- 18- 2-B	WSIEE	102- 17- 3-B	W2PIB	14- 7- 1-B	WIAOP	60- 15- 2-A-B
W2FRJ	48- 12- 2-B	WN8JXU	48- 12- 2-B	W2BKX	12- 9- 1-B	WNIVAY	56- 14- 2-B
W2WKI	48- 12- 2-B	W8GYU	44 11 2-B	W2MIZ	12- 6- I-B	WINZR	20- 10- 1-B
W2PZX/2	44- 11- 2-B	W8BGY	40- 10- 2-B	W2ZUC	12- 6- 1-B	W1PAZ	12- 6- 1-B
W2DGN/2	32- 8- 2-B	WSNOH	10- 5- 1-B	W2BXT	8- I- I-B	WIKKR	8- 4- 1-B
W2UKU/2	28- 7- 2-B	Webro	Ohio -	W2FDU	8- 4- 1-B	W1BGM	8- 4-1-B
W2UNT	24- 6- 2-B	W8BFQ	896- 64- 7-A-B-C-D	K2ATV	6- 3- 1-B		Vermont
W2PTM/2	8- 4- 1-B	W8LPD	252- 42- 3-A-B	W2GG1	366 61 3-B	W10UZ/1	2- 1- 1-B
W2PZX	6- 3- 1-B	W8LUZ W8SVI	234- 39- 3-B 204- 34- 3-B	W2HNG1	198- 50- 2-B		1 200- 20- 5-II
W2UQ	2- 1- 1-B	W8BMO	198- 33- 3-B		thern New Jersey	WATE BALL	200 20 0 11
W	estern New York	WSSDJ	186- 31- 3-B	W2DWJ	2144-134- 8-B	NOR	THWESTERN
W2ORI	780- 78- 5-B-D	WNSKJT	168 - 28 - 3 - B	W2QNZ	1440 91 8-B	1401	DIVISION
W2RUI	720- 90- 4-A-B	WN8KQV	162- 27- 3-B	W2COT	1242-104- 6-A-B		Washington
W2ALR	480- 60- 4-B	WSLTT	112- 28- 4-B	W2AGL	670- 67- 5-B	W7IEE	56- 28- 1-A-B
W2CCR	288- 48- 3-B	WSLOF	102- 17- 3-B	W2RQI	472- 59- 4-B	W7KO	38- 19- 1-A-B
W2OWF	288- 36- 4-B	WSUEY	38- 10- 2-B	W2PEV	128- 16- 4-A-B	W7PXB	38- 19- 1-B
KN2ALZ	264- 44- 3-B	WN8MCW	22- 11- 1-B	W2DZA	114- 19- 3-A-B-C	W7AX8	24- 12- 1-A-B
W2SFW/2	132- 22- 3-B	W MODILO W	44-11-1-11	KN2AIO	48- 12- 2-B	W7BB4	12- 6- 1-B
W2UTH	128- 32- 2-A-B	HUDS	NOIBIVID NO	****	mon punctos		
W2TBD	120- 30- 2-B		tern New York	MIDW	EST DIVISION	PACI	IFIC DIVISION
W2ZHB	108- 27- 2-B	W2PCQ	784- 56- 7-B		Missouri	~ ~ ~ ~ ~	nia Clara Valley
W2QY	92- 23- 2-B	W2BVU	584- 37- 8-A-B	WeIHD	12- 3- 2-B	WeTFZ	1200-120- 5-B
W2ELS	84-21-2-B	W2PV	290- 20- 7-B	2000	IN THAT IND		850- 85- 5-B
W2VVG	80- 20- 2-B	W2ACY	180 18 5-B	NE	W ENGLAND DIVISION	W6CGA W6ZBS	180- 18- 5-A-B
W2UVF	64- 16- 2-B	W2RTE	150- 25- 6-B			W6ZTJ	72- 12- 3-B
W2YIE	34- 17- 1-B	W2KQ	2- 1-1-C	W-1170*	Connecticut	W6LMN*	72- 9- 4-B
W2UAD	32- 16- 1-B		V. Y. CL. I.	W1HDQs	2046- 93-11-A-B-D	WePBV	6- 3- 1-B
W2UY8	32- 16- 1-B	W2AOC	2320-145- 8-В	WIPHR	516- 43- 6-B	MOTBA	
W2QHG	20- 10- 1-B	W2GMT	1820-130- 7-B	WIHDF	492- 33- 6-A-B-D	TET 4 4 400	East Bay
	296- 37- 4-B	W2DHB	1764-147- 6-B	WNIVLH	375-38-5-B	W6AJF	1070-107- 5-A-B-C-D
W2FCG/21	ern Pennsylvania		1135-114- 5-B	WIQBH	144- 36- 2-A-B-D	W6NHU	300- 50- 3-B
	case a commendation to our	W2GLU	1000-100- 5-B	WIVLK	128- 32- 2-A-B-D		San Francisco
Weste	72- 12- 2-B		865- 86- 5-B	WIRVZ	124- 31- 2-B	WN6MGO	114- 19- 3-B
Wash W3KWH	72- 12- 3-B 72- 18- 2-B			W1KOW	116 29 2-B	W6DTV	102- 17- 3-B
Wash W3KWH W3KWL	72 18 2-B	W2QAN			100 10 9 0	MODELA	
Wash W3KWH		W2QAN W2HG	700- 50- 7-B	WIOLG	108-18-3-B	WOOTW	103- 17- 3-B
WaskWH W3KWL W3CJF	72 18 2-B	W2QAN W2HG W2KFV	700- 50- 7-B 606- 87- 4-B	W10LG W1KHM	100- 25- 2-A-B	WOOTW	102- 17- 3-B
WaskWH W3KWL W3CJF	72- 18- 2-B 44- 11- 2-B	W2QAN W2HG W2KFV KN2BGM	700- 50- 7-B 606- 87- 4-B 696- 87- 4-B	WIOLG WIKHM WIRFJ	100- 25- 2-A-B 78- 13- 3-B	W6OTW Se	
Weste W3KWH W3KWL W3CJF	72- 18- 2-B 44- 11- 2-B RAL DIVISION	W2QAN W2HG W2KFV KN2BGM W2CET	700- 50- 7-B 606- 87- 4-B	WIOLG WIKHM WIRFJ WIRNT	100- 25- 2-A-B 78- 13- 3-B 64- 16- 2-A-B	W6OTW W6MIW	103- 17- 3-B scramente Valley 305- 31- 5-B
Woode W3KWH W3KWL W3CJF CENTI W9QXP	72- 18- 2-B 44- 11- 2-B RAL DIVISION Illinoia 366- 61- 3-B	W2QAN W2HG W2KFV KN2BGM W2CET W2BTA	700- 50- 7-B 606- 87- 4-B 696- 87- 4-B 696- 58- 6-B	WIOLG WIKHM WIRFJ WIRNT WIAW	100- 25- 2-A-B 78- 13- 3-B 64- 16- 2-A-B 60- 30- 2-A-B	W60TW W6MIW W60TN	102— 17— 3—B scramento Valley
Woode W3KWH W3KWL W3CJF CENTI W9QXP W9JGA	72- 18- 2-B 44- 11- 2-B RAL DIVISION Illinois 306- 61- 3-B 306- 51- 3-B	W2QAN W2HG W2KFV KN2BGM W2CET W2BTA W2IEJ	700- 50- 7-B 606- 87- 4-B 606- 87- 4-B 606- 58- 6-B 680- 85- 4-B	W10LG W1KHM W1RFJ W1RNT W1AW* W1VXJ	100- 25- 2-A-B 78- 13- 3-B 64- 16- 2-A-B 60- 30- 2-A-B 56- 14- 2-B	W6OTW W6MIW W6OTN WN6RZZ	102- 17- 3-B accumento Valtey 305- 31- 5-B 240- 30- 4-B 96- 12- 4-B
WaskWH WaskWL WacJF CENTI WagyP Wajga WagkM	72- 18- 2-B 44- 11- 2-B RAL DIVISION Illinois 306- 61- 3-B 306- 51- 3-B 270- 45- 3-B	W2QAN W2HG W2KFV KN2BGM W2CET W2BTA W2IEJ W2KDI	700- 50- 7-B 696- 87- 4-B 696- 87- 4-B 696- 58- 6-B 680- 85- 4-B 680- 68- 5-B 573- 96- 3-B	W10LG W1KHM W1RFJ W1RNT W1AW* W1VXJ W1BDI*	100- 25- 2-A-B 78- 13- 3-B 64- 16- 2-A-B 60- 30- 2-A-B 56- 14- 2-B 53- 13- 2-B	W6OTW S6 W6MIW W6OTN WN6RZZ S6	102- 17- 3-B acramento Valley 305- 31- 5-B 240- 30- 4-B 96- 12- 4-B a Joaquin Valley
Woode W3KWH W3KWL W3CJF CENTI W9QXP W9JGA	72- 18- 2-B 44- 11- 2-B RAL DIVISION Illinois 306- 61- 3-B 306- 51- 3-B	W2QAN W2HG W2KFV KN2BGM W2CET W2BTA W2IEJ	700- 50- 7-B 696- 87- 4-B 696- 87- 4-B 696- 58- 6-B 680- 85- 4-B 680- 68- 5-B	W10LG W1KHM W1RFJ W1RNT W1AW* W1VXJ	100- 25- 2-A-B 78- 13- 3-B 64- 16- 2-A-B 60- 30- 2-A-B 56- 14- 2-B 53- 13- 2-B	W6OTW W6MIW W6OTN WN6RZZ	102- 17- 3-B scramento Valtey 305- 31- 5-B 240- 30- 4-B 96- 12- 4-B



CONDUCTED BY E. P. TILTON, WIHDQ

The January success of Project Moonbeam, reported last month, was no one-shot proposition. With a fixed antenna, the opportunities for tests don't come too often, but W4AO and W3GKP were ready for another try on Feb. 20th, the next time the moon was in the right place. With W3GKP at the controls, a series of test transmissions beginning at 10:15 a.m. was made from W4AO. Optimum time for echoes was expected to be between 10:40 and 10:50, and it turned out very nearly that way.

Many moon echoes were received at Falls Church between 10:34 and 10:53. The peak strength of the returning signals was slightly lower than in January, and fading was more rapid and violent. Up in Dunmore, Pa., W3LZD was having the best results to date. Ted's reception of the moon-reflected W4AO signal ran from 10:37 to 10:43, reappearing briefly

at 10:49.

The release of information on the first successful amateur moon-reflection efforts, by means of W1AW Bulletins, nationwide ARRL press releases, and the story in March QST has caused widespread interest in further attempts at lunar DX. Many hams, it seems, have been working in this direction; quite a few of them with a good understanding of the difficulties involved. We offer the services of this department as a means of correlating effort. If you are working on a moon project, send us the information on your equipment and schedules. If there is sufficient response, we will arrange to supply interested workers with up-to-date information by mimeograph.

For those who would like to know more about what it takes to bounce a 2-meter signal off the moon, W4AO and W3GKP are in the process of compiling a comprehensive report on Project Moonbeam. We hope to have it for you in an

early issue of QST.

Here and There on the V.H.F. Bands

For years 6-meter men have wondered about the possibility of working Alaska on 50 Me. There was a KL7 on for one big week end back in 1947 when the F₃ m.u.f. was well above 50 Me., and he made plenty of contacts all over the United States, but there has never been anyone on up there since, at the right times for sporadic-B DX. Teletype circuits operating close to the 50-Me. band in the Pacific Northwest have been heard in many parts of this country and Canada, but so far as is known, no KL7 has been worked on 6 since the fall of '47.

Now we have prospects that something may be done about the lack of 50-Mc. KL7 DX this spring and summer. W8NQD, Ashland, Ohio, writes that W3JBB is Alaska bound, and equipment for 50 Mc. is ready to be sent to him as soon as he gets Air Force permission to operate.

The frequency will be 50.7 Me., to get him out of the lowend QRM, and provision has been made to key the transmitter automatically for beacon purposes.

In one way or another, W8NQD provides us with most of our 6-meter news this month. Tom was listening on 6 the evening of Feb. 15th when he heard a foreign-language station calling CQ. The signal was typical DX, with a pronounced ripple and considerable earrier instability, and though it was heard only briefly (around 10:58 r.m. EST) it was tentatively identified as Italian. (It was definitely not Spanish, though somewhat similar.) The operator was calling CQ, but no call sign was heard. The frequency was about 50.1 Mc. Can anyone help out on this one? Foreign DX reports are rare enough these days to be of real interest!

Lastly, Tom reports that the 6-meter operators of Asbland County have gotten out a neat little certificate, the object of which is to stimulate activity in the area. This will be sent to anyone who can show proof of having worked three or more Ashland County stations on 50 Mc. Send calls and time of contacts to Tom Stence. R.D. 3.

Ashland Ohio

At a time of year when 50-Mc. activity is at a low ebb in some quarters, it is refreshing to hear of groups that are working to promote greater use of this valueble portion of the spectrum. The Region 9 Amateur Radio Club (the area around Fitchburg, Mass.) has been particularly successful in this respect. Largely through the efforts of Wis GJO OOY BNO ACP GUI and EHH, there are now some 20 6-meter stations active, and more are in prospect. A v.h.f. night and hamfest in Fitchburg. February 20th, brought out more than 125 hams, mostly v.h.f. enthusiasts, from within a radius of 30 miles.

A newcomer to 50 Mc. in the Pittaburgh area is W3OHK. Art has been plugging away each Monday and Tuesday evening, but so far his only contact has been W3RUE, also of Pittaburgh. Art is on other evenings after 11:30 P.M. but has had no luck at this late hour to date. He expects to do all right when the band openings begin this spring, but in the meantime he'd like to hear from others within working radius, with a view to keeping regular

6-meterskeds.

The 6-meter band is working out nicely for civil defense communication in the Terre Haute, Indiana, area. WOZHL says that there are now 14 fixed-frequency f.m. mobile units on 50.6 Mc., and another fixed or portable station for Red Cross or c.d. headquarters use. The range, mobile to base station, is about 35 miles, and mobile to mobile is good for 15 to 20 miles. In addition, nine battery portables, similar to the one described in May, 1951, have been built. These are all on 50.12 Mc. at present. WOZHL wants it known that the big Turkey Run V.H.F. Picnic (that has developed into something of a national convention of v.h.f. enthusiasts) will be held this year on July 19th.

enthusiasts) will be held this year on July 19th.
Up in Regina, Sask., VE5JK is working on 50 Me. with
VE5CO in Moose Jaw. Tests have also been made between
Saskatoon and the two above cities, but no contacts have
been made as yet. Here's hoping these boys are on deck
when the spring band openings come along. VE5 contacts

are none too common on 50 Mc.!

W9QBH, Riverside, Ill., writes that he is compiling a directory of stations using fixed-frequency f.m. mobile or fixed-station gear on the v.h.f. bands. He will reproduce the list and send copies to anyone interested. The idea is to circulate this information so that fellows so equipped will be able to make maximum use of their mobile gear when traveling. Send details of equipment and frequency used to Robert J. Hajek, 495 Selbourne Road, Riverside, Ill.

Two-meter operation is on a nightly basis in northeastern South Dakota and northwestern Minnesota. The 9:30 p.m. schedule, started nearly five years ago, finds Wess BJV TI DID KQO and DXY calling in regularly. Wiss

V.H.F. Editor, QST.

DB ORE and CJS are also heard from frequently. Coverage up to 100 miles is solid around the clock, in any season, and the 3-meter band is superior to any other for this sort of work. WθRRN, South Dakota SCM, passes along this information in the hope that more operators will join in, and that others at distant points will aim in that direction. Good contacts over distances of 150 to 200 miles are considered normal, despite an average power of only 100 watts.

Tried the new closed-spaced open-wire u.h.f. TV transmission lines yet? Gonset now supplies half-inch spaced line, and W#TJF is making it in quarter-inch spacing.

2-METER STANDINGS

Z-M	7	-E-BC	STANDINGS		
	all			all	
States As		1600	States A		Miles
					Mitten
W1HDQ18			W58WV 7	2	-
W1IZY16	6	750	W5FBT 6		500
	7	1150	W5IRP 6		410
W1MNF14		600		2	200
W1BCN14		590	W5DFU 5	2	275
W1DJK18		520			
W1CTW12	4	500	W6PJA 3	3	1390
W1KLC12	4	500	W6ZL 2	2	1400
Diality W. an	-		W6W8Q 2	2	1390
W2NLY22	7	1050	W6NLZ 2	2	297
W2UK 21	7	1075	W6GCG 2	2	210
W2QED18	7	1020	W6EXH 2	2	193
W2AZL18	7	1050	W6ZEM/61	1	415
W2ORI16	7	830	W6GGM 1	1	300
W2PAU16	6	740	W6YYG 1	1	300
W2QNZ14	8	400		_	-
W28FK13	6	-	W8WJC21	7	775
W2DFV13	5	350	W8BFQ21	7	775
W2CET13	5	405	W8WRN19	7	670
W2UTH12	7	880	W8WXV18	8	1200
W2DPB12	5	500	W8UKS18	7	720
W2FHJ12	5		W8DX17	7	675
W2BVU12	4	260	W8EP17	7	-
			W8WSE16	7	830
W3RUE19	7	760	W8RWW16	7	500
W3NKM 19	7	660	W8BAX 15	6	655
W3QKI17	7	820			
W3KWL16	7	720	W9FVJ22	7	850
W3LNA16	7	720	W9EQC21	8	820
W3FPH16	7	-	W9BPV20	7	1000
W3GKP15	6	650	W9UCH20	7	750
W30WW 13	6	600	W9LF19	-	-
W3KUX12	5	575	W9WOK17	6	600
W3PGV 12	5	-	W9MBI16	7	660
W3LMC11	4	400	W9BOV15	6	ment.
			W9LEE14	5	780
W4AO20	7	950	W9AFT14	-	parent.
W4HHK19	6	710	W9FAN13	-	680
W4JFV18	7	830	W9UIA12	7	540
W4MKJ16	7	665	W9GTA11	5	540
W40XC13	7	500		5	760
W4IKZ13	5	650	W9DSP10	4	700
W4JFU 13	5	720			
W4CLY12	5	720	WØEMS 21	8	1175
W4JHC12	5	720	WNØGUD20	7	1065
W40LK12	5	720	WØIHD16	6	725
W4FJ12	5	700	WØNFM14	7	660
W4UMF12	5	600	WØZJB 12	7	1097
W4LRR 5	2	900	WØINI 12	5	830
			W#WGZ11	5	760
W5JTI14	5	670	WØOAC 11	5	725
	4	790	WøJHS 9 WøHXY 9	3	MARKET .
W5QNL10	5	1400	WØHXY 9	3	-
W5CVW10 W5MWW9	2	1180			
W5MWW 9	4	570	VE3AIB17	7	850
W5AJG 9	3	1260	VE3DIR14	7	790
	3	700	VE3BPB12	6	715
W5ERD 8	3	570	VE3AQG11	7	800
	2	780	VE1QY11	4	900
	4	-	VE3DER10	6	800
W5VY 7	3	1200	VE3BOW 8	5	520
	2	580	VE3QN 7	3	540
	2	950	VE3TN 7	4	480
		-	The state of the s	130	1

Either of these lines should be fine for 220- and 420-Mc. use, if the problems posed by rotatable arrays can be solved. One way of fastening the line in place is suggested by W#TF, who uses the standard insulated screw-eye fastener designed for TV installation work. Dick's quarter-inch spaced line will not permit use of these in the usual way (as a support for the polyethylene spreaders) but he finds that the mounting ring may be compressed so that the soft plastic insert clamps around the two wires. If this is done just below the spreader, the line is kept from slipping through the insulating mount. To keep the portion of the line between the last mount and the rotating portion of the array from shorting against the tower. Dick says that some fellows are covering the line with half-inch plastic tape, one thickness on each side, for the distance where there is danger of the line shorting to the metal tower. Flexible inserts of Twin-Lead may be used readily, as the impedance of the u.h.f. line is close to 300 ohms.

The 2-meter band can be "sold," Last month we reported that in crossband contacts with various 2-meter stations, while transmitting on 75, WGGFL, Green Bay, Wia., was able to receive on 2 solidly, while the fellows be worked had to battle QRM on his frequency. This sort of demonstration of the utility of 144 Mc. for extended-local communication has had a good effect, and several new stations are now using the band in the Green Bay area. W9s OPA HID and IKY are among recent arrivals. A new v.h.f. club has been formed, with 28 members at the start. W9GFL leub has deen formed, with 28 members at the start. W9GFL heard 19 different 2-meter stations during the last month of

operation.

W9LEE, Weetboro, Wis., reports that his skeds with
W9BBN, Grand Marais, Minn., now well into the second
year, are running about 95 per cent successful, well ahead
of last winter's record. This is a hop of more than 160 miles,
the northern half of which is over Lake Superior, making
it perhaps the northernmost path that is covered regularly
on 144 Me, in this country.

on 144 Mc, in this country.

The new 6AJ4 and 6AM4 tubes are working out well in r.f. amplifier service at 144 Mc, and higher. The January issue of I.R.E. Proceedings shows the 6AJ4 as a grounded-grid amplifier that provides 7 db, gain on 900 Mc, so the tubes should do OK on 420. W9KQX is getting good results with two 6AJ4s in a push-pull grounded-grid amplifier on 144 Mc. This arrangement is particularly well adapted to use with balanced lines. Balanced tuned circuits are used in both eathode and plate circuits, with the input and eathode tapped down in the former. The output is taken off through small fixed condensers tapped on the plate coil, and a balanced line runs to the converter input. The preamplifier is made on a copper plate, with the five grid terminals of each socket soldered directly to this chassis. A shield across the two sockets further isolates the input and output circuits.

Not much 420-Mc. operating news this month, but there is much talk. Our guess is that both 220 and 420 are going to see big things being done this apring and summer. W2QED reports that he has been able to make at least a few contacts each Thursday night on his 10 r.m. 420-Mc. schedules, and now he is trying Tuesdays, also.

schedules, and now he is trying Tuesdays, also.
W2GTY and W2UZR, near neighbors in Brooklyn, are
looking for 420-Mc. Q80s. One or the other calls CQ on
428 Mc. nightly at 2300, and at 1630 on Saturdays. Both
use converted BC-645s.

Here in West Hartford, W1QVF has a beautiful 4X-150A amplifier running straight through on 432 Me., driven by a 5994 (9903) amplifier. He is working toward TV operation. W1AVK, in Springfield, also has a TV rig about ready to go. W1VLK, Wethersfield, Conn., has gone to crystal control, having come on 432.9 Me., with an 832A tribler.

Out in Detroit, W8JXV is on the air with a flying-spot scanner and a 9903 final stage. A modified Mallory 101 TV converter is used for reception. He is working on a 5527 camera unit, that may be in operation before this appears in print. Another budding TV enthusiast is W2JAV, Hammonton, N. J.

On Using the 6.146 Single-Ended

In QST for November, 1952, W1JEQ described a pushpull amplifier for 144 Me. using a pair of 6146s. We know of many instances where this amplifier has been duplicated with good results, but some fellows who have tried to use a single 6146 on 144 Mc. have not been so fortunate. One



W0ZJB48	W4BEN 35	W8BFQ41
WØBJV48		W80JN39
WOCJS48	W5VY48	W8LPD37
W5AJG48	W5GNQ46	
W9ZHL 48	W5MJD46	W9ZHB48
W9OCA 48	W5ONS48	W9QUV48
W60B48	W5JT144	W9HGE 47
WØINI 48	W5ML44	W9PK47
W1HDQ48	W5JLY 43	W9VZP47
	W5JME48	W9RQM 47
W1CLS46	W58FW43	W9ALU47
W1CGY46	W5VV42	W9UIA45
W1LLL45	W5FAL41	W9UNS45
W1HM843	W5FSC 41	1100110
W1L8N 42	W5HLD40	W00IN47
W1DJ40	W5HEZ38	WøDZM47
***************************************	W5LIU37	WØNFM 47
W2AMJ 46		WØTKX 47
W2RLV45	W6WNN48	WØKYF47
W2MEU45	W6UXN 47	WØHVW45
W2IDZ45	W6ANN 45	WøMVG44
W2FHJ 44	W6TML45	WøJOL44
W2GYV40	W6IW841	WØTJF44
W2QVH38	W60VK40	WøJH843
W2ZUW35	W6GCG35	WØPKD43
W 221 W00	WOUCG00	WØIPI41
W30JU45	W7HEA47	White trees and
W3NKM 41	W7ERA47	VE3ANY42
W3MQU39	W7BQX 47	VE3AET38
W3RUE 37	W7FDJ46	VE1QZ34
W3OTC35	W7DYD 45	VE1QY31
W3FPH35	W7JRG44	CO6WW21
marrn	W7BOC42	XE1GE19
W4FBH 46	W7JPA42	ABIUE
W4EQM44	W7FIV41	Calle in bold-
W4QN44	W7CAM40	face are holders
W4FWH42	W7ACD 40	of special 50-Me.
W4CPZ42	W/ACD	WAS certificates
W4FLW42	W8N8846	listed in order of
W4MS40	W8NQD45	award numbers.
W40XC40	W8UZ45	Others are based
W4FNR39	W8CM843	on unverified re-
W4IUJ38	W8YL841	on unversised re-
W 11.03 38	W8RFW 41	ports.
	Want W41	

old hand who has made the 6146 tick in satisfactory fashion is WHIDF. Perhaps some of the tricks he employed will be helpful to others who want to use this popular bottle on 144 Mc.

Carl took on the 6146 when a local Novice-to-be brought him a rig he'd built. There was oscillation all over the place in this typical first attempt at transmitter construction, so WHHDF decided on a complete redesigning job. The result was the construction of the complete r.f. section on a copper plate, with a coaxial-line tank circuit for the 6146. Whether the coaxial plate tank contributes appreciably to the efficiency of the amplifier is debatable, but it does provide a highly effective method of isolating the input and output circuits. The outer conductor is a copper sleeve about 3 inches in diameter and 9 inches long, with rows of quarterineh boles drilled around the cylinder about a half inch from each end.

The inner conductor is a 5-inch piece of ½-inch copper tubing, with a slip-on plate cap at one end and a capacity plate at the other. The plate is separated from the flat end plate of the outer conductor by a thin sheet of polystyrene. Tuning is by means of a copper disk driven by a quarterinch shaft threaded through the outer conductor. A similar fixed plate is soldered to the inner conductor at the tube end of the line.

The 6146 socket is mounted so that the cathode connections can be soldered to the chassis in the most direct man-

ner possible. Neutralization is aided by capacity tabs soldered to the screen terminal and to the chassis. No other neutralisation was needed, though some layout variations may require plate-to-grid capacitance added to that inherent in the tube. Suitable capacitors for neutralising tetrodes have been hard to come by in the past, but the new lowrange plastic trimmers by Eric and others are practically tailor-made for the purpose.

Anyone thinking in terms of a half-watt driver stage for the 6146 amplifier is doomed to disappointment. Don't try to drive a 6146 amplifier on 144 Mc. with less than 4 or 5 watts output from the succeeding stage. This can be obtained from a 5763 doubler, but only if that stage, too, is adequately driven. This is a weak spot in many layouts. Don't try to skimp on the exciter stages, or plan on pushing exciter tubes to the limit of their capabilities on lower fre-

Tetrode amplifiers can be made to operate stably on 144 Me. A good check is to tune the plate circuit while watching the grid and plate currents simultaneously. If the stage is thoroughly neutralized, the plate current will dip to minimum and the grid current will rise to maximum at the same setting of the tank condenser. This is likely to be the most sensitive check on tetrode neutralization, and is preferable to the feed-through and no-plate-voltage grid-current reading tests more often used.



- April 1928
 . . . This month's editorial suggests cooperative DX-band subdivisioning to minimise anticipated QRM difficulties in international amateur communications.
- . . . ARRL Secretary Warner reports on much ground covered at the League's regular annual Board of Directors meeting held in late February.
- ... "Keying Master-Oscillator Circuits," by Beverly Dudley, 9BR, gives a discussion on the pros and cons of oscillator, amplifier, and oscillator-amplifier keying.
- . . . S. P. McMinn, 2WC, puts three Type 210 tubes to work in a crystal-controlled low-power transmitter capable of operation on four amateur bands.
- . . . James J. Lamb, 3CEI, furnishes constructional details on "A Portable Receiver" employing three tubes and covering 43.5 through 10 meters.
- . . . F. Austin Lidbury writes on "Easy Tuning in the Short-Wave Bands" and there appears an ARRL lab report on the newly available UX-250/350 tube.
- ... "Notes on the Design of Iron-Core Reactances
 Which Carry Direct Current," by D. E. Replogle, brings
 us word of late developments in this field.
- . . . R. C. Hitchcock, in "Designing Fixed Resistors," shows that the manufacturing of reliable resistance components is much more complex than meets the eye.
- "Variable A-, B- and C-Power from D.C. Mains" is readily obtainable if you follow the suggestions outlined by F. I. Anderson.
- . . . "Some Investigations of Short Waves at Nijni-Novgorod," by Wladyslaw W. Grzybowski, r1WX, gives us some details on the state of the art in the U.S.S.R.
- . . . The novel "Transmitter Without Transformers," by L. W. Hatry, uses two Type 171 tubes in a full-wave self-rectifying circuit.
- . . , A flash appears in the Communications Department to announce opening of the new ten-meter band for general amateur use.
- . . . A complete description of widely-worked 8DPO, Wheeling, W. Va., includes information on the station's effective two-tube multiband c.w. transmitter.
- . . . The Communications Department informs that ARRL Hq. station 1MK has moved to a new and more favorable location at Brainard Field, Hartford.

The Radio Amateur Civil Emergency Service

PART II — The Communications Plan, Station and Operator Authorizations

The Communications Plan

One of the knottiest problems in laying the groundwork for RACES is the preparation of the Communications Plan that must be approved through FCDA channels to FCC and back before any RACES authorizations can be issued. So far as RACES is concerned, this plan need not outline in detail all phases of c.d. communications planning for operation on the designated RACES frequencies. However, the plan, in order to qualify for FCC approval, must satisfactorily meet the requirements as stated in the regulations. The first thing to do is read them, and read them

carefully.

There have been many questions and much correspondence concerning this RACES Communications Plan, so let's dwell on it for a moment. The Communications Plan is by far the most important element of a RACES application and must be approved and on file at FCC before any authorizations whatsoever will be issued or even considered. The Plan comes first. Of the several which have been submitted so far, some have not been approved because of lack of detail. They are too vague, too general, show all too clearly that communications wise the local CD organization is not ready to go. Your RACES organization cannot proceed faster than the rest of your civil defense organization; that is, it cannot set up plans to provide communications for civil defense activities or installations until such activities or installations exist or are definitely planned. Thus, there is no use trying to get ahead with RACES by submitting a communications plan full of blanks cloaked in generalities. We amateurs, as amateurs, can do nothing to organize civil defense. We can only provide a radio communications service for a civil defense organization that exists or is well along in planning stages. If there is no civil defense, there can be no RACES. That much is a cold, hard fact.

FCDA has written up a "check list" for the RACES communications plan to assist in ironing out this problem, which has been one of the toughest ones for most communities to meet. Space does not permit its reproduction here, but we'll gladly send you a copy on request if you have not already received it through other channels. If all items in this check list are covered, there should be little doubt that the plan will be

approved by both FCC and FCDA.

Every well-organized community will have a civil defense plan. The plan may be included under one cover or under several, one for each phase, depending largely on the size of the community in question. Such plans are the culmina• Much of the confusion concerning RACES implementation which now exists stems from one principal cause failure to read the new RACES regulations carefully. This installment dwells on matters about which there is considerable uncertainty in the field. It may help you to understand the regulations, but we hope you will read them carefully first.

tion of the combined efforts of the various community civil defense heads, of which the communications officer is one. Radio and RACES will be worked into it, depending on the extent to which this is possible at the time the plan is devised. The Radio Officer, when preparing his Communications Plan for RACES, might use this as a basis, enlarging on it as required by the RACES regulations.


State Communications Plans

Some states have detailed civil defense communications plans already worked out and on file at FCDA. Others have their plans under way. Since RACES plans must be approved at state civil defense level, it is best to examine the state plan (if any) before filing your own, to make sure that nothing in your local plan contradicts anything in the state plan. This is particularly important in regard to assignment of frequencies, for a haphazard frequency-use plan could be disastrous in an emergency. In some sections of the country groups of states have gotten together on a uniform system of frequency allocations to avoid this, and this is all to the good.

More recently, FCDA has prepared a suggested nationwide allocation of RACES frequencies, based on the week-long December, 1951, Communications Conference and subsequent data from individual states. If a state communications plah does not exist, this does not necessarily mean that it is no use submitting a local plan for RACES. Neither FCDA nor FCC will turn down RACES Communications Plans simply because a state plan does not exist. However, compliance with the regulations concerning coördination and liaison of frequency usage with other nets in the area is most important [12.201 (i) (5)].

Certification of Radio Officer

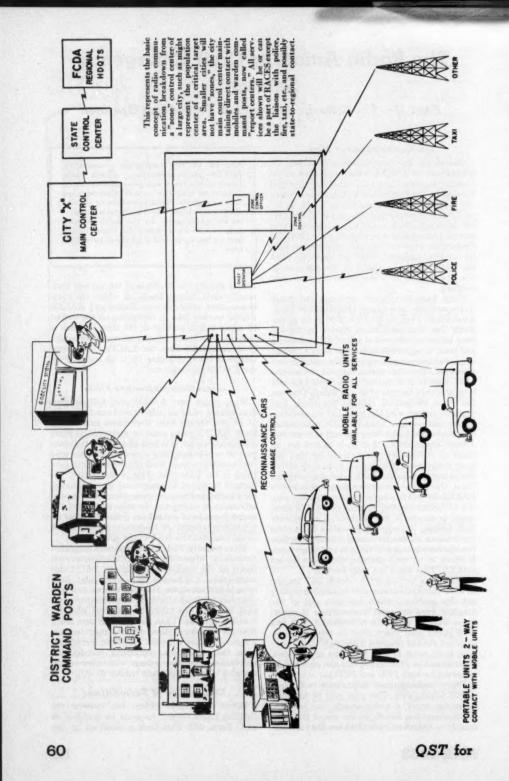Before the Radio Officer can become the RACES Radio Officer, he must be certified on FCC Form 482. This form is executed by the



local civil defense director and usually can and should accompany the local Communications Plan when it is submitted, but no RO certifications can be made until or unless the communications plan has been approved at all levels. So far as FCC is concerned, the filing of this form is informational; no approval or disapproval is involved. FCC merely wants to know who the RO is and that he has been investigated as to loyalty and reliability. The RO may be a licensed amateur of Conditional Class or better, or a commercial radiotelegraph or radiotelephone operator of first or second class. It goes without saying that 90% or more of them will be amateurs.

Station Authorizations

These are applied for on FCC Form 481 after or concurrent with submission of the Communications Plan and Certification of the Radio Officer. No new station licenses are issued; the presently-held amateur station license is simply made valid for RACES operation. Novice and Technician station licenses are not eligible to be made valid for RACES operation. FCC Form 481 is divided into three segments, labeled 481-1, 481-2 and 481-3. The applicant fills in only 481-1 (which must also be signed by the Radio Officer). FCC detaches this application, returns the RACES authorization (481-2) to the Radio Officer who detaches the stub (481-3) for his records before passing the station authorization along to the applicant. Once the Communications Plan and Form 482 have been approved at all necessary civil defense levels and are on file at FCC, applications for station authorizations should be submitted direct to FCC, referring to the approved plan in each application in the space provided. Such applications should be submitted in groups if feasible. Applications will be returned without action unless FCC has an approved RACES Communications Plan for that community or other local area (not state) on file. Authorizations at community level will not be issued on the basis of a state plan alone.

Some communities are preparing to operate their entire RACES establishment under a single station authorization. In such cases it is planned to have the Radio Officer (or other participating amateur) take out a separate station license other than his own, on the basis of communityowned equipment at a separate location. The community or whoever owns the equipment must assign technical control of the equipment to that amateur. All other station units in the local RACES organization will then operate as sub-units of that licensee under the RACES rules [12.245 (b)]. This plan has the advantage of simplicity in licensing, control and identification; that is, only one station authorization need be obtained, control is centralized in the licensee of that station, and identification is by unit number under a common amateur call.

1 In this discussion we shall use the term "community" to refer to any local area (not state) covered by a single

civil defense instrumentality. It might be a town, city, borough, county or group of counties.

This system of authorization also has the following disadvantages: (1) The licensee would bear the legal responsibility for operation of all station units. (2) If for any reason his license was revoked, or he simply withdrew, the com-munity would find itself completely without legal RACES station identification. (3) Each participating amateur would be required to subjugate his amateur identity - a disadvantage from the morale standpoint.

How best to seek RACES station authorizations is a matter entirely within the discretion of the radio officer. Between the two extremes mentioned above are many middle courses. For example, station authorizations may be obtained for a selected few amateurs (but not all available) and each one assigned a certain number of operators to operate whatever subunits are available. Or it can be left on a voluntary basis, each participating amateur being invited but not urged to apply for station authorization. Still another way is to have all amateurs (Conditional Class and higher) apply for station authorization, then assigning to each a certain number of non-amateurs (as or if required) to work with him toward operation of his station in RACES, and/or any subunits of his station; or the amateur could

pick his own non-amateur personnel.

In planning use of non-amateur personnel, let's have one thing understood; they do not operate anything anytime, except as a part of a specific drill or test promulgated by their RACES Radio Officer. Usually they will be required to follow a strict operating procedure, and always they are forbidden to touch the transmitting equipment (other than to turn it off and on). So far as RACES is concerned, this applies to Novice amateur licensees as well, and except for the restriction on adjusting the equipment, to Technician amateurs. During peacetime, the only difference between regular amateur operation and RACES operation is that in the latter certain non-amateur personnel may operate RACES equipment under the above restrictions. During wartime (or any other intensification of the present national emergency which causes to silence casual amateur operation) RACES will be the only amateur radio.

Operator Authorizations

FCC will issue no operator authorizations or licenses specifically for this service. Existing operator licenses of certain types will be considered sufficient authorization to operate in RACES provided they are supplemented by a certification of the local civil defense director indicating that the holder has satisfied the requirements outlined in the RACES regulations [12.241 (a)].

As mentioned heretofore, there will probably not be enough amateurs fully to implement RACES in most communities. As in WERS, a new source of operators must be tapped. Undoubtedly, those RACES groups which suffer from operator shortage will want to train the required personnel in the shortest possible time.

(Continued on page 140)

Simulated Emergency Test-1952

Sixth Annual Test Shows Progress from Past Years—Civil Defense Is Again the Theme

BY GEORGE HART, WINJM

DURING the month of October, 1952, 253
ARRL Emergency Coördinators are known to have put on some kind of Simulated Emergency Test of their local Amateur Radio Emergency Corps facilities and personnel. Some reported by mail, some by radio, some both ways. We know that there were many more groups active who did not report either way; perhaps 500 in all. This is still only a third of the total number of ECs, but each year we show a little progress; and today, with the emphasis on civil defense, we have to show a lot of progress.

defense, we have to show a lot of progress.

That the character of most tests revolved about civil defense is evidenced from the fact that of the 206 ECs who sent in mail reports, 107 of them indicated that operation was conducted partly or entirely on RACES frequencies, and many of those who stayed off the RACES frequencies to avoid QRM nevertheless were simulating an emergency brought about by enemy attack. Along with the reports came dozens of questions concerning getting set up for RACES, some of them thought-provoking, most of them answerable by close study of the RACES regulations.

As usual, publicity was favorable and there was lots of it. Most reports had newspaper clippings attached to them ranging from small items tucked away in the back pages to a two- or three-column front page spread. Most ECs have found inviting the press to the demonstration one of the best ways of exciting public interest and creating an awareness that amateur radio is really doing something of public benefit.

The turnover of SET reports from one year to the next remains high. Of the 206 mail reports, 85 also reported last year. This leaves 121 "newcomers," although some of them have reported in previous years. Of the 85 "repeaters," 50 bettered last year's scores and 32 fell behind. The total number of points accumulated nationally exceeded by considerable last year's total, although based on fewer reports this year.

* National Emergency Coördinator, ARRL.



The following figures are actual totals based on the 206 mail reports, with figures in parentheses being the comparable totals for last year (based on 214 reports):

n 214 reports);
Total mail reports of activity — 206 (214)
Total participation — 3012 (2757)
Participation reported by radio — 1106
Mobiles & portables — 1553 (1305)
Fixed stations on emergency power — 241 (254)
Messages from participants to EC — 2021 (1996)
EC radio reports sent to ARRL — 163 (173)
EC radio reports received at ARRL — 140
Total Points — 28,515 (24,114)

If we adjust some of the above figures to the 253 groups we know participated, we come up with what is probably a pretty accurate estimate of 3700 total amateur participation, 1900 mobiles or portables in action and 300 fixed stations on emergency power. Then if we get on our horses and assume that as many who did report their activity (either by mail or radio) did not report their activity, we make a wild-eyed and hopeful estimate of 7300 amateur participants, 3750 mobiles and portables, and 500 fixed stations on emergency power. If you think this is pretty rough guesswork (and we admit it), you ought to help see to it that your EC reports your SET.

For those of you who do not care for statistical pie, we can summarize the activity by saying that it was an improvement over last year. Not a big improvement, to be sure, but still an improvement, and that's what we are aiming for. Congratulations, gang, on bettering your 1951 SET performance! And now, take a look at the points tabulation which follows to see if your town, city, county or area is represented.

Allen Co., Ind. (W9EOG)	206
Amesbury, Mass. (W1ICU)	24
Androscoggin Co., Me. (W1SEJ)	141
Arlington, Mass. (W1BAQ)*	126
Atchison, Doniphon, Brown Co., Kans. (W#IWS)	64
Atlantic City, N. J., & vic. (W2CYI)	92
Augusta, Ga. (W4AAY)	78
Bakersfield & E. Kern Co., Calif. (W6EHN)	77
Bangor, Me. (W1OLQ)	134
Belleville, N. J. (W2JYW)	68

The Mayor of Jackson, Tenn., speaks to AREC members through the microphone of W4RKN/M, thus-illustrating an important use of mobiles—the ability to transmit "command" instructions to a large group of people simultaneously while on the scene of or engaged actively in an emergency operation.

Benton & Franklin Co., Wash. (W7OHS)	176
Bergen Co., N. J. (W2CVF). Berrien Co., Mich. (W8FGB). Bibb Co., Ga. (W4LXE). Billings Most (W7SAW)	818
Berrien Co., Mich. (WSFGR)	72
Bibb Co. Go. (W4LXE)	112
Billings, Mont. (W7SAW)	
	171
Black Hawk Co., Iowa (W@TWB)	170
Bonnam, Texas (World)	44
Bonham, Texas (W5RJM). Boonton, N. J. (W2RQI). Boulder City, Nev. (W7LGS).	87
Boulier City, Nev. (W7LG8)	126
Bristol, Tenn. /Va. (W4IYI)*	112
Brookline, Mass. (W1PST). Broome Co., N. Y. (W2FCG). Broward Co., Fla. (W4IM)*	121
Broome Co., N. Y. (W2FCG)	110
Broward Co., Fla. (W4IM)*	206
	26
	70
Caledonia Co., Vt. (WLJLZ)	53
Caledonia Co., Vt. (WIJLZ). Camden Co., N. J. (W2UCV). Canal Zone (KZ5RM).	124
Canal Zone (KZSPM)	
Camin Co. Idaha (W7UAU)	147
Cassia Co., Idaho (W7HAH)	23
Cedar Rapids, Ia. (WØHDX). Chambly & LaPrairie Co., Que. (VE2KG)	164
Chambly & LaPrairie Co., Que. (VE2KG)	115
Chester, Conn. (W1AOS)	- 1
Chippewa, Mackinaw & Luce Co., Mich. (W8III)	63
Chittenden Co., Vt. (W1QQN)*	126
Cincinnati, Ohio (W4NRA)	145
	35
Colo. Springs, Colo. (W#TV) Columbus & Franklin Co., Ohio (W8APF)* Concord-Walnut Creek, Calif. (W6TCU)	108
Columbus & Franklin Co. Obio (W&A PE)	297
Concord-Walnut Creek, Calif. (W6TCU).	
Cont. Co. Th. (Brottpeys	123
Cook Co., Ill. (W9HPG)* Crescent Bay Area, Calif. (W6ZFA)*	1030
Crescent Bay Area, Calif. (W6ZFA)*	348
	160
Dade Co., Fla. (W48KC)*	184
Dallas Co., Texas (W5LEZ)	111
Dane Co. Wie (WOTPS)	135
Danbury, Conn. (WIADW)*. Daytona Beach, Fla. (W4RWM). Dedham, Mass. (W1SH)*.	71
Daytona Beach, Fla. (W4RWM)	79
Dedham, Mam. (W1SH)*	90
Dekalb & Fulton Co., Ga. (W4EYQ)	190
DeLand & W. Volusia Co., Fla. (W4WS)	
Delaware Co., N. Y. (W2RZP)	54
Delaware Co., N. I. (WZRZP)	62
Delmar, N. Y. (W2GTI) Denwer, Colo. (WØGQY)	1
Denver, Colo. (WØGQY) Detroit Metropolitan Area, Mich. (W8WFA)*	171
Detroit Metropolitan Area, Mich. (W8WFA)*	2243
Dresden & Weakley Co., Tenn. (W4FLW)*	50
Duluth, Minn. (WØHRY)* Dumont, N. J. (W2NCY)	132
Dumont, N. J. (W2NCY)	191
Eads, Colo. (WøKHQ)	15
Eau Claire Co., Wis. (W9MUM)*	132
East Haddam, Conn. (W18UD)	22
Enfield Conn (WILEP)	54
Enfield, Conn. (W1LEP) Erie Co., Pa. (W3QN)*. Eureka Area, Calif. (W68LX)*.	158
Purch Asse Calif (Wall Va	
Fanwood, N. J. (W2NXP)	116
Fanwood, N. J. (WZNAP)	29
FOR WARREN, FIR. (WHI LAS)	
Fort Worth, Texas (W5ARK)	108
Frederick, Md., & vic. (W3WN).	27
Genessee Co., N. Y. (W2UVF)	60
Frederick, Md., & vic. (W3WN). Genessee Co., N. Y. (W3UVF). Great Falls, Mont. (W7DSS). Green Bay, Brown Co., Wis. (W9WLZ)* Greene Co., Ill. (W9IFA).	43
Green Bay, Brown Co., Wis. (W9WLZ)*	145
Greene Co., Ill. (W9IFA)	38
Groton, Conn. (W1CUH)	77
Groveland, Mass. (W1MRQ)	39
Guavama P R (KP4CP)	60
Cuifford Conn (WIDM f)	77
Guayama, P. R. (KP4CP) Guilford, Conn. (W1RM F) Hamilton, Ont., & vic. (VE3KM)	
Wannell Man (W.OTA)	130
Haverbill, Mass. (W18TA)	57
Herkimer Co., N. Y. (W2PYC)*	55
Holyoke, Mass. (W1CJK)	79

^{*}Bettered last year's score.

W2GNP operates a local AREC station at the Baldwin office of Civil Defense, Baldwin, L. I., N. Y., during the Simulated Emergency Test.

April 1953

Howard-Martin Co., Big Spring, Texas (WSAW)	60
Hughes Co., Okla. (W5ADC)	24
Imbella Co., Mich. (W8YNG)	39
Jackson, Tenn. (W4GEH)*	174
Jackson Co., Mins. (W5LBY)	97
Jay Co., Ind. (W9OAC)	35
Jersey City, N. Y. (W2NGX)	130
Joplin, Mo. (WøFKM)	41
Kankakee Co., Ill. (W9ILW)*	162
Kapunkasing, Out. (VE3AVS)	22
Kearney N. J. (W2LSH)	80
Kearney, N. J. (W2LSH) Kenosha Co., Wis. (W91LR)	75
Kent Co., Mich. (W8FCP)*	181
Kinga Co., Brooklyn, N. Y. (W2BIV)*	259
Kingsport, Tenn. (W4CBU)*	123
Kitsap Co., Wash. (W7HAD)*	112
Knox Co., Tenn. (W4HHQ)	71
	88
	225
Lake Co., Ind. (W9KRJ)	
Lancaster Co., Pa. (W3GJA)	143
Lebanon Co., Pa. (W3OTI) Litchfield, Conn. (W1ODG)	125
Litchfield, Conn. (W10DG)	72
Long Beach Area, Calif. (W6N8X)	289
Los Angeles & Les Angeles Co., Calif. (W60NI)	53
Luserne Co., Pa. (W3DUI).	48
Madison Co., Ill. (W9DJG/THB)	346
Madiron Co., N. Y. (W2RXW)	43
Marion Co., Ind. (W9KAS)	159
Melbourne, Fla. (W4PLZ)	43
Mercer Co., Pa. (W3CJF)	65
Mercer Co., Pa. (W3CJF) Memphia, Tenn. & vic. (W4BAQ)*	224
Merrimack Co., N. H. (W1BXU)	172
Mismi Co Obio (WOTHI)	79
Middleboro, Mass. (W1FEC)	51
Middleboro, Mans. (W1FEC) Midland Co., Mich. (W8BVY)	119
Middletown, R. I. (W1TRX)	72
Milwaukee, Wis. (W9RUF)	408
Minneapolis, Minn. (WØMXC)*	299
Missoula, Mont. (W7COH)*	72
Missoula, Mont. (W7COH)* Monroe, La. (W5MWE)	. 54
Monroe Co., N. Y. (W2QY)	172
Monroe Co., Ill. (W9ICF)	43
Montreal, Que., NW Section (VE2AFT)	105
Montreal, Que., SW Section (VE2XZ)	109
Morgan & Noble Co., Ohio (W8LG)	76
Morgan Co., Ala. (W4BFM)	23
Morgan Co., Ind. (W9DUD)	80
Muskingum Co., Ohio (W8GUZ)	108
Myrtle Creek, Ore. (W7OLU)	44
Nashville-Davidson Co., Tenn. (W4AY)*.	146
Nashville-Davidson Co., Tenn. (W4A1)* Neenah-Menasha. Wis. (W9GJY)	
	84 59
Newburyport, Mam. (W1RZZ)	
Newcastle-Henry Co., Ind. (W9MBL)	60
New Bedford, Mass. (W1AVY)	73
New Britain, Conn. (W1AYY)	34
New Port Richey, Fla. (W4KJ)* Newton, Mass. (W1EK)	39
Newton, Mass. (W1EK)	77
Niagara Co., Lockport, N. Y. (W2ZOC)*	181
Norwich, Conn. (W1EBO)	82
Oak Ridge, Tenn. (W4NDE)	176
Ogden City & Weber Co., Utah (W7GPN)	78



Fourth 10-Meter WAS Contest Results

PINIONS on 10-meter band conditions for the first two week ends of this past December are completely in accord. The most descriptive (and mildest) comment was from W9JYJ, "Band openings were poor and scattered. . . ." Infrequent openings and erratic conditions cut down considerably on the number of reports received for this fourth annual 28-Mc. activity. The largest number of logs turned in, sectionwise, came from the State of Washington. High scorers, however, represented scattered areas indicating pretty similar operating conditions.

Let's get down to facts! While competition is based on entries vithin an individual section, high interest is generally shown about those entrants making the highest over-all scores. Who worked the most states? W7PUM, Warner Thompson, of Arizona, came up with four more states than in 1951 for a total of 42. Closely following him was W4PJU of Clewiston, Florida, with 40 states worked. Two West Coast entries, W7BGH and W6MLW, tied for third-place honors with 37 states apiece.

High scorer? Leading for the third consecutive year was W7PUM with a total of 14,994 hard-toget points. W7BGH from the State of Washington placed second with 8584 points. Pointwise, W4PJU placed as third high scorer with 7880 points, and a WAS contest newcomer, W6MLW, was close behind with 7585 points.

How did your score compare with the leaders in the most active call areas? Let's see

THE PARTY WATCHES COUNTY OF LABOUR CR	I COMP : ANC U D DUC :
W1TMA1440	W6MLW 7585
W2LOD968	W7PUM 14,994
W3RVM3780	W8AJW2142
W4PJU7880	W9JYJ1736
W5OUT 6195	

Comments

"Conditions on both week ends were very poor for us W1s. During the entire contest we had two very poor openings that lasted for about 10–15 minutes." — W1AOQ. "... Worked over 110 locals. Boy they sure came out and provided the contacts!" — W6BUR. "Too bad that the good short skip was a week late. Could have added about ten more states." — W8PNJ. "Over half



of the stations worked were ground-wave locals, giving a pretty good idea of what band conditions were like." — W6ORD."... The real low point of the contest was on December 7th when I listened for 30 minutes to California stations discussing the sad fact that the band folded up so soon!" — W9KLR."... No signals other than local were heard during the whole week end (second). Ten-meter openings so far this winter have been few and far between." — VE2KG. "Youse boids been punchin too mni holes in the ionosphere — it's tired!" — W6VPV [whose log measured approximately three feet].

SCORES

Scores are grouped by Divisions and Sections. . . . The operator of the station first-listed in each Section is winner for that Section. . . . Listings show score, number of contacts, number of states worked.

ATLANTIC DIVISION	GREAT LAKES DIVISION
Eastern Pennsylvania	
W3RVM3780-210-18	Kentucky
W3PQB2780-139-20	W4SMU 567- 63- 9
W3MQC2032-127-16	Michigan
W3QOR 1360- 80-17	
W3OCU 935- 85-11	W8RXY1260-105-12
	W8KNR 371- 53- 7
Maryland	W8IFO 344- 43- 8
W3EF1442-103-14	W8NOH 264- 33- 8
W3CVW1155- 77-15	Ohio
W3OSF 315- 35- 9	W8AJW2142-126-17
Southern New Jersey	
	W8PNJ
W2DMR 644- 46-14	W8KC 168- 24- 7
	W8hC 108- 24- 7
Western Pennsylvania	
W3QN 270- 30- 9	HUDSON DIVISION
W3LXE 40- 8-5	Eastern New York
	W2LOD 968- 88-11
CENTRAL DIVISION	
Illinois	New York City & Long Island
W9JYJ1736-124-14	W2KZE 207- 23- 9
W9CCH 581- 83- 7	W2EEY 12- 6- 2
W9NII 336- 42- 8	W2NNB 9- 3-3
	V 44 - V - I
Indiana	Northern New Jersey
W9KLR 910- 65-14	W2DJT 275- 25-11
Maria Carlo	K2BCK. 30- 6- 5
Wisconsin	W2EQS 14- 7- 2
W9VHA 200- 40- 5	
W9RQM 175- 35- 5	MIDWEST DIVISION
W9AQD 128- 32- 4	Mimouri
DELTA DIVISION	WØMCX 24- 8-3
Louisiana	
W5PXW1360- 68-20	NEW ENGLAND
	DIVISION
Tennessee	Connecticut
W4VJX2210-130-17	W1TMA1440- 90-16
W4WLH1400-100-14	W1AJO 350- 35-10

Meet John Stephens, W3RVM, leading both the Eastern Pennsylvania section and the W3 call area entrants with 3780 points.

W1UFW 176- 44- 4 W1UCA/1 50- 28- 2	South Carolina W4UUB
Eastern Massachusetts	
· W1VPR1 364- 91- 4	Virginia
W10NV 345-115- 3	W4RQK1032- 86-12
W1PLJ 46- 46- 1	W4UHG 484- 44-11
New Hampshire	SOUTHEASTERN
W1AOQ1012- 92-11	DIVISION
Rhode Island	Eastern Florida
W1GBQ1417-109-13	W4PJU7880-197-40
WIGDQ	WILLI
NORTHWESTERN	W4TRA2150- 86-25
DIVISION	W4RRK1206- 67-18
Idaho	W4DRK 80- 16- 5
W7PCZ1880- 62-25	Georgia
Oregon	W4SCU4450-178-25
W7OVA3836-137-28	West Indies
W/UVA3539-137-25	
Washington	KV4AZ 322- 23-14
W7BGH	SOUTHWESTERN DIVISION
W7PHG2448-102-24	Los Angeles
W7PQE1540- 70-22	W6CZL4061-131-31
W7JVF 105- 21- 5	W6AEO3038- 98-31
W1SIC/7 22- 11- 2	W6NSV2033-107-19
	W6NJU 600- 75- 8
PACIFIC DIVISION	W6LYG 3- 2-1
Nevada	Arizona
W7K105814-171-34	W7PUM14,994-357-42
East Bey	W7ENA 741- 39-19
W6EFD4104-171-24	San Diego
San Francisco	W6MLW7585-205-37
W6BUR6420-214-30	W6EYF3596-116-31
11 045 0.1	W6ORD 3224-124-26



San Joaquin Valley

W6VPV 5880-168-35 W6NCG 5145-147-35

ROANOKE DIVISION

W4KE..... 30- 6-5

North Carolina



W6MLW, San Diego Section and California high scorer, relaxing from the strains of the WAS Contest while operating mobile. Home-station transmitter used during the contest ran about 150 watts input.

Southern Texas	New Mexico
W5OUT6195-177-35	W5NXF
W5PRO4890-163-30	CANADA
W5QXZ3960-120-33	Quebec
W5UBN1350- 75-18	VE2KG 138- 23- 6

Errors in scoring consisted, for the most part, of claiming credit for both Maryland and Washington, D. C., as state multipliers and failing to interpret contest rule No. 1, which declares as eligible only those amateurs in the sections compromising the field organization of the League. This would eliminate DX and maritime-mobile stations in scoring. (U. S. possessions in the Pacific are counted as the Pacific Division, however.)

A-Strays 3

W6ORD......3224-124-26

WEST GULF DIVISION

Northern Texas

W5SUD......3498-159-22

W5SFW......1335- 89-15

W5QF..... 330- 30-11

If your city is named Aberdeen - there are several in the U.S. - you may be in line for an honorary membership in the Aberdeen Amateur Radio Society. This goes along with a certificate the society is awarding to any amateur who contacts four or more A.A.R.S. member stations in 1953, marking the coronation of Queen Elizabeth this year.

TVI LECTURE

At 8:00 P.M. on Friday, May 1st, Phil Rand, W1DBM, ARRL Technical Consultant, assisted by Lewis G. McCoy, W1ICP, of ARRL's technical staff, will give another in his series of talks on TVI problems. This special meeting, to be held under the auspices of the Amateur Transmitters' Association of Western Pennsylvania, will take place in the auditorium of the Allegheny High School on Sherman Avenue, North Side, Pittsburgh. Amateurs, radio and television servicemen and their friends are invited.

Silent Keps

It is with deep regret that we record the passing of these amateurs:

W1FRP, Everett H. Gray, Westport, Mass. W2CCO, Joseph Bush, Irvington, N. J. W2HDK, Clifford E. Friend, Elmhurst, L. L. N. Y. W3GQ8, Charles B. Ware, Langhorne, Penna W5MR, Robert L. Rolfe, Dallas, Texas W58YD, Robert G. Hoover, Lawton, Okla. W5UAA, W. Lynn Wilson, Little Rock, Ark, W5UK, Charles A. Freitag, New Orleans, La. W6BVK, Wilbert V. Falck, Sacramento, Calif. W6GON, Hugh E. Green, Baldwin Park, Calif. WTPQA, Noel J. Halliday, Provo, Utah WNTRUQ, Elsa O. Derthick, Maupin, Ore. W8AHN, N. Guinn Warnock, Portsmouth, Ohio W8RJG, James K. Keathley, Huntington, W. Va. W8SLO, Elmer J. Byard, Cincinnati, Ohio W9MUC, Charles Weber, Park Ridge, Ill. W9NMY, Edmund Z. Vitkauskas, Collinsville, Ill. WAANZ, Louis F. Leuck, Lincoln, Nebr. VE3QS, Perey C. Organ, Toronto, Ontario VE4AM, A. W. Morley, St. Vital, Manitoba



Amateur-Naval Reserve Cooperation

The Lancaster Radio Transmitting Society holds monthly meetings at the Naval Reserve Training Center, Lancaster, Peana. In cooperation with the Naval Reserve, the society also holds weekly emergency communications drills at the center. The call KSNRL is used with fixed, portable and mobile equipment available to the society during drills. The equipment is also available for use in the event of local disaster. The society plans to conduct classes for prospective amateurs at the training center under the supervision of W3KKG. Members are W3s GJA KKG OY PTD and SNI.

Naval Reserve Liaison

The District Reserve Electronics Program Officer, Sixth Naval District, and the ARRL's South Carolina Section Communications Manager have worked out a program of providing assistance to local amateurs in eliminating harmonic radiation. In several instances the second harmonics of local Novice stations have been logged on 7455 kc. by the local Reserve Master Control Station. When this occurs, the calls of the stations concerned are forwarded to the SCM. The latter notifies the amateurs and offers assistance in eliminating the harmonic radiation. In cases where a Reserve electronics unit is near by, the amateurs are invited to visit the unit and request technical assistance.

Here and There

K5NRZ, the Naval Reserve Electronics Facility at Shawnee, Oklas, conducts a weekly radio class for prospective amateurs. The class is held on Saturdays under the supervision of W5HQ, C. I. Cunningham, ETC, USNR.

K6NAK, Naval Reserve Electronics Facility, Chico, Calif., is the meeting place for Electronics Division 12-10. W6GUV, Lt. W. E. Roberts, USNR, is commanding office. Other amateurs associated with the unit include W6MWR, Fred Will, Jr., ET2, USNR, and W6JRY, Jerry Fuller, SN, USNR. Two other members of the unit have applied for Novice Class licenses and several more are working toward this goal.

The following amateurs were present at a conference of Naval Reserve electronics program officers in Washington, D. C., January 13-16, 1953; WINK W2BBH W3QAF W3TDH W4CE W4LW W4RPI W4YEV W5HNW W5PLQ W6BOM W6BVY K6DL and K6DY.



Naval Reservists receive training in both automatic and manual communications. Lawrence J. Grant, RM1, USNR, is shown transmitting a message using radioteletype equipment at the Twelfth Naval District Reserve Master Control Radio Station, K6USN, Treasure Island. California.



A Military Affiliate Radio System advisory group has been formed to coordinate activities of the MARS in planning possible assistance for civil defense forces.

The six-man group consists of Major Robert A. Wood, Office of the Secretary of Defense, chairman; Major James A. Long (W3UWI), chief, MARS (Army); Captain Walter S. Browne, jr., chief, MARS (Air Force); Mr. C. P. Horne, Federal Civil Defense Administration; Mr. George K. Rollins (W3GA), Federal Communications Commission; and Mr. F. E. Handy (W1BDI), the American Radio Relay League.

The first objective of the group is to make a thorough study of MARS capabilities as they relate to other radio facilities which may be available to civil defense forces — principally the Radio Amateur Civil Emergency Service (RACES). Based on this study, plans will be coordinated to insure that there is no duplication of effort and to make certain that assistance by MARS-trained operators, using military frequencies, is furnished and furnished only when adequate facilities are not available to civil defense forces from other sources. Facts about MARS:

What It Is -

The Military Affiliate Radio System is an organization of and for United States licensed radio amateurs who are interested in military communications. The system exists primarily for training and to provide in-place facilities which will be available to the Armed Forces in the event of communications emergency.

Who Can Join -

MARS membership is open to members of the Armed Services or any of the reserve components who possess valid amateur radio operator licenses. Civilian amateurs may join if they are 21 years of age, possess a licensed amateur radio station and agree to operate in accordance with prescribed MARS rules.

How It Operates -

MARS is organized to follow existing channels of command within the Army and the Air Force. A MARS Advisory Committee, consisting of representatives of the Armed Forces, other governmental agencies and civilians, meets quarterly to discuss MARS-amateur relations and to advise the Chief Signal Officer and the Director of Communications on policy.

The system is organized into training, traffic and emergency nets according to local requirements. Military frequencies and call signs are provided for that purpose. Operating instructions and training aids are furnished MARS members to improve their techniques and foster study of military radio operations.



CONDUCTED BY ROD NEWKIRK.* WIVMW

How:

February's W6SRY article on the Ultimatic Key really set Jeeves a-mulling—he's worn out a dozen pencils already. Really, the potentialities of the keying gadgets he's dreaming up are too numerous(and almost too frightening) to list.

Let's take a peek at just a random few. You'll agree that it requires no great retch of the imagination to dig the merit in these models:

The U.O.I Key. Automatically checks log for back QSOs, goes after an AC5 or VQ9 sans prompting to send WHERE'S MY QSL? I WORKED YOU YESTERDAY.

The Okedokey. Instinctively gives out with OK ON THIS and OK ON THAT after commencing with RRRR.

The QSZ22 Key. Sends everything three or four times whenever anyone dares give you a readability report of R4.

The Whiskey. Don't be distressed if you "ain't got that awing." This job takes tedious tape-fist input and gives out with good old Lake Erie.

The Lyncher. Just the thing for D.Xers who hunt the stuff pack-style, overpowering unsuspecting rare ones through sheer force of numbers. Its circuit is rigard up to (1) memorize blank spaces on other guys Countries Lists; (2) dial their numbers on the landline; and (3) spontaneously apply results obtained in Steps 1 and 2 by sending PSE LISSEN FOR MY BUDDIES — AND — CUZ THEY NEED TANNU TUVA TOO

Anyone for chassis chess?

What:

California DX Club's DXer.

W6ZZ collected his 30th country on Fifteen c.w. and won his long battle for Europe and WAC. He has a nice 21-Mc. rotary cooking now which pinned down CE3AX, CP1BX, F8AT, FA9RZ, G5JU, KB6AY, KG4AF, KL7AMA, KP4QR, KV4AA, KZ5IF, LUs 2DAW 5AQ, OA4N, FY1ADA, VKs 3EG 4FJ, VPs 4LZ 68D, XE1SA, ZLz 1AH 2GS 3IA and YS10. W6ZZ has 44 of 45 states worked on 15 meters confirmed, As this column begins to get around W/Ks will be able to put 'phone to work on the 21-Mc. band and this development should liven things up there a-plenty.

One-Sizty is dying hard. The 1.8-Mc, situation got so lively this season that some of the boys switched to 'phone.



^{*} DX Editor, QST.

W3EIS had a 2-way A3 QSO with G5JU and W4NTZ did likewise with VP9BDA. Don at W3EIS also telegraphed with Ga 3GGN 3GZK 3US 5JU 5RI 6BQ 6GM 8JR and KV4AA. Z83K, ZL1AH and OH3NY reported hearing of their getting across to the States. ZS3K was rumored getting set with a 10-watter. All in all, it's been quite a season for old 160!

season for old 160!

Sesenty-Fies 'phone has been stealing the show at times.

TA3AA (3780) worked W1ATE and has heard just about every W/K call area on the band. Andy is gunning for the boys around 0300 daily, according to W1VG.....

W2ESO chatted with CT1BS, EA2CQ and G2PU while W3EIS found the same EA2, V768D and VPBDA available...... Listener A. L. Caldwell, Brockton, Mass., overheard HR1s BG (3785), SO (3785), CO2FN (3790), MS (3785) and HP3FL (3790) doing fine business...... The WGDXC gang add CN8FR (3785), EL2P (3751), ZL1WW (3798) and ZS6BW (3793) to the team.

team.

On Eighty c.w W6ZAT put the bite on CE3AX, DU6s IV RG, EASAP, EL2P, FF8AG, GI5UR, LU4ZI, PASXYZ, VK1RG, V86CG, VU2AT, YN1AA, ZE3JP and Z89I. No, this isn't 20 meters — we said 80! Del says W6DFY landed VQSKIF on the band and that VKs 2GW 5JE and 5KO are consistently on the lookout for W/VEs. W6ZAT heard that ZLICI caught up with a VU4CN but was a little doubtful about him LU4ZI (3509) and ZE3JF doubtful about him.....LU4ZI (3509) and ZE3JP (3510) came back to KH6ARA; W6EJA snapped up QSO with G4VF, LU1EP and ZL1CI. Two more customers SP3PL, ZL1HM and over a dozen assorted Europeans



One of the more potent 'phone signals out of Europe these days is that of CTICL. Eugénio has over 150 'phone countries to his DXCC credit.



LZ2AX manipulates the key at LZ1KAB, Vasco also operates Bulgarian club station LZ1SKA. (Photo via W1NWO and 984AX)

spot for KL7APH and ZL4IE.

.....Three-hundred watts and a 2-element array helped W9BDW to 'phones (times CST) CN8s EJ 0840, FI 1259, CT1s BS 1612, CL 1640, CX2CO (295-305) 0710, EL9A 1409, KA2IM (290) 1825, KG4AU 1819, OE13USA (350) 1145, OQ5EB (140) 1350, OX3BD 1025, VP3LF (180) 1740, Y81MS 1740, ZL2ACT (220) 2250 and ZP5CF (220) 1732 WIMCW is keeping her fingers crossed on IIAHR/9A2 (170) whose English was quite limited on IIAHR/9A2 (170) whose English was quite limited
......WIWIQ was without a rig but Norm checked
receiving conditions on 14-Me. 'phone and encountered
CR6AI (150), EL2P, FASBG (179), HH3FL (183 n.f.m.),
KV4BB (207), MI3US (140), MP4KAC (131), PIIJ (169),
PJ2s AA (150), AK (115), CA (107), OF (132), TAs 2EFAA
(140), 3AA (190-303), VPs 2AF (140), 2GH (122), 3HAG
(137), VQ2DT (131), ZD4AB (134), ZS3S (115), SAS 1TC
(197), 3TY (194) and IIYAK (340) of Trieste. WIWIQ
spots lots of VK boys coming through on the long path of
an afternoonA. L. Caldwell informs us of the
activities of CS3AB (195), EL2R (240), HRIs EW (330), SO activities of CS3AB (195), EL2R (340), HR1s FV (330), SO

Twenty c.w. we take up last this month but by no means least. W91HN carbonized his Lazy-H insulators on CNSFL least. WHINN carbonized his Lazy-H insulators on CNSFL (14,009), CTITY/446 (030), FF8AG (030), FQ8A G (030), AS (050), GD3UB (020), OY3HRS (050), TA3AA (020), TF3MB (035), ZBIBR (040), ZESJA (095), ZS3T (025), SA3s TC (050) and TZ (055), CX4CZ (014), an FF8, VPs IAA (005), 3VN (080), 4LZ (020), 6GT (007) and ZB1AH (037) enraptured WSDLZ..... WSJGU liked CN8EY (035), CN8MI (040), KV4AQ (060) and VESMC while W2DEC was occupied with EA9AP (005) at 1117 (009), LU3ZO (055) on Deception Iale, TF3s AB (025),

First U.S.A.-Asia Q50 on 160!

On March 8th W1BB, Winthrop, Mass., worked ZC4XP. Nicosia, Cyprus, for the first U.S.A.-Asia 160-meter QSO on record. VE1EA worked ZC4XP the previous week end for VE1EA's second 160eter Asia QSO. As will be recalled, VE1EA worked HZ1KE on January 14th, 1951, for the first North America-Asia 160-meter QSO.

NA (015), VPSAP (011) and numerous YUs...... W2TXB swapped code with CRs 6CZ (030), 7CN, EA9BD, FQ8AR, OQ5CP, VQ2DX, VQ4NZK (090) and ZE5JLLZ2KSK (075), MD5RS (080), SV\$WE (098), VSs 1FE (075), 2DF (061) and ZD2HAH (065) replied to DLAJN; Bill is still pursuing AP4A (018), F9AE/FB (075) 15GO (060), JAIAA (020), ODS AB (020), AI (060), BH (050), OY2AZ (085), VKIJC (080), VS2DU (070), ZDs 2FFB (080), 9AA (050), 3V8AV (010) and one peculiar SSSEE (082), [Sounds like Gene Krupa with a bug, Bossa — Jeeses]......W4TVQ would like a boom lowered on phoney XZ2FT. Art grabbed FD8BQ (071) and has fresh QSLs from GD3UB, PJ2AD and 3A2AV..... WIRST also ran into the demented character around 1600 PST. Gary hooked KA2s GU and ZZ......Among the trophies of VE3AVS we see FP8AP, KA9AA, OX3s HK UD, TF3SG and VP6EB; W2LYO got the same TF3 and VP6 as well as an FF8, OE13RN, VP6UN, YU1DF approached successfully by W2PZM.....HH2FL was country number 58 for W2TKG and W9MQK did well . HH2FL was with EASBC, FFSAT, GD3UB, PI1LS, TA3AA, VQ4CW and ZB2A.....Only six to go for the century mark at WSYGR after YU3BC (020)....The WGDXC DX Bulletin (W5s KUC and UCQ) stresses the availability of Bulletin (W3s KUC and UCQ) stresses the availability of those in this c.w. glossary: CR7s AF (045), AK (018), IZ (052), CT2BO (030), EASAP (070), EL2P (054), FF8s AH (020), AJ (078-100), GP (010), FMTWD (112), FR7ZA (028), GCZCNC (050), HH3L (046), HR2HZ (030), KA2HQ (012), KF3AA (060), W5QDF [KG6 (059), MF2AG (078), PJ2CH (073), VP6As O (028), R (060), S (058), T (021), U (065), VQs 2DS (012), ZGW (024), 3BU (020), 3KIF (075), UNIT (075), CRS (050), CRS (05 4HJP (020), SCL (050), ZD2S (072), ZE4JK (078), ZS7s C (045) and D (010) in the r.m.; EA9AK (083), FB8ZZ (050), FQ8AL (080-100), MI3LK (012), MP4BBD (048), OD5AD (055), OY2Z (050), TFSSV (010-055), SP6KKA (020), VP8AK (015), VQ3BM (042), ZB1BU (005), ZC4IP (005), ZD9AA (033) and ZS3U (018) in the A.M.

Haiti's QSL bureau has had a change of address, according to W2DEC. It's now Radio Club of Haiti, P. O. Box 943, Port-au-Prince OD5s AH and AK inform us via W1RWS that Lebanon amateurs have formed the Association des Radio-Amateurs Libanais. We presume that QSLs addressed in care of this society, B. P. 1202, Beyrouth, Lebanon, will be relayed to any OD5s. Authorities there have now issued call letters from OD5AA through OD5AR - Lebanon's amateur radio boom is really on,

CN2AN, S. P. Proskauer, ex-PASOA, % RCA, British P. O. Box 57,

CARAN, S. F. Fremanner, ext. Andra, 7, R.C.A., Drinnin F. U. Box of, Tangier, Morrocco CRoBX, P. O. Box 2163, Luanda, Angola DL4YK, SFC E. F. Diehl, ir., 512th Sig. Base Main. Co., Pirmaeena Signal Depot, APO 189, % Postmaster, New York, N. Y. EATDT, P. O. Box 313, Malaga, Spain

EA7EV, (QSL to EA7DT) EL2P, Roberts Field, Liberia

FF8AC, Yves Rangin, SNA, Aeroport de Yoff, Dakar, F.W.A. FF8AG, Ivan Pastre, Box 253, Bamako, French Sudan, F.W.A.

On the occasion of a visit by 4X4BX (right), SM5LI (seated) and SM5RM discuss some QST circuits in SM5LI's Stockholm shack.

FF8AI, Jean Maillet, Bloc N2, Appartement N13, 113 Avenue William Fonty, Dakar, F.W.A.

FF8AT, Box 6020, Dakar, F.W.A. FM7WF, (QSL via W6ARI)

FQ8AT, R. Franchot, Etat-Major Transmissions, Brassaville, F.E.A. Y7YX, % Pan-American Airways, Cayenne, French Guian HH2RS, Raymond Scott, P. O. Box 427, Port-au-Prince, Haiti HH3FL, Fernard Labelle, Hotel Majestic, P.O. Box 991, Petionville,

HRIFV, American Embassy, Tegucigalpa, Honduras JA1CU, Kazutada Ohira, 2–4817 Asahicho Warabi, Saitama, Japan KR6LZ, A. W. Dale, jr., VP-22, APO 331, % Postmaster, San Fran-

KR6MW, Tony E. Welzel, 8111th AU, APO 331, % Postmaster, San Francisco, Calif. KR6PN, Perry W. Esten, % GSW&K, APO 331, % Postmaster, San

KR6USA, RYCOM MARS, Signal Office, APO 331, % Postmasters

San Francisco, Calif. KT1LU. % Air Attache Officer, American Legation, Tangiers

OD5AO, Raymond Saidah, P. O. Box 161, Beyrouth, Lebanon OQØDZ, (QSL to OQ5DZ or OQ5RA)

ex-VESRY, John W. Smith, VE3DCQ, RR 1, Billings Bridge, Ont. VP3VN, 9 Howes Street, Georgetown, British Guiana VQ4NZK, % U. S. Consul, Nairobi, Kenya (or via W1PIJ) ex-VS6BA, W. A. Musty, 21 Grosvenor Ave., Chatham, Kent, England

VS6JH, (QSL via VS6AJ) W1JNE/VO6, (QSL to W1JNE) W5WLM/V06, MARS Director, APO 677, % Postmaster, New

York, N. Y. YN4CB, P. O. Box 10, Bluefields, Nicaragua ZC6UNJ, (QSL via RSGB)


ZD4BK, P. O. Box 154, Takoradi, Gold Coast ZD4BL, (ex-G2ATU) P. O. Box 201, Sekondi, Gold Const ZE5JL, P. O. Box 860, Bulawayo, So. Rhodesia ZS3N, P. O. Box 15, Luderitz, Southwest Africa 283T, Box 263, Tsumeb, Southwest Africa ZS6FN, R. Goldblatt, Box 7243, Johannesburg, Union of So. Africa

5A3TC, (QSL via W8JUW)

Instrumental in assembly of the preceding batting order were W1s BTQ RWS VG WPO, W2s DEC TXB VMX/1, W4QCW, W8DLZ, W9s IHN OIN and the WGDXC DX

Tidbits:

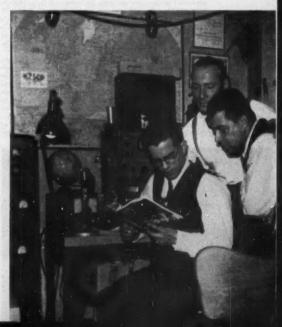Asia - Of considerable interest from W9KOK: "I've noted you mentioned Reg Fox, ACAYN. Yes, he is safe and as well as can be expected. . . . I've been in constant communication with Reg for several years now. Bob Ford, AC4RF, fared much worse and is reported still in prison in This bears upon repercussions of the ensnarled



Tibetan political situation . Tibetan political situation Ex-MP4KAE, heading back to the United Kingdom and G4IX, gives us some lowdown on Kuwait Hamdom as he left it: MP4KAA now operates ZC4DT to westward; MP4Ks AB and AC working a lot of 20-meter 'phone; MP4Ks AD AE AF and AH have closed down for other assignments; MP4KAG is now in Brazil; and MP4KAI currently inhabits the 14-Mc. region, 'phone and c.w. Don't forget that MP4KAC inherited Kuwait's Q8L managership.....KA KA9AA notes that 4UAS QSLs carry no indication of location not even "India". This omission does not necessarily bar such cards for DXCC credit but the information certainly seems called for on any QSL!.....ZC6UNJ of Jerusalem has this to say: ". . . I have sent a card to every new station I have worked. It might be interesting for We to know that we read their mobile twenty-meter 'phones. I listened to a W4 mobile the other day putting in an R5 89 signal here and all he was doing was 'testing'. . . . If he had just cut his carrier and listened on his frequency he would have had ZCGUNJ calling him." And that would have been some pretty good mobile DXI Bill, as you may know, is ex-W8RAU-W9WUI-W5LLQ-KP4EZ. We have on hand a letter from a would-be amateur in India who desires to enlist the services of an American ham to guide him toward getting on the air. Anyone inclined to tackle this worth-while task on a correspondence basis may

write Mr. T. Singh, c/o 22 Medico, Agra, India.

Africa — Old-school DXer Ivan Pastre, FF8AG, carned the first French West African DXCC over recorded, finds WIWPO. Ivan previously ran down DXCC as FESAB. All this and W QSOs, too! "Please . . . request W stations to call me a little higher or lower in frequency as my own frequency is always covered with a three-layer pile of European stations calling me continuously for several minutes. This has prevented me . . . solid contacts with the States." So writes CN2AN, proving that our hemisphere has no corner on the boor market. Swapping his PA# label for a CN2 prefix allows Stefan to raise people like ZL1HY, V86CG and V87MC on a single short CQ. CN2AN rolled 50 countries in his first two weeks on the air and is on 14 Mc. almost daily with a 350-watter From July 11th through July 17th NRARS will operate VQ2RCC in conjunction with the Rhodes Centenary Celebration Festival to be held in Nkana-Kitwe, The 40-, 20-, 15- and 10-meter bands will be operated with separate rigs and a special QSL will be sent to each station worked. Amateurs 332, Kitwe W9IHN learns that Z82AG is on the lookout for Idaho — WAS, of course If FQ8AP suddenly during QSOs, don't junk your receivers. He tells W4LHT that Fort Archambault's airport power generator shuts down abruptly and stays off from 1800 to 0400 GCT...... A remark by FB8BB to W1MCW asserts that his returns are mighty, mighty scant from a 100-per-cent outgo to all VE stations worked ZS6FN would appreciate an assist on the procurement of tardy W6WVJ/KW6 and KG4AO (W4RLL op.) Q8Ls now

long overdue.

Oceania — ZLiMP and XYL have been visiting Panama Gecans — ZLIMY and AYL have been visiting ranama and the Canal Zone on the first leg of their jeep jaunt overland through Central America north to the U. S. Bon massags, folks. HGGI visited KZ5-land, too, and was thus QRT for a couple of weeks......... The new VK9YY is former VK2AIR and VK2YC says he likes to QSL. He's not to be confused with the former holder of the call From KB6AY on Canton Island: "Band conditions remain very poor on all bands except 40 meters, so there is not much new in the way of DX to report. We are

ready to utilize the new 40-meter 'phone band (as soon as possible. It may turn up something interesting in the way of DX contacts. Twenty meters has been even worse this month than last — if that is possible. We would like to do a little more work on 15 but there has been so little activity on that band that it is a bit difficult to hear anything out here. On week ends we hear a few Stateside signals and an



KB6AY apportions Canton Island QSOs on 10 through 40 meters with this orderly installation. Fred was formerly active as KM6AH and KM6AH/KB6.

occasional South American." By the way, Fred seems to be on the trail of a new type of DXCC. His oldest son was

be to the trail of a new type of DXCC. His oldest son was born in California, his second on Midway Island and his latest offspring just saw his first light of day on Canton Lile. [He'd better settle for WAC, Boss.— Jeeses.]

Europe — The c.w. session of Switserland's Helvetia-22 Contest, sponsored by USKA, falls on April 18th-19th, beginning at 1300 GCT and ending at 1900. The object for WAC. W/VEs is to work as many Swiss cantons (provinces) and wiss stations as possible. Briefly, each QSO earns 3 points, this QSO-points total to be multiplied by the number of cantons contacted. An HB may be worked but once per band. Watch for "CQ H22" and call signs like HB1KB/NW,

- Intriguing tale from LU3BAC: "On South America -January 15th at 1355 Argentina time LU@MA, installed on the summit of Aconcagua, 7035 meters [over 23,000 feet] high, effected 'a 'phone transmission . . . on the 7-Mc. band with LU stations operating in an encampment in the vicinity of 4600 meters high and San Rafael (Mendosa) around 290 kilometers away. . . . We consider this experience from such a high altitude a first in amateur ra history." If any counterclaims develop we'll be mighty surprised — Aconcagua is this hemisphere's highest peak! The radio gear was handled by a crew of three, weighed four kilos, had a transmitter output of approximately one watt.

DX 25 Years Ago in QST - The Wilkins Arctic Expedition, naKDZ, was reported worked by 7ABH on 33.1 neters. . . . 8CFR and sb1IB are congratulated for DX traffic assistance given GMD, the Dyott Brazil Expedition.
... WNP, the Boudoin in Arctic waters, rolled up a February traffic total of 349 message points. . , Some DX reported worked in early 1928: ai2KT and ai2KW, India; agRIL, Tiflis, Georgia; aq1LM, Iraq; auRABS, Turkestan; zep1MA, China; and WWD in the Pribiloffs.



At Mile 1235 on the Alaskan Highway you'll find KL7AFR. Bill possesses the only DXCC membership in the Territory. (Photo via KL7AI)



Hints and Kinks



SELENIUM-RECTIFIER AUDIO LIMITER

CHANGE-OVER relay clicks, extra-loud heterodyne howls, etc., are deadened at the output of the HRO here at W1BDF by an extremely simple limiter consisting of nothing more than a pair of 115-volt 60-ma. selenium rectifiers. The rectifiers are connected in parallel with opposing polarity and this combination is in turn tied across the 500-ohm output terminals of the receiver. The 'speaker is connected to 8-ohm terminals of the output strip. — Edgar Seeler, W1BDF

USING BLOWN INDUSTRIAL FUSES AS LOADING-COIL FORMS

BLOWN industrial fuses that are ordinarily discarded by factories, construction concerns, etc., can be modified for use as mobile antenna loading-coil forms. The fuse best suited for this application is one having a diameter of 1¾ inches, a length of 6 inches and an electrical rating of 600 volts at 150 amperes.

To prepare a fuse for use as a form, it is necessary to remove the end bells so that the lime-dust contents and the copper fuse blades can be discarded. The contact arms must be cut from the end bells and the label should be removed from the tube.

Fig. 1 shows before and after sketches of a modified fuse. Notice that the finished job has a

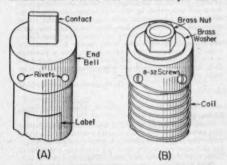


Fig. 1—(A) shows one end of an industrial fuse before modification and (B) shows the same unit adapted for use as a mobile antenna loading coil.

brass nut and a brass washer brazed to each end bell. The brazing operation can usually be handled by a local welder. Naturally, the nuts used should match the threads of the antenna sections. Type 8–32 machine screws are used to tie the end bells and the tube together and also serve as the termination points for the loading winding.

Loading coils of the type just described can be turned for almost negligible cost and, as a result, it is advisable to prepare a number of fuses at one time. This procedure will save a trip to the welding shop each time that a new form is needed.

— Kenneth M. Rude, W6TEN

FEEDER-SPREADER HINTS

Some newcomers may not be familiar with the established practice of making feeder spreaders. Inexpensive substitutes for the commercial jobs can be made with ordinary \(^3\)-inch wooden dowels. Cut the dowels into lengths that are 1 inch longer than the spacing of the proposed transmission line and then drill a clearance hole for the wire at each end of each spreader. The holes should be located \(^1\)2 inch in from the ends of the rods and should provide a snug fit for the wire. Next, dip the spreaders in hot paraffin and then set them aside to dry.

Dowels can usually be bought at a local hardware outlet for approximately 10 cents per 3-foot length. Thus, it is possible to make spreaders for a 6-inch line at a cost of only a nickel apiece.

— Jack C. Andrews, W9YWE

Toni hair curlers that are to be used as feeder spreaders can be held securely in place with fast-drying model airplane cement. Just apply cement on each side (where the wire passes through) and over the ends of the curler and then allow adequate drying time. After the cement has hardened the feeder will break before the tie gives way. — Ken Cary, WOIXM/2

VISE SUBSTITUTE

One good substitute for a small portable vise when the latter is not available is an ordinary adjustable wrench. Soldering lugs or other miniature components can be clamped in the jaws of the tool and then worked on with two hands after the wrench has been laid flat on a box, table, bench or other handy surface. — Steve Graham, W9REV

SOLDER WHEN YOU NEED IT

D to you ever get ready to start an outdoor soldering job and then find that everything is on hand except the solder? This won't happen again if you make a practice of keeping a few turns of solder wrapped around the handle of the iron.

Incidentally, if the iron is a short-barrel job (gun or low-wattage type) the end of the wrap can be pigtailed out to the tip. If this is done, it is frequently possible to complete a soldering operation that normally calls for a third hand.



Correspondence From Members-

The publishers of QST assume no responsibility for statements made herein by correspondents.

DOCKET 10173

P. O. Box 1061 San Juan 5, P. R.

Editor, QST:

The General Class boys sure have my sympathy. Think of it, for twenty odd years they have been deprived of privi-leges enjoyed by Advanced Class licensees just by decision of the powers that be, who have now reversed their decision.

And what have the General Class boys who stampeded FCC offices to take the Advanced Class examination before Dec. 31, 1952, gained? Just 18 or 20 days 75- and 20-meter phone operation over the General Class boys who will now get those privileges next February, without further exami-

Good-by to the good old days before the nippers cut their amateur eye-teeth on a kilowatt 'phone transmitter before they had been in the hobby long enough to learn proper operating ethics.

- E. W. Mayer, KP4KD

2310 S. 61st Court Cicero, Illino

Editor, QST:

The FCC is to be commended for this startling move. It will give hamdom a shot in the arm similar to that given it by the opening of the ham bands to Novices. Ham radio is not a profession; it is a hobby, and as such it should be made available to as many as possible, and not hamstrung with technical requirements far in excess of that needed for minimum ham needs.

Allowing General Class ham operators to work in 'phone bands is no different from allowing Novice in those portions of the ham bands previously restricted to higher class licensees. These new regulations will give many hams a "foot in the door of further ham progress." From there, I am sure, many of them will become just as proficient if not more so, than some of those Extra Class squawkers whose letters appeared in your column.

William J. Suhajda, W9AOD

88 Esso Paterso Esso Shipping Co. 115 Broadway New York 6, N. Y.

Editor, QST:

, . . If the Commission's purpose was to idealistically equalise operational privileges, then it did so at the expense of lost initiative on the new amateur's part. Further, it attracts rash inexperience that could easily reflect discredit to the amateur fraternity and art.

I am fanatically opposed to catering to special interest with disregard for the majority. Such action is undemocratic and precludes the principle that a mass has the wisdom to govern itself.

- Theodore Pedersen, W2DEB

369 3rd Avenue Phoenixville, Penna.

Editor, OST:

Your stand on the FCC action to open 20 and 75 to General Class licensees seems rather childish and founded on sentiment rather than fact. The Class A license has simply become a ticket to the privileges it authorises; it does not signify that the holder is head and shoulders above the General Class peasantry, nor that he is engaged in furthering the cause of amateur radio through his technical com-petence. His "advanced techniques" often include such things as burning a hole in the 75-meter band with a full kilowatt while engaged in bigoted conversation with some-one a few miles away. Is this a step forward? Can be copy code as well as the average Boy Scout? . .

. . The Extra Class license can be an achievement for which to strive, without any strings or inducements other than the deep personal satisfaction thus gained. This is as it should be. The old Class A never interested me sufficiently to prompt me to take the exam; now I find myself itching to hang an Extra Class license on the wall.

- Clifford J. Bader, WSNNL

1115 So. Wall St. Los Angeles, Calif.

Editor, QST:

I have only this comment to make -Class radio operator license No. AE-11-88-E, so proudly and conspicuously displayed over my operating table, is now relegated to the junkpile.

George S. Chan, W&GCD

1134 W. State Street Milwaukee 3, Wisconsin

Editor, QST:

. . . I join in the gnashing of teeth against this incredible and astonishingly inconsistent FCC action. It is difficult to conceive a more desultory approach in the service of the nation than to abolish an equitable incentive system promoting progressive development of knowledge in this nation's greatest electronics and communications manpower reservoir. When one considers that this pool of knowledge is probably the principal justification, from a national standpoint, for supporting the amateur service it is small wonder that certain amateurs have expressed a fear of more sinister intent in the formulation of such a destructive policy as that presented by the FCC.

When the Commission delivers a coup d'état to a time-honored system of advancement, based on self-improvement and supported by the well-proven principle of incentive reward for human endeavor; and when this action represents a 100% about-face from the excessively rigid dictum proposed immediately preceding this latest fiasco; and when the effect of this latest vagary is to seriously jeopardise amateur spirit and progress; then a thorough review is most absolutely indicated. It is certain that if the FCC is working in good faith this apparent error in judgment will be quickly re-assayed.

- H. W. Bardenwerper, W90LW

Puddinbrook E. Pembroke, Mass.

When I subscribed to QST I was under the impression that editorially it was a fair-minded publication. I am still under that impression and excuse your oversight by believing that someone on your staff was overdoing it in favor of as A, or is that the only group of amateurs you favor? 10 to 0 (I spell - ten to nothing) a very poor S reading

from where I sit.

Even Life prints the other side. But QST -- not one word. It is entirely possible that you had no correspondence favoring the FCC Rulings. This I doubt. However, if this be the case I apologize. . .

- Emerson Corson, W1TTI

[Enrron's Note: Apology accepted. As of copy time for February QST, we had several dozen letters on the subject, every single one opposed to the Commission action. To date we have received 133 letters; of these, 42 expressed support of the new license privileges and 91 opposed them. Included are letters from 7 clubs and 2 nets, all indicating unanimous opposition by members. The official Docket file, at the time FCC decision was made, showed an even higher proportion of individual opposition.]

HARMONIC GENERATION

550 So. G St. Oxnard, Calif.

Editor, QST.


I enjoyed W2RYI's article, Dec. QST, very much. Think his conclusion is last paragraph in error. I believe many hams have suffered from this type of TVI, but could not determine what was the cause. About six months ago I started having TVI on Channel 4 when operating on 20-meter 'phone. This TVI was not constant from day to day or from transmission to transmission. After spending many, many hours on the transmitter and TV receiver I finally came to the conclusion that something else was amiss. To make a long story short I finally replaced my bare wire clothesline with plastic-covered lines and the TVI cleared up. As a matter of interest, the 20-meter antenna was a center-fed doublet about 15 feet from the TV antenna and the clothesline was about 40 feet from the TV antenna. Transmitter power input 100 watts, TV station 60 miles from my QTH.

- W. W. Deane WERET

West State St. W. Lafayette, Ind.

Editor OST:

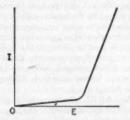Mack Seybold's article on nonlinear conductors and TVI salt solutions are nonlinear conductors. Below their decomposition potential, salt solutions are poor conductors. Above this potential electrolytic decomposition occurs, enhancing the conductivity of the solution. The following curve illustrates the EI relationship for a salt solution.



The decomposition potential is in the order of 1 volt and depends on the salts in solution. Traces of copper in salt water will markedly lower this break in the curve, giving a smaller linear region.

Mack Seybold's comment on sea-water corrosion and TVI suggests that this may be one of the sources of external harmonic production.

- Volney Wallace, W78JZ

"CARE" GIFT SUBSCRIPTION

Zeelsterstraat 95B Eindhoven, Netherlands

Received your so welcome letter just a day ago. Thank you so very much for selecting my name as a member of the American Radio Relay League for the period of one year.

I also wrote a letter to the donor, and thanked him for his kindnes

I wish you all a very happy New Year, and will never forget the great friendship between your nation and mine.

— Louis A. Esseling, PASEP

WORKED ALL STATES AIDS

2429 S. Harvey Ave. Berwyn, Illinoi

Editor, OST:

As a ham who has spent two years, mostly on 40, working for a WAS certificate I would like to thank you for the SS contest during which I was able to work stations in two states which were still needed. A QSL card has already been received from one state and I hope to get the other soon.

I would like to suggest that more of the hard-to-get states

have QSO parties to help hams to get their WAS. I will always be grateful to the Vermont gang for having such a QSO party for otherwise I am sure I would still be without a

contact from that State.

From my experience, I would auggest that hame in the States of Idaho, Nevada and Utah organize QSO parties similar to that held by the Vermont gang. No doubt other hams would add other States to the list.

Such QSO parties should get good publicity in QST and not be buried in the section news.

- George Nesbed, W9LQF

QRP TEST

1209 S. Madison mington, Ind.

Editor, QST:

We, the undersigned amateurs, would like to see a test run with all amateur stations using an input power to final stage of 50 watts or less on all amateur frequencies. This test could be run on Sundays, starting at 6 a.m. EST and ending at 3 P.M. EST. The day and time is given only as a sugges-

Would you give this a thought and publish it in QST to

get the reaction of other amateurs?

— A. Ray Elliott, W9HMA, and W9a EPJ, YYX, NZK, IBO, HIQ, INL, LPQ.

ULTIMATIC

1207 Main Street E. Rochester, N. Y.

Editor, QST:
The "Ultimatic" key described in February QST is a development which should cause us all to pause and reflect on the direction toward which amateur radio is heading. A ham used to be proud of his fist. It was his trademark, the yardstick by which he was measured by the gang. Time was when a station could be identified by the speed of the rotary gap as well as by the operator's fast. Then came.c.w. and all notes are "T9X," if we are to believe the reports. Now we believe there is something very personal about a man's fist. We learned code largely by copying the boats on Lake Erie and Lake Ontario. Any attempt to strip the individuality from a fellow's fist we regard as a serious threat to the future of amateur radio. Personally, we don't recall ever having been faced with the necessity of sending the word MICE for the last 33 years, but when some Johnny Come Lately pounds out NNGT, we want to hear it that way, and not as CQ. Webster defines "ultimate" as "to bring or come to an "The "Ultimatic," coupled with the opening of 7 Mc. to 'phone, prompts me to break up my Audiotron and tear the wire off my honeycombs. - Howard B. Mouatt, WAVVO

> Hamden Connecticut

Editor, QST:

Description of the marvelous intelligence of Ultimatic is quite intriguing. If the transmitted copy actually were ZTRE, would the operator have to be particularly careful, to avoid sending MICE?

- Elmer E. Preston, WIAYC

QRM TO NOVICES

W. Cornwall

Editor, QST:

I am just an ignorant new ham with a great deal to learn and doing my utmost to derive some enjoyment from a rig recently put on the air after years of hopeful wishing. Now what happens? With a Novice ticket and the limitations of bandspread the VEs plaster half of it on phone!

It would seem to me that steps might be taken to keep these fellows and gals up in the "wide-open spaces" and not have them jamming up the one-by-one "closet" the Novices have to operate in. Perhaps steps are underway for I certainly am not the only one they bother.

- Lee C. Warner, jr., WN1WPT



RULES AND REGULATIONS OF THE COMMUNICATIONS DEPARTMENT

1. The League maintains a Communications Department to effectuate the following purposes and objectives: The organization of members for practical communication, with particular attention to emergency preparedness and communications service in the public interest; the promotion and sponsorship of message traffic and emergency networks and systems; the promulgation of contests and other tests dedicated to furthering skill in amateur radio operating; the conduct of training aids and other programs for societies affiliated with the League; the recognition of outstanding public service and operator proficiency by the issuance of appropriate awards; the advancement through its operations of the spirit of fraternalism and a high standard of conduct among the members.

2. For the activities of the Communications Department the operating territory of the League is defined as consisting of the territorial Divisions described in By-Laws 25, plus the Republic of Cuba which shall be deemed for these purposes attached to the Southeastern Division. This operating territory is apportioned from time to time within the Divisions into Sections for the purpose of Communications Department field organization, by the Communications Manager.

3. In each Section there will be a Section Communications Manager (SCM), who, under the direction of the Communications Manager, will have authority over field organization appointments and ARRL operational programs within his Section. He shall be responsible to and report to the Communications Manager.

4. Any candidate for the office of Section Communications Manager must have been both a member of the League for a continuous term of at least one year and a licensed radio amateur operator for at least two years preceding receipt of his petition of nomination.

5. Each Section Communications Manager shall be elected for a two-year term of office. Whenever a vacancy occurs in the office of a Section Communications Manager, the Communications Manager will announce such vacancy, and the date for receipt of petitions, and call for nominating petitions signed by five or more Full Members of the Section in which the vacancy exists, and naming a Full Member of the Section as candidate for Section Communications Manager. After the closing date the Communications Manager will arrange for an election by mail and set a closing date for receipt of ballots. Ballots shall be sent to every Full Member of the League residing in the Section concerned. Candidates' names shall appear on the ballots in alphabetical order. The Communications Manager will determine the count of the ballots at the conclusion of the election. The candidate receiving a plurality of the votes will become the Section Communications Manager. If there be but one eligible nomince, the Communications Manager shall declare him elected. Provided, however, that whenever the operating territory of a Section includes additional territory not part of the administrative divisions of the League but attached thereto for the activities of the Communications Department, Associate Members residing in the said attached territory and possessing amateur radio licenses shall be eligible equally with Full Members of the Section to hold or to nominate for and vote for the office of Section Communications Manager, provided they otherwise comply with the requirements of these Regulations. Section administration during the period required to complete an election may be covered by interim appointment by the Communications Manager.

6. The office of any Section Communications Manager may be declared vacant by the Executive Committee upon recommendation of the Communications Manager whenever it appears to be in the best interests of the membership so to do. On such declaration the Communications Manager will thereupon cause the election of a new Section Communications Manager as provided in paragraph 5.

7. Only ARRL members are eligible for field organization appointments. Station and leadership appointments shall be made available by the SCM to interested members possessing General Class license or higher, or equivalent Canadian license, also to members with Novice and Technician license in the case of the OES appointment, on application when their appointment qualifications and guarantees of activity and reporting may be demonstrated as adequate. Operating radio tests or station inspections under his direction may be required at the discretion of the SCM as pre-requisite to appointment.

8. The Section Communications Manager shall be responsible for operational planning and the holding of organization-meetings in his Section. He shall render monthly summary reports for QST, comprising the reports of section stations and clubs. He shall be responsible for maintenance of accurate records of dates of appointments and cancellations in all the leadership and station appointment categories; likewise he shall issue ARRL Section Net certificates to amateurs in ARRL sponsored nets, providing those so recognized meet a minimum standard of participation and activity as from time to time provided by him. He shall issue Brass Pounders' League certificates to those members whose traffic records meet the standards set forth in QST from time to time.

9. An Amateur Radio Emergency Corps is sponsored by ARRL. Every licensed amateur in the League's operating territory is eligible to register in either of two AREC membership grades, Full or Supporting. Emergency-powered equipment while desirable is not pre-requisite but will be recognized appropriately. (a) Full AREC membership will consist of those AREC registrants pledged to active participation as proved through drills, tests and regular activities. (b) The Supporting AREC membership will require

only limited participation.

10. One Section Emergency Coordinator (SEC) shall be appointed by the SCM in each Section for section-level responsibilities pertaining to emergency communication and the organization of an Amateur Radio Emergency Corps. It shall be his duty (a) to promote AREC membership drives, meetings, activities, tests, procedures, etc., at section level (b) to recommend appointments and terminations of appointment for community Emergency Coordinators in areas of jurisdiction which he shall define as required (e) to recommend and report policy-planning on section emergency matters monthly (d) to maintain contact with other communications services and liaison at section level with all agencies served in the public interest, particularly in connection with civil defense and Red Cross functions.

11. The Emergency Coordinator (EC) shall have full responsibility (a) for preparing and keeping up-to-date emergency communications plans for the amateur service for the city, county or other local area jurisdiction designated by the SEC, for fullest utilization of all amateur stations and facilities (b) for maintaining full and current information on registrations in the Amateur Radio Emergency Corps. (Registrations are not considered an "appointment," so not subject to the restriction of paragraph 7.) (c) For certification of Assistant Emergency Coordinators (likewise not an SCM appointment) for advisory and operational duties (d) for records of agencies served and for continuing personal contact with their representatives for the purpose of evaluating emergency needs, recording the availability of amateur facilities, capabilities and limitations (e) for establishing and reporting appropriate drill periods and simulated emergency tests, including the designation of stations and operators and specification of recurrent drills to insure an efficient or adequate facility.

The Emergency Coordinator shall issue ARRL Official Mobile Unit, and Emergency Radio Unit cards to registered AREC members having operative units, as appropriate. Assistant Emergency Coordinators where appointed shall constitute a

local amateur service emergency planning committee.

12. A National Traffic System is sponsored by ARRL to facilitate the overall expeditious relay and delivery of message traffic. The system recognizes the need for handling traffic beyond section-level networks throughout the field organization territory. Definite provisions to facilitate this are therefore set up by areas and regions. Appointments in the National Traffic System for leadership above the section level are made under the direction of the Communications Manager.

13. One or more Route Managers (RM) shall be appointed by the SCM to coordinate and supervise c.w. traffic-handling activities in the section. Route Managers' areas of jurisdiction shall be as designated by the SCM. Route Manager duties shall be: (a) To organize and promote the section c.w. traffic net or nets. (b) To keep posted on c.w. traffic outlets maintained by section amateurs. (c) To provide liaison for the National Traffic System. (d) To recommend and test all applicants for Official Relay Station (ORS) as directed by the SCM. (e) To make recommendations and reports of c.w. traffic progressions.

ress monthly to the SCM.

14. One or more Phone Activities Managers (PAM) shall be appointed by the SCM to coordinate and arrange organized communication activities within the Section by voice circuits. Phone Activities Managers' areas of jurisdiction shall be as designated by the SCM. Phone Activities Managers' duties shall be: (a) To organize and further a section radiotelephone station net to bear ARRL recognition; (b) to stand sponsor to other 'phone operating activities from time to time as appropriate in the name of the League; (c) to promote 'phone nets and round-tables and meetings devoted to handling communications, operator training and fraternal purposes; (d) to recommend candidates for Official Phone Station appointments and conduct station inspections and radio operating tests as directed by the SCM; (e) to report monthly progress in 'phone activities to the SCM.

15. Station and Observer Appointments. Each of the following station appointees shall (a) report activities monthly to the SCM; (b) keep his station in readiness for operation; (c) follow ARRL operating practices; (d) participate in League activities; (e) hold message files ready for call for verification of numbers or traffic count.

The Official Relay Station (ORS) appointment shall be granted by SCMs on application to those members meeting the general appointment qualifications who especially (a) display a high

(Continued on page 144)

. On these pages we reproduce the new Rules and Regulations of the Communications Department, as adopted by the Executive Committee in January. This section completes the revision of the governing instruments in ARRL affairs; the Articles of Association, By-Laws, and other rules, earlier adopted, appear in the July, 1952, issue of QST.



Operating News



P. E. HANDY, WIBDI, Communications Mgr. R. L. WHITE, WIWPO, Asst. Comm. Mgr., C.W. GEORGE HART, WINJM, Natl. Emerg. Coordinator J. A. MOSKEY, WIJMY, Deputy Comm. Mgr., ELLEN WHITE, WIYYM, Asst. Comm. Mgr., 'Phone LILLIAN M. SALTER, Administrative Aide

The New Order of Things. Amateur radio is normally a hobby of evolutionary development rather than one in which radical or revolutionary departures mark our progress. Our amateur bands are a "proving ground of communica-tions." The development of the crystal filter, first transoceanic success on h.f., our inclusion as amateurs in civil defense (RACES), the progress of s.s.b. and RTTY, are all in this pattern. We have constantly to look forward and not backward. Nostalgia they tell us is but momentary escape from a world in which change is the rule. Just for example, five-point star system schedules for traffic relaying are outdated and the National Traffic System offers advantages above earlier plans giving only some states as outlets. The section net is today the unit for individual participation in NTS, and a radiogram to Hq. will bring a directory of nets, net frequencies and operational times to any amateur on the air.

The month of February marked operation under new FCC regulations permitting General and Conditional class amateur licensees use of the 20- and 75-meter 'phone subbands; allocating 7175-7200 kc. for Novices; permitting all except Novice and Technician licensees 7.2-7.3 Mc. 'phone and use of F-1 teletype in those band sectors not open to voice work. It's no use to be nostalgic about the yesterdays in amateur radio; the thing is to do the best job with what we've

got.

'Phone on Forty is new, and the general use of 20- and 75- 'phone, likewise for all except Novice and Technician amateurs, is a new order of operations. The bands aren't any larger and how we use them, as always, determines the level of interference, and how much intelligence we can convey in the course of our two-way communications. The 7175-7200 kc. earmarked for Novices isn't a large band as bands go, but is in the direction of your Board's recommendation, and is sure to become popular with Novices for code and WAS progress. F-1 radioteletype in those 20-, 40- and 80-band sectors not open to voice work opens up opportunity for some traffic circuits to be maintained by this means. What we do with these new tools depends on how we handle them. We can do well if we have vision and sense and a working of all amateur groups together instead of at cross-purposes. Our early adjustment to changes is the keynote to success and progress. Full integration and tie-ins between c.w. and 'phone nets and any new RTTY circuits, using the customary method of common membership in different kinds of nets, should give us the best over-all communication means of message distribution to every town and city in the land.

The use of 20 and 75 meters for 'phone will be especially welcomed by those amateurs who have felt the pinch of fewer good operating hours on 10 meters in this part of the sunspot cycle. A number of ARRL section 'phone nets have already issued cordial invitations to newcomers to join in net operations. For still greater extension of traffic coverage, ARRL suggests the appointment in each such net by the NCS of a liaison station that can secure messages from and take messages to the c.w. net in that same state. This should assure message deliveries via the city and outside coverage of both our 'phone and c.w. nets. Cordial invitation to all is likewise extended to review page 130, Jan. QST, on the Official 'Phone Station appointment. Report monthly voice activity to your SCM (address on p. 6) and ask him for the OPS application form.

Early indications are that 40-meter 'phone will be quite popular. Some will already have tried it in the second week of ARRL's DX Test. Forty is a proven band, a favorite for years of consistent productive amateur use, both tops in general contact work and for specific purpose schedules. Some c.w. nets are registered there; some are planning moves within Forty in which they hope to find clear operating spots, some frequencies free from broadcast interferences from outside the Americas or from amateurs. There will be some new 'phone nets. We're happy to consult present and future Net Registration lists to help coordinate any and all plans for net or systematized use, to avoid or minimize potential interference. What happens DX-wise in distribution of amateur stations in this band in the face of these changes remains to be seen.

Frequency-shift radioteletype now can be used as an additional h.f. band privilege. Such circuits with 60-w.p.m. capability can be envisioned as paralleling, assisting and supplementing present organized c.w. and 'phone networks. RTTY work to date has been more experimental than trafficwise. Single RTTY circuits set up by amateurs have proved themselves ideal for distribution from a collection point (as from N.Y.C. and Los Angeles exhibit stations last holiday season) to the c.w. and 'phone nets having organized outlets. Bearing in mind that until there are many more stations active by this mode than now only full tie-ins with existing nets can give wide distribution of traffic to all points, this can all be changed if enough of the teletype gang set their sights on a traffic objective to

prove the real merit such equipment possesses in that direction. SCMs will welcome reports of traffic and other results from all using RTTY, and our same net registration facilities can be used to minimize QRM. If their interest is "traffic interest" those reporting members using c.w. or RTTY are likewise eligible for ORS appointment if they report their traffic activity and apply to

the SCM for such recognition.

Now there's one thing more we can try to do to help give point (and place) to organized teletypers. That's to specify by voluntary agreement and designation additional National Calling and Emergency frequencies for RTTY, and another working frequency in each band, for traffic or extensive rag-chewing using this mode. Such voluntary planning in this field corresponds closely to accepted amateur pattern and practice. Ham nets call their roll on one channel, with extensive operation and traffic on neighboring channels. A large group in v.h.f. mobile and teletype work with interest in auto alarms has already utilized the principle on one ARRL common calling frequency, 29,640 kc. Having such a frequency helps any group get together, promoting ease of getting results. For RTTY users, as with the c.w. or 'phone counterpart, such a plan calls for a minimum number of TTuser crystals (for stability and frequency insurance). From the standpoint of the general amateur user of a band, it minimizes danger of sporadic RTTY interference to have such designations. This is the best protection for the RTTY gang itself, since general squawks to FCC about QRM might lead to tighter frequency-band restrictions for the teletype. If the RTTY gang is to have a chance to use such gear in RACES, a channel or two in the 3500- to 3510-kc. RACES segment should be suggested soon by FCDA. Such is under consideration at present. A working frequency here is not at this date of writing possible, but word is awaited soon. Tentatively a calling frequency at 3620 kc. has been designated, after study in the Amateur Radio Teletype Society of ARRL Net Directory registrations. Word is awaited likewise from the Southern California Radio Teletype Society concerning additional radioteletype calling and working frequencies that have been tentatively put forward by ARRL for study and comment; these have the advantage of keeping clear of VE 'phone and DX band-edge frequencies and allow doubling and tripling from single (control) frequencies.

mugae (contrary) mode	
RTTY Calling and Emergency Frequency	RTTY Working Frequency
3620 kc. 7070 kc.	3.5-3.51 Me. (under study) 7075 kc.
14,140 kc.	14,150 kc.
21,210 kc.	21,225 kc.

All readers and especially those with RTTY interest are invited to try out the above channels for calling and working and then to comment. Interest in teletype work is on the increase; note that two societies are already making RTTY their major purpose. If there are still others, let's hear from you.

—F. E. H.

MEET THE SCM.

Vermont's SCM, Raymond N. Flood, received his first literate with his present call, WIFPS, in February, 1933. His station, located in the bedroom, consists of an HT-18 VFO, 807 buffer-doubler, two T-55s final, 200 watts, and an SX-71 receiver. Folded dipoles are in regular use for 10, 20, 40, and 80 meters.

SCM Flood has held Official Relay Station, Official 'Phone Station, Official Bulletin Station, and Emergency Coordinator appointments and is a charter member and president of the Tri-County Amateur Radio Club. An ardent participant in ARRI. contests, he was section winner in the 1950 10-Meter WAS Contest, the 1951 Sweepatakes, and the 1951 DX (c.w.) Contest. In addition to Code Proficiency, DXCC, and WAS certificates, W1FPS also



has been issued Public Service certificates for his noteworthy work during the New England Flood of 1936 and the 1930 Northeastern Hurricane. During the 1936 flood he set up his transmitter at police headquarters in Brattleboro and, operating with emergency power, handled a quantity of press and other information.

Ray also is interested in astronomy and science and participates in such active sports as swimning and sking. He obtained his commercial radio experience as radio operator and monitoring officer for the Federal Communications Commission and as radio operator for the Merchant Marine. At present he is a bindery foreman, employed by the Vermont Printing Company.

WIAW OPERATING SCHEDULE

A detailed schedule of W1AW operations appeared on page 67 of March QST. This schedule remains in effect without change. The next listing of Headquarters Station operations will appear in the April issue.

A.R.R.L. ACTIVITIES CALENDAR

Apr. 11th-12th; CD QSO Party (c.w.)
Apr. 16th CP Qualifying Run — W1AW
Apr. 18th-19th; CD QSO Party ('phone)
May 9th; CP Qualifying Run — W60WP
May 15th; CP Qualifying Run — W60WP
June 6th-7th; V.H.F. Contest
June 7th; CP Qualifying Run — W60WP
June 15th; CP Qualifying Run — W60WP
June 15th; CP Qualifying Run — W60WP
July 3rd; CP Qualifying Run — W60WP
July 14th; CP Qualifying Run — W60WP
July 18th-19th; CD QSO Party (c.w.)
July 25th-26th; CD QSO Party ('phone)
Aug. 1st; CP Qualifying Run — W60WP
Aug. 1st; CP Qualifying Run — W60WP
Aug. 1st; CP Qualifying Run — W60WP

Apr. 3rd: CP Qualifying Run



Most amateurs who jump in at the crucial time and perform a public service using their own time, their own facilities, and more often than not their own pocketbooks, do it because of the satisfaction they get out of knowing that their effort have brought comfort, safety or preservation to someone. Once the thing is over, they forget it and look added to see how they might be better prepared next time. We think this is the proper and most beneficial attitude, and the attitude with which most service-minded amateurs approach this phase of annateur radio.

Tais is the real spirit of public service, which the League recognizes by issuing Public Service Awards. Thousands of these awards have been made and most of them have been will deserved. A few may inadvertently have been given to amateurs whose eligibility was questionable. The question as to who shall and who shall not get a Public Service Award has been troublecome. One doesn't ask for such an award, you know. For general information and reference as need be we print the defirite policy to be followed now and henceforth on Public Service Award.

 Public Service Awards are issued only to amateurs who actually participated in a communications emergency involving the health or safety of a segment of the general

 The Public Service Award is a spontaneous recognition of service performed, and is not issued to any amateur who asks for or demands it.

3) It is issued only if the service performed is reported to ARRL and publicized in QST within a reasonable time. Such issuance is not normally made until after the issue of QST containing the account of the emergency is in distribution (so it can be referred to on the certificate).

4) ARR will value the recommendations made by SCMs or other field officials and will act on them provided the above requirements are met. But an amateur should work for a Public Service Award. The aim should be performance, not reward. The PSA is simply a means of recognitions of the provided that t

nition, not an end in itself.

We want to keep the standards high, and we think you do too. As indicative of this, some recipients of the award have on occasion even returned their certificates saying they did not feel they really deserved them, that all they did was report into an emergency net during an emergency. These fellows deserve at least an A for attitude as compared to one "demanding" the certificate, which states on its face it is unsolicited! The general experience gives fraternity approval to the above policy.

Note we have a new National Calling and Emergency Frequency for 40-meter 'phone, Still to be selected are similar frequencies on 21 Mc., both 'phone and c.w. Who has some suggestions? We have not yet picked NCE frequencies on this band, pending some expressions of sentiment from the field. If we don't get any, we'll have to pick them at random. Let's hear from you, gang.

Speaking of NCE frequencies, we have recently received a crequest from W68LX that we ask all amateurs to tisten before transmitting on NCE frequencies. A good suggestion, but it should apply to all frequencies. Always listen on your transmitter frequency before throwing on that carrier! We cannot avoid QRM on our bands, but if we are a little careful we can avoid QRM to emergency operations. All it takes is a little consideration.

As for the NCE frequencies, particular care should be taken to listen before transmitting. We do not believe in the practicability of keeping them clear for calling purposes only, but we ought to have one frequency on each band on which we on make directional or general calls for assistance, be it emergency or otherwise. If you must use one of them for other purposes, please give a listen first to make sure you are not camping on something important.

On January 14th, southwestern Minnesota was hit by a severe sleet storm followed by a blizzard that crippled

telephone and telegraph communications in that area. The town of Fairmont was the hardest hit. WBRPT and WBBZT of Fairmont immediately went on the air on a full time basis. During the bliszard they acted as emergency control stations and alerted stations in St. Paul, Minneapolis, Albert Lea, Mankato, Worthington, Jackson, Faribault, Sioux City and Mason City as outlets for traffic. Much Western Union traffic was handled, and new reports were relayed from WBRHT in Minneapolis to WBRPT and then to the local radio station for transmission. Approximately 200 emergency messages were handled. Stations participating were WS RPT ZTB FIT RHT JDO MXC BQJ LCM FAJ ATD BHY UCV JIE and TJA, — WSMXC, SCM Minn.

We have a brief statistical report from WIRFJ on "Operation Icicle," detailing some of the work performed by the Stratford AREC gang during an early-January ice storm in southern Connecticut. The operation was largely concerned with servicing units of the Stratford Public Works Department. Operating on the 10-meter band, main control was WIWIG, with subcontrols WITLO and WIRCV also active, WITLO was operating on emergency power. Mobile units participating were WIs BGP FMU GVK IAY and TCW. Operation was conducted over a period of 21 hours. The clock-like efficiency of this well-organised AREC unit was much appreciated by Stratford officials.

Approximately 100 amateurs assisted in "Operation Palisades," a civil defense alert conducted in N. J. Civil Defense Area I on Nov. 22, 1952. Nineteen fixed stations and 20 mobiles were spotted throughout the area, with some 100 or more messages being handled during the exercise which lasted from 1300 until 1500. Two networks — one of fixed stations and the other of mobiles and portables were in operation. Amateur Radio Coördinator Steve McCallum, WZZBY, expresses pride with which the boys maintained strict on-the-air discipline and performed their jobs with efficiency and dispatch. He also asserts that conscientious drilling was the biggest single factor that made this possible.

A great deal was learned by the San Bernardino AREC gang during a simulated emergency on Nov. 23, 1952. The simulated disaster was an A-bomb drop on Los Angeles. The alert was at 0300 and when it was wrapped up at 1811 all the AREC members knew that they had had a workout like they never had before. The expert traffic handlers (and we have many) carried the load, but all available operators got a chance to operate, which was a real initiation to some of them. The traffic count at the San Bernardino County NCS (W6IZP) was 380. All stations except two were portable. Twenty-five mobiles were on call but not used in this operation as all operators were needed to handle the unexpected volume of official c.d. traffic. Over 50 amateurs participated. The two most important things we learned are: (1) all (even the experts) need more net and traffic experience; (2) more portable self-powered gear is needed.

— W6HKD, EC San Bernardino Area, Calif.

On December 7, 1952, thirty Milwaukee Radio Amateurs' Club mobileers and Emergency Radio Truck crew members participated in a highly successful civil defense exercise involving every piece of fire apparatus in the city. After a briefing session, 19 mobiles traveled to dispersal points where they were joined by fire trucks and supporting vehicles. Communications to the mobile dispersal battalions was provided by using the MRAC Emergency Radio Truck, which was connected to the control center by field telephone. Operation was simultaneous on 75- and 10-meter 'phone so any mobile in the area would be able to take part. The Emergency Truck operated under its call W9HRM. The Marquette University Amateur Club station W9ODD assisted as a repeater.

Sixty messages were handled in all, mostly involving the movement of fire-fighting equipment. Officials were amased at the excellent dispatch with which traffic was handled. The test was well reported in the local press and TV news shows with full credit to the amateurs participating.

Sixteen SEC reports received for December, 1952, activities, representing 2891 AREC members. This winds up the year, and perhaps a brief summary is in order. The following

sections were represented 100% in 1952: East Bay, E. Fla., Tenn., W. N. Y. These reported better than 6 of the 12 months: Ark, B. C., Colo., Ga., Los A., Santa Clara Valley, Saak., Wis., S. N. J., So. Dak., Nevada, N. Y. C. These reported 6 times or less (but they did report); Maine, San Diego, Ala., Montans, Okla., W. Mass., Wash., Indiana. Iowa, W. Va., Vt., Nebr., Mo. A total of 29 sections out of 72. It shouldn't be much of a trick to do better than that in 1953, should it? Remember, it isn't necessarily your SEC who is at fault. He can't very well report anything if he doesn't receive any EC reports to base reports on.

CODE-PRACTICE STATIONS

The following is an up-to-date list of all stations transmitting code practice in the ARRL Code-Practice Program:

W1ACT, Fall River ARC, 57 Richmond Street, Fall River, Mass. 3545 ke., Mon., Wed., Thurs. and Fri. 1900 EST, beginners' speeds.

WIMNG, Arthur Zavarella, 1702 Main Street, Agawam, Mass. 29,500 kc., Tues, and Thurs. 1900–1930 EST, advanced speeds.

WISRB, Al Vesce, 84 North Main Street, Thompsonville, Conn. 29,600 ke., Mon., Wed. and Fri. 1930-2030 EST, beginners' speeds.

WIVEG, Carl Norris, 128 Meadow Street, Westfield, Mass. 29,500 ke., Tues, and Thurs. 1830-1900 EST, beginners' speeds.

W2FSL, Adolph F. Elster, 53 Commercial Avenue, Avenel, N. J. 3675 kc., Sat., Sun. and holidays. 0730-0800

EST, beginners' speeds.

W2GNI, Jim Chupp, 85 West Main Street, Smithtown
Branch, N. Y. 1895 kc., Mondays. 2000-2030 EST, beginners' speeds.

W2HEI, William Teso, Mountain Avenue, Hillburn, New York, 3950 ke., Sat. and Sun. 1400–1500 EST, 5–18 w.p.m. W4IYT, Andrew C. Clark, 41 Lenape Drive, Miami Springs, Fla. 28,700 ke., Mon. through Fri. 2030–2130 EST,

beginners' speeds.

W4RUR, E. J. Blatt, 536 16th Avenue So., St. Petersburg, Fla. 28,050 kc., Mon. and Wed. 1900-1950 EST, 6, 9, 14, 18 and 22 w.p.m.

9, 14, 18 and 22 w.p.m.
 W5MRD, Omer Sanders, Box 194, Danville, Arkansas.
 3885 ke., Mon., Wed. and Fri. 1600–1630 CST, 5, 7, 10

3885 Ke., Mon., Wed. and Fri. 1000-1030 CSF, 3, 7, 10 and 15 w.p.m.
W6JZ, Ray Cornell, 909 Curtis Street, Albany, Calif.
3590 ke., Mon. and Fri. 5, 7½, 10, 13 and 20 w.p.m., and

Wed. 15, 25, 30, 35 and 45 w.p.m., 1845 PST.
W7FWD, O. U. Tatro, 513 N. Central, Olympia, Wash.
3646 ke., Mon. through Fri. 1700 PST, 4, 6, 16 and 25

w.p.m. W7RKA, Zane Casey, Route 2, Box 73, Hood River, Oregon. 7290 ke., Mon. through Thurs. 1930-2000 PST, 3, 5 and 8 w.p.m.

5 and 8 w.p.m.
 W9ODD, Stephen P. Victor, 615 N. 15th St., Milwaukse,
 Wis. 29,224 kc., Mon., Wed. and Fri. 1930–2030 CST,

beginners' speeds.
W9U1N, Joseph H. Kadlee, 1148 Ashland Ave., Evanston, Ill. 7240 kc., Sat. and Sun. 0800-0900 CST, 5-7½
w.b.m.

W6BOL, R. A. Prehm, 1130 Delaware Avenue, St. Paul, Minn. 29,200 kc., Tues. and Wed. 1900-1930 CST, individual letters to 6 w.p.m. and 8-15 w.p.m. practice.

dividual letters to 6 w.p.m. and 8-15 w.p.m. practice.

WBEGQ, Robert McMullin, Route 1, Leigh, Nebr. 3690ke., Mon. through Fri. 1700-1745 CST, 5, 7½, 10 and 13
w.n.m. with text from the Braille Technical Press.

w.p.m. with text from the Braille Technical Press. W#PXH, Quentin Johnson, 125 N. Berry Rd., Glendale 19, Mo. 29,500 kc., Mon. and Wed. 1900-1945 CST, 3, 5 and 7 w.p.m.

W#QDF, W. H. Du Bord, 10247 Midland, Overland, Mo. 29,600 kc., Mon. and Wed. 2000-2100 CST, 5, 8, 10 and 13 w.p.m.

CODE-PROFICIENCY PROGRAM

Twice each month special transmissions are made to enable you to qualify for the ARRL Code Proficiency Certificate. The next qualifying run from W1AW will be made on April 16th at 2130 E8T. Identical texts will be sent simultaneously by automatic transmitters on 1887, 3855, 7130, 14,100, 21,020, 28,080, 52,000 and 146,000 kc. The next qualifying run from W60WP only will be transmitted on April 37d at 2100 PST on 3590 and 7248 kc.

Any person may apply; neither ARRL membership nor

an amateur license is required. Send copies of all qualifying runs to ARRL for grading, stating the call of the station you copied. If you qualify at one of the six speeds transmitted, 10 through 35 w.p.m., you will receive a certificate. If your initial qualification is for a speed below 35 w.p.m., you may try later for endorsement stickers.

Code-practice transmissions are made from W1AW each evening at 2130 EST. References to texts used on several of the transmissions are given below. These make it possible to check your copy. For practice purposes, the order of words in each line of QST text is reversed during certain of the slow-speed transmissions. To get sending practice, hook up your own key and busser and attempt to send in step with W1AW.

Date	Subject of	of	Practice	Text.	from	February	QST
------	------------	----	----------	-------	------	----------	-----

April 1st: The "Ultimatie". . . , p. 11

April 2nd: Structural Details of the Detroit C.D. Portables,

April 7th: An 80-and 40-Meter Antenna System for the

Novice, p. 29
April 10th: The Clapp Oscillator — and How, p. 19

April 13th: Mechanical Bandpass Filters, p. 22 April 15th: A Solf-Contained VFO Rig, p. 25

April 21st: Low-Voltage Filament Supplies, p. 35

April 24th: Practical Adjustment of the Gamma Match, p. 32

April 27th: Magnetie Ceramics: Ferrites, p. 44

April 30th: Notes on V.H.F. Conserter Design, p. 52

DX CENTURY CLUB AWARDS

HONOR ROLL

G2PL242	W3CPV235
W6AM 238	W6SN 235
W3GHD237	W4BPD234
W3JTC237	W6MEK234
W2BXA236	W8NBK 233
W3KT 236	W3EVW 233
G6ZO236	
	W6AM 238 W3GHD 237 W3JTC 237 W2BXA 236 W3KT 236

RADIOTELEPHONE

R.A	DIOTELEPHO	NE
W1FH223	W8HGW202	W6DI195
PY2CK222	ZS6BW 201	8M5KP 198
VQ4ERR216	W9RBI 200	W2APU 104
XE1AC 213	W1JCX200	W2BXA194
W1NWO204	W1MCW 195	

From January 15, 1953, to February 15, 1953, DXCC certificates and endorsements based on postwar contacts with 100-or-more countries have been issued to the amateurs listed bases.

NEW MEMBERS

G2WW178	W4DRK 103	W4EXO100
DL1KB127	EA9AP103	W4HYW100
DL3GZ118	SM7VX103	DL1VR100
WØVIP106	WØLWG 101	VS6BA 100
W2VRE103	W1D8F100	ZS5KF100

RADIOTELEPHONE

G2WW136 PY2AHS110	E12L 104	
	TIDOT A 100	

ENDORSEMENTS

W3GAU231	KG4AF166	W3AYS122
W3OCU220	CN8MI161	SM3AKM121
W6AMA220	W2UWD142	W2YTH 120
W6SAI 211	ZS5CU142	CE4AD 120
W4TM 202	ON4GC141	VS6AE 120
W5GEL 201	W1ZD134	W8YIN117
G8IG201	W6MEL 134	W5OLG116
W8BKP200	PAØLR 132	SM5AQW 112
W2BJ 190	SM5AQV132	W408U111
GM3DHD180	W2ATE 130	W5WI 110
WØTKX172	I1UB 130	W6YK 110
W8FJN171	LA2B129	VE3ADM 110
ON4NC171	PY2DV 128	VE3HB110
W7AH 166	W3CTJ 127	

BADIOTEL ERRONE

	ODSAB	ZS5CU	126

TRAFFIC TOPICS

A printed page without an illustration on it is something the average reader quickly skips and goes on to a page a little less dull. We try to get some kind of pictures, diagrams or cartoons on these pages every month, but we are scraping the bottom of the barrel and need some help.

Don't any of you traffic men own cameras? Send us a snap of yourself at your operating position, or some ideas for cartoons or something. Or do you want us to carry out a threat made long ago to start printing pictures of ourselves!

Miscellaneous January traffic reports: (1) The Transcontinental Relay Net handled 3034 messages in 31 sessions, averaging 98 per session; six stations were active. (2) The Transcontinental 'Phone Net handled 2154 messages during January; 43 stations participated. (3) The Early Bird Transcontinental 'Phone Net handled 177 in 13 sessions, averaging 13 per session; 31 stations participated.

National Trafic System: You have to hand it to the boys. We are having one of our best seasons yet, from an organizational standpoint, but it certainly is not because of the excellent traffic-handling conditions we have had. Propagationwise, the weather has been horrible. The few who have given up have our sympathy — but the fact is that they are very few. Generally speaking, it is heartwarming to hear the guys keep trying when signals are so weak and watery as to be all but inaudible. Once in a while we are treated to nothing worse than bad QRN, but when QRN and QSB combine it's wicked. And we have heard many DX men talk about the excellent conditions on 80 this year! Goes to show you, it's all in the point of view.

One noticeable thing has been that conditions for local contact are not too bad before 1900 local time. In view of the fact that most section nets are not observing the 2200 NTS-recommended session anyway, some of the regional nets are likewise ceasing operation of their 2130 sessions and/or having an early early session at 1800 or 1830. This early session can take the place of the night-before late regional

sessions, and can dovetail nicely into the 1900 section net.
Considering everything, it's not a bad idea. We are not
changing the NTS structure because of what (we hope) is a
temporary condition, but one might well consider that this
would come under the heading of a "temporary expedient to
insure movement of traffic." Regional managers might do
well to consider the possibility. Come apring or summer,
perhaps the long-skip evening characteristics of 80 will taper
off and we can return to normal schedules.

	J	an	ua	ry	re	po	ria:
--	---	----	----	----	----	----	------

Net	Sessions	Traffic	High	Average	Most Consistent
EAN	22	501	52	22.7	IRN. 4RN
CAN	18	394	77	22.1	9RN, TEN
PAN	22	693	268	31.5	All
IRN	39	189	21	4.8	W. Mass.
2RN	44	239	16	5.4	NJN
3RN	31	182	24	5.8	W. Pa.
4RN	39	268	29	6.8	Fla.
RN5	44	286	27	6.8	Ala., La., N. Tex.
RN6	40	805	93	20.2	BAN
RN7	54	512	71	9.5	Wash.
8RN	36	105	17	3.0	Ohio
9RN/TLJ	26	466	70	18.0	Ind.
TEN	30	743	62	24.7	Most 100%
TRN	44	82	- 8	1.8	Ont.
MSN (Min	n.) 27	148	15	5.5	
QIN (Ind.)	77	765	59	9.9	
TLCN (low	a) 22	413	43	18.7	
	-	ottomics.	-	,	
Total	614	6791	268	11.0	
Record	649	8064	268	14.2	

A very interesting EAN bulletin by WSSCW reveals that EAN handled 9120 messages in 1952, an average of 33.5 per session. The net got together 270 times, with ZRN missing only two sessions and 1RN only three. Forty-eight EAN certificates have been issued since the start of EAN, and they haven't been easy to get. Latest recipients of certificates are W1AYC, W4SHJ, W4UWS and VE2AMB. EAN has a record to be proud of.

has a record to be proud of.

Four CAN NCS reports were missing in January. W9JUJ appreciates the help received during this period.

IRN certificates have been issued to Wls CUH FTH HRV KYO MX and NDB. Due to bad conditions, W1BVR has promised to give credit for attendance to anyone who says he was on but couldn't be heard by the NCS.

Thirteen 3RN sessions were missed in January due to

4RN is getting some QRM on 3615 kc. from a Swim

commercial.

W5QHI, new RN5 manager, indicates bad need for a representative or two from Western Florida section. Any

RN6 now includes Arizona, Colorado, New Mexico and Utah, embracing the former twelfth Regional Net. W7UTM has been representing Utah. How about the rest?

New RN7 manager W7PKX says he received wonderful support from the gans for his first report. He suggests Hq. make available a printed form for weekly statistics, to be used by net managers. Anybody else feel a similar need? A new and very fine net bulletin has been put out by WSDSX, SRN manager.

W9PVH has received a 9RN certificate.

VE4HL has received a TEN certificate. He takes the place of an old standby, VE4AM, who passed away recently. VE2AMB is doing a big but lonely job in representing Quebec on TRN.

BRASS POUNDERS LEAGUE

Winners of BPL Certificates for January traffic:

Call	Orig.	Reed.	Rel.	Del.	Total
W6IAB	. 62	2573	2413	74	5122
KG6FAA	. 276	1469	1363	76	3184
W6KYV	. 113	1372	718	648	2851
W7IOQ	. 43	1364	1	1372	2780
W2BTB	. 42	1239	1310	32	2623
WØTQD	. 4	972	940	12	1928
W4U8A	. 103	696	699	97	1595
W9JUJ	. 35	825	683	19	1562
W4PL	. 12	763	666	84	1525
KA2HQ	. 325	476	204	258	1260
KG6ADZ	. 28	596	596	26	1246
W8AUJ	. 15	605	512	55	1187
K6FCA	. 14	540	495	32	1081
KZ5AA	. 84	436	387	49	986
W7BA		435	407	28	901
WØKHQ	. 5	438	434	4	881
WØSCA	. 3	428	424	4	850
K4WAR	. 146	305	298	75	824
WØCPI	. 10	375	348	27	760
W2ZOL	. 5	412	294	18	726
W6HK		318	251	67	707
W8RJC	. 18	319	291	27	655
W2RUF		319	259	39	651
W70NM	. 7	305	301	7	620
W6GQY		401	197	4	607
W6GYH		296	172	119	601
W8NZZ		281	274	6	569
KL7AIR		265	266	15	562
W5MN		260	67	201	559
WØBVL		209	265	8	547
WØBDR		267	255	6	531
W9NZZ		189	0	189	527
W2BO		252	210	42	519
W6VHN		256	239	13	516
W4AKC	. 8	277	204	20	500
Late Reports:					
W3PZW (Dec.)	. 30	1248	1208	40	2526
KL7LJ (Dec.)	. 150	800	689	111	1750
W2NSD/2 (Dec.)	.1683	0	0	0	1683
KG6ADZ (Dec.).	. 29	517	517	31	1094
KASAB (Dec.)	. 141	230	191	39	601

BPL for 100 or more originations-plus-deliveries:

The BPL is open to all operators who report to their SCM a message total of 500 or more or 100 or more originations-plus-deliveries for any calendar month.

ELECTION NOTICE

(To all ARRL members residing in the Sections listed below.) You are hereby notified that an election for Section Communications Manager is about to be held in your respective Sections. This notice supersedes previous notices.

Nominating petitions are solicited. The signatures of five or more ARRL full members of the Section concerned, in good standing, are required on each petition. No member shall sign more than one petition.

Each candidate for Section Communications Manager must have been a licensed amateur for at least two years and similarly a full member of the League for at least one

continuous year immediately prior to his nomination.

Petitions must be in West Hartford, Conn., on or before noon on the closing dates specified. In cases where no valid nominating petitions were received in response to previous notices, the closing dates are set ahead to the dates given herewith. The complete name, address, and station call of the candidate should be included with the petition. It is advisable that eight or ten full member signatures be obtained, since on checking names against Headquarters files, with no time to return invalid petitions for additions, a petition may be found invalid by reason of expiring memberships, individual signers uncertain or ignorant of their membership status, etc.

The following nomination form is suggested: (Signers will please add city and street address to facilitate checking membership.)

Communications Manager, ARRL 38 La Salle Road, West Hartford, Conn.	[place	and	d	at	e]
We, the undersigned full members of the					
Division, hereby nominate					
as candidate for Section Communications Section for the next two-year term of office		er fo	OF	th	is

Elections will take place immediately after the closing dates specified for receipt of nominating petitions. The ballots mailed from Headquarters to full members will list in alphabetical sequence the names of all eligible candidates.

You are urged to take the initiative and file nominating

petitions immediately. This is your opportunity to put the man of your choice in office.

— F. E. Handy, Communications Manager

Section	Closing Date	SCM	Present Term Ends
Iowa	Apr. 1, 1953	William G. Davis	June 16, 1953
Yukon *	Apr. 15, 1953	W. R. Williamson	Mar. 17, 1949
West Indies	Apr. 15, 1953	William Werner	Aug. 15, 1952
Maritime *	Apr. 15, 1953	Arthur M. Crowell	Oct. 16, 1952
Hawaii	Apr. 15, 1953	John R. Sanders	Jan. 14, 1953
Maine	Apr. 15, 1953	Orestes R. Brackett	Apr. 16, 1953
South Dakota	Apr. 15, 1953	John W. Sikorski	July 2, 1953
Western Florida	May 15, 1953	Edward J. Collins	July 29, 1953
N. Y. CL. I.	May 15, 1953	George V. Cooke, jr.	July 31, 1953
Eastern Florida	May 15, 1953	John W. Hollister	July 31, 1953
North Carolina	June 1, 1953	J. C. Geaslen	Aug. 15, 1953
East Bay Southern New	June 1, 1953	Ray H. Cornell	Aug. 16, 1953
Lonnous	Tone 15 1082	Lloyd L. Gainer	Aug. 26 1053

* In Canadian Sections nominating petitions for Section Managers must be addressed to Canadian Director Alex Reid, 160 Logan Ave., St. Lambert, Quebec. To be valid such petitions must be filed with him on or before the closing dates named.

ELECTION RESULTS

Valid petitions nominating a single candidate as Section Manager were filed by members in the following Sections, completing their election in accordance with regular League policy, each term of office starting on the date given.

Edgar M. Cameron, jr., W6FJH	Dec. 15, 1952
Charles M. Bove, WØMXC	Feb. 17, 1953
C. L. Arundale, WøGBJ	Mar. 1, 1953
L. L. Daily, W7JDB	Mar. 1, 1953
R. M. Heck, W3NCD	Mar. 17, 1953
Arthur W. Plummer, W3EQK	Mar. 21, 1953
Howard C. Bellman, W6YVJ	Apr. 13, 1953
Vincent J. Haggerty, W6IOX	Apr. 12, 1953
	Charles M. Bove, WøMXC C. L. Arundale, WøGBJ L. L. Daily, W7JDB R. M. Heek, W3NCD Arthur W. Plummer, W3EQK Howard C. Bellman, W6YVJ

JANUARY CD OSO PARTIES

Both the e.w. and 'phone sections of the January CD Parties were lively affairs. The usual large group of ap-pointees were in there pounding away on c.w. and the 'phone shindig brought out more than the usual number of participants. Leading contender for c.w. score honors was W6CMN; Bill scored 125,104 points and carried on the determined effort made by the West Coast contingent to keep their area of the field organization in the limelight. Runner up on points, and leading all comers in number of contacts was W4KFC with 117,150 points and 419 Q8Os. W1EOB was third in line, 112,720, and earned the distinction of working more sections than any other contestant, 59. In the 'phone fracas, W4NYN turned in a sterling performance, scoring 31,500 from 140 contacts with 45 sections. Second highest phone total was chalked up by WSNOH, who worked the same number of sections as third place entrant W4NYN, but managed thirteen more contacts. Listed below are the other high claimed scores. The figures following each call indicate the claimed score, number of contacts and number of ARRL sections worked. Final and complete results will appear in the April CD Bulletin.

C.	W.
W6CMN 125,104-246-56	W2KEL56,870-235-47
W4KFC117,150-419-88	WSHOX 56,810-242-46
W1EOB 112,720-411-50	W9GIL 56,250-225-50
W8NBK96,990-359-53	WØJNC55,750-217-50
W4SHJ96,600-338-56	W9LRG/955,500-222-50
W7KWC 89,964-196-81	W9CMC 54,315-209-51
W4SAT 85,860-319-83	W2VNJ 53,970-250-42
W4BZE 84,270-313-53	W1AQE 52,140-237-44
W1MX80,580-316-51	W3AXA50,095-228-43
W1AW* 77,000-301-80	W2CWK 50,095-227-43
W8NOH73,185-282-51	W9SDK 49,750-192-50
W8ZJM71,655-275-61	W9MEM 49,220-211-46
W7OPO69,975-165-47	W3NRE48,600-180-54
W#VBQ68,380-258-52	WØPHR 47,150-205-46
W3LXE 65,250-261-80	W2NIY 46,440-210-43
W4FF63,450-264-47	W4LK
W2ZVW62,500-243-80	W2ATE 45,100-205-44
W6YHM61,908-153-44	W4SNH 45,000-195-45
W1CRW59,670-234-51	W1LHE43,475-179-47
W10DW58,800-245-48	W2GUM 43,200-216-40
W2COU58,000-225-50	W3NOE43,000-200-43

'PH	SNC
W4NYN 31,500-140-48	W2MHE14,100- 94-30
W8NOH22,800-115-38	W9FYM13,695-75-33
W4FV20,786-102-38	W4HUW12,410- 72-34
W6CHV18,810- 60-33	W7KWC10,530- 45-26
W6UGA 17,010- 63-30	W2COU10,500- 68-35
W5DEJ 15,840- 81-36	W8ZJM8,820- 57-28
W4SHJ 15,680- 91-32	W8HOX8,620- 69-26
WØIQY15,390- 81-38	WØPHR7,140- 51-28
W3MLY 15,015- 91-33	W8MGC7,105- 49-29
W2ZVW 14,960- 81-34	W2ATE7,080- 59-24
W9KDV14,700- 84-38	W3LXE6,500- 50-26

WIWPR one.

NATIONAL CALLING AND **EMERGENCY FREQUENCIES**

C. W.		PHONE					
3550	ke.	14,050	ke.	3875	kc.	14,225	kc.
7100	len	99 100	bo	7950	ko	90 640	ko

During periods of communications emergency these channels will be monitored for emergency traffic. At other times, these frequencies can be used as general calling frequencies to expedite general traffic movement between amateur stations. Emergency traffic has precedence. After contact has been made the frequency should be racated immediately

to accommodate other callers.

The following are the National Calling and Emergency Frequencies for Canada: c.s....3335, 7050, 14,060; 'phone — 3815, 14,160 kc., 28,250 kc.



 All operating amateurs are invited to report to the SCM on the first of each month, covering station activities for the preceding month. Radio Club news is also desired by SCMs for inclusion in these columns. The addresses of all SCMs will be found on page 6.

ATLANTIC DIVISION

EASTERN PENNS YLVANIA — SCM. John H. DuBois, W3BXE — SEC: 1GW. RMs: AXA, BIP. PAM:
PYF. E. Pa. Nets: 2610, 3915 kc, On Jan. 31st at Fogelaville,
an AREC/c.d. meeting was held, attended by appronimately 25 officials and their families. Highlights of this successful get-together included introduction of ECs, new
emergency net organization, present Fa. e.d. system and
policies. New officers of the Frankford RC for 1953 are as
follows: LEZ, press. LXN. vice-press; BES, seey. treas., RT
sctivities mgr. On Jan. 20th, officials of Pa. C.D. Council
witnessed as on-the-air demonstration of Philadelphia of
c.d. communications truck, ADE: represented Pennsylvania
in the Governors-to-President Relay held Jan. 19th. Traffic:
Jan.) W3HGW 156, QLZ 71. CHU 13, BES 3, (Nov.)
W3HGW 144. Obet.) W3HGW 85.

MARYLAND-DELAWARE-DISTRICT OF COLUMBIA — SCM, James W. John, W3OMN — PWB, Civil
Defense Radio Officer for the District of Columbia, reports
RCCS plan for D. C. has been approved by FCDA and
FCC. This was the first RACES plan approved in the
country. RGX and 4NTZ presented RTMA, at their Feb.
3rd meeting in New York City, with the problems encountered in TV1 and by TV1 Committees. Newly-elected
officers of the Aberdeen Proving Ground Radio Society are
UCR, pres.; LDD, vice-pres.; TFQ, secy-treas.; 4RDT,
station manager; and 6DTR, station trustee. LJV is completing a 100-wat rig with bandpase coils and a BC-221
as VFO. HC originated GPR message for Delaware and
JE originated the same for Maryland. QZC had his antenna
cut down by the telephone company but is working out FB
by using a radiator. QCB is QNI on ESN and SSN Nets.
FVRC had its annual dinner meeting with the Frankford
Radio Club on Jan. 17th at the New Colonial Hotel in
D. C. Sixty members of both clubs, plus 910P, had an FB
time. The Washington Mobile Club has started a club
publication which is called Road Noise. CDQ made a
broadcast on V.O.A. with QQS regarding the Governors-toPerceident Relay. Twenty-two stations in the GPR. The Washington
Radio Club held it

hard work. UCV is sporting a well-modulated signal on 75 meters with his new Viking. EFM is taking a stab at 2 meters with a nice signal. FXT, with a new transmitter and receiver, is all ready for 75 meters. Traffic: K2BG 215, W2RG 90, Z1 15, ZQ 5, ASG 2, HAZ 2.

WESTERN NEW YORK — SCM, Edward G. Graf, W2BJV — SEC: UTH. RM: RUF. PAM: GSS, NYS meets 3615 kc, 7 and 10 p.m.; 3980 kc, 630 p.m. and Sun, 8:30 a.m. NYSS is on 3595 kc, at 8 p.m. NYSCD is on 3509.5 kc, and 3993 kc, at 9 a.m. Sun; also on 3509.5 kc, at 7:30 p.m. Tues, and Thurs. QNA is on 160 meters with 75 watts. WN2NHW visited ORI. IPC worked VE2AEV, the Mail Atric Exp. Force. CEZ is in the Vets Hospital at Buffalo. QHH worked E1 and G on 160 meters with single 616 and worked FR7ZA on 14 Mc. for the 217th country with 35 watts. CPN has a new antenns farm. The RAWNY held its annual auction. GTI was picked to send the QTC from the Governor of New York to the President. The Black River Valley ARC now is affiliated with ARRL. Officers are YQQ, pres.; KN2APW, secy.-treas. GHS is instructing friends so they can take the Novice Class exams. QLL is on s.s.b. with WE357B at a kw. New officers of the Lockport ARC are ZOC, pres.; ALR, vice-pres.; KLL, secy., EHO, treas. UTH and QY visited the Lockport Radio Club; the SEC discussed AREC work in conjunction with c.d. The C.D. Net on 3509.5 kc. now handles ARRL and 10-meter rig with 2E26 final. New officers of the Corning Radio Club are UMJ, pres.; YLY, vice-pres.; QLI, act. dir. QAA is building "scope, audio oscillator, and s.ab. rig. UX Phas sixteen-element beam on 2 meters. PPA and VLL are on 2 meters. RJY is on 10-meter n.f.m. with a kw. NYS C.W. didn't miss a night during 1952. SSCW, manager of EAN, reports that 2RN was tops in attendance with only two misses in 1952 and that this attendance mark was due to the faithful representation of NYS members. GHS is on 80 meters with 10 watts and random-length antenna. An NYSS Net certificate has been issued to HKA. Appointments renewed: QNA. UYG, RXW, and FAN as OPS; U

RUT 45, ZRC 45, IFF 29, HKA 24, CPN 23, CYD 20, FEB 44, RJJ I3, PYC 12, K2DG 11, W2JWU 11, ZHU 7, QLI 5, KN2CBM 2, W2GHS 1. (Dec.) K2DG 28, W2ZHU 9, HKA 6.

WESTERN PENNSYLVANIA—SCM, Ernest J. Hlinsky, W3KWL—RM: GEG, NUG, PAM: AER. New appointees are AEV as OO, Class III, RSB as OPS, and KWL as OES. Up Erie way, QN reports that there are 29 AREC members. 6 mobile units and 4 emergency radio units. CNSEQ, better known as 3LFK, returned for a visit with the old gang. In tribute to the late SLM's enthusiastic interest in amateur radio his parents have turned over his station to the Radio Association of Erie as a permanent emorrial to their son. A3NQA has been appointed as Pennsylvania Director of the MARS. LKJ, MED, NXK, NOJ, ODF, OIE, and PIE are hitting it hard on Able and Baker 75 'phone nets. The Bucktail Amateur Radio Clubtlells us that the McKean County Net on 3825 Kc. at 9:00 A.M. Sun. has been fairly active. IIX, club correspondent, can be reached by writing to him eare of Bucktail Club is active. Looks like £1Q is back on 2 meters. LQD is working DX on 80 meters with low-power rig. Officers of the WPARCC are GEG, pres.; MPO, vice-chairman; NCD, secy.; and OD, treas. Club interest in holding a Division Convention is needed. Send a representative to the WPARCC are dech meeting, learn the facts, and give your convention is needed. Send a representative to the WPARCC are ache meeting, learn the facts, and give your mount of the sendent of the monthly program Phil Rand and hard has part of its monthly program Phil Rand and hard the sendent of the monthly program Phil Rand and hard the sendent of the monthly program Phil Rand and hard progr



A FAIRLY WELL KNOWN and popular tank circuit, the MB-40L, was recently mentioned in several transmitter articles. One of these, by George Grammer, described a transmitter using a Pi network in the plate circuit and an MB-40L tank in the grid circuit. However, one complaint George had was that obtaining constant grid drive over all bands from a low impedance line was difficult and might require some compromise.

Fortunately, we at National had already anticipated the need for a variable coupling system and were in the process of adding a swinging link to the MB-40L when the article by George Grammer was printed.

This new, more flexible model is called the MB-40SL and it is now in production. The link is electrostatically shielded and in the normal installation is completely adjustable from the front panel. The new tank duplicates the electrical performance of the MB-40L and can be used in the same type of installations. These include final tank assembly, grid tank, push-pull or single ended, or interstage tuning with capacity coupling. The tank tunes through 80, 40, 20, 15, 11 and 10 meters without switching or coil changing. You can see how this will encourage operation in more than just the favorite band where the rig happens to be all tuned up.

Although the MB-40SL was originally intended for operation in the grid circuit of a medium to high power transmitter, there are other applications of equal value such as the final tank in that new Field Day rig or the low power standby emergency transmitter.

Another application that frequently arises is use as a multi-band antenna tuner. In this regard, the MB-40SL can be used anywhere that conventional tuned circuits can be used, provided that proper loading of the tank by the antenna system is obtained. In any antenna tuner this condition must be satisfied to prevent the loss of power in the tuner.

The MB-40SL should be used with low impedance tubes for best results. Tubes that operate with 300 to 400 volts on the plate are the best bet. Much greater efficiency will result with the use of a tube operated at 400 volts drawing 100 ma. than with one operated at 600 volts at 65 ma. In addition, the chance of condenser arc-over is much greater with the 600 volt supply than with the 400 volt supply. When too high a supply voltage is used, the unloaded current will be excessively high.

The MB-40SL provides a compact flexible unit that can be entirely front panel operated. Don't forget this when planning your new rig.

WALTER T. HYNES



(Continued from page 8.2)
does fairly well. AJN wonders if he is the first U. S. station to work a VE2 on 40-meter 'phone shortly after the Canadians were authorized 'phone operation on that band. AER says 20 meters is very erratic. LXE piled up a nice 'phone score in the SS Contest. CA did a nice job of handling: nessages in the Governors-to-President Relay. Traffic (Jan.) W3NCD 80, NUG 65, UHN 60, CA 33, KUN 26, NRE 25, LXE 8, AER 7. (Dec.) W3NCD 25, KUN 19, AER 9, MIZ 6, KNQ 4.

CENTRAL DIVISION

NRE 26, LXE 3, AER 7. (Dec.) W3NCD 25, KUN 19, AER 9, MIZ 6, KNQ 4.


CENTRAL DIVISION

ILLINOIS — SCM, H. F. Lund, W9KQL — Section Notes: ILN (c.w.) 3515 kc.; IEN ('phone) 3940 kc. SEC: HOA. PAM: UQT. RM: BUK. A. B. Brand, HOA, 1211 Harlem, Rockford, is the new SEC for this section. This will effectively tie the amateur service to State c.d. work. QLZ has moved up to Asst. Director. Chicago Area Radio Club Council officers for '53 are A'H, chairman; GGX, vice-chairman; GVO, secy. VEZ, treas. The Council is looking forward to a successful year and expects many additional clubs in its membership. PYT has replaced FHP as c.d. director for the North Suburban Club; the club station, UXB, now is active. New club officers are OLU, pres; INN, vice-pres; QSJ, secy.; 27N, treas. QSJ is playing nreemaid to the electronic brain at U. of L. Peterson and the council of the club station, UXB, now is active. New club officers are than at Ripon as Dad can use his 260-wat trig. ONN and IJX are recuperating nicely from tummy slicings, QBJ, OLU, WYO, and ZPK are s.b.bing. State CD Headquarters is planning to purchase a rig for use in emergencies. NN has given up chassing DX on 20 meters and has settled down on 40-meter c.w. JMG got so enthused selling equipment that he forgot to keep enough to remain on the air. OS is enjoying his new Globe King and finds the whole world at his doorstep without any TVI. BVY has constructed new antenna coupler to get more soup into the wire. NOO has moved to Wheaton, YIX and CEE are learning the ropes at State Police station K8HA as saxuilary operators. Blooming ton Club cd. committee consists of SXL, BFZ, and KYW. IMD has retured from the railroad and is living in Florida. Or an oversea QTH. GUW is rebuilding his kw. rig. KFX constructed a new mobile rig for 10, 20, and 75 meters. HUX debugged his bandwitching exiter in time for the DX Contest. SIE, QCQ, QAB, and OWP received Ad. Ct. tickets. The Midway Radio Club (Zion) and Lake County Club (Waukegan) combined facilities to supply communication f

as 765. New ORS are HQF, STW, RBX, OWZ, and SKP.
ZIB, WBA, KRJ, LZI, and GUX assisted in the attempt to locate FFI and his aircraft. OXH, SVC, and PPO received their Gen. Cl. licenses. Tr reports the 147.3-Mc. net in Indianapolis is operating. QAV is building a new shaek; FII has new Monitone. PQR is building 150-wat rig. POW has new VFO and BC-221. NJR is TVI-proofing his rig. UNT has emergency receiver and transmitter for 7 Mc. Traffic: (Jan.) W9JUJ 1562, NZZ 527, YWE 313, WWT 218, TT 217, GLW 174. TG 142, BKJ 98, JBG 93, GMT 49, OLX 32, SKP 30, DGA 27, DKR 25, FSA 23, QID 22, WBA 22, KDV 19, FYM 17, DOK 16, NTA 16, BDP 14, PMT 14, ZIB 14, HQF 12, IFR 10, KLR 6, NTR 5, NHR 2, RDJ 2, Cbec.) W9WBA 45, NXU 23, GUX 20, IFR 5, NHR 2, RDJ 2, Cbec.) W9WBA 45, NXU 23, GUX 20, IFR 5, WISCONSIN — SCM. Reno W. Goetsch, W9RQM — SEC; GVO, FAM: ESJ. RMs: IQW, SFL. Thone Net GEN) 3950 kc., 6 F.M. daily. CW. Net (WIN) 3625 kc., 7 F.M. daily: slow speed 6:30 F.M. Mon.-Fri. Mobile and c.d. requency, 29,620 kc. CXY received CAN net certificate. UCR was designated as Acting NCS of WIN slow net for February by SFL. Licensed operators at ODD include FCK, IDW, JGG, KMO, LSK. GOA, ORQ, and WNs RUF, SFJ, WKF, and WKS. OTL is interested in schedules with other schools. SDK had a score of 49,750 in the CD Party. FCF is the proud owner of a Viking II. HHD is working on a 75-meter vertical of empty juice cans! HID has a squelch circuit on the receiver for monitoring net frequency. Business will take VLL to Detroit for 3 months. Winners of the MRAC achievement award for 1952 are GIL 1st, RKP 2nd, and BSR 3rd. In the Novice competition we find Wn9VBZ 1st, RZD 2nd, and VOD 3rd. LVR is back in Milwaukee. FDX collected some new walpaper in the form of Extra Class amateur, 1st Phone, and 2nd Telegraph Commercial licenses. BEN net certificate was issued to QJB. WIN net certificates were issued to CXY, FCF, and ERW. The FLARC, at Madison, elected RBI, TRC, at Madison, elected RBI, TRC, at Madison, elected RBI, TRC, at Madison, elected RBI, TRC,

DAKOTA DIVISION

SOUTH DAKOTA — SCM. J. W. Sikorski. W#RRN — SEC: GCP. RM: OLB. PAM: UVL. Ex-5PKC now is #URN at Rapid City AFPs, where he is a captain in the USAF. He is building an 813 final and now is working 40 meters. The Prairie Dog ARC is publishing a club builetin. The club divided into two groups and conducted a simulated emergency at this month's meeting. DTB. Centerville, has joined USNR. ZVV is working for KVV at Yankton. KVV, after an absence of many years, is building a new rig. GDE now is using Meissner 150B. A new call in Sioux Falls is WN#NAB. K#PAL. Rapid City AFFs, has been changed to K#FCR. TI is working 160-meter mobile. Two-meter enthusiasts will find a nightly 2-meter net operating in the northeast corner of the State at 2130 CST. Is there any other 2- or 6-meter activity in the State? After an absence of many years SMV is on 80 and 40 meters with 35 watts, and needs only Delaware for WAS in two months of operation. Black Hills ARC: How about station activities? Traffic: (Jan.) W#UVL 103, OLB 91, PHR 54, EHO 34, W18WX/#914, K#FAL9. (Dec.) W#FAL94 W18WX/#931. MINNESOTA — SCM, Charles M. Bove, W#MXC—Asst. SCM: Jean Walter, #KYE, SEC: BOL. RMs: DQL. RPT. PAMs: UCV, HEO. A new club known as the 8t. Johns University. For information call the president, John Theisen. #BPI, of Wadens, or C. T. Kcogh, at Collegeville, Minn., has applied for membership in the ARRL. Code classes are held live evenings per week at the club rooms at 8t. Johns University. For information call the president, John Theisen. #BPI, of Wadens, or C. T. Kcogh, at Collegeville. All Novices are urged to check into the Minnesota Junior Net which meets daily except Sun. at 1800 CST on 3690 kc. Single side-banders progressing in the State. Llw. TLE. DXZ, and ATD cas he heard just about every evening on the high end of 75 meters. Prospective single side-banders are AlS. BWF, BJR, BFK, AUS, and HXR. Two new Novices in St. Paul are WNBLSH and LQF. The MSN now has a roll call of 31 members. I think DQL is doing a swell job. Our Director, PHR, has a s

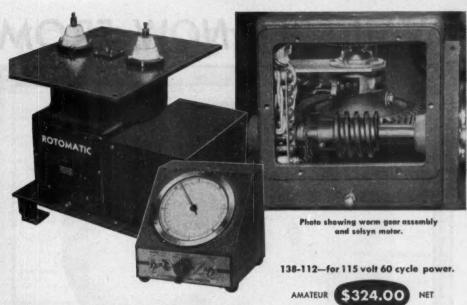

RUGGED, ALL-WEATHER CONSTRUCTION JOHNSON antenna rotators and parasitic beam arrays Withstands high wind loading—Severe temperature changes

Safely supports heavy multiple arrays. Heavy wind loads absorbed by oversized steel worm gears. Ball bearing gear motor delivers full torque at low temperatures. Heavily plated, corrosion resistant, slip rings and contacts.

1200 to 1 Gear Reduction Continuous Rotation Positive Locking

Instantly Reversible Motor Noiseless Slip Rings RF Rating 21/2 KW

Selsyn Direction Indicator Rotator housed in a sturdy aluminum casting . . . % " steel rotating table . . . ¼" steel tilt type base plate. The 138-112 Rotamatic assembly includes a control box with an illuminated bearing indicator, antenna relay switch and beam reversing switch. Auxiliary slip rings permit beam switching with an accessory antenna relay (138-108).

JOHNSON Parasitic Arrays

Strong, lightweight elements of aluminum alloy tubing grounded to the center of the boom assembly. Element length and spacing is continuously variable. Balanced open wire transmission lines may be ing section. Coaxial transmission lines matched by "Gamma" or half "I" section. matched to the driven element by means of an adjustable "T" match-

Boom assemblies are of 2" galvanized steel tubing. U-bolts and element support clamps fasten each element securely to the boom, yet their positions are readily adjustable. The assembled beam requires no cross-bracing and has low wind resistance.

Write direct or ask your distributor for your free copy of Catalog 715, giving complete information on JOHNSON parasitic arrays, element kits, boom assemblies and other available beam accessories.



Low temperature gear drive system with weatherproof cover removed.



Elements clamp anywhere along boom.




E. F. JOHNSON COMPANY

CAPACITORS, INDUCTORS, SOCRETS, INSULATORS, PLUGS, JACKS, DIALS, AND PILOT LIGHTS

210 SECOND AVENUE SOUTHWEST . WASECA, MINNESOTA

AVAILABLE NOW FROM

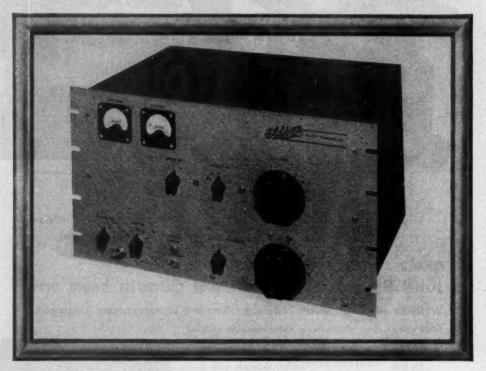

EXCITER/FINAL TR-1 TV

Amateurs throughout the country have rigs which were ideal before the Tennessee Valley Indians. Too much time . . . too much money is invested in them to discard. Now you and Eldico have the answer. Use your present rig with the Eldico TR-1 TV Exciter/Final and operate TVI Proofed.* Just replace your R.F. Section with the TR-1 TV Exciter/Final, Use your own power supplies and modulator—and go on the air TVI Proofed.*

300 watts AM Phone or CW; Band switching 80-40-20-15-10 meters; Complete shielded tetrode final; Each circuit metered—will fit standard 19" rack panel cabinet; Pi Network Output—Built-in Low Pass Filter. Remember. Operate your own rig — TVI Proofed.*



* TV1 Proofed means special circuitry, shielding, and filtering to eliminate spurious and harmonic energies that result in television interference.

44-31 DOUGLASTON PARKWAY, DOUGLASTON. L. I., N. Y. - BAyside 9-8686

YOUR DISTRIBUTOR!

ACK RADIO SUPPLY CO. Birmingham 3, Alobama

ALLEN & HURLEY Trenton, New Jersey

ALLIED RADIO CORP. Chicago 7, Illinois

ALMO RADIO CO. Philodelphia 6, Penna.

ALMO RADIO CO. Atlantic City, N. J.

ALMO RADIO CO. Wilmington, Delaware

ARROW ELECTRONICS INC. New York 7, New York

WALTER ASHE RADIO CO. St. Louis 1, Missouri

GEORGE D. BARBEY CO. Reading, Penna.

BLUFF CITY DIST. CO. Memphis 3, Tenn.

CAMERADIO CO. Pittsburgh 22, Penna.

CONSOLIDATED RADIO CO. Philadelphia 6, Penna.

CRAWFORD RADIO Hamilton, Ont., Conada

DE MAMBRO RADIO Providence, R. I.

DOW RADIO, INC. Pasadena 4, Calif.

M. N. BUFFY & CO. Detroit 26, Michigan

W. H. EDWARDS CO. Providence 3, R. I.

THE ELECTRONIC EQUIPMENT CO. Fort Worth 3, Texas

EVANS RABIO Concord, New Hampshire

FORT ORANGE RADIO DIST. CO. Albany 7, New York

R. C. & L. F. HALL, INC. Beaumont, Galveston, Houston, Texas

HARRISON RADIO CORP. New York 7, N. Y.

HARRISON RADIO CORP. Jamaica 3, L. L., N. Y.

COMPARE THESE REASONABLE COSTS WITH ANY TRANSMITTER

Chassis, panels, meters, tubes, components, hardware all included. Nothing else to buy!

SEE YOUR DISTRIBUTOR TODAY!

HARVEY RADIO CO. INC. New York 18, N. Y.

HENRY RADIO STORES

HENRY RADIO STORES

NUDSON RADIO

HUBSON RADIO New York 19, N. Y.

KIERULFF & CO.

MONTAGUE RADIO

MYTRONIC CORP.

NEWARK ELECTRIC CO.

OFFENBACH & REMUS CO. San Francisco 2, Calif.

OLSON RADIO WAREHOUSE Akron 8, Ohio

PURCHASE RADIO SUPPLY Ann Arbor, Michigan RADIO, INC. Tulsa, Oktahomo

RADIO AMATEUR CENTER Raleigh, N. Carolina

RADIO ELECT. SERV. CO. OF PENNA. INC. Philadelphia 6, Penna.

RADIO ELECT. SERV. CO. OF PENNA. INC. Allentown, Penna.

RADIO ELECT. SERV. CO. OF PENNA. INC. Euston, Penns.

RADIO ELECT. SERV. CO. OF DEL. INC. Wilmington 22,

RADIO ELECT. SERV. CO. OF N. J. Affantic City, N. J.

RADIO ELECT. SERV. CO. OF N. J. Camden, New Jersey

RADIO EQUIPMENT CO. Lexington, Kentucky

RADIO EQUIPMENT CO. Norfolk 10, Virginia Charleston 5 5 C

RADIO PARTS, INC.

RADIO PARTS CO. INC.

RADIO PRODUCTS SALES Los Angeles 15, Calif.

RADIO PRODUCTS SALES CO. Denver 2, Colorado

Seattle, Washington

BADIO SHACK CORP.

RADIO TELEVISION RAYTELL S. A.

RADIO WHOLESALE & SUPPLY CO. Honolulu 11, Hawaii

TELEVISION INC. New York 13, N. Y.

TELEVISION INC. Boston 10, Mass.

RABIO WIRE TELEVISION INC. Newark 2, New Jersey

THE RADIO CENTRE Montreal, Quebec Canada

SEATTLE RADIO SUPPLY, INC. Seattle 1, Wash.

SREPCO INC. Dayton 2, Ohio

VALLEY ELECTRONIC SUPPLY Burbank, Colif.

VALLEY RADIO DIST.

VAN SICKLE RADIO SUPPLY

WESTERN DISTRIBUTORS

WIRELESS RADIO & TELEVISION Conton, Ohio

YUKON RADIO SUPPLY INC. Anchorage, Alaska

Right for the Job!

DELCO-REMY
EXTRA-OUTPUT
GENERATORS
AND MATCHING
REGULATORS


(Medium Duty-40 and 50 Amperes)

Delco-Remy extra-output generators are an economical answer to the electrical needs of cruising taxicabs, suburban police cars, rural mail cars... other vehicles with additional lights, two-way radios, special electrical equipment in moderate to heavy-duty service. For this type of operation, these Delco-Remy extra-output generators offer the triple advantages of low initial cost, simple installation and economical maintenance.

DELCO-REMY 40-AMP. GENERATOR has low cut-in...charges at curb idle from 11 to 17 amperes... attains full output at 18 mph when using a three-inch pulley.

DELCO-REMY 50-AMP. GENERATOR has slightly higher cut-in, about 9 mph... attains full output at 19 mph... for vehicles customarily operating at higher speeds, with minimum of allow driving.

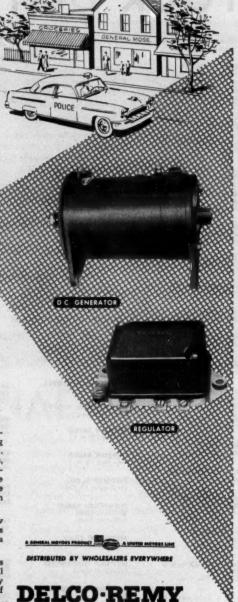
See your nearest United Motors distributor for further information and application data.



Division, General Motors Corporation

Anderson, Indiana

WHEREVER WHEELS TURN OR PROPELLERS SPIN

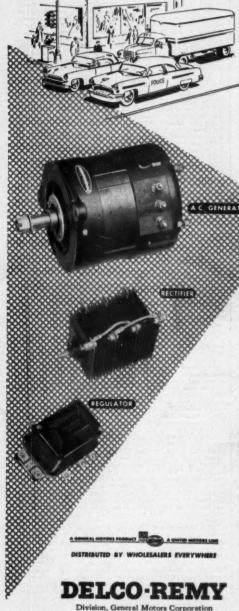

Anderson, Indiana

Right for the Job!

DELCO-REMY
ALTERNATING
CURRENT
GENERATOR

(ALTERNATOR)

A. C. - D. C. charging system for vehicles with extra-heavy electrical loads

Here's the answer for "problem" vehicles—Delco-Remy's new long-lived A.C.-D.C. charging system! It's specifically designed to meet the extra-heavy electrical demands of police prowl cars, big city taxis, and other vehicles equipped with two-way radio, floodlights or any extra electrical units . . . ample current reserve picks up discharged battery quickly in operation.

With output ranging from 30-40 amperes at curb idle to 90 amperes at higher engine speeds, the new Delco-Remy A.C.-D.C. charging system meets all electrical needs under the toughest operating conditions. Included in the new system is the A.C. generator (alternator), a matching regulator for accurate voltage control and a rugged, dependable dry-plate rectifier which converts generator A.C. output to direct current.

Application packages for popular makes of cars and trucks are now available. The conversion job is simple, complete and profitable. For further details and for application data, call on your nearest United Motors distributor.

WHEREVER WHEELS TURN OR PROPELLERS SPIN



"MAPC"-everything reduced **but Quality & Performance**

The "MAPC", a miniature "APC", was engineered for use in equipment where an unusually compact, high-quality air dielectric trimmer is required. Its base size is only 15/16 inches by 25/32 inches.

This capacitor was carefully designed to resist effects of temperature, moisture and vibration. Rotors and stators are fabricated by soldering brass plates to supporting members and then nickel-plating the assemblies. Terminals are tinned to permit easily made solder joints. Two tapped brass mounting studs fastened to the silicone-treated steatite base make it possible to mount the capacitor without grounding the rotor.

The "MAPC" is available in six standard models with capacities ranging from 2.3 mmf to 100 mmf. Because of its low minimum capacity and low inductance, it is ideal for VHF applications.

Have you received your copy of the new Capacitor Catalog? It lists Hammarlund's complete line of standard capacitors sold by responsible dealers from coast to coast.

SEND TODAY!



HAMMARLUND

HAMMARLUND MANUFACTURING CO., INC. 460 WEST 34th STREET . NEW YORK 1, N.Y.

(Continued from page 84)
band. The Mobile Amateur Radio Corps now has a 1-kw.
rig on 75 and 80 meters and plans to use it as a control
station for the 75-meter mobile rigs. The Mobile Corps put
on one of the largest simulated emergencies in the State
called "Operation Crystal." This operation covered all of
Hennepin County. The Civil Air Patrol, under the control
of Col. Webber, supplied about thirty planes to act as a
bomber squadron. The local fire departments and civil
defense also participated, Traffic: WBTQ 456, QYZ 176,
UCV 154, FDS 142, DQI, 133, RPT 128, SWB 111, CGK
104, ZTB 71, GGQ 41, JIE 38, HFY 33, FIT 32, TJA 26,
RXL 24, BUO 23, CID 23, GTX 21, K6EA/9 20, WBBWM
17, CQY 16, CXM 16, BQK 14, MXC 12, DYD 11.

DELTA DIVISION


RXL 24, BUO 23, CID 23, GTX 21, KOEA/s 20, W9BWM 17, CQY 16, CXM 16, BQR 14, MXC 12, DYD 11.

DELTA DIVISION

ARKANSAS—SCM, Fred Ward, W5LUX—Thanks for the reports, fellows. EA has resigned as SEC so that he will be free to move to a broadcast job. MRD is new SEC. AY handled the Governors-to-President message in good shape. We all were grieved to learn of the passing of UAA. WUH says the boys at Searcy are organising a club and QIP reports the ASTC Amateur Radio Club has a new call for the club station, YUZ. The rig is p.p. 813s, 800 watts. PHP won the G. E. Award as the outstanding amateur of 1952 for his fine service during the Judsonia emergency. PZB renewed his appointment as EC for Fort Smith, HPL renewed as EC for Sebastian County, and RW1, although still having some TVI, has renewed his EC and RM appointments. We are indebted to WNSWVD and the Little Rock Amrad Club for putting the license-tag bill into the Legislature. WUH and YHV claim the Novice QSO record of 5 hours and 4 minutes. MRD has a new Viking rig for the ir, operator. MRD is starting code practice transmissions. Times and frequency will be announced. Traffic: W5VN 23, EA 16, LUX 11.

LOUISIANA — SCM, Robert E. Barr, W5GHF—FTU now is portable W7 in Idaho and is an operator at K7FBL. FTU has been quite a rolling stone, having formerly been JAZCV, AliAV, JA3AR, W3EVG, W3EVG, water at the work of the company of t

LOOK at any part UP CLOSE!

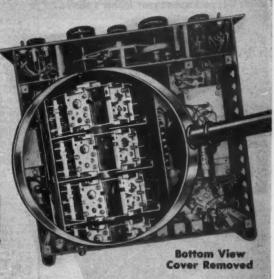

THE SP-600-JX Communications Receiver USES ROTARY TURRET FOR MAXIMUM SENSITIVITY!

A rotary turret, uniquely incorporated into the "Super-Pro 600-JX," makes possible the placement of the coil assemblies of the two RF Amplifier stages, Mixer stage and First Heterodyne Oscillator stage directly adjacent to their respective sections of the four-gang tuning capacitor and the individual tubes.

Coil assemblies are mounted on the turret. Turning the band selector switch to any one of the six frequency bands places the required coils immediately in their correct positions. This arrangement increases receiver stability, provides uniform maximum performance from band to band, and simplifies servicing.

Every part of the "SP-600-JX" is designed to the highest standards of receiver design. The rotary turret is one example of the fine engineering in this magnificent 20-tube receiver.



The "SP-600-JX", the only professional communications receiver available that provides up to six crystal controlled frequencies, has a range of 540 kc to 54 mc. It is now being used by amateurs, the military services and by commercial organizations. Write to The Hammarlund Mfg. Co., Inc., 460 W. 34th St., New York I, N. Y.

Ask for Bulletin A4.

HAMMARLUND #

inside this package on your Jobber's shelf...



is the world's toughest transformer



there's nothing tougher than CHICAGO'S Sealed-in-Steel construction



H-TYPE

Hermetic sealing meets all MIL-T-27 specs. Steel base cover is deep-seal soldered into case. Terminals hermetically sealed. Ceramic bushings. Stud-mounted.




With 10" color-coded leads brought out through fibre board base cover. Lead ends are stripped and sinned far easy solCHICAGO "New Equipment" transformers (available in 3 mountings) feature one-piece drawn-steel cases—the strongest, toughest, best-looking units you can buy. The one-piece seamless design, enclosing an electronically perfect construction, provides the best possible electrostatic and magnetic shielding, with complete netic shielding, with complete protection against adverse at-mospheric conditions. For every application: Power, Bias, Filament, Filter Reactor, Audio, MIL-T-27, Stepdown—ask your electronic parts distributor for CHICAGO "Sealed-in-Steel" Transformers—the world's toughest with that ex-tra margin of dependability.

FREE "New Equipment" Catalog



CHICAGO TRANSFORMER

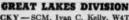SECT ADDISON STREET + CHICAGO 18, ILLINOIS



GREAT LAKES DIVISION

KENTUCKY—SCM, Ivan C. Kelly, W4TUT—Bad operating conditions and poor DX prospects made for lots of inactivity in and about Kentucky during January. Building and planning meets seem to have taken the place of activity. JUI now is a member of the Quarter Century Wireless Club; he still can hit the nose in frequency measuring as our only Class I OO. JCN splits time ragchewing and dreaming of Lake Cumberland fishing. &MWV/4, the main operator at K4WBG, is getting Harvey Wells mobile going on all bands. TAV reports meeting three regular nets and seven out-of-state net schedules. Kentucky would be lost without Marty. CDA proudly reports Delaware and now needs but two more for his WAS. URF was busy helping to prepare for the big exhibit of the University of Louisville Ham Club on Engineer Day. He also found time to build all-band exciter and new antenna-tuner system for all bands. URF is back in the fold again. JPP is fixed portable in Florida. The more reports you fellows send in the better this report will be. Traffic: W4TAV 349, WHC 119, K4WBG 56, W4JCN 21, PXX 16, CDA 11, JUI 3, URF 1.

MICHIGAN—SCM, Fabian T. McAllister, W8HKT—Ast, SCMs; J. R. Beljan, SSCW; R. B. Cooper, SAQA; M. C. Wills, SCPB. SEC: GJH. RMs; YKC, UKV. New use in nominating me as SCM. I assure you that the same democratic principles and ideals so well preserved by our former SCMs will be retained during my term of office. Let us all work together to keep amateur radio in this section truly "of, by, and for the amateur," Just as it required your help to put the job over. It is no accident that the Michigan section ranks as one of the leading traffic acctions of the country. You fellows have worked hard to put it there, New officers of the Edison Radio Club har AV, pres' YRB, vice-pres; MTH, secy-treas; EQY, act. mgr. ZWM is sporting a beginner's traffic net in the Novice band. All are welcome, on 3735 ke. at 2:00 r.m. Sundays. Traffic: (Jan.) WSRJC 655, NZZ 569, SCW 140, ILP 112, NOH 107, KLK 165, RTN 103, ELW 88, QLX 84, IK

FIRST ANNUAL OHIO INTRASTATE QSO PARTY APRIL 18-19

The Ohio Council of Amateur Radio Clubs will sponsor a QSO party, open to all Ohio amateurs, which will be held April 18-19, 1953, from 6:00 P.M. EST Saturday until 6:00 P.M. EST Sunday. All Ohio amateurs are urged to participate in this affair and to submit their logs to the contest man-

affair and to submit their logs to the contest manager.

Any and all amateur bands and any mode of emission may be used. There will be no power restrictions. Scoring: multiply the number of Ohio catations worked by the number of Ohio counties contacted. Each station may be worked but once regardless of band or mode of emission used. Logs should include call signs of stations worked, time, date, signal reports sent and received and the county in which the station is located. Operation about the following frequencies is recommended: 3550, 3740, 3860, 7100, and 7250. On the other bands, take your pick. The call "CQ Ohio" should be used on both 'phone and c.w. At least five appropriate certificates will be awarded to the highest seoring stations. Certificates will also be awarded to the Novices, the number of certificates being contingent upon the degree of activity.

All contest logs must be postmarked no later than May 1st, 1953, and should be sent to the contest manager, Hamlin King, WSEQN, 353 So. Arlington Ave., Springfield, Ohio.

OHIO — SCM, John E. Siringer, WSAJW — Asst. SCMa: C. D. Hall, SPUN, and J. Erickson, SDAE, SEC: (Continued on page 94)



IS THIS YOUR NEIGHBOR'S SET?

TVI CAN BE CURED

If your rig has Einsec radial-beam power tetrades and modern circuits you can be free of TVI worries, despite the steady increase in the number of VHF and UHF stations and receivers. Through the design of Einsec tetrodes, driving power requirements are exceptionally low—thus generation of TVI producing harmonics in the driver stages is practically eliminated. For a deluxe rig take advantage of quality construction and dependable performance, without complicated circuits, neutralization or TVI problems, that Einsec's complete line of radial-beam power tetrodes offers the amateur radio operator.

Eimac

For further information or a free copy of the handy 28-page booklet, "Care and Feeding of Power Tetrodes", write our Amateurs' Service Bureau.

SAN BRUNO, CALIFORNIA

Export Agents: Frazar & Hansen, 301 Clay St., San Francisco, California



UPB. PAM: PUN. RMs: DAE and PMJ. HNP is new EC for Lucas County. DAE is back home after a stay at University Hospital. On Jan. 17th. the OCARC met in Columbus. Topics discussed included Docket 10175. The process of the Columbus. The OCARC field Day Trophy was awarded to the Plusco Radio Club of Canton The next meeting will be field April 1th, and on the following wech and the OCARC intrastate 980 Party will be field. PBX is in charge of a.d. activities in Indian Hill Village as per approval of the village council. RO has just worked his 48th state and recently received his OTC certificate. The BCWRA now meets at the Akron Municipal Airport; Newly-elected officers are PWA, pres. HGJ, vice-pres. KDW, secy.: HH, treas.; NYS and BFH, signs, at arms. DG has a new 100-watt rig for 15 meters. MDW, MGW, MFA, and MGM are new operators in Dayton. Recently-elected Fort Hamilton officers are HXB, pres.; IUV, vice-pres.; UFF, secy.; and UNW, treas. New 10 meyers in the area are MDJ, MDT, and MDF, and HKK received his Extra Class license. DAD received his Extra Class license. DAD received his Extra Class license. DAD received his Extra Class license and WAS certificate. Our sympathies to BCQ, who recently lost his father. FVV is a newcomer to 220 Mc., with ULL about ready to go on. YPT, now in active service in the Far East, writes that he operated for awhile OYC certificate and that his sister passed her Novice Class scann. YGR, TRC secy., states that he, along with HSW, IZQ, and HNP, have readied their two operating rooms at the Red Cross Hq. A Viking II transmitter will be used. UZJ soon will be back on the air with a new rig from a new location. OVG writes that the Dayton gang is going to town in their Hamvention preparations. Other Dayton thems are being sponsored by the DARC, that the club membership is approaching the 300 mark, and that the musical-voiced ACE now is talking with his fingers with pronounced success on the DX bands. New QCEN Offeers are HQH, pres. CQM, vice-pres.; 4TP2, socy.; L. Dieselberg, treas., and

HUDSON DIVISION

HUDSON DIVISION

EASTERN NEW YORK — SCM, Stephen J. Neason, W2ILI — SEC: RTE. RMs: TYC. KBT. PAMs: IJG. K2CA. YOK is busy with new home. K2ACC is the temporary manager of our Section Novice Net (3716 kc.). UKA reports that a permanent manager will be selected soon. If interested in this net, contact UKA promptly so that your name can be included in the next bulletin and directory. IFP has a new Lysco 600 all-band exciter. Dave was awarded a Section Net certificate for activity on NYS. YDX and ZFL have been discharged from the Army. BTV is with WKNY part time. DVZ has moved to Dutchess County and is working for IBM. BSH has seven states to go on 3.5 Me. for WAS. George is to be congratulated for his help to KNs CKS, BSD, and CKO, who recently received their tickets. It's nice to hear Helen, BNC, back on the nets these days. VP is QRL on NYSEPN. ZQV, a longime member of ARSC, has been appointed Schenectady County EC. GTI was designated to handle the Governora-Decident message. RTE has been appointed as our new SEC. Ted is considered an excellent choice for the post and he will be very active in the section. I am sure that he will receive full cooperation from all concerned. Plans for a section: Ahd, net are well under way. For information, please contact PCQ. Activity is an indication of a live section; a proud member will report his activity as well as keep his endorsement up to date. Are you a proud member? Appointments: RTE as SEC. ZQV as EC, MHE and MRQ as OBS, MRQ as OO, RTE as OPS and OES. The cock of Official Observers is urgent. Inquire now. Traffic: (Jan.) WYTYC 175, EFU 71, MHE 56, ILI 55, AAO 40, IFP 29, BNC 24, CFU 22, KBT 16, (Dec.) WZWSS 124, IFP 60, LRW 49, BSH 13.

NEW YORK CITY AND LONG ISLAND — SCM, George V. Cooke, jr., W2OBU — Asst. SCM: Harry Dannals, 2TUK. SEC: KTF. RM: VNJ. PAM: YBT. AREC/(Conlinued on page 98)

SOUTHBRIDGE.

MASSACHUSETTS

EXPORT DEPT., - 13 East 40th Street, New York CANADIAN DISTRIBUTOR: Canadian Marcani Co. 861 Bay St., Tarento, Ontario

MALLORY HAM BULLETIN

Power for

Civil Defense Communications

-from MALLORY Vibrapacks

Amateurs active in the Civil Defense program report consistently that a Mallory Vibrapack (vibrator operated power supply) is the best all around source of high D-C voltage for portable-mobile transmitters and receivers. Anyone planning Civil Defense radio apparatus can save time and money by considering these Vibrapack features:

Versatility. Vibrapacks, unlike other power supplies, can operate as "double duty"

units, supplying both receiver and transmitter without special precautions. Because they are quiet electrically and mechanically, they can be mounted right next to sensitive equipment without fear of interaction. Light and compact, they fulfill every need of transportable equipment.

Dependable Power. They permit operation from a wet-cell storage battery—the most reliable and most widely available source of power for a really practical emergency equipment layout. They can be supplied to work with 6-volt automobile batteries, or with the 12, 24 or 32-volt batteries used in trucks, airplanes, boats and farm lighting systems.

Easy Service. Vibrapacks need no special tools or parts. They are built entirely of standard electronic components familiar to all amateurs.



Low Drain. Because Vibrapacks operate at higher efficiency than other types of power supplies, there is less battery drain—making possible the continuous operation so often vital during emergency communication.

Variety of Models. Seven different models of Mallory Vibrapacks are available to supply 125 to 400 volts at 15 to 60 watts. Thus, the power requirements of the transmitter or receiver can be matched exactly. The power supply operates at high efficiency, without power-wasting voltage dividers or dropping resistors.

Plan your power supply now—it's an important step in establishing a reliable and really workable emergency communication system. See your Mallory distributor for any further data you may need. Or write to us. If we can help smooth out a rough spot in vibrator power supply design, we're at your service!

P. R. MALLORY & CO., Inc. P. O. Box 1558 INDIANAPOLIS 6 INDIANA





A HIGHLY USEFUL INSTRUMENT FOR THE

Amateur * Engineer * Service Man Laboratory Technician • Experimenter

The New B & W Model 600 Dip Meter provides you with a convenient means of doing the job in a minimum of time with dependable accuracy.

It is an extremely sensitive and reliable piece of test equipment having innumerable uses in the Ham Shack, Service Shop, Electronic Laboratory, or Production Plant.

Armed with this versatile and indispensable Instrument, you eliminate the guess-work dur-Ing measurement of-tank circuit frequencies, antennas, feed line systems, parasitics, and other pertinent tuned circuit characteristics, with speed and accuracy.

The handy instruction manual furnished with each instrument covers full information on how to use the Model 600 as an Absorption Meter. Auxiliary Signal Generator, R. F. Signal Monitor, and several special applications as well. See it at all leading electronic parts distributors throughout the U.S. A. and Canada; or write for descriptive bulletin.

BARKER & WILLIAMSON, INC.

c.d. activity is moving along with excellent results. JSV, Queens EC, reports the 2-meter net very active (25 net membership, 16 stations active average attendance). This net is strictly AREC — no c.d. affiliation yet. There is close cooperation with the Red Cross with a station installed at Flushing Hospital, one at Flushing Red Cross, and another ready for installation at Jannices and control of the contro

FREQUENCY CONTROL A



(6)						
MIL CRYSTAL UNIT	BLILEY CRYSTAL HOLDER	PREQUENCY RANGE MEGLETICS S	OPERATING PERATURE MANGE (Contigrado)	FREQUENCY TOLERANCE OVER OPERATING RANGE		
CR-15	ARMANA	0.080 - 0.19999	-40° to +70°	上 .01%		
CR-16	AR23W	0.080 - 0.19999	-40: 10-472	± .01%		
CR-18	BH6A	0.8 - 15.0	E-846 +90°	土 ,005%		
CR-19	внел	DEMBA	55° to +90°	+ .005%		
CR-23	The DE	10.0 - 75.0	-55° to +90°	+ .005%		
CR-24	вн7А	15.0 - 50.0	-55 WERY	+ .005%		
CR-27	BHSA	0.8 - 15.0	DELLIO +80	± .002%		
CR-28	BHSA	DELTABLE	+70° to +80°	± .002%		
CR-29	AR2	0.080 - 0.19999	+70° to +80°	02 4000)		
CR-30	AR23W	0.080 - 0.19999	+70 12 10 15	± .002%		
CR-32	BH6A	10.0 - 75.0	DER-10 +80.	± .002%		
CR-33	BH6A	TONG F	-55° to +90°	+ .005%		
CR-35	BH6A	0.800 - 20.0	+80° to +90°	+ .002%		
CR-36	BHGA	0.800 - 15.0	80° to +90°	VSTALOZ%		
CR-37	вняя	0.090 -0.050	700	+ .02%		
CR-42	вня	0.050 2000	470° to 4-80°	± .003%		
CR-44	внел	15. 30	+80° to +90°	+ .002%		
CR-45	BHGA	0.455	-40° to +70°	<u>+ .02%</u>		
CR-46	BHGA	0.2 - 0.500	-40° to +70°	士 .01%		
CR-47	BHGA	0.2 - 0.500	+70° to +80°	± .002%		

BULLETIN NO. 43 CONTAINS A QUICK REFERENCE INDEX FOR MILITARY TYPE CRYSTAL UNITS-SENT UPON REQUEST

Bliley enverses

BLILEY ELECTRIC COMPANY UNION STATION BUILDING, ERIE, PA.



om molded carrying case. Series 40 is ideally dimen I engineered as a portable, compact test set to with hard usage of amateur radio, servicing, production

ties 40 offers features and components as incorporated in claign's" larger test sets, including: Retary Selection = 1% is and multipliers = heavy duty insulated pin lacks = large railed, easy reading mater.

SPECIFICATIONS

6 A.C.-D.C. & Output Voltage Ranges
all of 1000 ohms per volt.

\$\frac{4}{2}\$ B.C. & Output Voltage Ranges
all of 1000 ohms per volt.

\$\frac{4}{2}\$ B.C. Current Ranges: 0.-6-6-0-600 MA.

\$\frac{3}{3}\$ Resistence Ranges: self-contained batterles.

\$0\$000.500,000 ohms and 0.5 megehms.

\$\frac{4}{2}\$ Becibel Ranges from --2 to +70 DB.

\$\frac{4}{2}\$ Wirewound & Mertallized Resisters.

\$\frac{4}{2}\$ Only 2 Pin Justic serve all standard functions.

\$\frac{4}{2}\$ Recessed 6000 volt selery jack.

\$\frac{4}{2}\$ Anadized, etched aluminum panels

resistant to meisture and wear.

For this fine "Precision" Test Set at all leading radio parts and ham equipment distributors.

While for latest Precision entalog describing quality Electronic Test Instruments for all phases of modern radio-electronics—A.M., F.M. and T.V.

Precision Apparatus Co., Inc.

xport: 450 B'way, N. Y. City, U.S.A. Cables: MORHANEX In Canada: Atlas Radio Corp. Ltd., Toronto, Ontario

assistant to BAI, the communications chairman, has signed up all the county hams in the RACES program. Middlessex County C.D. HQ., at Rutgers Stadium, is a popular gathering spot for e.d.-minded hams. ENM, C.D. Arca 9 Radio Officer, conducted a successful communications test employing amateur radio facilities for c.d. alerts in Belmar, Bradley Beach, Avon, and Spring Lake, YLS, CGH, and SJI are very active in mobile work on 75 meters. NIE is aporting a new 32V-3 and 75A-2 receiver. HNY was a recent speaker at the GSARA. WSN is active again after a long lay-off. Reports still are coming in so will combine both Jan. and Feb. traffic in next month's report.

MIDWEST DIVISION


after a long lay-off. Reports still are coming in so will combine both Jan. and Feb. traffic in next month's report.

MIDWEST DIVISION

10WA—SCM, William G. Davis, W#PP—FZO has completed "Operation Flood," a 22-page story on the amateurs work during the Missouri River Flood. He reports election results of the club as follows: HFT, pres.; SVS, vice-pres; DJU, treas.; CXN, secy.; FZO, "immy-legs." AZR heads Woodbury County Comm. Dept. of Civil Decises, as well as being chairman of the Red Cross Disaster Committee. QVA reports that RQJ is a new member of TLCN and is active on TEN and RN7. NAY is active after a 3-year lapse. BBZ is working on rig and receiver for TLCN and is active in the AF MARS. CQL now is on with 300 watts. YBV has a new jr. operator, born at 12-31 F.M. just as the lowar 5 Net got underway. BLH, DIT, MIE, YKS, BVE, FDM, and YBV have received Section Net certificates. The Burlington Club elected MDU, pres.; NLA, vice-pres.; ex-9QGU, secy-treas. The IJARC has club night on the air each Fri. on 29.6 Mc. BWL reports two new hams in his area, WNEJSG and W9NAN. ATA will have a new QTA at Cedar Falls. FDL reports on the Muscatine gang as follows: KZW is going to college, GLJ is rebuilding, LJ is a newcomer on 40-meter c.w., VRD is chasing bugs in the rig, WNESF is colly for 60-meter phone. BGN now is on 75-meter phones. GDL reports to TEN and TLCN and calls DX. SCA and BDR make BPL again. AEH reports from Mesa. Aris. Traffic: WBSCA 859, BDR 531, YTA 198, CZ 156, BQJ 138, GVA 135, BZ 64, BVE 42, PZO 40, NYX 22. ELH 23. SCA and BDR make BPL again. AEH reports from Mesa. Aris. Traffic: WBSCA 859, BDR 531, YTA 198, CZ 156, BQJ 138, GVA 135, BZ 64, BVE 42, PZO 40, NYX 22. ELH 23. SCA and BDR make BPL again. AEH reports from Mesa. Aris. Traffic: WBSCA 859, BDR 651, YZA 198, CZ 156, BQJ 138, GVA 135, BZ 64, BVE 42, PZO 40, NYX 22. ELH 23. SCA and BDR make BPL again. AEH reports from Mesa. Aris. Traffic: WBSCA 859, BDR 651, YZA 198, CZ 156, BQJ 138, GVA 135, BZ 64, BVE 85, BDR 165, FDR 178, FDR 178, FDR 178, F

- SCM, Floyd B. Campbell, W#CBH - (Continued on page 100)

To You, Boldon's Goldon Be Sure of Your Installations . . . Use **Auniversury Moons** product performance that an come only from a "kno Aptitude-Tested how" that has grown thro ictual service since the inception of Radio. **MULTIPLE CONDUCTOR** an ability to co-op ate in pioneering new wires to meet or antici-• You know what you are doing when you use Belden Multiple Conductor Cables — they're ap-titude rated. They are designed to provide desir-able electrical characteristics, and rigid control pate industry's gro In the years that constant quality.
Specify Belden Radio Wires. This Belden Program Is-Belden Manufacturing Co., 4621 W. Van Buren St., Chicago 44, Ill. - 10 BE CONTINUED . . 41:34 tion Thickness 1/32" Radio WIRE Aptitude-Tested LINE

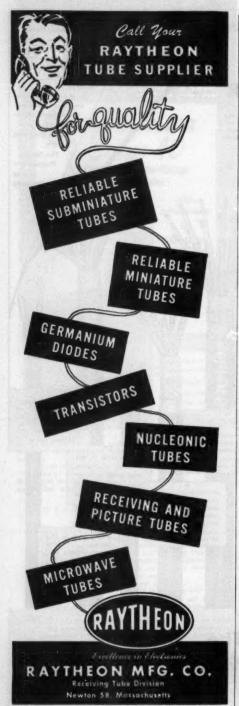

Asst. SCM: Thomas S. Boydston, \$VYX. SEC: JDJ. RMs: VYX, LJO. PAM: EUT. ODB is having QRM in the form of a new YL. AUH informs us that he is enjoying HO Railroading as another hobby. Anyone wishing to exchange ideas on HO RR, contact him at 705 E. 12th St., Grand Island, Nebr. Comes a report from RYG with Nebraska C.W., TEN, TLAP, RN7, and PAN net affiliations. VYX has accepted the appointment of Assistant SCM. We want to take space here to congratulate the AK-SAR-BEN Club and VYX and his gang for the swell job they did on the License Plate Bill. DW deserves congrats also. The Nebraska C.W. Net is perking in good shape. RDN is a new member of the Net. QXR and VEC are working on teletype circuit on 2 meters. Your SCM would like applications for OBS or any other appointment you might want. CBH, ATU, and CKZ are the interference committee for North Platte. AIN is bullding a portable rig in addition to helping ex-9RR regain his ticket and build up a rig. WNBMAO keeps Mon. through Fri. sked with LTD and CGM. For those interested, the Rocky Mountain Division Convention will be held at Estes Park on June 20-21. Traffic: Jan. W\$TQD 1928, RYG 297, FQB 79, YYX 70. CBH 48, AIN 34, ZJF 27, FMW 24, UVQ 11, WN\$MAO 11, W\$AUH, 7, IDO 6, QOU 6, EEA, 4, BWK 4, HXH 4, THF 4, YSK 4, HQQ 3, KBR 3, BUR 1, VPR/M 1. (Dec.)

NEW ENGLAND DIVISION

NEW ENGLAND DIVISION

NEW ENGLAND DIVISION

CONNECTICUT — SCM. Roger C. Amundsen, W1HYF—SEC: LKF. PAM: FOB. RM: KYQ. CN-3640, CPN-3880, CEN-29,680 & UNG is DXing on 40 meters. BGT now is on a.s.b. NFG is new EC for Hamden. New officers of Stratford ARC are TCW. pres; RFJ. view-pres; FMU, seep; UAC, treas.; URC. comm. off. A new claimant as the youngest ham in Connecticut is WN1WYF, Don Forshund, of Stratford. Another new Stratford Novice is YL WN1WZK. RRE lost his antenns in a school fire. NBP/WBO is going RTTY. Life spends more time on b.c. station WNAB selling ham radio. WN1WVI is new in Fairfield. Ellen, ex-6YYM, now is 1YYM but hubby Bob, ex-6YYM, only gets 1WPO. They are looking for a DX farm. LKF handled Governors-to-President Relay message through T1A. WIG now is on 2 meters. UZJ is interested in OPS appointment, URM in ORS. KGT is on 160 meters. PEA and ODW had antenna trouble in the ice atorm while DBM tried out his generator. Stratford had a RACES meeting Jan. 29th. UGL is interested in OPS appointments. Officers of the Hamden ARA are UJG, pres; DDT, vice-pres. UZJ, seep; FKQ, trees; NFG, act. mgr. MVII and DDF are sa.b. During "Operation Icole," Jan. 9th and 1DF are sa.b. During "Operation Icole," Jan. 9th and 1DF transmissions from 7 P.M. Fri. to 2:30 a.M., then 8:30 a.M. of 4:55 F.M. Sat. Operators were TCW, RFJ, UAC, SKO. and BEA. Mobiles were FMU, TCW, IAY, KUO, GVK, BGP. Traffic: (Jan.) W1800 303, AW 150, KYQ 111, BDI 70, CUH 60, RRE 59, FOB 45, NBP 22, HYF 21, NEK 20, RFJ 18, KV17, LIG 8, QMM 7, ODW 3. (Dec.) W10DW 20.

MAINE—SCM, Orestes R. Brackett, W1PTL—SEC: BYK, PAM; OLQ. RM; LKP. The Pine Tree Net operates on 3596 &c. at 1900 Mon. through Fri; Thanks to BWR, who operates K1NAI, we were able to get the message from our Governor to the President in plenty of time, originated from K1NAI to W1PTL, then on the Sea Gull Net to LKP and via the Pine Tree Net to Washington, D.C. BYK, PAM; OLQ. RM; LKP, The Pine Tree Net operates here in this State. I don't know just what will happen but Ed Hudon,

UHF
INSULATION


ALSIMAG

Custom Made Technical Ceramics

FOR ELECTRONIC AND ELECTRICAL USES SOLD ONLY TO MANUFACTURERS

CORPORATION

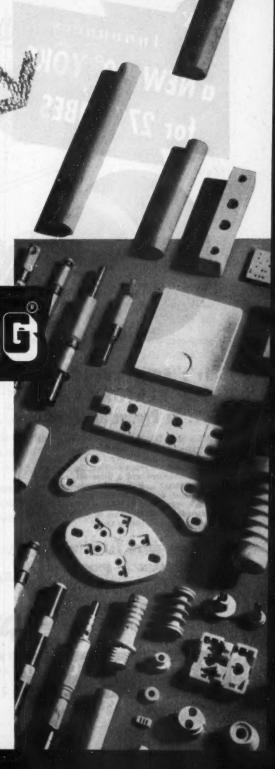52ND YEAR OF CERAMIC LEADERSHIP Chattanooga 5, Tennessee





It's Engineered for TOP PERFORMANCE ... in Production NOW!

This new DX 90° Deflection Yoke has everything a television receiver manufacturer wants . . . a sharp full-screen focus, a minimum of pincushioning, the ultimate in compactness and a price that's down-right attractive. Because this yoke has been brilliantly designed for mass production on DX's specialized equipment, it warrants immediate consideration in your 27" receiver plans. Write us today.

DEFLECTION YOKES . . . TOROID COILS . . .

I. F. TRANSFORMERS . . . DISCRIMINATORS . .

SPEAKERS . . . R. F. COILS . . .

TV TUNERS ... CRYSTALS

ION TRAPS . . . TRANSFORMERS



DX RADIO PRODUCTS

is on 144 Mc. WJJ now has General Class license. ALP attended a meeting of the Quannapowitt Radio Asan. WB is in Rome. TOQ is on several bands, as.b. on 3.9 Mc. The Braintree Amsteur Radio Club had a film from ARRI.. TNK is building a 3" scope for monitoring. Bl handled the Governors-to-President Relay message for Massachusetts and in the 160-Meter DX Text using a 25° Kytoona antenna worked Df3NY. DWO has a mobile rig on 3.5 Mc. Under the Meter DX Text using a 25° Kytoona antenna worked Df3NY. DWO has a mobile rig on 3.5 Mc. Under the Meter DX Text using a 25° Kytoona antenna worked Df3NY. DWO has a mobile rig on 3.5 Mc. Under the Meter DX Text using a 25° Kytoona antenna worked Df3NY. DWO has a mobile rig on 3.5 Mc. Under the Meter DX Text using a 25° Kytoona antenna worked Df3NY. DWO has a mobile rig on 3.5 Mc. Under the Meter DX Text using a 25° Kytoona antenna worked the Meter DX Text using a 25° Kytoona antenna worked the Meter DX Text using a 25° Kytoona Meter DX Text using a 25° Kytoona antenna worked the Meter DX Text using a 25° Kytoona Meter DX Text using a 25° Kytoon



The art of cutting jewels is a thing of consummate skill and delicate touch. Gem cutting requires great accuracy.

But even gem cutting is not so precise or exacting as crystal processing by Midland's methods. As a result, you get the finest quality and highest accuracy scientific skill can produce in a frequency control crystal.

Midland Crystal Processing operations in many respects exceed the requirements of gem-cutting. Raw quartz is selected with regard to high electrical quality . . . proceeds through slicing, lapping, etching; and the final plating and sealing corresponds to setting a jewel. And at every step Midland's critical inspection and test procedures are applied, including precise angular control by X-ray.

Your Midland crystal is a gem of stability, accuracy, high output, long life. Whatever may be your requirements for better crystal performance, you'll get them in fullest measure from Midland.

Whatever your Crystal need, conventional or specialized
When it has to be exactly right, contact

MANUFACTURING COMPANY, INC.
3155 Fiberglas Road • Kansas City, Kansus

WORLD'S LARGEST PRODUCER OF QUARTZ CRYSTALS

ENGINEERING OPPORTUNITIES

AT **NOSNHOL**

We invite QST readers to consider technical employment in the following categories made necessary by an expanding products development program.

COMMUNICATIONS ENGINEERS ... With EE DEGREES

.. or equivalent professional experience in the communications field.

MECHANICAL ENGINEERS

... with design experience on small mechanical and electrical parts similar to those used in electronics equipment.

DESIGNER-DRAFTSMEN

... for diversified work on equipment and components.

These openings are the result of steady growth of our company over 30 years. The excellent reputation and wide acceptance of Johnson products have been the result of sound engineering, close control of manufacturing, conservative but progressive management and adequate financial strength. These factors, plus widely diversified lines, lead to job security that is unsurpassed in the industry.

Waseca offers an attractive small city environment, ideal for family life, close to work, to good schools and recreational opportunities in the Land of Ten Thousand Lakes.

If you feel you are qualified and interested in working with a compatible and highly respected group on projects ranging from component items to broadcast and amateur equipment and without the disadvantages of over-specialization and resultant boredom, write to A. M. Pichtino, Chief Engineer. We would appreciate a resume of your education and experience in your first letter together with a recent photo. All responses will, of course, be held in strict

E. F. JOHNSON COMPANY

210 2nd Avenue, SW

Waseca, Minn.

Club elected the following officers: RZD, pres.; FTJ, vice-pres.; TTU, secy-treas. BBI has a Viking II. The Merrimack County 16-Meter Net has a better than 50 per cent attendance. FTJ is the proud possessor of certificate No. 2 for YL/WAS and also won the YL. Anniversary C.W. Contest for the third consecutive year to retain the cup. Why not call in the NHEN on 3850 at 1:00 r.M. on Sunday? BXU will be glad to welcome you all. UNV is going to town with his new Viking II on 20 meters. COC is the new Merrimack County EC. CDX is doing a fine job recruiting members for NHEN. He is our new Rockingham County EC. We welcome APM to New Hampsbire from Massachusetts. TDH now is 3UUO. What about applying for an appointment that seems interesting? BFT has received a certificate for WACE from the Radio Club de Chile. Why don't some of you appointees get in on LO-NITEs? Notice how our traffic reports are on the increas? FBI CDX has been trying out the 21-Mc. band. Traffic: WICRW 374, GMH 41, QJX 16, FZ 9, CDX 8.

RHODE ISLAND—SCM, Merrill D. Randall, WIJBB—SEC: MIJ, RM: BTV, PAM: BFB. A meeting of the R. I. C. W. Net members was held at JBF's QTH with BTV prosiding. New net rules were decided upon and several new members were recruited. The RIN meets Monthrough Fri. at 1900 EST on 3540 k. QR, BTV, TGD, BBN, and JBB were present. New certificates will be issued as 600 ns all applications are passed upon. Certificates endorsed: TRX as OPS, BBN as ORS, R. I. C. D. Pione Net. OIK control, meeting Sun. at 1000 EST on 3993 &c., is contemplating revision to regular traffic net. All interested, talk to OIK, OMC, ONZ, or TRX. TRX. because of an unfortunate fire in his shack, has been strictly mobile for the past two months but now is back on 75 meters from his renovated home. We could use a couple of applications and recommendations for OO appointment. Newly-elected officials of NCRC are TXL, pres.; UOO, vice-pres.; ULS, secy.; OMC, corr. secy.; TXF, treas. NCRC's meetings are held every Mon. at 2000 EST at Seamen's Institute on Mill S

SECOND VERMONT OSO PARTY

The Tri-County Amateur Radio Club of Brattle-

The Tri-County Amateur Radio Club of Brattle-boro, Vermont announce their sponsorship of the 2nd Vermont QSO Party and invite all interested radio amateurs to participate. Here are the details: (1) Time: 24 hour week-end period Saturday, April 26, 1963, 6 r.m., to Sunday, April 26, 1963, 6 r.m. to Sunday, April 26, 1963, 1984, 1985, 198

station with the man frequencies are suggested to county.

(5) The following frequencies are suggested to congregate near-1810, 3520, 3740, 3860, 7050, 7250, 14,100, 14,250, 28,100, 28,800 ke; 51, 145 and 221 Mc. Stations are urged to spread out to keep QRM down and to allow low power Vermont stations to be heard. Use more than one band if you wish, but remember that a station may be worked only once for credit. There are 14 counties in the state of Vermont.

wish, but remember that a station may be worked only once for credit. There are 14 counties in the state of Vermont.

(6) General Call: "CQ VT." Vermont c.w. stations should identify themselves by signing de Vermont (call) K. Phones say "In Vermont."

(7) Contact Information required: Vermont stations send RST or RS and county. All others: RST or RS and state, possession, province or country.

(8) Logs and scores must be postmarked not later than May 25, 1953, and should be sent to Tri-County Amateur Radio Club, % Val Morehouse, W1AZV, 27 Grove St., Brattleboro, Vermont.

VERMONT — SCM, Raymond N. Flood, W1FPS — SEC: JEN. PAM: AXN. RM: OAK. Asst. RM: TAN. OAK met the Governor and got Vermont's message for the Governora-to-Fresident Relay. CUX is home from the hospital. FPS is rebuilding transmitter using a 2E28 to an 813 final but is having trouble trying to drive the 2E26! Vermont's c.d. net now is holding weekly drills regularly. No other news was received here this month. Please send in items. Traffic: W1RNA 120, OAK 103, NDB 31, IT 19, FPS 18, TAN 13, ELJ. 7, TXY 6.

(Continued on page 106)

GET AN ANSWER TO EVERY CALL!

You Can Do It - On Low Power, Too - If You Have

An Efficient ROTARY BEAM Mounted On A

VEST

SELF-SUPPORTING STEEL TOWER WITH TILT-TOP HEAD*

Ask Any 'Old-Timer' - He'll Tell You "IT'S THE ANTENNA THAT DOES THE JOB!"

· YOU CAN AFFORD A VESTO TOWER!

Look at these low prices! Our prices have remained the same for over 2 years? 22 ft \$94.75 217.75 50 ft 61 ft..... 33 ft 135,75 279.75 100 ft. . 157.75 1060.00 Tilt-Top Head. \$34.50

• EASY TIME PAYMENTS-12 MONTHS to Pay!

If you wish, we will include freight charges in time payment plan. For example: A 33 ft. tower delivered to New England requires only \$30 payment with order, and 12 monthly payments of \$10.65. Our most popular size—the 61 ft.—may be had for \$30 canh, and 12 payments of \$23.25. These figures will vary, of course, according to the freight rate to your city.

• PERMANENT-SAFE-EASY TO ERECT!

One man can erect a VESTO TOWER in just a few hours. All you do is dig 4 holes for anchor posts, then assemble from the ground up, one piece at a time. Bolt on ladder sections as you go. Every part fits. Heaviest piece weighs only 22 lbs. Only tools needed are a spade, wrench and pair of pliers.

. IT'S EASY TO MOVE A VESTO TOWER!

A Vesto Tower dismantles quickly for easy moving to a new location.

• PLENTY OF ROOM IN YOUR BACK YARD!

You don't need a lot of space. For instance, a 61 ft, VESTO Tower requires a space only 12 feet square!

. TOWERS SHIPPED DIRECT TO YOUR HOME!

The complete tower, knocked down, and securely packaged is shipped to you FOB Kansas City, Mo. by 4th class freight. Prices subject to change, so order new! Send check or money order . . . or write for free information.



idth of Base Equal to 1/5 Height

ATTRACTIVE! No Guy Wires

4-POST CONSTRUCTION

Assures More Strength

SAFE

Ladder to Top Platform

COMPLETE!

Ready to Assemble

GALVANIZED STEEL

Will Last a Lifetime

PERMANENT!

Withstands Heaviest Winds

VESTO TOWERS

Are Used by Both

HAM and COMMERCIAL

Stations in All 48 States

And Many Foreign Countries!

* VESTO TILT-TOP HEAD makes it easy to tilt director or reflector down ov for replacement or adjustment. It

for accurate tune-up and sure performance.

WRITE TODAY

for

VESTO COMPANY, INC.

FULL INFORMATION 20th & Clay, North Kansas City, Mo. . Cable Address: "VESTO"

105

Designed to the Miniaturization Trend

GRAYHILL Series 5000 **Multi-Deck Miniature Tap Switch**



NORTHWESTERN DIVISION

NORTHWESTERN DIVISION

ALASKA—SCM, Glen Jefferson, KI.7NT — Business on 2 meters is getting under way; AMZ was heard making a schedule with VT for a try, VT has arrays on 2 and 6 meters and has time to check out with anyone who can work in those bands. AH and AGU will modify their Vikings for 6 meters soon. BK and NT are building for 2 meters. AEE is working hard as NCS for the Sourdough Net with all hands having rough going on account of the persistent type or signal conditions Recent high winds in Anchorage laid low a few antennas and persistent cold weather dampened enthusiasm for repairing the damage. Traffic: (Jan.) KL7AIR 562, AEE 77 (Dec.) KA7LJ 1750. IDAHO—SCM, Alan K. Ross. WTIWU — Lewiston: IDZ reports OWA has a Lysco mobile rig. POZ traded his 5-20R for an SA-28, and is working on a new rig. HD7 is QRL with new jr. YL in the family, Will each chulplease write. Reports from individuals are especially velocated to the control of the control of

PACIFIC DIVISION

HAWAII — SCM, John R. Sanders, KHORU — HARC planning is well under way for a full-scale Convention to be held in Honolulu Aug. 15th. All section residents, as well as those annateurs who may be military transients, are invited and urged to attend. This will be the largest get-together ever staged in the Pacific Area! Details will appear later. The Honolulu Mobile Club really resurrected 28 Mc. by holding a mobile-to-mobile and mobile-to-fixed contest (Continued on page 108)

Proven Performance

MOBILE or FIXED . BAND-SWITCHING . 100 WATT XMITTER

SONAR SRT-120 COMPLETELY



TAL CONTROL
ATIACHMENT
ATIACHMENT
ATIACHMENT
ATIACHMENT
ATIACHMENT
ATIACHMENT
ATIACHMENT
ATIACHMENT
AND
LOW PASS FILTER

ONE KNOB 8AND SWITCHING 80.75.40.20.15-10.11

80 - 75 - 40 - 20 - 15 - 10 - 11 METERS

Here's the "Ideal" xmtr you have been waiting for — The SONAR SRT-120 - designed by a ham — priced for the ham — and engineered for commercial performance. The SRT-120 band switches faster than many receivers — switch and tune the final — THAT'S ALL. Changing crystals or using the VPO is just as simple, Here is a rig that has real versatility — 120 wastes when the confidence that TVI suppression is excellent — compact in size (14 x 8½ x 8), six bands, with an extra provision for 160 or a CD assignment — complete meter switching from front panel — crystal or VPO — all you want in a medium powered rig — complete with all tubes: 128 Y Osc. multi. 128 Y Buffer multi, 9901/994A straight thru final, 1-6C 86 at 6A, up to 600 VDC at 350 ma. max. Also available for 12 vot operation.

SRT-120 P — a complete home station unit, with pwr. sup, housed in one complete copper plated cabinet with extra shi-iding, Built in push-to-talk relay.

COMPLETE WITH TUBES. . \$279.50 Net

\$19850 NET

COMPLETE LESS PWR. SUP.

XTAL

PS-500 \$49.50 PS-501 (de luxe) \$59.50

THE SRT-120 IS AT YOUR FAVORITE DEALER

ACK RADIO SUPPLY Birmingham 3, Alabama

ADIRONDACK RADIO SUPPLY Amsterdam, N. Y.

ALLIED RADIO Chicago 7, Ill.

ALPHA ARACON RADIO CO., LTD. Toronto 1, Canada

ARROW ELECTRONICS New York 7, N. Y.

GEORGE D. BARBEY CO. Reading, Penna.

CONCORD RADIO New York 7, N. Y.

C & G RADIO SUPPLY Tacoma 6, Wash.

M. N. DUFFY & CO. Detroit 26, Michigan

ELECTRONIC SUPPLY CO

EVANS RADIO Concord, N. H.

> LITERATURE ON ALL SONAR EQUIPMENT FREE ON REQUEST.

FLYING EQUIPMENT SALES CO. Chicago 13, III.

FORT ORANGE RADIO DIST. CO., INC.

R. C. & L. F. HALL, INC. Houston, Texas Galveston, Texas

HARRISON RADIO CORP. New York 7, N. Y. Jamaica 3, L. I., N. Y.

Jamaica 3, L. I., N. HARVEY RADIO New York 36, N. Y

HENRY RADIO Butler 1, Mo. Los Angeles 64, Calif.

Los Angeles 64, Calif.
KIERULFF ELECTRONICS, INC.
Los Angeles 15, Calif.

OFFENBACH & REIMUS, CO.

San Francisco 2, Calif.
OLSON RADIO
WAREHOUSE
Cleveland, Ohio
Akron 8, Ohio

PAYETTE RADIO, LTD. Montreal, Canada

PRESTWOOD ELEC-TRONICS CO. Augusta, Ga.

RADCOM ENGINEERING

RADELCO, INC. Mount Vernon, N. Y.

Mount Vernon, N. 1

RADIO ELECT. SERV. CO., OF PENNA., INC. Philadelphia, Penna. Easton, Penna. Allentown, Penna.

RADIO EQUIPMENT, CO. Norfolk 10, Va.

RADIO SHACK, CORP. Boston 8, Mass.

RADIO SUPPLY Richmond, Va.

RADIO WIRE TELEVISION, INC. New York 13, N. Y. RADIO WIRE TELEVISION INC. Boston, Mass.

E. A. ROSS & CO.

SELECTRONIC SUPPLIES, INC. Toledo 2, Ohio

SHAW DISTRIBUTING CO. Charlotte 2, N. C.

J. V. STOUT CO. Baltimore 12, Md.

Baltimore 12, Md. SUN PARTS DISTR. Washington 4, D. C.

Washington 4, D. C.

TERMINAL RADIO CORP. New York 7, N. Y. UNIVERSAL SERVICE Columbus 15, Obio

VAN SICKLE RADIO SUPPLY CO. Fort Wayne, Indiana

WEST INDIES AIRWAYS
Puerto Rico

SONAR RADIO CORPORATION

3050 W. 21 ST. BROOKLYN 24, N. Y.

INSIST ON SONAR.

to the

E. E. or PHYSICS GRADUATE

with an interest

or experience in

RADAR or ELECTRONICS

Here is what one of these positions offers you

Hughes Research and Development Laboratories, one of the nation's large electronic organizations, is now creating a number of new openings in an important phase of its operation.

OUR COMPANY

located in Southern California, is presently engaged in the development of advanced radar devices, electronic computers and guided missiles.

THESE NEW POSITIONS

are for men who will serve as technical advisors to the companies and government agencies purchasing Hughes equipment.

YOU WILL BE TRAINED

(at full pay) in our Laboratories for several months until you are thoroughly familiar with the equipment that you will later help the Services to understand and properly employ.

AFTER TRAINING

you may (1) remain with the Laboratories in Southern California in an instruction or administrative capacity, (2) become the Hughes representative at a company where our equipment is being installed, or (3) be the Hughes representative at a military base in this country-or overseas (single men only) Adequate traveling allowances are given, and married men keep their families with them at all times.

YOUR FUTURE

in the expanding electronics field will be enhanced by the all-around experience gained. As the employment of commercial electronic systems increases, you will find this training in the most advanced techniques extremely valuable.

How to apply

Assurance is required that the relocation of the

applicant will

If you are under 35 years of age and have an E.E. or Physics degree and an interest or experience in radar or electronics,

write to

HUGHES

RESEARCH AND DEVELOPMENT LABORATORIES

Scientific and Engineering Staff Culver City, Los Angeles County, California

with juicy prizes. The activity was fierce, both day and night! W5RT/KH6 now activates the Kona Coast as National Guard instructor at Kealackus. His XYL, WNSUGT, also will convert to KH6. W6UWL/KH6 has a traffic total of more than 200 this month, all mobile! KG6AEP, now Oo on Guam, is our old friend, KH6PY. HARC now has a TVI Committee functioning and urges all troubled brethren to avail themselves of the service. The was all the w

disruption of an urgent military

Are You the Most unpopular man in your neighborhood?




Are You forced to become a swing shift ham?

You can be on the air more hours by explaining to your neighbors how the.

BUD HIGH PASS FILTER

Reduces T.V.I.

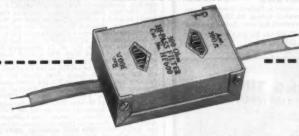

If your neighbors complain about T.V.I. everytime you're on the air, if you're forced to restrict your operations until after midnight you'll lose a lot of friends and sleep, tool

You can solve these problems by suggesting to your neighbors the installation of a BUD HIGH PASS FILTER. Not only will it reduce or eliminate interference from your rig but also from auto ignition systems, electrical storms, diathermy and X-Ray machines and from other annoying sources.

It is small, compact and easy to install. It's worth many times its low cost.

See the Bud High Pass Filter at your nearest Bud distributor—test it on your own TV set and you'll be sure to recommend it to your friends and neighbors.

Model HF 600

Amateur Net \$3.00



The Mark of Perfection BUD RADIO, Inc. 2118 East 55th Street Cleveland 3, Ohio





2 MFD 600 VOLT OIL-FILLED CAPACITOR 89¢



EFFECTIVE QRM Eliminator

PHONE - CW FILTER MODEL FL-8-A

Completely elim inates 1020 cycle CW signals when used on Phone bands - or - flip a switch



or — flip a switch and only 1020 cycle
CW signals come thru! Neutral switch position cuts filter out of receiver circuit. Fully self-contained in cast aluminum case 3½" x 2½" x 2½" self-contained in cast aluminum case 3½" x 2½" x 2½" self-contained witning required. Plugs between set phone jack and speaker. Used, excellent condition.

MODEL FL-5-F Similar to above, less switch. Designed either to pass or reject 1000 cycle signals. Originally made for Army SCR274N and ARC-5 equipment. \$419 BRAND NEW, in original boxes, ea.. \$419





BRITISH WESTON METERS - Super Values!

Precision-made in England, brought to you at tremendous savings. All BRAND NEW, fully guaranteed, Buy now—limited quantity!

O-20 VDC O-40 VDC O-500 RF Me with built-in Thermocouple

	DIAM	TUBES
RECE	AIMA	TUBES
100/- (SEE LIST	LKIOT
60%	BRAN	B HEW-Rexed-
All Standard	Brands-BRAN Guaranteed	Max Type

Majorda Table Cala Table Cal

MINIMUM ORDERS \$5.00

Concord Radio 55 Vesey Street New York 7: N

Phone Dlaby 9-1132

at El Monte Drive-In. Attending were KG6ABW/6, W6HJE, LGW, LTE, MEZ, NVJ, RVC, and WOW, YHQ has built a beautiful YFO and driver. ZHU, AFC, and WGM have been checking in on Region C.D. Net on 6 meters. CAN regularly checks into staff net on 3900 kc. Sun. mornings. BS has new Elmae in the car. PHI has a BC-312 and GF-11 on 80 meters. NTU and ELW now are working with TVI committee. AFC is E.E. student at Cal. JOH is doing a whale of a job on BAN. IPW missed BPL by 5 messages. Traffic: W6IPW 495, JOH 242, HHX 60.

SAN FRANCISCO.—SCM. R. F. Czeikowits, W6ATO.—JU 7-5561. BEC: NL. PL 5-6457. Eurska Arac: EC: SLX. The Emergency Corps. under SLX, agasin proved its great usefulness during the severe storms and floods of sunuary, and maintained communication throughout the critical period. CWR is using a new 50-watt rig on all bands. LE now is operating with his stacked 10 and 20 beams. EQQ now is in his new home. AEY is working 160 meters. QCS has a new flam with 813s. KTU is the new c.d. director, assisted by CWR. JTD is antenna building. FYY is trying out the 21-Mc. band. ZSE has a new 28-Mc. rig. MCC has a new National receiver. BME is operating both at home and mobile. SLX has joined the Seabees (USNR). The Christmas party was a great success, being attended by over 80 people. The HARC Emergency Net meete each Tues. at 7 r. m. on 29, 160 kc. GQY, of Fortuna, has been appointed an Official Relay Station, and handled 607 messages during January, plus messages on MARS circuits. He rates BPL on the January total. The Humboldt Amsteur Radio Club meets the 2nd and 4th Fri. in the YMCA rooms, Municipal Auditorium, entrance on "E" St., Eureka. San Francisco Area: EC: BYS. Many thanks to the San Francisco con continued to the TVI Committee of the proceeds of a special auction held for the purpose at a dinner held at the New Tivoli Restaurant. This will provide a 300-ohm Drake high-pass filter for each investigating head of the TVI Committee. Thanks also to the Zack Radio Suppit of a motordriven sander and drill. Reporting he

ROANOKE DIVISION


ROANOKE DIVISION

NORTH CAROLINA — SCM, J. C. Geaslen, W4DLX
— Many thanks to VG for the nice two-page report from
the Asheville Area. Through the courtesy of WN4WWYfather the Asheville Club has a nice new shack for the
club station, MOE. New officers for 1953 are AFM, pros.;
MZS, vice-pres.; VG, treas,; and R. J. Echerd, i.r., nec;
BMG is bragging about his new 32V-3. Novices USJ,
YBW, and YBX are racing for WAS and General Class.
Congrats to AFM on his fine emergency traffic for the
Southern Railroad during the recont blissard. AKC reports
the Gastonia Club now is 100 per cent ARRL. VGB is a
new member of NCN. BDU, Charlotte, is racking up a nice
score in the DX Contest with new antennas. 8AJ now is
on 75-meter mobile. That makes 14 in Charlotte. The
Greensboro Civil Emergency Mobile Net did some fine
work nicking up late donations for the March of Dimes.
SGD, Fuquay Springs, a new OPS, had the honor of originating the North Carolina Governor's message in the Goverroors-to-President Relay. Thanks to ANU, ONM, and
PZE for the assist on this. North Carolina, to to traffic man,
AKC, the RM, made BPI, this month. How about some
(Centinued on page 112)

AT ANY PRICE...you couldn't

ask for more in a MOBILE TRANSMITTER!



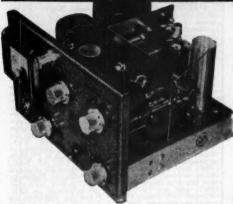

40 Watt BABCOCK MOBILE **D-XMITTER**

6 Band - Band Switching

- 2 Bands (3.5-7.3 mc) (14-30 mc)
- 2 Crystal Frequencies per band
- Instantaneous Antonna change-over with LS-1 or LS-2 Units into 8 ft. whip

Features:

- · Finest components available
- 68K5 escillator
- 6146 final amplifier
- · Complete metering, including watts output into 52 ohm antenna load
- Small Size-5" hi., 8" wi., 7" d.

Readily adaptable to mobile or home use

ABSOLUTELY GUARANTEED

COMPLETE TRANSMITTER	99.50
(6vdc) Dual Vibrator Power Supply, Complete	67.50
(11Ovac) Power Supply Complete	44.50
(12vdc) Dynamator Power Supply, Complete	79.50
Antenna Tuning Unit (75 and 10 maters)	15.00
Antenna Tuning Unit (20 and 40 meters)	15.00
	(évdc) Dual Vibrator Pawer Supply, Camplete





BABCOCK . RADIO ENGINEERING, INC. 7942 Woodley Ave., Van Nuys, Calif.



more traffic men getting up there? Traffic: W4AKC 500, RRH 85, BDU 64, PIC 47, SGD 17, HUW 10, DLX 6. GOB 1.

more traffic men getting up there? Traffic: W4AKC 500, RRR 86, BDU 64, PIC 47, 8GD 17, HUW 10, DLX 6, GOB 1.

GOB 1. TH CAROLINA.— SCM, T. Hunter Wood, W4ANK.— Tentative date for the Spring 8. C. Hamfest is set for April 26th at the State Park near Columbia. As usual it will be picnic style with MW H. Roanoke Division Director, as guess speaker. DM3, obtained and transmitted which was delivered to a Washin message on Jan. 19th which was delivered to a Washin message on Jan. 19th which was delivered to a Washin message on Jan. 19th which was delivered to a Washin Market of the Market of the Columbia and operates from Hartaville week ends. 19th with the was delivered to a Washin was delivered to the air from the laic of Painas. UMV and his father, WN4-WKL, have moved to Camden, WN4WKL is being transferred to Korea. New officers of the Rock Hill Club are UOS, pres.; TTX. vice-pres.; NTD, seey.; WN4UMW, treas.; UMV, custodian; UNO, clerk; and NDH, trustee. The Charleston Club is forming a TVI committee. The Anderson Club is sponsoring a program intended to promote a National Amateur Radio Week and to obtain license plates for South Carolina hams. FfH is Alternate NCS on the 8. C. MARS 'Phone Net. The Spartanburg Club has applied for ARRL affiliation. Traffic: W4FFH 140, ANK 117, FM 5, JGM 5, DMX 1.

VIRGINIA.—SCM, H. Edgar Lindsuer, W4FF—A total of 35 stations reported traffic during January. An additional 12 stations passed on other kinds of information pertinent to all of us. The March of Dimes Campaign found the mobile units throughout the State organized to help in picking up contributions. Stations known to have participated were CJJ, GEB, JKX, BF, CU, EHO, FWO, GMY, LW, WGM, GW, KPF, KPC, RMF, KFK, KRG, LKJ, NUW, GMR, GY, SCF, TYC, UHN, WRH, THM, QCT, JGS, SAQ, SSW, and JL, MLIC departed for an assignment appreciated the help of ham as Costeeville, Penna. FOR appreciated who leads to the second contract of the second columns of the second columns of the second columns of the second columns of the second colum

ROCKY MOUNTAIN DIVISION

COMING: Rocky Mountain Division QSO Party, May 16-17. Watch this space in May QST for details and rules.

COLORADO — Acting SCM, Karl Brueggeman, WSCDX — SEC: KHQ. Asst. SEC: PGX. RM: KHQ.

PAM: KHQ. The Rocky Mountain Convention now is a fact. It is planned for June 20th and 21st at the Elkhorn Lodge at Eates Park, Colo. Contact WRO for registration details. A QSO Party also is planned in order to acquaint everybody with the convention. It will come off on the week end of May 16th and 17th. Prises and rules will be announced next month. The El Paso Radio Club. Colorado Springs, election results were ANX, pres., EVT, secy.-treas. RCU later took over as secretary as EVT is working most of the time. The Club now is conducting demonstrations on all types of test equipment. COB is knocking off DX on 40 meters. CVI, RCU, WPK, HEM, GBX, and BYW are holding their own on 75 meters. CCG and ANX are rebuilding their mobile rigs and COF has a new all-band mobile. COB will be working us from the Far East soon. KHQ is in there pitching in traffic work. We have a new father-and-son team: WN\$MPH, Dick, jr., and his dad, QCX. OTR is our only Denver OO. Bill would like to see more OOs in our section. Contact him for details. CNK is in Denver now, having been transferred from Ft. Dodge, Iowa. 9NLZ/8 is here from Chicago. Our Director, DD, has been transferred to Turkey and is turning the directorship over to IC. We all wish Frank the best of luck and success in his new assignment. We will miss his able and sincere guidance of the Division. Traffic: W\$KRQ 881, EKQ 365, K\$FAM 345. UTAH—SCM, Floyd L. Hanhaw, W7UTM—The GPR message was secured by JPN and relayed on TLAP GPR message was secured by JPN and relayed on TLAP GPR message was secured by JPN and relayed on TLAP GPR message was secured by JPN and relayed on TLAP GPR message was secured by JPN and relayed in have clicated to washington, D. C. QDY advises that he has built a modulator for his HT-17 to take advantage of the new CTAR details in the secure of the Utah section space is relinquished in layor of the Division QSO Party announcement. Let's all help, and become better acquainted.) Traffic: W7UTM 232.

SOUTHEASTERN DIVISION

SOUTHEASTERN DIVISION

ALABAMA — SCM, Dr. Arthur W. Woods, W4GJW —
TMH has joined the AREC and is building up emergency
equipment. KCQ has revised his directional antennas
and has beams on top of beams with 144 Mc. on top. Bill
Stanfield, of Jacksonville State College, has expressed an
interest in our hobby and will be visiting the Anniston gang
for help. HA, in Anniston, hash his OBS and OPS appointments endorsed and is developing a final for 75 meters. OHO
is regularly heard on both section nets. BFM continues to
deliver traffic from several nets to the North Alabama Area.
PFK is looking for crystals 4528, 4486, 4472, and
451.4. Going s.as.b.? KiX continues to keep AENB in
business although he claims 85 per cent of his time is spent
in ragehewing. UHA soon will be ORS and meet the
AENB and DON Nets. The Birmingham Club is publishing
a really good monthly builetin. The Huntaville Club pursues
an ambitious program schedule with films, code and theory
practices, auctions, etc. TKL is scheduled to start meeting
AENP in March. Traffic: WaUHA 117, KIX 91, PFK 43,
QAT 36, BFM 23, OAO 19, GJW 7, HA 2.

EASTERN FLORIDA — SCM, John W. Hollister, jr.,
W4FWZ — JFH put new life into the FN net in January
and the 3675 kc. spot sounded good. The Net meets each
night except Sun. at 8 F.M. Traffic-handlers, your help is
needed on 3675 kc. February was the Tampa Fair month
and from early indications both 'phone and c.w. nets had
heir hands full of traffic. Daytona: The hamfest at RWM's
place went over with a bang. Clewiston: Visitors at PJU
were 8WBL, 9DDC, SLAK, 9EH, and 3PWW. Fort Lauderdale: Our new SEC reports the Pelican Net off to a big
start with MYR as NCS, Jacksonville: The JARS will get
Doo's call, W4DU. New Novice is W4ZSE. UHE has
National 18D, OGD is going mobile, HKR has HRO-90T.
PI has left Jacksonville. Miami: 1YT sends beginners' code
practice on 28.7 Mc. We welcome YM to Florida. Louis is
on with a Bandmaster. IEH sporte new 32V-2 Collins,
W8J has a 75-A, SAT soored about 85,000 points in the
January CD P

UNV works KH6s without an antenna. VAQ is a faithful 10-meter operator. #JTB is on from Mary Eather. UTB. ERR, and M8 keep MARS Nets keds. VCB is working 20-meter c.w. HJA is buny with mobile rig. QK changed final amplifier tubes. DAO is on 75 meters. UQZ keeps 20-meter c.w. hot. ART is on 144 Mc. WN4YRF keeps keds with his brother in Mississippi. PQW keeps constant monitor on 29,560 kc. with vertical polarised antenna for the mobile gang. ODO is active again. BFD is on all bands. VR has invasible antenna. WN4U 78 made Technical Class. JPD has had ICI (intercom interference). NOX-NYZ received a visit from a Korean veteran for whom they handled traffic. Traffic: W4GGM 9, M8 3.

GEORGIA — SCM, James P. Born, jr., W4ZD — New officers of the Augusta Radio Club for 1953 are CBH, pres.; Confederate Signal Corps has formed a cw. Movice ed. which meets at 063 E287 c. EBK. a NCS and WIX is Alternate NCS. YEK requests Novice stations interested to send her a radiogram or drop a card to 572 Wella Avenue, Hapeville, Ga. WRV is the new EC for Cobb County. WDW has moved to Connecticut. IMQ has returned to the air with a Viking II. EJN now is on 3.8-5 Mc. 'phone with a spair of 4-125As. The Camp Gordon Radio Club of Augusta now has a membership of 260. EPM has a new mobile rig on 3.85-Mc. 'phone. EGK has a new 28- and 14-Mc. beam and is looking for DX. The Kennehocchee Amateur Radio Club's hamfest will be held May 31st at Lithia Springs, Ga. A Johnson Viking II will be given to soome lucky attendant. KL still is looking for DX. However, he finds time to do an FB job as 00. Our new Route Manager, MTS, thanks all of you for interests and cooperation in the c.w. nets and would like to have your icless and augestions for improving net operations. Avoid loss of appointment, check your endorsement of the Viking III. Rib build have been appointment, check your endorsement of the Viking III. Rib build have been pointment, check your endorsement of the Viking Ribands. Rib had a provided to the November of the November of the November

SOUTHWESTERN DIVISION

LOS ANGELES — SCM, Samuel A. Greenlee, W6ESR — Aart. SCM: Kenneth L. Kime, 6KSX. PAM: QR. RMs: FMG, FVW, GJP, JQB. Section Traffic Nets: LSN, Mon. through Sat., 3600 kc. at 2030. ECN, Mon. through Fri., 3655 kc. at 2030. This is the last report by your conductor. Your new SCM, YVJ, will take office in April but meanwhile will function as Acting SCM. I know you will give (Continued on page 114)

more

for the hi-power man-



Merit Coil and Transformer Corp. - 4427 North Clark St. - Chicago 40

him the same magnificent copperation you have given me—to keep the section on top! BPL this month was made by K6FCA, W6GYH, HK, KYV, and VHN. KLD is rarin' to go on RTY. An FB traffic team is PWZ and PXC (XYL). MU reports new officers of 3C Club: MU, chairman; RW. seg-et-a-miss, and CMN, Bd. of Dir. Fat-on-the Back-Dept. ic. to in our fight for call-license plates. EPL still is working on surplus gear. COZ says that JMV is on 75 with ARC-5, QE is sporting FB modulation meter; FKH is back on the air after an illness; SGF is Viking-H-issed; COD got the nod from Uncle Sam. CAK conducts code classes for beginners at J. Burroughs H. S., Burbank, Mon. and Wed. at 1830. Contact him. New c.w. traffic man is LQZ—good, too! FYW, RM, says CMR dropped the "N" in his call. BLY reports that YUY again is a proud papa; that patience award should go to JQI and SPR for working on 2-meter RTY; FAN (CEA's XYL), monitors 3925 kc. Keepither RTY; FAN (CEA



Join the Gang on Mobile... Make Your "Call of the Open Road" a CQ! Double your motoring pleasure and make new friends wherever you go

TOP MOBILE EQUIPMENT

on the Highway

JOHNSON VIKING MOBILE XMITTER KIT



ASTER MORILE MOUNTS & WHIPS

BODY MOUNTS.	MOBILE MOUNTS Spring swivel base. With coax connector. \$10.75 \$10.75 \$10.75 \$9.85 \$10.75 \$10.
132KC-Heavy d	uty, for loaded willips Heavy duty \$7.65
STAINLESS STE	1405-Stainless Steel 1405-Stainless Steel 1408-Stainless Steel 1408-Stai

Alt-Band Mobile Antennes

Complete with one coll (specify), Fits 3/6 SAE
thread. Less spring mount.
thread. Less spring mount.
20 meter coll. AB/W20.
20 meter coll. AB/W40.
27 5 meter coll. AB/W75.
57 meter coll. AB/W75.
Extra colls for 20, 40, 75 meters.
Each \$3.30

2-Meter Coax Antenna

Model Hi-O 20 meter coil. Heavily plated ½" solid copper wire. Weatherproof plaxiflas housing. Removable threaded plastic nylon end-action. Model Hi-Q 75 meter coil. Two piewould ni-d /3 merer cell, two pie-wound coils; powdered iron-cor-slug. Easily adjustable to exact in-ductance. Simple installation. \$7.95



SHURE CARBON MIKE



Ideal for mobile. Clear, crisp voice response. High output. Heavy duty switch for push-to-talk operation. Output level 5 db below IV. for 100 microbar speech signal. With hook for suspension and bracket for wall mounting

GONSET "COMMUNICATOR"

Complete 2-way, 2-meter station for Comparer 2-way, 2-mater station to mobile of fixed use, Superhet receiver and built-in noise clipper 15 watts input. Crystal or carbon mike, Built-in speaker and 19" whip. 10½x9½x 7". For 110 V. AC or 6V. DC. With fubes. Less crystal and mike \$199.50



GONSET "SUPER 6" AMATEUR CONVERTER

Covers 10, 11, 13, 20, 40 and 75 meter phone bands with plenty of bandspread. Also 49 and 19 meter SW broadcast bands. High sensitivity on 8-ft, whip, High-law impedance antenna switch for 40 and 75 meters. RF gain switch and separate broadcast antenna input jock. With these tubes \$52,50

ELMAC 50-WATT VFO TRANSMITTER

Ideal for under-dash or fixed station operation. VFO or crystal control on all bands.



New GONSET Fixed-Mobile



"Commander" TRANSMITTER 35-50 Watts \$124.50

Multi-band model featuring high "Q" high output final. Range: 1.7 to 54 mc continuous. Small enough for under-dash mounting. Universal input for any standard carbon or high impedance dynamic or crystal mixs. Matches any antenna. With tubes (6AG7, 8146, 12AT7, 2.6AQ5), and plug-in final coils 10 thru 30 meters. 5½ "Hs8" x". Requires 300V. DC @ 200 te 225 ma (phone) and 6.3V. AC or DC @3.15 amps.....

VFO UNIT. Exceptionally stable and compact. Cable plugs into "Commander," \$29.95

FREE! HARRISON HAM-A-LOG

Includes New Gear, erticles, bargains, ham kinks, etc.

Write today for your



225 Greenwich St. • N. Y. 7, N. Y. BArclay 7-7777

JAMAICA BRANCH: Hillside Ave. at 172nd St.

FOR YOUR SHOPPING AND PARKING EASE!

OPEN NITES 'TIL 9

y York — Wednesde Jamaica — Fridays SATURDAYS: 9-6

this sword challenges CANCER

Inder the sign of the cancer sword the American Cancer Society seeks to save lives by spreading vital facts to you, your neighbors, and your physicians . . . by supporting research that will find the final answers to cancer . . . by providing improved services for cancer patients.

Only under the sign of this sword is there a three-fold, national attack on cancer.

Cancer Strikes One in Five Your Dollars Will Strike Back

Mail Your Gift to "Cancer" Care of Your Local Postoffice

AMERICAN CANCER SOCIETY



CANDLER SYSTEM CO.
Dept. 4-D. P. O. Box 928, Denver 1, Colo., U. S. A.
nd at 52h, Ahingdon Road, Kensington High St., Lendon W. 8, England

OMs and XYLs. UDU, local R.I., also was present. Appointments of LRB and of HLB will give SK needed help in northern San Diego County AREC work. Certificates were awarded at the January meeting of the Palomar Radio Club. From PRC pray, HAW, we hear a warm thanks to all for attending this all-important c.d. and club reorganization meeting. HLB foresees trouble with the Palomar Club's 3-kw. F.D. generator — flat tire! The high school gang at 1AC is getting fun and FB training on "Escohinet," meeting at 1900 on 3702 kc., Tues., Wed. Thurs., with alternating NCS duty. All are invited to check in. Recent Novices-to-Generals at IAC are OXT, QBN, and KKC. IWQ made Advanced Class one day before the deadline. AKY, LRB, FVA, BLL, and FJH are active in county AREC nets on 3.825 and 29.5 Mc. Sun. and Tues. Confirmed v.h.f. man CDQ checks in regularly on 2-meter circuit. FUY is losing hair over the A-5 rig at Vista QTH. BLL and FJH visited the famous Coronado Club gang, It is an FB bunch with a top-notch anti-TVI program and a pair of FB leaders in OCJ and OQY. Hearty thanks from all to EWU for doing a great job as Acting SCM. Your new SCM truly hopes to be able to live up to the standards set by Ellen White and Tom Wells. Asst. SCM DLN joins TJH in voicing the mutual pride of the section for Wls YYM and WPO, now at ARRL Headquarters. Traffic: WeIAB 5122, ELQ 414, MUE 100, IZG 31, FCT S, CHV 6

WEST GULF DIVISION

WEST GULF DIVISION

NORTHERN TEXAS—SCM, William J. Gentry, W5GF—Asst. SCM: Thomas B. Craig. 51QD. SEC: QHI. RM: BKH. PAM: IQW. CVW has a new sky wire up. SRQ made 1365 points in the CD Party. MK is going back into the Air Force soon. PTE is out of the Navy and is a student at E.T.S.T.C. LOY is trying to get another emergency rig on the air. We sincerely regret to report the passing on of Aubrey W. Williams, MRR. Sure glad to hear from CF again. JQD has a new transmitter on 75-meter phone now. WBU is on 40- and 80-meter c.w. now. TDR/5. ONA. SRQ. ARK. RRM. BKH, CF, USA, TFB, TFY, K5FBP, and K5FKF did some nice message-handling at the Worth Theater. PZU has a new beam up. TYX has a Class A ticket now and also is reporting in on the New Mexico Y12* MARS Net. The South Plains Amateur Radio Club is setting up an assembly line for hand-talkies. BYG is back from Korea and in active on 14-Mc. cw. WHG is a new ORS. Traffic: W5BHK 296, PAK 161. SRQ 134. CVW 74, RRM 72, CF 52. VRX 44, CWE 42, ARK 38, UFF 15, LOY 12, ROH 6, GF 4.

OKLAHOMA—SCM, Jesse M. Langford, W5GVV—SEC: AGM. RM: MQI. OQD resigned as RM because of business and MQI accepted the appointment. MQI is located in Oklahoma City and operates both phone and c.w. TRC, TMY, and EHC put on a demonstration of amateur radio operation for a church group. Areo Center ARC had a "Boiled Ow!" meeting, vit all-night operating Traffic has picked up and inquiries regarding appointments are coming in each day. We need PAMs for each of the armateur bands and the boys who are working v.b.f. should apply for CES appointment. VBQ has moved to Idaho, State Civil Defense certificates were presented to the members of the AREC in Tulsa. The Canton Club has found the ARRL quisses very interesting and informative. The Pioneer Radio Club has started a campaign to relieve the TVI situation by news rivilegal and informative. The Pioneer Radio Club has started a campaign to relieve the ravilegal paper and the use of a TVI committee. The Enid Club has 33-kw. generator for use in emergency o



It's Mobile Time

get your gear for the road at ALL









Gonset 3016 "Commander"

Gonset 3016 "Commander All-band phone-CW xmitter for under-dash mount. Covers 1.7 to 54 mc continuously. With plug-in coils for 80, 75, 40, 20, 15 and 11-10 meters. Up to 50 watts input on CW, 35 watts on phone. Complete with tubes and 2 plug-in coils; less crystal, mike and key. Requires 300 v. DC at 200-225 ms and 6.3 v. at 200-225 ms and 6.3 v. 3.15 amps. Shpg. wt., 8 lbs. 98-041. Net ... \$124.50

VFO 3020 Tuning Head for VFO control on 75, 20, 15 and 10 meters. Shpg. wt.,

"Super-Six" Converter

Covers 75, 40, 20, 15, 11-10 meters, and 19 and 49 me-ter bands. For use with any 1430 ke receiver. Sup-plied complete with tubes. Shpg. wt., 5 lbs. \$52.50

Bahcock MT-5A D-X Mitter

PS-4A Mobile Power Supply. Operates from 6 v. DC. Shpg. wt., 15 lbs. 98-792. Net.......\$67.50 ...\$67.50

LS-1 2-Band Antenna Tuner. Use with 8-ft. whips. Easily pre-tuned for 10 and 75 meters. Built-in 6 v. relay meters. Built-in 6 v. relay selects proper section of tuning unit. Shpg. wt., 7 Ibs. 98-793. Net \$15.00

(12 v. DC equipment also available)

RME MC-55 Converter

The MC-3D Converter to the converted to

RME MC-53 Converter

Sonar MR-3 Receiver

Julia Mn.7 received.

Ideal compact mobile set covering 3.5-4.0 mc, 14-14.4 mc and 26-9.30 mc (80, 75, 20 and 11-10 meters). Unusual sensitivity, 1 mv for 1½ watt of audio; ANL; BFO for single sideband reception; temperature-compensated oscillator; edge-lighted dial. Very russed construction. Retor; eage-ignied dist. very rugged construction. Re-quires 200-300 v. at 60-100 ma and 6.3 v. at 2.4 amps. Coax antenna input. Com-plete with tubes and uni-versal mounting bracket. Shore wt 6 lbs. Shpg. wt., 6 lbs. 98-781. Net ...

MOBILE ACCESSORIES

Dow Coax Releys for coax antenna changeover. Handle up to 1000 watts. Simultaneously operates external SPDT switch (below) for opening receiver B+ when transmitting.
75-798, for 110 v. AC, \$10.50.75-797, for 6 v. DC, \$9.30
75-799. SPDT Switch. Actuated by relay...\$1.00

FREE

Buying

Guide

Johnson Viking Mobile Kit

Elmac A54 Xmitter

For mobile or fixed station. Up to 50 watts input, phone or CW. For 80, 75, 20, 11-10 meters. VFO and Pierce crystal osc. Requires 6 v. at 4.5 amps, 500 v. DC at 225 ms. With tubes; less crystals and mike. Wt., 17½ lbs. 98-044. For carbon mike. Net. . \$139.00 Medel A\$4H. As above, but for use with crystal or dynamic mike. 98-035. Net. . \$149.00 P\$A-300 Power Supply. Delivers 375 v. DC at 250 ms, 6.3 v. AC at 5 amps. For 115 v. 60c. AC. 19 lbs. 98-086.

Prompt Shipment from Stock!



NEW AMATEUR EQUIPMENT RELEASES

Bud CPO-128 Codemaster

CPO-130 Codemester. As above, but without built-in speaker. 73-045. Net... \$12.94

Gonset "Communicator

Complete 2-meter Amateur phone station in one portable case—for hattery or AC operation. Puts you on the air with a 15-watt AM phone smitter; receives with a highly sensitive superhet. Has 19° whip for receiving and xmitting, 10¼ x 9½ x 7°. Complete with tubes; less mike and 8 mc crystal. For 110-120 v 50-60 c. AC or 6 v. DC. Wt., 24 lbs.

Refer to your ALLIED Catalog for everything in station gear. If you haven't a copy, ask for

Terms: the best in all Handom—ask for the details.

Trade-ins: we'll make you the kind of deals that are FB for you.

ORDER FROM ALLIED RADIO

833 W. Jackson Blvd., Chicago 7, III.



Electrical Weather-stripping by Eimac-Now Available!

Silver-plated, spring alloy, preformed finger stock especially suited for electrical "weatherstripping" for TVI-proofing cabinet access doors, etc. Also ideal for making coaxially constructed tube connections and many other uses. Available in 17/32", 31/32", and 1 %" widths.

 Write for new Eimac Catalogue Summary showing Eimac tubes and other accessories.

Eitel-McCullough, Inc. San Bruno, California

EaZon

Correct matching will put that lost wer into the antenna. The EaZon type 3WA is designed for this purpose. Strong easy to install and foolproof, Fits RG8/U or any coax of similar dimensions. Weight 4 oss. Satisfied users throughout the U.S. Types 3W and 4W are ideal junctions for stubs or harmonic traps.

Type 3WA (see cut) Antenna Match Type 3W Tee Junction Type 4W Cross Junction

\$4.60 Nes 3.00 Nes 3.60 Nes

No. 2587676

DALLAS C. AKERS CO. East Orange, N. J. TVI, DX, ham TV, radioteletype, mobile, single side-band, v.h.f., modulation, antennas, instrumentation, emergency communication, traffic-handling, and other subjects. A complete ham station will be given for a preregistration prize. Watch for newspaper and QST notices. The papers will go to ARRI, members only but all are invited, so please spread the word around in person and on the air. If you wish to register now send a check for \$13.50 for each person to Registration Committee, HARC. P.O. Box 10173, Garden Oaks Station, Houston, Texas. Traffic: W5MN 559, QFA 35, FJF 10.

NEW MEXICO — Acting SCM, R. J. Matthias, W5BIW

The New Mexico amateurs are making another effort to

Garden Oaks Station, Houston, Texas. Traffic: W5M N 559, QFA 35, RJF 10:

NEW MEXICO — Acting SCM, R. J. Matthias, W5BIW
— The New Mexico amateurs are making another effort to obtain legislation for call-letter license plates. Much work has been done and it is hoped that this time we will meet with success. Band conditions have been better on the N. Mex. 75-Meter Emergency 'Phore Net. 3838 kc. (Tues. and Thurs., 6 p.m. MST; Sun. 7:30 a.m. MST). The New Mexico MARS Net functions daily at noon, 5 p.m., and 9 p.m. MST. The New Mexico YL MARS Net now meets on Tues. and Thurs. 9-10 a.m. MST, and studies proper procedure. There now are approximately 8 members. A "Spare Parts Auction" was held by the Sandia Base Radio Club, the club receiving 50 per cent of the amount received over the club receiving 50 per cent of the amount received over the club receiving 50 per cent of the amount received over the club receiving 50 per cent of the amount received over the club receiving 50 per cent of the Amount received over the club receiving 50 per cent of the Amount received over the club receiving 50 per cent of the Amount received over the club receiving 50 per cent of the Amount received over the club receiving 50 per cent of the Amount received over the club receiving 50 per cent of the Amount received over the club receiving 50 per cent of the Amount received over the club receiving 50 per cent of the Amount received over the club rece

MARITIME — SCM, A. M. Crowell, VEIDQ — SEC: FQ. RM: OM. EC: EK. Orchids to the Maritime Fone Net, which now meets nightly as a traffic net and really is showing some snappy operating. Seven o'clock AST is the time. HH, ex-VE7Y, now is in Korea. PX is out in VE7-Land. AGC can be heard signing VE3CBS. A report to hand says that DB is going on 'phone. RR is QRP with ATR-5. DQ II, RU, and SI have been on 7-Mc. 'phone. SI has returned home from a visit to VE3. ET has changed QTH to the country and is back on 3.7-Mc. 'phone. PQ, WI, OM. and HJ have been on 21 Mc. The HARC executives are considering fund-raising plans for the coming season. PT has resigned as treasurer because of work and has been on 14 Mc. a bit with 'phone. FQ still is handling traffic with the "north." HD has the new mobile going but finds contacts few this time of year. OM reports VO2A. VO6N, and VO6A how are MTN members. We hear the Sunday Am. "Fat Man's Club" is active on 3.8-Mc. 'phone. ME and TF have been giving 7-Mc. 'phone a whirl, Sorry to hear that XR (Continued on page 180)

THIRD ANNUAL ONTARIO SECTION QSO CONTEST

A QSO contest between Ontario section amateurs, sponsored by the Ontario 'Phone club, will be held on two consecutive Sundays, April 26th and May 3rd, 1953, from 10 a.m. to 10 p.m. EST each period. The purpose of the contest is to enable c.w. and 'phone operators to become more acquainted with both types of operating. Two awards and one consolation prise will be made. The c.w. award will be known as the "Sparton Radio Trophy." and the 'phone award will be known as the "Columbia Record Trophy." Both trophies, donated by Spartan of Canada, will be suitably engraved with the winner's call and the year of presentation. Permanent possession of the trophy will be given to the station winning it on three occasions. After the winners have been selected, the remaining contestants who have submitted logs shall be eligible for a draw prize. Following are the rules: Frequencies from 3500 kc. to 3725 kc. for c.w. operation, 3500 kc. for 'phone-to-'phone, 'Phone-to-'phone, 'Phone-to-'phone, 'Phone-to-cw., and c.w.-to-'phone, provided the contacts are made in the portion of the band absted eligible for a draw dimed and time. Any station may operate 'phone or c.w., provided his operation takes place in the proper portion of the band. Stations may be worked only once regardless of type of emission. One contestant cannot win both trophies. "CQ VE3 Contest logs are to be sent to S. Moir, P.O. Box 191, Simcec. Ontario, and must be postmarked prior to midnight May 16, 1953.



ARVEY FIRST TO STOCK ...

ELDICO TR-75-TV



TRANSMITTER

This is an ideal unit for the novice. Very simple to assemble. New, revised circuit to

aid in the elimination of TVI. Uses 6L6 oscillator — 807 amplifier com-bination P1-network output. Husky power supply delivers 600 volts to the 807. Complete . . . including a punched chassis and shielded cabinet. Unbelievably low priced at \$64.95

MD-40	mod	iulator	kit	for	above	49.95
MD-40P	-	above				
but v	with	Dawer	598	miv.		59.95

GONSET "COMMUNICATOR"

A complete two-way station for 2 meter-band operation. Suit-able for mobile or fixed location use. Receiver is a sensi-tive superheterodyne with built-in noise clipper circuit and 6BQ7 Cascode rf stage. Transmitter



stage. Transmitter
uses 2E26 in final 15
watts input. Employs 8 mc. crystals for
stability, and has a range of over 100
miles. Operates on either 110 volts AC or
6 volts DC. Weight approx. 16 pounds. Complete with Tubes (less crysta

and microphone) Also available for commercial or

airp-rt Unicom applications. \$299.50 With crystal ..

SUPERIOR POWERSTATS

Smooth, efficient valt-Smooth, efficient valtage control, 0-135 volts output from 115 volt AC line. Medels also for 230 volt laput. Write for fraput. Write for fraput. Write for fraput able and penel menuation.



Type	10, 1,25 amps	5 8.50
	20. 3 omps	12.50
	116, 7.5 amps, table mtg	23.00
	116U, 7.5 amps, panel mtg	18.00
	1126, 15 amps	46.00
	1156, 45 amps	118.00

Complete Stock Always On Hand For Immediate Delivery

NOTE: In view of the rapidly changing market conditions, all prices shown are subject to change without notice and are Net, F. O. B., New York City.

SONAR

Model SRT-120

Transmitter

For mobile and fixed location operation. Mas band-switch for 80, 75, 40, 20, 15, and 10 or 11 meters, plus spare position for any future band. Has provision for two crystals or external VFO head. Final amplifler employs the new Amperex 9903/5894A tube. Power input is 120 watts on CW, ner emptoys the new Amperex YVUJ/30V4A.
tube. Power input is 120 warts on CW,
and 100 warts en phone. All circuits
metered. Power requirements: 600 voits
dc at 330 me, and 6.3 voits at 6.4 A.
Complete with Tubes.

\$198.50

External VFO Head.

19.50



The New Model **DB-23**

RME PRESELECTOR

Radically new in design, the D8-23 increases communications receiver efficiency by providing an average overall gain on all amateur bands from 3.5 through 30 mc. of approximately 25 db. Centrals include: 'on/off' band selector and antenna peak-ing. Band selector, when set at 0-position, provides through-coupling of antenna to receiver directly. Employs unique 3-tube, broad-band, lew noise circuit. Pewer supply is self contained.

Dimensions: 5" high, 71/3" wide, 6" deep. Cabinet: Blue-gray steel. Complete with tubes \$49.50

FOR YOUR SPECIAL NEEDS **Harvey Carries**

Complete Stocks for Immediate 'Off-the-Shelf' Delivery

. SINGLE SIDEBAND EQUIPMENT

By Central Electronics, Eldico, Millen and others.

All makes and types TRANSITORS. GERMANIUM DIODES. SUBMINIATURE TUBES, ETC.

SPRAGUE NON-INDUCTIVE RESISTORS


For Rhombic Antenna Termination, and other applications.

CAMBRIDGE THERMIONIC COILS

Brand New WESTON RF AMMETER

Model 425 3½" dial, non-plare glass. Range: From 0 to 2.5 amps.

Special \$8.95

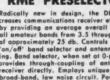



The New ELMAC PMR 6-A

Portable Mobile Receiver

A complete 10-tube dual conversion, communications receiver. Provides coverage of 6 bands from 10 to 80 meters as well as broadcast and 160 meter band.

features include: High Selectivity Other teatures include: High Selectivity , Built-in noise limiter . . Built-in BFO...Thermal-Compensated Oscillator . . Panel-centrolled A V C'on/off'switch. Designed for 30-ohm antenna. Power requirements: 6 volts AC or DC at 3.3 Amps. and 250 volts DC at 90 mA. Dimensions: 41/3" high, 6" wide, 81/2" deep

Weight: 61/2 fbs. Complete with tubes... \$134.50

Brand New Specially Priced DYNAMOTORS

CARTER Input Voltage	Output Valtage	Output Current in ma. 270	SPECIAL PRICE \$35.00
5.8	375	325	35.00
5.8	600	175	29.50
12.3	375	325	39.50

5.8 375 35.00 35.00 6.0 600 270 5.75 410 275

QUANTITIES LIMITED . Subject to Prior Sale

We reserve right to ship either brand.



ELECTRON TUBE TECHNICIANS

We now have several openings for technicians to work in the fabrication and processing of advanced type electron tube research models.

To qualify for one of these openings you should be experienced in experimental work for research and development in vacuum tubes, which includes the fields of mechanics, electronics, chemistry and high-vacuum techniques.

ADDRESS RESUME OF TRAINING AND EXPERIENCE

HUGHE!

RESEARCH AND DEVELOPMENT LABORATORIES

Technical Personnel Department

CULVER CITY, LOS ANGELES COUNTY, CALIFORNIA



LOOK HERE, **FELLOWS!**

We will gladly pay the highest possible price for the purchase of any Heterodyne Frequency Meter as illustrated here, including the BC-221, the TS-173, the TS-174, the TS-175, and the TS-323.

Please write, giving complete sclature and condition to

WESTON LABORATORIES, Inc.

has been on the sick list. Traffic: (Jan.) VE1FQ 148, VO6N 86, 80 64, VE1OM 43, VO6M 32, VE1LY 18, VO6AB 5, 6R 3. (Dec.) VE1OM 93, VO6M 20.

ONTARIO—SCM, G. Eric Farquhar, VE3IA—The Ritchener-Waterloo Radio Club and the Hamilton ARC now occupy new club quarters. Possibly the biggest news of the month was the announcement by the Department of Transport permitting Canadian hams the use of 7200 to for 'phone. This became effective Jan. 12th and no time was lost getting on. Terrific QRM has been experienced on this segment for nearly two years by the c.w. boys from foreign broadcast stations. Feb. 20th acv our W-Land cousins joining this part of the band with 'phone. It will be interesting to see if foreign QRM can be overridden by the high-power fraternity. We understand the v.h.f. boys had a get-together in Oakville during the month, but no information was received on same. It's a girl at the QTH of DFE. Congratulations! AV8 completed the modulator and now awaits the R.L.'s blessing. To ATR, possibly this section's most consistent "reported in 1466 times. Lack of material regarding activity in this section makes this report rather short. Please let your doings in our hobby be known to your representative who, from time to time, get as blast for not mentioning more happenings. NG reports the Nortown Amateur Radio Club was on as VE3BRR at the International Hobby Show, Toronto, in February, Traffic: VE3WY 192, ATR 181, IA 127, BUR 115, DGZ 97, NO 74, IL 40, BMG 33, Gl 32, AUU 15, DU 10, BSF 9, VZ 9, DQA 5, OJ 3, VD 2, AVS 1.

QUEBEC—SCM, Gordon A. Lynn, VE2GL—TA is active on SSN on 7280 kc. daily at 1230 and on QEN at 1100 Sun, on 7275 kc. Ww has worked 49 countries on 21-Mc. e.w. and 13 on 'phone, and on 40-meter' phone has worked all VE call districts except 6, XE, and all We call districts except 6, XE, and all We all dis

CA reports his activity confined to week ends because 20 meters is no good evenings. He had OX3BQ as a visitor. Traffic: VEZCA 49, DR 23, EC 10, LO 8.

ALBERTA—SCM, Sydney T. Jones, VE6MJ—YD has erected a new antenns and is on 3.75-Mc, 'phone with good signals. AO was a recent visitor to Edmonton and worked mobile with the local gang, WC, who has done some good work on the Maple Loaf Net, is a new ORS. HM, FB, CP, LQ, and MJ have been working 40-meter 'phone since the opening of this band on Jan. 12th. YZ, at Fort Chipeyan, is a new ORS and is Alberta contact on Trunk Line "I." YM has recovered from a spell of illness. OD advises that the Alberta 'Phone Net will meet at 1830 Mon., Wed., and Fri. ZR has moved to a new QTH. Za is working or antenna tuner. EY has a new job at the "Mac." This monthly report is made possible only through your reports to your SCM on or before the 7th of each month. Reports have been few in the past months. Let your SCM know what you are doing, His address? See page 6 of any QST. Traffic: VE6HM 100, OD 4, YM 4, MJ 3.

MANITOBA — Acting SCM, Leonard E. Cuff, VE4LC.—It is with the deepest regret that I have to report the death of our SCM, Arthur W. Morley, VE4AM, at the Winnipeg General Hospital Jan. 23rd. He is survived by his widow Jean, VE4JM, and two children. Our sympathics on the family in this very sand loss. DU has put in 6L0 modulators and also has built new 6-meter receiver and 100-kc. erzystal-control frequency standard. CU is heard quite consistently on 20-meter cw. HS has constructed new grid-dip meter and 6-meter receiver. DI is going strong on 6 meters and has new NC-57 receiver. IM, ex-3CDJ, at \$1. Stoniface, has SX-71 receiver and is running 5 watts to a 6AQS final and a half-wave doublet on 40-meter c.w. Has no is building new 815 final. GO is on 20-meter c.w. with 100 watts to pair of \$07s and modulated with a pair of \$07s in Class ABZ. HT was a recent visitor to Winnipeg. MX and JN took part in the Brandon Bonspiel recently. Rh has to be limp caused by dropping a tra



HENRY RADIO offers YOU:

LOW PRICES: You can't beat my wholesale prices,

FAST SERVICE: You get fast service. I have big stocks of Collins, National, Hallicrafters, Hammarlund, RME, Johnson, Harvey-Wells, Lysco, Gonset, Millen, Morrow, Mallard, Elmac, Master Mobile, Hy-Lite, Babcock, all other receivers, transmitters, parts at lowest prices.


BIG TRADES: I want trade-ins. I trade big. Tell me what you want—what you have to trade. Get my offer. I pay cash for receivers and transmitters

TIME PAYMENTS: Get what you want and pay by the month. I give you

better terms because I finance all terms myself. Write for details, SATISFACTION: Try any communications receiver ten days—if you return

it your only cost is shipping charges. I want you to be satisfied. Ask any ham about Henry Radio.

PERSONAL ATTENTION: You get personal attention. Bob Henry, WØARA, runs the Butler store. Ted Henry, W6UOU, runs the Los Angeles store. Bob Henry can be reached nearly 24 hours a day, 7 days a week, Write, phone, with a store Cand in Mark and insulving Eventy inquiring menry can be reached hearly 24 hours a day, 7 days a week, virile, phone, wire or visit either store. Send us your orders and inquiries. Export inquiries solicited too.

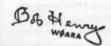

HENRY RADIO STORES Phone: 395

PAYING PROPOSITION

Hams maintain many mobile-radio systems for police, power, petroleum, taxicab and other commercials. You need a 2nd class ticket, PLUS frequency and modulation test gear. Here's a way to

PICK UP EXTRA CASH!



105-B Micrometer Frequency Measures center frequency, any number nearby transmitters, CW, AM, FM, 0.1 to 175 MC. Meets FCC mobile specs. Price \$220.00.



Type 205 FM Modulation Meter. Indicates peak modulation deviation. Tunable, 25 to 200 MC. Meets FCC mobile specs. Weight 12 lb. Width 12". Price \$240.00.

LAMPKIN LABORATORIES, INC.

Mfg. Division, Bradenton, Florida

Please send more dope on the 105-8 and 205.

We Carry a Complete Line of Amateur Equipment including: National . Hallicrafters . E. F. Johnson Co. . Bud . Barker & Williamson, etc.

VARIETY ELECTRIC CO., INC. 468-470 Broad Street, Newark 2, New Jersey

	RADI	O C	OURS	SES
	RADIO (• cot	
The second		ERVICING		TELEVISION
	Preparation for	license requ		and reavy
	Personal C	ounselling S	iervices for Ve	terans
W 14 C A		Walte for Cal	Inles T.O.	

TRADE & TECH. 15 W. 63 51, N. Y. 23

ENdicolt 2-8117

in charge of communications at Fort Qu'Appelle Civil Defense School and did an FB job despite conditions. EX is heard on 75-meter 'phone after a long absence. M'N moved to Suskatoon, adding another mobile rig to the list. GM is a new call heard from Carrot River. MY has a new NC-183. "-Mc. 'phone is proving to be a good 'phone band and should relieve congestion on 75 meters and provide longer hauls for daylight hours. Our sympathy goes to Mrs. Morley and family on the passing away of VEAAM. Art did a fine job as SCM, was a consistent not station, and will be missed by all. Traffic: VE5TE 28, PJ 20, HR 10, GO 4, LU 2.

ARRL Appointments:

OFFICIAL RELAY STATION

Throughout the history of amateur radio, the c.w. traffic-handler has carved for himself an enviable niche. Traffic-handling has brought high credit to all stations engaged. Early ARRL recognition of the public service and dedication to properly systematized procedures created the Official Relay Station post as the first and basic ARRL appointment.

Today ORS appointment is the most popular of all station posts in the field organization. If you enjoy operating c.w. and consistent traffic and net operation, here is something really worth

What is it going to cost you? Learning and using standard ARRL operating practices (proper message form, ending signals, abbreviations) keeping a transmitter and receiver in operating condition at all times . . . reporting monthly to your SCM . . . ability to handle the code at 15

What are you going to get in return? The greatest single benefit is probably the development of operating ability and know-how. You'll find that there's a great deal of satisfaction to be had in being able to efficiently check in on your traffic net and handle your station properly. There's fraternalism in net operating with a group



of top performers. The opportunity to be a part of the ARRL field organization is yours. We get more fun and accomplishment as part of an operating team, not from going it alone in casual work. Added to enjoyment is the privilege of participation in the quarterly CD Parties. Late news and operating aids from Headquarters go along with your appointment.

Where can you apply for an Official Relay Station appointment? Your SCM is the one to contact. You'll find his name and address on page 6 of any QST. He'll be glad to help you.

STEINBERGS 4

IMMEDIATE DELIVERY

Single Sideband Exciter SS-75

Check these specifications and you'll see why the 55-75 is now the one piece of equipment that places all the advantages of single sideband at your finger

- * Built-in stable VFO, with voltage regulation.
- Carrier injection to receiver antenna terminals . . . tune in SSSC signals the same as AM, no other gadgets necessary.
- Illuminated VFO tuning dial provides 31 inches of band-spread 3800-4000 KC in 4 bands, with 5 to 1 goor reduction.
- Built-in voice control and receiver disabling circuit. Also provides for break-in CW operation.
- Specially designed crystal filter network for maximum stability and reliability.
- * Carrier injection to transmitter available for working single sideband WITH CARRIER, for tune-up adjustments, or CW.
- ★ 10 watts cuput, with additional 807 scaket for up to 100 watt operation with external power supply.



WRIGHT T-R SWITCH

For break-in operation on CW, AM, or SSSC. Use one antenna for transmitting and receiving. It's instantaneous! No moving parts, no power needed to operate. Coax fitting for connections to feeder and receiver will handle 1 Kw. With 75 meter plug-in coil . . \$9.95

Extra coils \$1.75 per band

LIMITED QUANTITY

RG8/U coax, 12", plug each end	\$.70
831 SP standard coax plug	.60
Coax angle plug	.45
3-conductor Koiled Kord, 6' ext	1.79
3-gang heavy 365 mmf variable	.60
4-prong steatite socket	.15
110V. relay, DPST 20 Amp contacts	5.95
15 Henry, 50 Ma. filter choke	.59


PHOSPHOR BRONZE AERIAL

125 ft, of the finest aerial wire obtainable. 42-strand phosphor-branze with linen center, Will not stretch, very high tensile strength, diameter approximately same as No. 14 copper, very flexible. Excellent for transmitting or re-

MINIMUM ORDER \$2.00. Send 20% deposit with COD orders. Please include sufficient postage or instruct us to ship by Express Collect. Overpayment will be refunded by check.



633 WALNUT STREET . CINCINNATI 2, OHIO

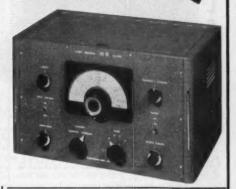

ELMAC-A54 Under-dash Mobile Xmtr.



VFO or Crystal control. Direct-reading VFO on all bands—75 20, 11, 10 • Plate modulation • Completely bands-witching fone or CW. • 50 Waths max. input. Power required: 300–500 V.D.C. at 250 ma., 6.3 V AC or DC at 4.5A. • Uses 3-6AG5, 6AB5, 6CA, 12AU7, 2-6L6G, 807 (Included). • Only 7½" x 7½" x 12", 14½ lbs.

For carbon mike input For Caron mike imposition of the control of the con 149.00 39.50 17.10 23.10



8/8/8 MFD. 500 V. D.C.

Triple 8 mfd, 500 v-orking volt D.C. all-filled condenser, common negative, solder terminals, hermetically sealed. 5" x 3%" x 2¼"

> Your order will receive my personal attention and will be shipped the same day order is received. We dis-tribute all top-flight ana-teur lines . . . let us know teur lines...let us know what you need. 73, Jule Burnett W8WHE

MULTI-BAND OPERATION

SIZGLI



SIDEBAND

8 TIMES THE VOICE POWER

HARMONIC TVI VIRTUALLY ELIMINATED

MULTIPHASE EXCITER MODEL 18A (apper left). Approx. 10 watta peak output 160 to 20 meters, somewhat less on 10-15 meters. Will drive beam power tetrodes to more than 1 KW input from 20 to 160 meters. SWITCHABLE SSB, with or without carrier, double sideband AM, PM, break-in CW, VOICE OPERATED BREAK-IN and receiver disabling, it's ALL BUILT-IN to this truly versatile exciter. Built-in power supply also furnishes blocking bias for linear amplifier and band. Wired and tested \$159.58. Complete kit \$112.58, Extra coil sets for \$3.95 per band.

Plug your 40 or 80 meter stals into the MULTIPHASE EX-CITER for break-in CW operation. Later it's an excellent fone exciter, for use with your General Class ticket. No expensive high-level modulator required.

MODEL A RECEIVER ADAPTER (upper right). Improves any receiver, SWITCHABLE upper and lower sideband reception of SSB, AM. PM and CW. Cuts interference and heterodynes in half. Eliminate distortion caused by selective fading. Works into any receiver having 450-500 KC 18. Built-in power supply. Use a Model A Slicer — notice the "holes" in even our most crowded bands and hear signals you kit \$49.56. Eliminate of the complete of th

P8-1 Plug-in prealigned 90° phase shift network and socket available separately for use with GE Signal Slicer and SSB Jr. 87.95 postpaid.

WRITE FOR LITERATURE

Central Electronics. Inc.

2125 W. Giddings Street

Chicago 25, Illinois



RADIO TELEPHONY
RADIO TELEGRAPHY
RADAR & TELEVISION

Courses ranging in length from 7 to 12 months. Dormitory room and board on campus for \$48.00 a month. The college owns KPAC, 5 KW broadcast station with studios located on campus. New students accepted monthly. If interested in radio training necessary to pass F.C.C. examinations for write-for details. New Advanced TV Engineering Course.

PORT ARTHUR COLLEGE PORT ARTHUR

Approved for G.I. training

Meteor Scatter

(Continued from page 15)

Signal Strength

The strength of the meteor-scatter signal, and hence its usefulness in ham communication, will depend on the efficiency of the stations involved. The antenna system is very important, and should be designed to concentrate power where the most meteor scatter is taking place — namely, in the E region over the midpoint of the great circle path. For an 800-mile path, the main lobe of the pattern in the vertical plane should ideally be at 6 degrees above the horizontal. At 20 meters a dipole should be 165 feet over perfectly-conducting earth, for the lowest lobe to be at 6 degrees! In practice, whatever arrangement affords the highest gain consistent with a low vertical angle will be best.

Almost any good station will be able to take advantage of meteor-scatter transmission at 20 meters. At 15 meters, however, it is probable that only the kilowatt boys will be able to transmit a usable background signal over the path. Stations having good locations and rotary beams (or preferably rhombics), and willing to use maximum receiver crystal selectivity, will no doubt be able to make a go of it. (As frequency goes up, echo strengths and durations go down, but since the echoes are exponential, the net loss can be overcome by an increase in power or receiver sensitivity.) In any case, a c.w. clipper or limiter will be very worth-while. Otherwise, when gain is advanced enough to copy weak passages. meteor bursts tend to be deafening.

Note that the preceding remarks on signal strength apply to those times of day when meteor scatter is the only form of transmission taking place. Actually, for much of any given day the signal will be well above the purely meteor level. Any sporadic-E activity, for example, will enormously increase the strength of the received field. (During one memorable test with W7PZ, sporadic-E set in and within a minute or so transformed his randomly-fading S1 meteor-scatter transmission into a rock-solid S9 signal with a very slow, almost perfectly sinusoidal amplitude variation.) Whenever any F-layer transmission is in at all, of course, there will be a strong ground back-scatter component present along with the meteor-scatter.

Thus the timetable for 14-Mc. transmission over a New York-Chicago path, during the winter months of the year, might run something like the following:

8 p.m. — 7 a.m. meteor scatter alone
7 a.m. — 9 a.m. meteor plus F-layer

ground scatter

9 A.M. — 5 P.M. direct F-layer
transmission

5 P.M. — S P.M. meteor plus F-layer ground scatter

weak signal medium signal

> very strong signal

er medium signal

(Sporadic E, which might come in at any hour (Continued on page 196)




UNBELIEVABLE Price!

BIG NAME BRAND HEARING AID





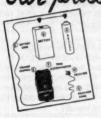

Now Anybody Can Afford One!

Unbelievable! But a fortunate purchase by Lafayette makes available a top-brand hearing aid regularly priced at \$185.00 for only \$24.50. Because

of our low price we may not advertise the name but you will recognize the high quality of the manufacturer the moment you see it. Excellent as a spare aid, and a real opportunity if you could not afford one before. Brand new, packed in original manufacturer's jewelled case as illustrated. Supplied with receiver, receiver cord, battery cord and plug (less batteries). Order sample immediately. In lots of 3, \$23.50. Uses Burgess XX30E and 8R batteries at \$1.55 per set.

HAMMARLUND HQ-129X COMMUNICATIONS RECEIVER 199.50

10" PM Matching Speaker for HQ-Net 129X Receiver.

Brand New GUARANTEED!



RAYTHEON HEARING AID TUBES

Stock No. CK-505AX. pentade volt. amp. CK-506AX.

in lets of 10

CK-507AX, pentode power amp.

59c single, ea.

49c.

CK-536AX, power amp.

HEADQUARTERS FOR GONSET AMATEUR EQUIPMENT







GONSET 2-METER AMATEUR AND C.A.P. CONVERTER For fixed or mobile use on 144-152.2 mc, High stability permits use with auto or home budgests for the stability permits use with auto or home presed, appeal, appeal, appeal summer and avoids immediate from TV, policy of the other stations of the stability of the stationary of the stability of the

GONSET 10-30 MC SHORT WAYE CONVERTER Continuous corrections one on three bands. For use in all-band mobile station installations, 1500 ke output. High sensitivity on short with, 4 tubes, Uses power supply of receiver to which attached. Size: 3½ x 3½ x 5½°, Shpg. wt. 4 tis.

STEERING POST MOUNTING BRACKET — For installing any Gonset Conset No. 3002 Convertor.... Gonset 3005 Tri-Band Converter......NET 47.60

OONSET MODEL 3017 SINGLE BAND CONVERTERS

Available in 10, 13, 20 and 75

meter models (specify band))

Available in 10, 13, 20 and 75

motor models (specify band)

motor models (specify band)

The NEW GONSET 2 Meter XMTR-RECEIVER

NET 189.00

afayette Radio FAMOUS IN RADIO FOR 32 YEARS

NEW YORK, N. Y.	1:00 Sixth Ave
BRONX, N. Y.	542 E. Fordham Rd
NEWARK, N. J.	24 Central Ave.
PLAINFIELD, N. J.	139 West 2nd St.
BOSTON, MASS	. 110 Federal St.



RADIO and TELEVISION

Over 30 years N.E. Radio Training Center. Train for all types FCC operators' licenses. Also Radio and Television servicing. FM-AM broadcasting transmitters at school. Send for Catalog O.


MASS. RADIO SCHOOL

271 Hunfington Avenue Boston 15, Massachusi Lic. by Comm. Mass. Dapt. Educ.

LEARN CODE!

SPEED UP Your RECEIVING with G-C Automatic Sender

Type S \$24.00 Postpaid in U. S. A.

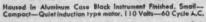

Adjustable speed control, maintains constant speed at any Setting. Complete with ten rolls of double perforated tape. A wide variety of other practice tapes available at 50c per roll.

GARDINER & COMPANY

STRATFORD

NEW JERSEY

of the day or night, would provide a strong signal directly, or a weaker signal via ground scatter.)

Commercial Stations

The reader is probably wondering, at this point, why meteor-scatter propagation has not previously been noticed on transmission from commercial stations. The answer is that it probably has, but simply was not identified as such. Most broadcast or commercial stations are in the habit of signing off after F-layer transmission fails, so listeners seldom get much of an opportunity to hear meteor scatter. Once in a while a station, transmitting according to a prearranged schedule, will stay on the air after its frequency has "gone dead." This has happened, for example, in the case of a 17-megacycle short-wave broadcasting station roughly two hundred miles south of Palo Alto. Their beam points right at Stanford, on its way to the Orient, and what is believed to be meteor scatter has been heard on many occasions.

WWV's transmissions on 15 and 20 megacycles, of course, provide a wonderful opportunity to check for meteor scatter, and hams living within a radius of 1000 miles of Beltsville, Maryland, are urged to tune in on WWV and satisfy themselves that the 20-meter band really doesn't go entirely dead, at night, after all!

Acknowledgment

The authors are indebted to W6VUW, W6UGL, W6LLK, W6AOF and other members of the Stanford Radio Club for assistance during the tests. The help of Larry and Clayte at W7TMK is also appreciated. The loan of recording equipment belonging to a joint-Service-sponsored research project is gratefully acknowledged. The photograph of meteors during a shower was taken by L. A. Manning, W6QHJ.

YL News & Views

(Continued from page 53)

who works ten LARK members. Send members' calls and dates and frequencies of the QSOs to Gladys, W9MYC. The LARK now meet at 1400 CST on Wednesday (10 meters) each week, except the first week of the month when they meet at 2200 CST on Tuesday.

April elevanth is the date of the semi-annual W1 YL Luncheon (YLRL members and nonmembers alike). The place is the Smith House in Cambridge, Massachusetts. Write Helen Wright, W1UPZ, P. O. Box 126, Brookline 46, Mass., for further information.



Wava Harlan, W8FPT, is the YLRL District Chairman of the eighth call area. First licensed in 1950, Wava is active on 10, 20 and 75. Her OM is W8EAM. Since the start of her term last July, Wava regularly has sent postcards to each of the licensed YLs in her district, in quest of information and news. Other DCs who follow this practice find it's worth the little extra time and effort.



LEO I. MEYERSON WEGFO CU ON 10-20 & 75 METERS

FELLOWS...LET ME PROVE

that you can afford the world's best buy . . . a

WRL GLOBE KING TRANSMITTER

We allow you more on trade-ins—our large volume of sales means faster turn-over and greater savings for you. We finance our own paper—there's no red tape. We accept low down payments-name your own terms. WRL buys more equipment-WRL sells more equipment. We offer the most personalized service anywhere.

It pays to deal with WRL-"One of the World's Largest Distributors of Amateur Radio Transmitting Equipment."

FREE 1953 WRL CATALOG



"I FOUND GLOBE KING LOWER IN PRICE, HIGHER IN POWER, & EQUAL IN QUALITY TO ALL OTHER RIGS!"

Writes Jack Ashley, W405C.

"When I first began considering purchasing a new commercial transmitter, there were three main factors which I had in mind: Price; Power; and Quality. After several months of consideration, viewing the specifications of most all of the commercial rigs available on the market, I finally made my decision on the "GLOBE KING"

. I found the Globe King lower in price, higher in power, and equal in quality to all other rigs . . I've enjoyed using the GLOBE KING very much and it has held up to all my expectations. I can recommend it to any "Ham" who wants a transmitter with plenty of

punch and at a reasonable price." Signed/Jack H. Ashley W405C, Box 254, Ware Shoals, S.C.

Jack Ashley with his Globe King

NEW WRL 400-WATTS Phone-CW

SA75.00 SA95.00 GLOBE KING XMTR Send for complete data sheet

ENGINEERING TRIUI



WIRED

(By our ngineers)

\$99.95

WRL 165 WATT

KIT FORM

(Incl. all parts and tubes)

\$89.95.

THE WRL GLOBE SCOUT (50 WATTS PHONE - CW)

The WRL GLOBE SCOUT is the latest triumph of the WRL engineering staff. It is a beautiful, compact XMTR, completely self-contained, including power supply — 8H X 141/2W X 81/4D. Contains new 6146 tube in final; covers 160M thru 10M. Metering provided for final grid and

final plate circuits. Complete kit includes all parts, chassis, panel, power supply, cabinet, tubes, meter and one set of coils. Can be used for mobile work with suitable power supply. (Auxiliary socket provided.) An ideal XMTR for the novice or the experienced ham.

GLOBE SCOUT ACCESSORIES

Coil sets available for 160, 80, 40, 20, 15 and 11-10,

40 Meter Cells for new 40M Phone Band......\$3.00 KIT-FORM WIRED (less GLOBE CHAMPION XMTR accessories \$329.50 \$349.50

GET READY FOR THE **40 METER PHONE BAND**

See us for all of the latest 40 Meter Gear, including Gonset Super Six—\$52.50, and new Morrow 58R-\$74.95. We will be first with the latest gear as it is released from the factory.

We have in stock 40 Meter crystals, coils, antennas. Crystals for new 40 Meter Phone Band.

7200-7300 K.C.-\$1.50 ea.

Amphenol 40 M folded dipoi-\$7.80

Globe King XMTR 40 M Ceils-\$7.75 per set

Globe Champion XMTR 40 M Coils-\$7.60 per set

RADIO REFERENCE MAP



HANDY WALL SIZE

W#/11 FOR 2	STALLED SPECIFICATION	FOURMENT SHEETS
WRITE	150	PHONE
WIRE		7795
World	INTERVITHING IN PAR	Radio
LABORATOR		COUNCIL BLUFFS

World Radio Laboratories, Inc. 744 West Broadway Council Bluffs, Iowa	0-4
Please send me:	Glabe Scout Infa
☐ New Log Book 25c	Globe King info
☐ Free Catalog	Globe Champion Info
Radio Map 25c	☐ Used Equipment List
Name	
Address	
Citys	late

DOW CO-AX RELA



Causes negligible change in s.w.r. up to 100 Mc. Handles power up to 1000 watts. Fits standard connectors for co-ax. No chatter. Specially built for "Silent operation". Over-allienth 44". Over-allienth 3". Note new magnetcover. Externally mounted SPDT switch operated by relay can be used for opening B+ of receiver when transmitting, or for other control purposes. Add to prices below \$1.00. When in transmit position a built-in shorting connector grounds receiver antenna lead. This protects receiver against injury from r.f. and reduces to a minimum the capacity coupling between receiver and relay contacts. Add to prices below, \$1.00.

Types (all voltages). Amateur Met.

ur distributor, but if he has not yet stocked Dow Co-ax Relays, now direct from factory. Send check, money order, or will. O.D. Prices are Net, FOB shipping point: Warren, Minn, mipeg and Montreal, Canada. C.O.D.

Dealer Inquiries Invited

THE DOW-KEY CO., INC. Minnesota

THE DOW-KEY CO. 578 Goulding Street Winnipeg, Canada

THE DOW-KEY CO. 2310 Wilson Avenue Montreal, Canada



Folded & Loaded Antennas

(Continued from page 27)

\/32 Monopole

(Eight integrals)

$$R_{\frac{\lambda}{32}} = R_{\frac{\lambda}{32}} = R_{\frac{\lambda}{32}} = 0.3 \text{ ohm.} \qquad (9)$$

Top- and Bottom-Loaded $\frac{\lambda}{8}$ Monopole (Fig. 5)

In this case the far-field factor is twice the cosine integral from 0 to The In calculating the impedance, however, we

must divide by the square of the cosine of $\frac{\pi}{2}$ or 22.5 degrees, since we are feeding at a point 22.5 degrees from the current loop. This is similar to the case considered in equation (5). Therefore,

$$R_{\frac{\lambda}{8}\text{TBL}} = 30 \left(\frac{2 \int_{0}^{\pi} \frac{1}{8} \sin \theta d\theta}{\cos \frac{\pi}{8}} \right)^{2}$$
 (10)

 $=30 (0.830)^2 = 21$ ohms.

Folded Dipole (Fig. 7C)

The far-field factor for this case is found by calculating the difference between the cosine integral from 0 to $\frac{3\pi}{4}$ and

the integral from $\frac{3\pi}{4}$ to $\frac{3\pi}{2}$. This figure is 2.414 and from this the impedance of the folded 3/4-wave dipole comes out to be about 420 ohms.

'Phone Receiver

(Continued from page 34)

usually encumbered by the time constants in the a.v.c. circuit. In this receiver, a.v.c., is applied only to the two i.f. amplifying stages, so the blocking bias is applied to all other stages: r.f., mixer, and the i.f. branch stages. The latter circuit has only a few 0.01-µfd. r.f. by-pass condensers involved, so its time constant is quite short. Normally, an external bias is applied when it is desired to cut the receiver off. If this is not available, however, the first r.f. grid will rectify the incoming signal and produce enough bias to cut off all the other stages and silence the receiver. Meanwhile, the a.v.c. detector experiences no signal because its branch amplifier is cut off, so the receiver comes back with full life the instant the transmitter is turned off.

Conclusion

It is, of course, a pleasure to have in the shack a receiver that within itself is capable of doing the full job for reception of all kinds of 'phone signals in a crowded band. At the same time it has been a refreshing experience to reaffirm the notion that with time and thought the amateur can still do as well or better than his commercial brethren. Try building your own "dream" receiver; you'll enjoy it.

Uncle Dave's Radio Shack

FORT ORANGE RADIO DISTRIBUTING COMPANY

April Brings Showers of Bargains

from Uncle Dave—You can depend on him for a Square Deal

Collins 32V-3 Transmitter



\$775

VFO Controlled, Bandswitching, Gangtuned Transmitter, Covers 80, 40, 20, 15, 11 and 10 meters; 150 watts CW; 120 watts phone; entire RF section enclosed in metal shield for harmonic radiation reduction.

The New Collins 75A-3

Receiver

\$550



The familiar Model 75A-2, redesigned and modified to provide for the use of mechanical filters. Supplied with one 3 kc. filter, and facilities for two additional. A 3-position front panel switch permits selection of filter desired.

Additional Mechanical Filters: 1 kc. and 6 kc.....each \$75.00

The NEW

National HRO SIXTY



\$483⁵⁰

Here's the latest and the greatest of the famous National HRO series! Features dual-conversion plus 12 permeabilitytuned 1F circuits!

We regularly stock all National receivers, occassories and parts.

Sure we take trade-ins TOP ALLOWANCE See us

ELDICO TR-75-TV TRANSMITTER KIT



The ideal novice transmitter. New TVI circuit. Uses 6L6 as oscillator and 807 amplifier to PI Network output.

Gonset "Commander"

35-50 West Metti-Seed Treasmitter 124⁵⁰



Frequency Range: 1.7 to 54 me. continuous. Fixed or Mobile. Wired, tested, complete with all tubes, 2 hi-Q final tank coils. 5\% x 8\% x 7\%

The ALL NEW

NATIONAL NC183-D

\$39660



Every feature you want in a truly modern receiver. 540 kc.55 mc, coverage. Let us send you descriptive literature on this great receiver.

SYLVAN CONVERTERS 2, 6, 10 Meters \$4500

USED EQUIPMENT

RME 70 with DB 20 Preselector	\$125.00
RME VHF 152A	\$50.00
Collins 75A-2 (Demonstrator — Like New)	\$390.00
Hallicrafter S38	\$32.95
Hallicrafter SX-25 and PM 23 Speaker	\$115.00
Gonset 3-30 Converter	
Gonset 2-Meter Converter	
Gonset Noise Clipper	
Meisner 150B Transmitter	\$250.00
Telvar 60 Watt Transmitter (10 and 20M Coils)	\$75.00
Collins 32V-3 (Display Model) Never Used	\$710.00
HT-9 Hallicrafter (Complete Coils)	\$225.00
Web 10-Meter Clamper Transmitter (New)	\$29.95
National 1" Medulation Scope	

JOHNSON VIKING II



Kit, complete with tubes— \$27950 less crystal, key and mike Wired and Tested \$334.50

ort Grange 904 BROADWAY, ALBANY, N. Y.

BUY OF A LIFETIME!

TRIED AND PROVEN THE WORLD OVER



LETTINE MODEL 240

TRANSMITTER WITH MOBILE CONNECTIONS AND A.C. POWER SUPPLY

\$25 deposit with order — balance C.O.D. 80, 20, 10 meter coils \$2.91 per set. 160 meter coils \$3.60. Also for CAP, Broadcast, MARS, Marine, State Guard, Novice.

LETTINE RADIO MFG. CO.

62 Berkeley Street

Valley Stream, N. Y.









PIONEER TOOL CO. LOS ANGELES 16, CALIFORNIA

High-Power Mobile

(Continued from page 29)

system and a subsequent linear amplifier. Although this involved a few problems not normally encountered in mobile work, we feel that the result is more than satisfactory.

As can be seen from the circuit diagram in Fig. 1, the low-level r.f. section uses one triode of a 12AU7 as a Pierce crystal oscillator and the other triode as a neutralized plate-modulated stage. For good quality, a crystal microphone is used with a 6CB6 speech amplifier ahead of the 6AQ5 Class A modulator. A volume control wasn't found to be necessary, so none is included. The 10,000-ohm dropping resistor and 10-µfd. by-pass condenser are necessary for 100 per cent modulation in a choke-coupled (Heising) circuit like this, and checks with a 'scope showed the modulation to be linear and complete. A 6AL5 with both sections in parallel is used as a negative peak clipper, and a small audio filter (0.25-henry choke and three condensers) completes the circuit.

A Class AB₁ linear amplifier follows the modulated stage, and we feel that this line-up has certain advantages, contrary to misunderstandings in the past. Although the efficiency of the final amplifier is not as high in this application as it would be if a Class C stage were modulated, the limit here is the total power available from the power supply, not the input to the final stage (as it might be in a home station). It can be shown that the transmitter in Fig. 1, which puts out a carrier of 220 watts, draws less total power than a high-level system giving the same carrier output. So far as compactness of the r.f. and audio systems is concerned, there is just no comparison, as a look at the photographs will prove. It must be admitted, however, that we took advantage of the small size of Eimac 4X150As and of Jennings vacuum condensers to obtain this small package. A variable vacuum capacitor, C_3 , is used for tuning, shunted by a fixed vacuum capacitor, C2. This latter condenser helped to suppress harmonics and parasitics.

Forced air cooling is required with the 4X-150As, and a small d.c.-motor-operated blower is used for this purpose, as can be seen in the photographs. The radio noise from the motor brushes was quite a problem at first, but a two-section r.f. filter cleaned up the "hash."

Antenna

As has been mentioned before in QST,1 corona discharge from the tip of the whip is a problem in high-powered mobile operation. We licked it with a 3-turn wire basket fastened to the tip of the whip. The wire was about 1/8 inch in diameter, and the finished sphere was about 11/4 inches in

At this power level the center loading coil in the antenna is likely to heat, and our first at-

(Continued on page 132)

Leavenworth, "75-Meter Mobile, California Style," QST, Jan., 1952.

FOR THE BEST RESULTS . . . THE BEST EQUIPMENT

HAMMARLUND

"Super-Pro 600" COMMUNICATIONS RECEIVER

The outstanding professional communications receiver, used in quantity by the U.S. Army, Navy and Air Force. Only recently available to the amateur, the SP-600 includes every feature essential to top performance, dependability and operating ease. Continuous coverage from 540 kcs to 54 mc in 6 ranges, including the 160, 80, 40, 20, 15, 11-10 and 6 meter bands. Double-conversion from 7.4-54 mcs. Highly efficient turret type range selector, plus provision for 6 crystal-controlled frequencies. 80-120 db rejection depending on frequency with virtually no images! Extremely accurate tuning—slow-turning frequency calibrated dial and fast-moving vernier bandspread dial controlled by single knob. Over 6000 readable setting for each range on vernier dial! Positive locking tuning lock does not affect frequency. High sensitivity and excellent selectivity, with 4 stages of IF amplification and 2 RF stages. Sensitivity 2.3 microvolts or better for 10.1 signal to noise ratio. Unusual stability, approaching, that of



IN STOCK FOR IMMEDIATE DELIVERY!

crystal oscillators. Complete with 20 tubes, voltage regulator, rectifier and operating manual (less speaker and fixed-frequency crystals). Handsoome dark grey wrinklefinish cabinet, 21% x 12% x 17% Operates on 95-260 V 60 cycle AC. Ship wt. approx. 100 lbs.

Order No. 36-392Q. \$985.00 Matching spkr 10" PM. Order No. 36-391Q \$14.50

FOR THE BEST EQUIPMENT ... RADIO SHACK CORP.

SIMPLE WAY TO PAY FOR BETTER EQUIPMENT!

TO ENABLE YOU TO BUY THE BEST EQUIPMENT WITHOUT RUINING YOUR BUDGET, RADIO SHACK HAS ARRANGED SIMPLE CREDIT TERMS FOR ANY PURCHASES OVER \$45.00. PAY ONLY 10% BOWN, FULL YEAR TO PAY THE BALANCE. NO INTEREST IS CHARGED IF ACCOUNT IS PAID IN FULL WITHIN GO DAYS. WRITE FOR CREDIT CLEARANCE SHEET IF YOU WANT TO BUY NEW EQUIPMENT THIS SIMPLE WAY.

KECEIVERS	5
Mfr., Model No. and Order No.	DOWN PAYMENT
Collins 75A-2 Order No. Q36-895	\$42.00
Gonset "Super-Six" Order No. Q36-295	5.25
Mailicrafters S-38G Order No. Q36-045	4.95
Hallicrafters S-53A Order No. Q36-064	9.00
Hallicrafters 5-40B Order No. Q36-052	12.00
Hallicrafters 5-76 Order No. Q36-048	17.95
Hallicrafters SX-71 Order No. Q36-199	22.45
Hallicrafters SX-62 Order No. Q36-061	29.95
Hallicrafters SX-73 Order No. Q38-198	97.50
Hammarlund HQ-129 Order No. Q36-390	x 23.95
Mallard M38 Conver Order No. Q36-523	ter 5.26
Morrow 2BR Convert Order No. Q36-510	er 5.50
National SW-54 Order No. Q36-141	5.00
National NC-125 Order No. Q38-043	14.95
National NC-183D Order No. Q36-038	36.95
National HRO-60 Order No. Q36-125	48.35
RME VHF-152A Order No. Q36-070	9.70
CONSET 2 METER XI	
Order No. 035-147	18.95

TRANSMITTERS

TRANSMITTE	RS
Mfr., Model No. and Order No.	DOWN PAYMENT
Collins 32V-3 Order No. Q35-001	\$77.50
Eldics TR-75 KIT Order No. Q35-137	6.50
Eldico TR-1TV KIT Order No. Q35-139	38.00
Eldico MD-40 KIT Order No. Q35-134	5.00
Elmac Mobile A54H Order No. Q35-200	14.90
Gonset "Commander Order No. Q35-145	12.45
Hallicrafters HT-20 Order No. Q35-107	44.95
Harvey-Wells TBS-50 Order No. Q35-161	
Harvey-Wells TBS-50 Order No. Q35-162	13.75
Johnson Viking II KI Order No. Q35-120	27.95
Johnson Viking Mobi Order No. Q35-122	9.95
Stancor ST-203A KIT Order No. Q35-041	4.75

OTORY NO. (33-04)

RADIO SHACK STOCKS ALL
COLLINS — ELDICO — ELMAC
GONSEY — HALLICRAFTERS
— HAMMARLUND — HARVEY
WELLS — JOHNSON — MALLARD — MEISSNER — MILLEN
— MONTORADIO — MORROW
— NATIONAL — PHILMORE

STANCOR AND ALL OTHER
WELL KNOWN AMATEUR RADIO
GEARI

SPECIAL BARGAIN!

\$10,00 SQUARE D UHF HEAVY DUTY KNIFE SWITCH!

3 POT 50 amp rating Blades and receptacles of heavy duty copper. 3" isolantite insulators, 7 x 8x1" bakelite base. Wt. 5-lbs.



ONLY \$1.50



COLLINS KW-1

AMATEUR TRANSMITTER FOR MAXIMUM PERMITTED POWER!

RADIO SHACK

CORPORATION

167 Washington St., Boston 8, Mass.

ATTENTION.

Complete mobile package — nothing else to buy. Outstanding mobile signals use MOTOROLA equipment — backed by years of communication equipment experience — wor of 2-way mobile equipment. world's largest producer

Double

verter . . .

\$10.75

A mobile transmitter 1325 Master Mobile with a double feature FM or AM at flip of the switch, the MOTOR-OLA FMT-30-DMS (27-30 C120 00 stainless steel soring Tapered.

MC.)... MOTOROLA P-69-13 or 18-ARS receiver with special noise limiter for use with any converter having 1440. 3000

\$60.00 KC. 100/96" Master Mobile

New Gon-set Tri-Band \$130.00 Spread Converter. . Gon-set "Super 6" Con-

P.327.E Fire Antenna. . \$5.25

loud speaker ... The above comes complete with all necessary accessories and mounting hardware. Order direct or through the Motorola National Service Organization member in

Motoroia National Service Organization which has been returned from the field, modified and rebuilt for Amateus Service.

Above units subject to State and Federal Excise Tax

where it applies.

MOTOROLA C. & E. INC.

Amateur Sales Dept. QST — April 1327 W. Washington Bivd. Chicago 7, Illin his Attention: Harry Harrison, WYLLX, Tel. Taylor 9-2200 Ext. 161

TURN "PRO" WITH "BIG" LEAGUE And you'll hat 1.00011 YOUR AMATEUR EXPERIENCE MAY QUALIFY YOU FOR A HIGH-PAYING **ELECTRONICS OR RADIO POSITION** WITH BENDIX RADIO.

 TECHNICAL WRITERS AND TRAINEES

· COMPONENTS ENGINEERING TRAINEES

· LAB TECHNICIANS

We have openings in excellent positions which carry engineering responsibility. If you have a good background of practical experience, you need not have a deg

Write, Wire or Phone MR. E. O. COLE Dept. L

Bendix Radio

DIVISION OF BENDIX AVIATION CORPORATION

BALTIMORE-4, MD. Phone: TOWSON 2200

Maker of the World's Finest Electronic Equipment

tempts were no exceptions. A high-Q coil was finally obtained from W6LXA that did the trick nicely, and we ended up with a 5-foot whip above the coil and a 51/2-foot section below the 1-foot long coil.

Tuning

The low-level portion of the transmitter needs no comment here, because it is similar to any other a.m. rig using Heising modulation. The linear amplifier will be handled a little differently than you are used to, however, and a few comments are in order. To obtain upward modulation, the antenna coupling is tighter than one is used to with Class C operation. The linear is first coupled for maximum antenna current, and the coupling is then increased until the antenna current drops down about 20 per cent. This is no particular trick, since the high-C tank makes it easy to couple to the load. When the antenna is properly coupled, the grid current on modulation peaks should never be allowed to exceed about 1 ma., if distortion is to be avoided. When trouble-shooting this rig, we found only three basic reasons why the output wasn't linear:

19

1) The grid bias does not remain constant.

2) Too much grid drive is used.

3) The antenna is not coupled tightly enough.

Operation

Having a high-powered mobile has allowed us to carry on successful communication where low power is inadequate. Our best DX in daylight is over 500 miles, with excellent signal strength. This is hard to duplicate in our valley with 1-kw. fixed stations. On one occasion we were parked near a fixed station of comparable power and 300 miles away the signal was 1 S-point better than that from the fixed.

Governors - President Relay

(Continued from page 43)

Georgia: W4MZO-W4ZD-W4CAK-W3HVL.

Idaho: W7IWU-W3CVE. Illinois: W9KQL-W3PZA

Indiana; W9LZI-W9TT-W3JZY-W3QZC.

Iowa: W@ATTL-W3CA-W3OZC

Kansas: WOKSY-K4USA

Kentucky: W4TFK-W4TUT-W4BAZ-W3FQB.

Louisiana: W5NG-K4USA.

Maine: K1NAI landline to W1RUO-W1PTL-?-W3NOE.

Massachusetts: W1BB-W3PZA. Michigan: W8SCW-W3PZA.

Minnesota: WØUCV-WØMXC-WØCGK-W3CA-W3OZC.

Mississippi: W5NPO-W3CIC.

Missouri: WØDSO-W3OMN.

Montana: W7IVY-W3PFO.

Nebraska: WØVYX landline to WØJDJ-W8AUJ-K3WBB-1-W308X-W3CLY

Nevada: W7ZT-W3BHV.

New Hampshire: Message originated twice: W1APK-W3CA-W3ECP, W1APK-W2FKN-W3TNA.

New Jersey: W2ZI-W3QZC

New Mexico: W5KCW-K4USA.

New York: No message filed. Message from W2GTI indi-cated that repeated attempts had not met with success. North Carolina; W48GD-W3OMN.

(Continued on page 134)

HIGHWAYS ind AIRWAVES! BOY OLE TIMER METER PHONE BAND WORRY ABOUT SURE IS WORKING IS GREAT! EM WITH HIS ALL-OUT HERE BAND MOBILE Jules



ELMAC Model A-54 Wired for 10, 11, 20, 40 and 75 meters. Only \$143.00

Model A-54H. Same as above but for crystal or dynamic mike. Only \$153.00

MORROW 5 BAND CONVERTER Model 5BR. Covers 10, 11, 15, 20, 40, 75 and 80 meters. Only \$74.95

ELMAC New Mobile Receiver Model PMR-6-A. Dual conversion, 10 tubes, BFO, noise limiter, covers all amateur bands, 10 through 160 meters plus BC band. Measures only 41/4" H. x 6" W. x 81/2" Deep. Only \$134.50

MASTER MOBILE All-Band center loaded mobile antennas with coil for one band (20, 40 or 75 meters). Only \$8.57. Extra coils for above bands. Only \$3.23 each

CARTER GENEMOTORS. Furnish "B" power for mobile transmitters. Small and compact. Model 450AS. 6 volts at 29 amps input. 400 volts DC at 250 MA output. Only \$45.68

Model 520AS. 6 volts at 28 amps input. 500 volts DC at 200 MA output. Only \$46.46

MALLARD New Mobile Antenna Base Loading Ceil for 40 Meters. Model HI-Q 40 Coil. Only \$7.95

STANCOR Model ST-203A 10-11 Meter Kit. (Simple conversion instructions for other bands.) Only \$47.50. Wired and tested. Only \$66.75

All prices f. o. b. St. Louis . Phone CHestnut 1125



THE PLEASURE IS ALL YOURS

When you hear the call of the open road, it's time to equip with a brand new mobile rig from Walter Ashe. His fabulous "Surprise" Trade-In Allowance enables you to get the new, compact, more efficient units of your choice at tremendous savings! And the creation of the 40 meter phone band makes a mobile installation more exciting than ever before. So get in on the fun. Trade your used (factory-built) communication equipment naw. Wire, write, phone or use the handy coupon.



GONSET SUPER 6 CONVERTER. Covers 10, 11, 15, 20, 40, 75 meters plus 19 and 49 meter BC bands. Only \$52.50

JOHNSON VIKING MOBILE KIT Model 240-141 Only \$99.50





BABCOCK Model MT-5A Mobile D-XMITTER Only \$99.50

- FREE CATAL	DIO COMPANY	Q-53-
1125 Pine St., St. Lo	ouis 1, Missouri	
Rush "Surprise" T	rade-In offer on my	
for		
(show make and r	model number of new equ	ipment desired)
(show make and r		ipment desired)
(show make and r		ipment desired)
(show make and r		ipment desired)

CRYSTAL CONTROLLED CONVERTERS

For

2, 6, 10-11, 15 or 20 Meters



supply, crystal and all tubesl

NET

Converter for any one band, complete with built-in power supply, crystal, tubes, output cable and input fitting for 52, 75, or 300 ohm line, \$45. Now available at leading distributors. Specify band and input impedance when ordering.

Crystal Convertor for Collins 75A2 \$55.00

For further information, write Dept. Q-4

SYLVAN ELECTRONICS LABORATORIES, INC.

303 No. Pearl St.

Albany, N. Y.

SENSATIONAL TVI NEWS!

We guarantee TVI suppression and absolute compliance with FCC requirements on harmonic radiation. Not a miracle, but all the tried and true methods, made easy to apply, and it works every

me! Use the Gotham Shielded Cabinet, an all-steel, pound, $13'' \times 24'' \times 16''$ shielded cabinet designed rouly one purpose: elimination of TVI. The other Shielded Cabinet makes it possible to ply all the TVI steps easily and quickly. 20 pound, 13

Gotham Shielded Cabinet makes it possible to apply all the TVI steps easily and quickly. No alterations on your present rig, no loss of resale value, no danger of damage, no paint scraping—in a few minutes your rig is completely shielded and you are testing for TVI. REMEMBER: IF YOU DON'T CLEAN UP YOUR TVI, WE REFUND IN FULL.
Full step-by-step instructions are included. End the bugsboos of FCC notices, quiet hours and disgruntled neighbors with the Gotham Shielded Cabinet. TRY IT AT OUR RISK, MONEY BACK IF YOU ARE NOT SATISFIED.

HOW TO ORDER: Send check or money order for \$12.95 and we will ship promptly by Railway Express, charges

Note: The Gotham Shielded Cabinet is for transmitters smaller than 13 x 24 x 16. If your rig is bigger, send dimensions for special quotation.

GOTHAM HOBBY Now York 35, N. Y.

North Dakula: WOHWD via WOGJJ-WOSSW-W2BO-?-W3MCG-K4U8A

Ohio: W8APF via W8YEW-W3QQ8. Ohlahoma: W5CKQ-K4USA.

Oregon: W7DAA-W7BA-K5WAC-K4USA.

Pennsylvania: W3A DE-W3FQB.
Rhode Island: W1WSY-W18JO-W5BTB-W4NFD/3-K4USA.

South Carolina: W4DMX-W4ANK-W4NF.

South Dakota: WOUVL-K4USA. Tennessee: W4AEE-W3OMN.

Texas: W5GQ-W4NF.
Utah: W7JPN via W7JVA landline to W7UTM-W4IMH-

Vermont: WIOAK-W3FQB.
Virginia: W4JHK-W4LW-W4NF.
Washington: No message filed. Repeated attempts by W7FWD and W7FIX met with no succe

West Virginia: Two separate originations reported. W8EVR-W3OMN, W8HZA-K4U8A.

Wisconsin: W9CBE-W3FQB. Wyoming: W7HRM-W3CVE

Canal Zone: KZ5WA-W4RYE-K4USA.

Puerto Rico: Two separate originations reported: KP4KD-W3JHW-W3QZC, KP4HZ-W4NTZ-K4USA.

13

Virgin Islanda: KV4AA-W3IL.

Miscellaneous Observations

W2ZI can well be proud of his personal file of GPR messages (attached to the original Governors' message) representing his activity in all 7 relays. . . . The Delaware message followed closely by the Texas message was the first GPR message received and confirmed in the Washington area. It was received from W3HC by W3AKB and duly confirmed by 5:05 P.M. EST, with Texas greetings arriving at 5:07 P.M. EST. W5GQ and W4NF did the FB job on the Texas message via 20-meter 'phone. . . . W9TT, manager of Trunk Line "J," reported that it was a miserably poor night, but good operators on the eastern end made up for the bad conditions. . . . W3QQS reversed the order of events for his participation in this year's GPR. In 1949, he originated the Ohio message. This year, W3QQS (ex-W8BKE) handled the Washington end of the Ohio message. . . . W7IWU, Idaho SCM, has his usual short trip to obtain his Governor's message. He lives just across the street from the Idaho Governor. . . . Due to the unusually long-skip conditions prevailing, the Arizona GPR message got to Washington the hard way; Arizona to Georgia to Virginia to Illinois, and then to Jeanne, W2BTB, in New York whereupon it was put into the Washington area. . . . WSSCW says he never felt as much like a DX station as when he heard the response to his "CQ Washington de W8SCW, GPR." The longest GPR hop was from California, W6CIS/6, to W4KFC. Of the two military commands relaying congratulations in the relay, the 5th Air Division in French Morocco relayed their best wishes from French Morocco to Washington, via W2BTB in New York. This was the longest single hop reported among the congratulatory messages received.-E. W.

Strays 3

W3ODU/1, operating W1AW on 75 'phone, had consecutive contacts with W4NN, W2YY, WSCCC and WSII. (!!)

NOW at NEWARK THE NEWEST IN

THE LATEST FROM licrafters

THE New HT-20



HT-20 TVI SUPPRESSED MULTI-BAND TRANSMITTER

HT-20 TVI SUPPRESSED MULTI-BAND TRANSMITTER
A complete new transmitter that incorporates all the Hallicrafters ingenuity and craftsmanship and practically eliminates "TVI" interference. Covers 160-10 meters, Delivers clean signals on both phone and CW. Power output for AM is 100 watts; for CW—115 watts. Uses bandswitching exciter and continuous-tuning final amplifier. All spurious outputs are at least 90 db below rated output. All control leads are filtered thoroughly. Pi-network tank circuit is followed by 4-section low-pass filter, dial and meter scales are covered with metal screening. 10-position crystal selector switch has additional positions for external VFO. Single meter with 8-position switch checks all stages and provides output tuning indication. Tube lineup. 6AH6 osc.-buffer, 6L6 buffer-doubler, 4D32 final amp., 6SL7GT speech, 6K6GT driver, 2-807 modulators, 5U4G LAV rectifier, 2-5R4GY H-V rectifiers, 6BL7 bias rectifier, 6AL5 RF carrier rectifier, Sizes; 20/xx119/xs1694". With tubes, cabinet and instructions. For 105-120 volts, 30-60 cycles AC. Wi., 130 lbs.

MODEL SX-71



DUAL-IF RECEIVER

A top-notch receiver. Has double superheterodyne circuit above 4.6 mc to provide extra selectivity and image rejection. Includes Narrow Band FM reception, as well as AM and CW. Provides continuous AM reception from 538 kc to 35 mc, and 46 to 56 mc. Five-range selector covers: 538-1650 kc, 1600-4800 kc, 4.6-13.5 mc, 12.5-35 mc and 46-56 mc. Built-in limiter and balanced detector stages for hiss-free Narrow Band FM reception. Double conversion (2075 and 455 kc IF channels) gives image rejection of better than 300 to 1 at 28 mc. One RF, two conversion, and 3 IF stages yield high gain for sensitivity in the order of .7 microvolt. 2½ kc selectivity with 11 tuned circuits. Audio peaked for communications frequencies, with 3 watt output. Has extra-wide dials for Main and Bandspread tuning. Controls: 3-step Crystal Filter with Phasing; RF, AF; Tone; BFO On-Off/Pitch; Limiter; Send/Receive Switch; AM/Narrow Band FM Switch. Has universal antenna input, "5" meter, 500-ohm speaker output, phone jack, external power socket and remote send/receive terminals. Circuit uses: 6BA6 RF, 6C4 oscillator. 6AU6 mixer, 6BE6 2nd conv., 3-6SK7 IF, 6H6 ANL—delayed AVC; 6SC7 BFO/1st audio, 6AL5 detector and 6K6GT audio out-put. Also has VR150 regulator and 5Y3GT rectifier. Satin black cabinet with chrome trim, hinged top. Size, 18/ys8%/xs/2*. For 105-125 volts, 60 cycles. With tubes, less speaker, 2244.50

Write to Department T-4



Just Out! NEWARKS NEW CATALOG NO. 55



MARMAX

MODEL MT-52 TRANSMITTER

Compact multi-band mobile or fixed phone-CW transmitter. Tube complement: 1-6AG7, 1transmitter. Tube complement: 1-6AG7, 1-6Q6GT, 1-12AU7, 1-6J6. Power requirements: 2.9 amperes @ 6 volts DC. Peak power rating of final stage: 50 watts. Size: 3½" high, 8½" wide, 9" deep. With tubes and 10 meter coils. Wt., 2 lbs.

97F190. NET......79.50

POLICALARM



MODEL PR-31

MODEL PR-31
Covers 30-50 mc. For police, fire and emergency calls. Superhet circuit uses ratio detector for quiet operation under "no signal" conditions. Sensitivity better than 10 microvolts. Drift compensated. With 5" speaker. Requires to 8 ft, vertical wire antenna. Walnut plastic cabinet, 11x6x6". 110-120 v., AC-DC. Shpg. vt. 8 lbs. cabinet, 11x6x6" wt., 8 lbs. 98F101, NET.,

NATIONAL



MODEL SW-54 RECEIVER

MODEL SW-54 RECEIVER
Outperforms receivers twice the size and twice the price. Covers entire frequency range from 540 kc to 30 in 4 bands. Police, Foreign, Amateur and Ship bands clearly marked. Unique plastic bandspread dial is adjustable to assure logging accuracy over entire range. Built-in speaker, Size, 11x/x/2". Wt., 15 lbs.

987318, NET.

49.95

LYSCO



MODEL 6005 TRANSMITTER


Latest from Lysco—a newly designed all-band TVI-suppressed transmitter. Operates on 160, 80, 40, 20, 15 and 10 meter bands. Temperature compensated. Uses 6AG7 oscillator, 6AG7 buffer, 807 amplifier, 5UdG rectifier, Power input, 35 watts. Black wrinkle-finish steel case, 170,0117, 190, 100. 35 watts. Black w 17x9x11". Wt., 50 lbs. 97F040. NET...... 189.95

FREE!




XTALS FOR ALL PURPOSES!

LOW FREQFT 241A for SSB, lat	- SCR.	BC-610	FT	234-1/2" apc
ice filter, 14.72 spc. 54th or 72nd harm channels fisted by fund. Fractions amitted.	522 1/10 1/2" sp.	2 banana pluga %" spc.	4190 5030 5485	1015 5940 6640 1129 5973 6673 2045 6273 6706
374 395 418 487 511 400 464 375 396 419 488 514 440 466 377 397 420 490 515 441 488 379 398 422 481 516 442 470 380 491 423 472 518 446 472 381 403 424 481 519 447 474	5910 6370 6450 6470 6497 6522	2030 2435 2045 2442 2105 2532 2125 2545 2145 2557 2155 3202	6040 6073 6106 6140 6173 6175	3735 6306 6740 5385 6325 7440 5677 6340 7506 5706 6373 7506 5725 6406 7540 5740 6450 7573
383 484 425 484 528 456 475 384 485 426 495 522 452 478 385 467 427 496 525 461 477 386 488 431 497 526 462 479 397 489 433 498 530 463 489 387 411 435 583 531 59 48 381 411 435 583 531 59 484 383 411 435 585 537 10 for	7350 7580 7810 C1 20	2228 3215 2258 3237 2280 3750 2282 3322 2290 3510 2300 3520 2305 3550 2320 3580	6206 6773 6573 6906 7740 7773 7806 7840	5760 6473 7606 5773 6475 7640 5800 6506 7650 5806 6540 7673 5825 6573 7706 5840 6575 7973 5850 6600 8240 5873 6606 8250
292 HIA 483 507 536 39.0) 393 415 484 506 Add 20¢ 394 HIB 485 500 10 stals o posta	r lass for	2360 3945 2300 3995 2415 \$1.29	7873 7996 7940 496	99 ¢ such 10 for 33.00

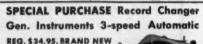

\$19.97

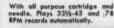



Calculator

(Continued from page 45)

smaller wire could be used and often is, where space is a major consideration.

Space-winding the turns invariably will result

Power Input	Band (Mc.)	N'ire Size
	21-28	6
1000	14-7	6 8
	3.5-1.8	10
View of the control o	28-21	8
500	14-7	12
500 14-7	3.5-1.7	14
	28-21	12
150	14-7	14
	14-7 3.5-1.8 28-21 14-7 3.5-1.7	18
	28-21	14
75	14-7	18
	3.5-1.7	22
25 W.*	28-21	18
and	14-7	24
Recv.	3.5-7	28

in a coil of higher Q, especially at frequencies above 7 Mc., and a form factor in which the turns spacing results in a coil length that is between 1 and 2 times the diameter is usually considered satisfactory. Space winding is especially desirable in transmitter circuits because the heat developed is dissipated more readily, although this is not a serious consideration, of course, at very low power. One point that is not understood by many with whom we have had contact is that coils having the same diameter, length and number of turns will have essentially the same inductance. You can close-wind a coil with heavy wire, or space-wind it with smaller wire and, so long as the diameter, length and number of turns are the same, the inductances will be the same within a few per cent. So, when you see a wire size specified for a coil, and power-handling capability or Q are not prime considerations, don't be afraid to use a size or two smaller (or larger if you can get

Effects of Shielding

it in the same winding length).

While on the subject of coil Q, it should be pointed out that the Q of a coil will drop off quite rapidly if it is placed close to shielding or the large metal surfaces. Also, if the coil is to be placed in a shielding compartment of a certain limited size, a coil with less Q in free air may have a greater Q, when enclosed, than a larger coil that has greater Q in free air. For instance, a $2\frac{1}{2}$ -inch-diameter coil that had a Q of 325 in free space, dropped to a Q of 230 when centered in a $5 \times 6 \times 9$ -inch aluminum box, while a coil with a diameter of $1\frac{1}{4}$ inches, wound with smaller wire and having a Q of 295 in free air dropped to a Q of 260. The answer, of course, is

(Continued on page 138)



ON A SOLID FOUNDATION!

3 efore a mason can lay up a brick wall he has to put in several years learning the trade, and so it goes with any calling.

7 ortunately, the beginner in amateur radio who is aiming for his Novice ticket as the Gateway to Advanced Amateur Radio need not have to contemplate long years ahead before he can enjoy this fascinating and useful hobby and ragehew with the best of them.

7he wise beginner will take advantage of the "package offer" we describe here. It consists of four of our publications which help to start him off on the highway to hamming:

- HOW TO BECOME A RADIO AMATEUR
- THE RADIO AMATEUR'S LICENSE MANUAL
- · LEARNING THE RADIOTELEGRAPH CODE
- OPERATING AN AMATEUR RADIO STATION

These four books should provide all the necessary information toward the coveted ticket and enviable privilege of going — and staying — on the air.

The four books, available at your dealer, \$1.25

The AMERICAN RADIO RELAY LEAGUE, Inc.
WEST HARTFORD 7, CONN.



The INSTRUMENT FOR HAMS — has numerous transmitter applications such as pretuning, neutralization, locating parasitics, correcting TVI, adjusting antennas, design and many others.

Receiver applications include measuring C, L and Q of components — determining RF circuit

and Q of components — determining RF circuit resonant frequencies, etc.

Covers the 80, 40, 20, 11, 10, 6, 2 and 1½ meter bands. Complete coverage from 2-250 MC.

Easy one hand, one unit operation. Convenient thumb wheel drive of tuning condenser leaves one hand free for making circuit adjustments. No tuning head and meter with connecting cable to worry about. It's compact — case only 2½" wide x 3" high x 7" long.

All plug-in coils (rack included) are wound and calibrated—no coil winding, drilling, punching, forming or painting to do—all fabrication is complete, and the kit goes together smoothly and easily.

The 500 microampere Simpson meter movement and easily.

The 500 microampere Simpson meter movement and sensitivity control allow operator to set instrument for easy detection of dips on all ranges. Instrument is transformer operated for safety. You'll like the appearance of this kit with its baked enamel panel and crackle finish cabinet.

Please include postage to cover par-cel post and insurance for 4 pounds.

BENTON HARBOR 9. MICHIGAN

that the smaller coil, although of about the same inductance, was spaced farther from the sides of the box. The inductance of a coil will also be affected to a certain extent by the presence of shielding or other metal surfaces in the vicinity of the coil. When the shielding on all sides approaches within one-half of the coil diameter, the reduction in inductance may be of the order of 10 to 15 per cent.

Single Sideband

(Continued from page 51)

For larger shifts, connect the two pins of the crystal holder together and to the negative pole of a 1½-volt battery.

Make the crystal the negative electrode of an electrolytic cell, the positive being a piece of copper wire and the electrocopper sulphate as before.

Run the system for a minute or so, wash and dry the crystal, check the frequency and repeat until the desired frequency is reached. This method moves the crystal to a lower frequency and is reversible, so if you go too far you

can go back by reversing the polarity.

"Two don'ts are: Don't use more than 1½ volts, and don't use too strong a solution. If you do, a black deposit forms and ruins the performance of the crystal."

Brian report: trying the scheme as suggested, and he succeeded in moving a Channel 27 crystal 2½ ke. lower. Using a solution of unknown strength, he got a black deposit that lowered the Q of the crystal tremendously. However, cleaning it off restored things to normal, except that one of the connecting wires pulled off the plating in the process. Soldering this lead back on was no fun, Brian admits.

Sweep-Tube Rig

(Continued from page 38)

amplifier grid current value of 5 or 6 ma. in mind and then adjust the oscillator accordingly.

It is not possible to recommend the antenna coupler connections that will be required for each and every installation. However, recent QST articles 2,3 and the ARRL Handbook are excellent sources of information on the subject. The operator should remember that the LC ratio of the coupler may be controlled not only by the jumper connections but also by selection of the inductor. In other words, the 7-Mc. coil and high-C may be best in some instances even though the transmitter is tuned to 3.5 Mc. On the other hand, the 3.5-Mc. coil and real low-C may work out best when the rig is set up for 7-Mc. operation.

Although very few TVI preventive measures were included in the design of the transmitter, it has taken the most rugged interference tests in stride. The rig has been operated right alongside a TV set that was tuned to a fringe-area Channel 6 signal. There was a slight bit of interference to the picture at the beginning of the operation, but every last trace of TVI was cleared up by addition to J_2 of those two all important capacitors — C_{10} and C_{11} .

² Smith, "Antenna Couplers for the Novice," QST.

August, 1952.

³ McCoy, "An 80- and 40-Meter Antenna System for the Novice," QST, February, 1953.





RCA INSTITUTES, INC.

A Service of Radio Corporation of America 350 West 4th St., New York 14, N. Y.

OFFERS COURSES IN ALL TECHNICAL PHASES OF RADIO, TELEVISION, ELECTRONICS

Approved for Veterans Write Dept. ST-53 for Catalog


AN/APR-4 COMPONENTS WANTED

In any condition. Also top prices for: ARC-1, ARC-3, APR-1, APR-5A, etc.; TS-34 and other "TS-" and standard Lab Test equipment, especially for the MICROWAVE RELION, ART-13, BC-248, BC-221, LAE, LAF, LAG, and other quality Surplus equipment; also quantity Spares, tubes, pluge and cable.

ENGINEERING ASSOCIATES

434 Patterson Road

Dayton 9, Ohio

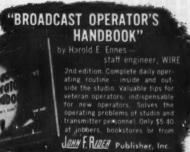



3 MODELS AVAILABLE

#310 10 mtr \$19.95

#302 2 mtr

MOUNTED WITH TV ANT. HARDWARE HOBOKEN, N. J

6 mtr \$16.95

#306

LITERATURE ON COMPLETE LINE OF LYSCO EQUIPMENT FREE ON REQUEST TO DEPT. Q

PROVISION FOR

GUY WIRES

NEW	LOW-PRICED BETTER	ANTENNAS
10 METER	DIPOLE	
6 METER	2 EL-BEAM	9.95
		11.95
6 METER	3 EL-BEAM	12.95
	2 EL-BEAM"	12.95
10 METER	3 EL-BEAM	16.95
10 METER	3 EL-BEAM"	18.95
15 METER	2 EL-BEAM*	22.95
15 METER	3 EL-BEAM*	29.95
20 METER	3 EL-BEAM"	39.95
10 111011011		24.95
20 METER		24.95

Furnished complete, easy and quick to assemble. Instructions and all data included. Strong aluminum castings and tubing, less mast and wire. Made by hams and sold to hams, no dealers. Literature on request. All antennas adjustable over entire band. ORDER NOW-IMMEDIATE SHIPMENT.

SENT ON APPROVAL

Send only \$1.00. We ship immediately, charges collect. Pay balance in 10 days or return Beam.

GOTHAM HOBBY New York 33, N. Y.

V.H.F. Sweepstakes

(Continued from page 55)

ROA	NOKE DIVISION	VE3AIB	402- 67- 3-A-B-D
	Virginia	VE3HW	264- 44- 3-B
W4UBY	380- 38- 5-B	VE3TW	213- 36- 3-B
W4JCJ	370- 37- 5-B	VE3AET	192- 48- 2-A-B
SOUTHWESTERN		VE3AQG	186- 31- 3-B
50	DIVISION	VE3ANY	168- 34- 2-A-B
W 74-34	Los Angeles	VE3UT	144- 36- 2-A-B
W6HZ	180- 30- 3-B	VE3DQW	128- 32- 2-A
		VE3BHQ	108- 27- 2-A
3 0 13	WEST GULF	VE3BCT	100- 25- 2-A
	DIVISION	VE3IZ	64- 16- 2-A-B
Menin	Southern Texas	VE3DHG	56- 14- 2-B
W5VDA	44- 22- 1-B-D	VE3DGF	18- 9- 1-A-B
WOYDA	40- 19- 1-B-D	VE3KM	18- 0- 1-A-B
000004	CANADA	VE3BBW	14- 7- 1-A
Tel III	Ontario	VE3OJ	14- 7- 1-A
VE3DIR	536 67 4-B	VE3ATC1	96- 24- 2-A

¹ Not eligible for award; more than 1 operator. ² WN#BKL, operator. 3 Headquarters staff; not eligible for award. 4 W7AXS, operator, 5 W6ZBS, operator.

17

R.A.C.E.S.

(Continued from page 61)


While it is all to the good to conduct classes in radio theory and in code looking toward the Novice or Technician Class amateur license (and such licensees may serve very well as operators in RACES), it is noteworthy that for radiotelephone operation the RACES regulations also permit use of any FCC operator license holder except for one or two very restricted types [12.241 (e)].

Probably the easiest of these to obtain is the commercial Radiotelephone Third Class, restricted operator permit. This requires no code or theory test and consists mainly of questions concerning radio laws and regulations that are easily learned by the non-technical radio person such as might volunteer locally for such operator training. Many of them will be willing to have community-owned mobile radio equipment installed in their private cars for use only during RACES drills, tests or in an actual emergency. Others can be useful as operators at fixed or portable stations as demand for operators requires. Close surveillance of these operators will of course be especially required.

EDITOR'S NOTE: The concluding installment of this article will appear in a future issue of QST. It will deal primarily with the crucial topics of funds for equipment and allocation of frequencies.

Answer to QUIST QUIZ on page 10-

the antenna system. become a significant part of the total radiation from capacity unbalance to ground, the antenna proper, or near-by objects) can cause feed-line radiation to in the currents in the two conductors (enused by pletely negligible when the line spacing is small (less than 0.01 wavelength). On the other hand, unbatance increases as the s.w.r. increases, this effect is comradiation from a perfectly-balanced two-wire line Put your money on B. While it is 3rue that the

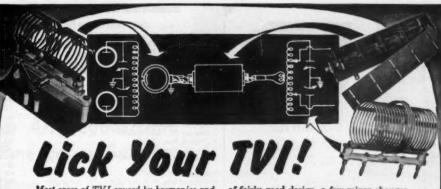

Most cases of TVI caused by harmonics and spurious radiations can be reduced to a negligible minimum.

In planning a new rig, the best bet, of course, is to use precision-made B&W components—from oscillator to final including antenna coupler. Filtering and shielding recommendations in our "Filter Facts" booklet show what to do, how to do it.

Should your present rig be

of fairly good design, a few minor changes as outlined in "Filter Facts" plus installation of B&W low-pass filters and Faraday shielded links will effectively throttle TVI. Many hams have proved it!

Send 15c today for a copy of "Filter Facts" giving details on how to lick your TVI and get silent rigs back on the air!

B&W Low-pass Filters, Models 52 and 75 Amateur net \$27.00.

BaW

BARKER & WILLIAMSON, Inc.

237 Fairfield Ave. Upper Darby, Pa.



MAKE THIS YOUR HOME FOR IMPORTANT WORK UNDER IDEAL CONDITIONS

- TV RECEIVER DESIGN ENGINEERS
- ELECTRONICS ENGINEERS
- FIELD ENGINEERS
- TEST & INSPECTION ENGINEERS
- . LAB. TECHNICIANS

NEEDED TO WORK ON: Radar, G.C.A., Mobile Radio, Auto Radio, Airborne Communication & Navigation Equipment, Television, Antennas, Microwave Equipment, Servo Mechanisms, Guided Missiles and Test Equipment Design.

YOU BENEFIT AT BENDIX RADIO:

from high wages, a modern, air-conditioned plant, paid vacations and holidays, group insurance and a good chance for advancement.

Housing immediately available in the beautiful suburban and country areas that surround the Bendix Radio plant.

Write, Wire or phone MR. E. O. COLE, DEPT. K




DIVISION OF BENDIX AVIATION CORPORATION

LOOK FELLAS

10, 11, 15, 20, 40, 80 METERS



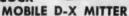

Can be tuned up to switch between 2 of the 6 bands with 2 crystals in each band—then one of the 4 frequencies and the proper antenna may be selected by the 4-position switch with no further tuning required.

- No plug-in colls
 The 4 xtals fit inside transmitter
- 8" wide x 5" high x 7" deep
 Tubes: 6AQ5 osc-doub-quad, 6146 final amp. 12AU7 speech ampl., 2 6AQ5 mods, Class AB
- Input to final amp, when using Babcock PS 4A power supply: 35 watts
- Complete metering, including RF output watts

PRICE \$99.50
Including tubes and connecting pluga less
Write for Details

P\$ 4A 6VDC • Dual vibrators, tubes and connecting pluga less
Write for Details

P\$ 4A 6VDC • Dual vibrator upon pluga to supply with vibrators, \$67.50

NET plugs librator (\$67.50 plugs librator upon pluga librato

C & G RADIO SUPPLY CO.

2505-6 Jefferson Ave.

Tacoma 2, Wash.

A complete meter s COMMUNICATOR pactness Without Compromise Self-centained, 6/110 universal power supply . . . a red hot superhet with "Cascade" front end . . . three LF, stages and a noise limiter that really performs. Covers 144-148.3 magazycles. Transmitter is crystal controlled, (uses standard-type 8 mc crystals) with 2226 final at 12 warts input. High-level plan modulation . . takes crystal or curbon mike . . modulater can be used for a PA system for emergency situations. Every feature of a well-designed fixed sto tion yet in a size and weight, (16 pounds that permits easy partability. Truly . . . competenss without compromise. at your pecial Commer-ial FM and AM usdels are also vailable. Write or details. 19950

Simulated Emergency Test

(Continued from page 63)

Okeechobee Co., Okeechobee, Fla. (W4PZT)	37
Okla. Co., Okla. (W&EHC)	244
Orange Co., Fla. (W4DQA)	186
Orange Co., Vt. (W1OAK)	47
Omining, N. Y., & vic. (W2P8H)	62
Oswego Co., N. Y. (W2ZHU)	64
Ottawa, Ont. (VE3OJ)	93
Paducah, Ky. (W4JLJ)	72
Parent Ter (WELLO)	95 73
Pampa, Tex. (W5IJQ). Passaic Co., N. J. (W2ZBY).	188
Pike Co., Petersburg, Ind. (W9QID)	26
Pittsburg Co., Okla. (W5BGC)*	109
Pittefield, Mass. (W1IZN)	122
Puyallup, Wash. (W7GWK)	58
Quebec, Que., & vic. (VE2QN)*	254
Racine, Wis. (W98ZL)	107
Raleigh, N. C. (W4HUW)	169
Richmond Boro, N. Y. (W2VKF). Ridgewood, N. J., & vic. (W2CGJ)*	162
Ridgewood, N. J., & vie. (W2CGJ)*	149
Roswell, N. M., & vie. (W5ZU)*	181
Rutherford, N. J. (W2DRA)	144
Rutland, Vt. (W1AVP)	106
St. Louis, Mo. (WØRCE)*	409
St. Paul & Ramsey Co., Minn. (WØHKF)	182
San Mateo Co., Calif. (W6QIE)	774
Sarasota Co., Fla. (W4LMT)*	51
Sauk Co., Wis. & Area (W9NLA)	86
Schenectady, N. Y. (W2GTC)	73
Sonoma Co., Calif. (W6LOU)	135
So. Pinellas Co., Fla. (W4HUY)	177
Southbridge Mass (W1EEC)	85
Southbridge, Mass. (W1EFC) So. Stanislaus & No. Merced Co., Calif. (W6FIP)	66
Spokane, Wash., & vic. (W7FQS)*	774
Springfield & Clark Co., Ohio (WSDCJ)	89
Springfield, Mo. & vie. (WØERF)*	176
Stark Co. Obio (WSAL)	112
Transport & Blazar Cla Work (W7MW3)8	247
Texas Co., Okla. (WSLWG	28
Tompkins Co., N. Y. (W2UYS)	67
Toronto & York Twp., Ont. (VE3IL)**	409
Trumbull, Conn. (W1JSC)	100
Trumbull Co., Ohio (W8ANN)	184
Trussville, Ala. (W4PPK)*	40
Tucson, Aris. (W7NYK)*	161
Tulm Co., Okia. (WSJBX)	165
Tuscarawas Co., Ohio (W8MEI)	54 57
Umetilla Co. Ore (W7RDN)	103
Umatilla Co., Ore. (W7BDN)	228
Wabash River Basin (W9TT)*	168
Waltham, Mass. (WiJSM)*	79
Washington Co., Okla. (W5CKT)	88
Wausau, Wis. (W9VHA)*	193
Wayne Co., Ind. (W9MUR)	73
Wayne Co., N. Y. (W2VEY)	53
Whittier, Calif. (W6BLY)	133
Wilkes-Lincoln-Taliafero, Ga. (W4PGV)	25
Will Co., III. (W9MTW)	207
Windham Co., Vt. (W1AZV)	36
Windoor Co., Vt. (W1ELJ)	100
Winnebago Co., Ill. (W9HOA)	108
Winthrop, Mass. (W1BB)*	213
Worcester, Mass. (W1SPF). Wyandotte & Johnson Co., Kans. (W#ZGK)	120 211
wyandowe & Johnson Co., Kam. (www.)	211
Grand total for nation	,515

Reported No Activity

12

Florence, Sheffield & Tuscumbia Co., Ala. (W4MEM) Beaver Dam, Wis. (W9APU) Kenilworth, N. J. (W2LSX) Lenox, Mass. (W1DPY) Millinocket, Me. (W1KEZ) Stearns Co., Minn. (WøBRA) Tualatin Valley, Ore. (W7FY) Van Wert Co., Ohio (W8CZR)

** Consolidated report of Toronto ECs VEBAZX, VEBAIB, VE3NG, VE3EAM and VE3RG.

SETICO



Mobile Antennas

For All Regular and Emergency Service

Car-top, Whip, Center-Loaded, Zone and Sector Civil Defense Control...a complete line for every purpose including Marine. Send for special bulletin.

PREMAX PRODUCTS DIVISION CHISHOLM-RYDER CO., INC.

5302 Highland Ave., Niagara Falls, N. Y.





GETS THROUGH LOUD AND CLEAR-

INCREASES RIG EFFICIENCY

phone Metching C-4 Stand

Turner 80 Crystal Micre-

Unit 61/2 inches high

TURNER 80

First Improvement in amateur microphones for years! You get excellent response to voice with the TURNER 80. Its response range is 80–7000 c.p.s.; level 58 db below 1 volt/dyne/sq. cm. High quality Bimorph moisture sealed crystal, mechanical and shock proofed. Stand and microphone solidly built of diecast zinc overlaid with satin chrome. 7 ft. attached cable. Stand has standard ¾"-27 thread, swings microphone in 135° arc. Compact, convenient unit gives increased efficiency to any amateur rig.

Model 80 Microphone. List Price......\$15.95
Model C-4 Stand. List Price......\$ 5.75

THE TURNER COMPANY

Microphones by TURNER

In Canada: Canadian Marconi Co., Toronto, Ont., and Branches Expert: Ad. Auriema, Inc., 89 Broad Street, New York 4







Communications Dept. Rules

(Continued from page 75)

degree of interest and activity in c.w. relay traffic work, nets and schedules; (b) demonstrate ability to transmit and receive at 15 w.p.m. or higher speeds; (e) follow standard message forms, ending signals, procedures and abbreviations coming under recommended ARRL operating practice and (d) follow exemplary technical and operating procedures such as tune-up using dummy antennas with major adjustment outside heavy operating hours.

The Official Phone Station (OPS) appointment shall be granted by SCMs on application to those members meeting the general appointment qualifications, who (a) display interest in major voice communications activities and agree to support section nets and schedules capable of relaying traffic or other practical communications; (b) utilize and follow message and procedure standards recommended by the League when so engaged; (c) employ circuit precautions avoiding overmodulation and frequency modulation on a.m. carriers, and transmitter indicators to detect maladjustments and (d) follow exemplary technical and operating procedures such as tune-up using dummy antennas with major adjustment outside heavy operating hours.

Official Bulletin Station (OBS) appointees shall be named by SCMs only in accordance with geographic needs for local coverage, preference being given stations having available considerable amounts of power, and preferably who can demonstrate ability to copy the Headquarters station in advance of receipt of mail information. Applicants must (a) guarantee a minimum of three scheduled transmissions per week; (b) adhere to schedules agreed upon with SCM and (c) return information on current or revised

schedules on periodic surveys.

Official Experimental Station (OES) appointees shall be appointed by SCMs from among those members active in developing successful communications systems and equipment applications and collecting propagation data in the v.h.f., u.h.f. and s.h.f. amateur bands. This appointment is to be available only to amateurs operating stations on one or more bands above 50 Mc. (a) Applicants shall indicate the problems and experimental projects in which they have continuing interest. (b) Appointees shall report monthly their contacts, observations and progress on the specific problems and communications justifying this type recognition. (c) Stabilized signals, non-radiating receivers and the like shall be used as appropriate to the frequency and mode of emission in accordance with the general progress of development in the designated bands.

Official Observers (OO) shall be appointed by SCMs to promote orderly operating and assist compliance with government regulatory provisions. Official observers will be appointed in the field organization to maintain an ARRL Cooperative Monitoring Service. Each Observer shall

(Continued on page 146)

WANTED

COMMUNICATIONS and RADAR PERSONNEL

WHO WANT TO EARN

7.000 Per Year, Or

BETTER

PHILCO TECHREP DIVISION

Offers Such Openings

... to men who are qualified by experience or training in the design, maintenance and instruction of Communications, Radar and Sonar Equipment.

FUTURE OPPORTUNITY AND JOB SECURITY

... are more than "sales talk" at Philco. Demands for our elec-ronics installation and service work throughout the entire world have been coming to us with increasing regularity since 1941. have been coming to us with a future with us.
This is YOUR best assurance of a future with us.

PLUS - OF COURSE

... the fact that in Civilian Radio and Television , PHILCO has led the industry for 20 years.

COMPENSATION IS TOPS!

Salary, bonus, subsistence up to \$6,500 stateside and \$7,500 foreign; PLUS, hospitalization, group insurance, profit sharing, retirement benefits, merit and faithful service solary increases and paid vacations.

TRAINING PROVIDED

Philico provides all necessary refresher courses and new courses, where required on new equipments, to insure your qualifications before assignment. Pay while training.

WRITE for complete details to

PHILCO TECHREP DIVISION

22ND & LEHIGH AVENUE

PHILADELPHIA 32, PA.

HAM COUNTERMAN ★

Ham wanted by large Northern New Jersey distributor to work as radio parts counterman. Large ham business. Excellent opportunity for right man. Inquiries held in strictest confidence.

Box 130, QST

"YOUR FRIENDLY SUPPLIER" Service to hams by hams. Nationally accepted brands of parts, tubes and equipment. Trade-ins and time payments. Write W1BFT. 10 HILLS AVENUE CONCORD, N. H.

ASY TO LEARN CODE

It is easy and pleasant to learn or increase speed the modern way — with an Instructograph Code Teacher. Excellent for the beginner or advanced student. A quick, practical and dependable method. Available tapes from beginner's alphabet to typical messages on aginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WFM. Always ready, no QRM, beats having someone eand to you.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of specessful operators have "nequired the code" with the Instructograph System. Write today for full particulars and convenient rental plans.

INSTRUCTOGRAPH COMPANY

4799 SHERIDAN ROAD, CHICAGO 49, ILLINOIS

- 4 E 2 - - \$8.75
- 8 E 2 - - \$20.50 2 MTR-TWO 4 ELEMENT
- PD 3 E10 - \$24.95 PLUMBER'S DELIGHT INCLUDES T MATCH 10 MTR-3 ELEMENT
- CLOSE SPACED • 3 E 10F ---- \$42.40 FOLDED DIPOLE 10 MTR-3 ELEMENT CLOSE SPACED
- 3 E 10T - - \$41.80 INCLUDES T MATCH 10 MTR-3 ELEMENT CLOSE SPACED
- 3 E 15T - - \$59.00 INCLUDES T MATCH 15 MTR-3 ELEMENT
- 2 E 20T - - \$47.95 INCLUDES T MATCH 20 MTR-2 ELEMENT
- 6 E 10-20T - 598.95 STACKED 10-20 3 FLEMENT

INCLUDES 2 T MATCHES Complete catalog on request; Dept . 4-43


HY-LITE

241 EAST 137th ST., N.Y. C. 51, N.Y.



NATIONAL

- · Proven
- Dependable
- · Quality

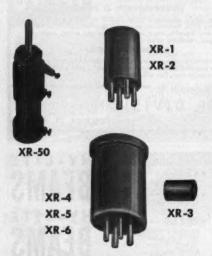

BAKELITE COIL FORMS

National mica-filled bakelite coil forms have been designed for the widest and most efficient electronic applications. They may be grooved, drilled and wound to meet any specifications. Available with 4 or 5 prongs or without prongs. XR-50 is permeability tuned coil form with iron slug. Write for drawings and specifications.



show continuing activity and send Cooperative Reports to stations heard radiating spurious emissions in violation of FCC regulations. A.c. notes, unstable signals, overmodulation, parasitics, harmonics, off-frequency signals, broadcasting and other abuses will be made the subject of report direct to the individual concerned. Observers will be classified by the SCM in accordance with demonstrated ability and interest as follows: I. Precise frequency checking (plus or minus 1 kc. at 14 Mc.). II. General frequency checking (plus or minus 5 kc. at 14 Mc.). III. Radiotelephone checks for modulation, stability, quality. IV. Radiotelegraph checks for notes, clicks, chirps and stability, and for radioteletype operation. Observers must possess equipment appropriate to the observing fields to be covered as pre-requisite to appointment. Class I and II Observers must measure within their prescribed limits of accuracy on two of four Frequency Measuring Tests run by ARRL each year to retain appointment. New Observers must pass such a test to qualify, all initial appointments otherwise to be made as Class III or IV. Observer appointments will be cancelled for inactivity of three months or more, subject to reinstatement for renewed and consistent activity. Monthly reports through SCMs are required.

16. Awards will be made and test or contest activities announced from time to time to extend encouragement to individual progress in operating procedures, in the accuracy and speed of making contacts and handling record communications and in furtherance of individual and group ability to render practical communications efficiently. Certifications or awards as recognition for progress and accomplishment in Amateur Radio will also be made under detailed provisions published in Operating an Amateur Radio Station or from time to time in QST. General operating procedures may be codified with consideration to the practice and suggestions from the field organization. The minimum procedures helpful to clear-cut and efficient operations will be recommended and set forth in Operating an Amateur Radio Station.

17. The League list of clubs or appointees must not be made available for commercial solicitation or advertising purposes. SCMs may make available such information to their sub-appointees as is desirable in effectuating amateur organization needs. On petition of an affiliated club or on request of the members signing petitions to nominate for ARRL office, such a list of section or division scope may be furnished.

18. These Rules and Regulations shall have the force and effect of By-Laws of the League. They may be amended as necessary from time to time by the Communications Manager, who shall cause more detailed provisions to be published as needed in the current edition of the League publication Operating an Amateur Radio Station. Amendments to the current edition shall be effective on publication in QST.

TRANSFORMERS



MILITARY COMPONENTS TO SPECIFICATIONS MIL-T-27 & ANE-19 AND COMMERCIAL TYPES

Pulse Transformers Filter Reactors Charging Reactors Saturable Reactors **Toroid Inductors** Low Pass Filters High Pass Filters **Band Pass Filters** Discriminators Plate Transformers **Power Transformers** **Filament Transformers Vibrator Transformers** Input Transformers Interstage Transformers Driver Transformers Output Transformers Modulation Transformers **Blocking Oscillator**

Transformers Band Elimination Filters

INSTRUMENTS



NO. 1020 B MEGOHMMETER DIRECT READING Self-centained and A.C. operated with electron-ically regulated sup-ply. 1 megohm to 2 million megohms.



NO. 1010 COMPARISON BRIDGE Self-contained and A.C. operated. For rapid and accurate test of Resisters, Condensors and Inductors.

OTHER FREED INSTRUMENTS

NO. 1030 Lew Frequency Q. Indicator NO. 1110A NO. 1170 D.C. Supply NO. 1210 Null Detector and Harmonic Distortion Meter Vacuum Tube Voltmeter | and . . . Decade Inductors

NO. 1140 Null Detector Amplifier NO. 1040 Incremental Inductance Bridge
NO. 1150 Universal Bridge
NO. 1250 Decade Condenser
NO. 1170 D.C. Supply
NO. 1410

SEND FOR COMPLETE CATALOG DESCRIBING ALL FREED INSTRUMENTS AND TRANSFORMERS

TRANSFORMER

1703 WEIRFIELD ST., BROOKLYN (RIDGEWOOD) 27, N. Y.

GET INTO ELECTRONICS

You can enter this uncrowded, interesting field, Defense expansion, new developments demand trained specialists. Study all phases radio & electronica theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required, Begin Jan., March, Jane, Sept. Campus life. Write for Catalog.

VALPARAISO TECHNICAL INSTITUTE Valparaiso, Ind.

STANDARD OF THE WORLD FOR QUALITY HEADSETS Personal Part of Any Communication System for a world of ... Wearing a light-weight TELEX head-set with no pres-sure on the ears and all background noise blocked out, you're all set for hours of traffic, DX or just plain chew-ing the rag. You'll never again wear an old fashioned headphone after.

"DYNASET

(dynamic) The modern styling, de-

YOU TELEGRAPH YOU NEED A BROPLEX

Semi-Automatic Key Suits

> any hand Choice of five models

Twice as EASY as hand sending

Saves the arm, gives a professional performance without arm-tiring effort. Simple to operate. Sults any hand or any style of sending. Vibropiex has a "touch" that lessens arm futigue and makes sending easier for you. Patented Jewel Movement balance lets you send SMOOTHLY! EASILY! NATURALLY! NO other key so easy on SMOOTHET EASILY: NATURALE IT TO GUER KEY SO case on the arm. Any old key won't do—get Vibroplex and be sure. Choice of five models, \$12.95 to \$29.95. Left-hand models, one dollar more. ORDER YOURS TODAY! At dealers or direct. FREE catalog.

Headquarters for NEW portables, all models and styles of type. Also, REBUILT standard and portable typewriters with ALL CAPITAL letters and other styles of type. Immediate delivery. Get our prices before you buy?

THE VIBROPLEX CO., INC.

New York 3, N. Y.



This lightweight 1.6 oz. TELEX Twinset pipes signal directly into the ear, blocking out background noises and banishing listening fatigue. Mag-

headsets. *Trade

For complete information on eny of the above headsets, write TELEX

ELECTRO-ACOUSTIC DIV. Department 16-4 . St. Paul 1, Minn. In Canada ATLAS RADIO CORP., Torente

"MONOSET

(magnetic)

The modern styling, de-pendability and superior performance of these under-chin TELEX headsets have made old fashioned headphones obsolete. With more highs and lows of both music and speech, they are the delight of radio and TV monitors.



an old fashioned headphone after you try one of the tatique-free, feath-erweight TELEX

HAM-ADS

(1) Advertising shall pertain to radio and shall be of nature of interest to radio amateurs or experimenters in their pursuit of the arc. character will be accepted, nor can any special typographical arrangement, such as all or part capital letters be used which would tend to make one advertisement stand out from the others.

(3) The Ham-Ad rate is 30¢ per word, except as noted in paragraph (6) below.

(4) Remittance in full must accompany copy. No cash or contract discount or agency commission will be accounted by the standard of the second month preceding publication date.

(5) Closing date for Ham-Ads is the 25th of the second month preceding publication date.

(6) A special rate of 7¢ per word will apply to advertising which, in our judgment, is obviously non-commercial in nature and is placed and signed by a member of the American Radio Relay League. Thus, advertising of bons fide surplus equipment owned, used and for sale by an individual or apparatus offered for exchange or of the American Radio Relay League take the 4f rate. An attempt to deal in apparatus in quantity for profit, even if by an individual, is commercial and all advertising by him takes the 30¢ rate. Provisions of paragraphs (1), (2) and (5), apply to all advertising in this column regardless of which rate may apply.

(7) Because error is more easily avoided, it is requested in the column regardless of which rate may apply.

(8) No advertiser may use more than 100 words in any one issue nor more than one ad in one issue.

Having made no investigation of the advertisers in the classified columns, the publishers of OST are unable to work for their integrity or for the grade or character of the products or services absertised.

QUARTZ — Direct importers from Brazil of best quality pure quartz suitable for making piezo-electric crystals. Diamond Drill Carbon Co., 719 World Bldg., New York City.

MOTOROLA used communication equipment bought and sold. WSBCO, Ralph Hicks, 204 E. Fairview, Tulsa, Otla. SUBSCRIPTIONS, Radio publications, Latest Call Books, \$3.00. Earl Mead, Huntley, Montana. WTLCM.

QSL's-SWL's Meade W#KXL, 1507 Central Avenue, Kansas City, Rans.

OSLS, SWLS, Samples, 106, C. Fritz, 1213 Briargate, Joliet, Ill.
OSLS: Fluorescent QSLs radiant and glowing with quality-control
OSLS Kromekote three colors and up. Rainbow maps. DX QSLS.
Samples raubed, 109, Uncle Fred. Box 86, Lynn. Pa.

QSL Samples 10 cents, Minner, WISQF Press, Candia, N. H.

WANTED: Cash or trade, fixed frequency receivers 28-42 Mc. W9YIY, Troy, Ill. OSIS, SWIS, High quality, Reasonable prices, Samples, Write to Bob Teachout, WIFSV, 40 Elm Street, Rutland, Vermont.

MANTED: Marconi multiple tuner, coherer, spark coil, magnetic detector, etc.; DeForest responder, coherer and other early equipment; Marconigraphe, Modern Electrics; Electrical Experiment and early Call Books and text books of wireless. Franklin Wingard, Rock Island, Illinois.

Rock Island, Illinois.

MICROWAVE test equipment wanted. Weston Laboratories Inc., of Weston 93, Massachusetts, will make you a high cash offer on any microwave test equipment, particularly such numbers as: TS-13, or was a such as the such as the

WANTED: BC610 or BC610 parts or components. State price and condition by letter, C. Porter, 8545 11th Ave., Silver Spring, Mary-

iand.

WANTED: Selsyns and syncros. Top dollar paid. Write full descriptions to: Box 84, Babson Park 87, Massachusetts.

WANTED: Nawy Selsyns, types 1DG, 1F, 16, 1CT, 5F, 56, 66, 76, etc. Autosyns: AV1, AV101D, AV201, etc. Tubes, test equipment, Signal Corps Equipment, Signal Corps Equipment, Send List. Top prices. Electro, 110 Pearl 84, Boston, Mass.

OSLS: Samples free. Big 18 page catalogue, 25¢. "Brownie," W3CJI, 3110 Lehigh, Allentown, Penna.

GONSET Triband Converter, new factory sealed cartons, guaranteed, Special, \$39.95, Variety Electric Co., Inc. 468-70 Broad St., Newark 2, N. J.

QSLS by Petty, W2HAZ, 17 Southard, Trenton, N. J. Samples, 10¢.

QSLS by Petty, W2HAZ, 17 Southard, Trenton, N. J. Samples, 104, WANTED: Electro Importing, DeForest, Marconi, Wireless Specialty Apparatus; QST, Wireless Age, Electrical Experimenter, Marconigraphs before 1920. Early catalogs, etc. Please describe Items in detail and give price wanted. Louis Risoli, W1AAT, 100 Bay View Ave., Salem, Mass.
CRYSTALS — Those hard-to-get spot amateur freqs. 1.8 to 7.4 Mc., \$2.50, Pennsylvania Crystal Co., R 2, Knox, Penns.
BEAT TVI, One 7" television receiver, \$35.00. One 10", \$50, Excellent as montor, other uses around shack. WAAPI, Spitz, 1420 South Randolph, Arlington, Virginia.
WANTED: BC448 receiver, State price and condition. Write to R. Wegelin, 410 Cedar Str., N.W., Washington, D. C.

QSLS? QSLS? America's finest and largest variety, super-gloss QSL samples, 25¢. Sakkers, W8DED, 53 East 7th St., Holland, Michigan. sampies, 25%. Sakkers, WDJED, 35 East 7(n St., Holiand, Michigan, SELLING out: Transmitter 500 watts (pair 4-125A), Meissner Delaue eignal shifter, Wilcox CW3 receiver, BC459A and power apply, BC454B, BC455B and power supply, Many other items. Send for list. Fred Graening, W9KHS, 444 St. Julian St., Pekin, Ili, FIRE extinguishers Underwritera sporoved, for ahack, 59,95 prepaid, Thompson, W3CQS, 735 Silver Spring, Silver Spring, Maryland, Free Folder.

DON'T faill Check yourself with a time-tested "Surecheck Test", similar to F.C.C. tests. Novice, \$1.50, General \$1.75, Amateur Extra, \$2.75. Your money back if not astisfied. Amateur Radio Supply, 1013 7th Ave., Worthington, Minn.

PRECISION-made, custom built antennas for all bands . . . literature available. Antenna, Incorporated, Wakefield, R. I. FREE list. Used Collins, Elmac, Hallicrafters, Hammarlund, Harvey-Wells, Lysco, National, RME, Sonar, etc. Lowest prices, Liberal trades. Dossett, W9BHV. 855 Burlington, Frankfort,

WANTED: ART-13 transmitter and parts. Write B. Spivey, 7013 Rolling Road, Chevy Chase, Md.

WANTED: RCH receivers, RBS receivers and SLR receivers, Navy type equipment. Also, 1-135 Test sets, Write immediately stating condition and best price in first letter, GME, Inc, 7315 Varna Ave., North Hollywood, Calli.

North Hollywood, Calif.

MOBILE Headquarters. All leading products including Elmac, Morrow, Gonset, RME, Mallard, Master Mount, Harvey-Wells, Sonar. New and used. Closing out superseded models. Outstanding trades and terms. Don't wait for Johnson Viking deliveries, We have huge atock and ready to do business immediately. Also complete stocks of Collins, National, Hallicrafters, RME equipment. Our trade-in department is builging with countless terms, large & small, read-on-trade-in department is builging with countless terms, large & small, and terms. Burghardt Radio Supply, Watertown, South Dakota. CRYSTAL nike, cable & switch, \$1.98; Diodes INA, en for \$5.98; power supply kit, 350 W VDC/60 Ma., transformer, tube, choke, condenser, \$3.99. Sell your surplus tubes, equipment. Free Tabogram. "TAB", 111 Liberty Sk., New York City, N. Y. SELL: Electro-Voice ancesh clipper Model 1000. slightly used.

SELL: Electro-Voice speech clipper Model 1000, slightly used, \$13.00. W#WUI, Box 171, Henderson, Minn. FOR Sale: PE103A's, \$20 each. Also have many ham items for sale or trade. W4VYN, 187 N. Lumpkin, Athens, Ga.

Octaine. Wav 11, 107 N. Junphan, Attens. Ca.

COLLINS Aircraft phone transmitter, like new condition with maintenance manual, uses 813 final, 811 modulators. 3105-6210 Kc 24 volt operation. Dynamotor mounted on transmitter chassis. Grant of the properties of the p

Bartiesville, Okia.

ATTENTION Hams! Beautiful closely woven cotton Throw Rug in pastel colors with your call letters hand-painted in large shaded letters. Rugs have beautiful fringe all way round, Fast dyes in the following colors: White, Green Spray, Grey Mist, Radiant Rose, Mimoax Yellow, We select colors for call letters to match. Sizes with the color of the colo

WANTED: Full KW final, modulator, and power supply. Complete or just the parts. Describe in detail with price. Your offer will be given every consideration. E. Johnson, W#PXH, 125 North Berry Road, Glendale 19, Mo.

Road, Glendale 19, Mo.

WANTED: Panoramic adaptor BC1031B or R.F. components and B.T.O. for same. Cash or trade. Wm. Alnick, W2Q1B, 128 Devon Terrace, Kearny, N. J.

WANTED: QST December 1915 thru February 1917 (except Oct. 16); October 1919, June and Aug., Oct. 1922. Trade or sell QST November 1920; April, May, June, July, November 1921; January, October 1926; also 1926 and 1927 complete, bound. Want also IRE Proceedings, Vol. 1 through IV, except Vol. I, No. 1 and Vol. III, No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April, May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Electronics for April May, June 1930; Bell Telephone System No. 4; Elec

Col. C. W. Janes, W48-S, C/O 186-SS, CHIRD DUPLON, CALL HAMMARLUND SP460X, looks like new, performs like new, includes matching speaker. Best offer over \$200.00 takes it. Brand new Millen 04060 transmitting conder, \$17.50; prewar DeLuxie Meissner Signal Shifter, \$25.00, W5MAM, Brieske, \$935 Southvie Ave., Houston 21, Texas.

Ave., routen 21, rexas.

2-METER mobile complete, less mike and antenna mount. Consists of RCA AVT-114 postwar aircraft VHF transmitter, 6, 12, 24 volts, 2 Gonset 2 meter converter, coar relay, Master coar antenna cycles. Crystala. Will mount under dash. \$120.00 or trade for receiver, Myers. WSQCP, 245 East Key Blvd., Oklahoma City 10, Okla.

w 3, Left, 23 Last Key Bivd., Uklahoma City 10, Okla.

OSLS two colors, \$7.00 a thousand, Samples, 10¢, VESJLG, G. LaFleur, 25 Queen Mary St., Ottawa 2, Canada.

FOR Sale: American components, 2, 100 amp. 110 volt transitadis,
\$75 each; 8, \$72 filament transformers, \$7.50 each, Oli filled choke
20HY, 5 amp. 15 Ky insulation, less oil, \$50,00. H. Clark, 299 NJ
RR Ave., Newark, N. J.

NR Ave., Newark, N. J.

YOUR Call Letters engraved in beautiful black plastic: white letters, Plexiglass base, Delivery about 6 weeks, only \$2.50. Cash, check, money order, Rocky Mountain Engraving Co., 3813 Calle Dell Monte, Albuquerque, N. Mex., W5THS, Larsen.

Monte, Albuquerque, N. Mex., W. F. Francis, Late and W. W. M. T. E. W. Mobile equipment, Gonset, and fixed station, Collins, in trade for Colt single action, Winchester Mod. 70, reloading tools, etc. W. E. Gallas, 533 Addison Rd., Riverside, Ill.

SALE: Jeanette rotary converter, 115 VDC 4.2 amps. Output 110 VAC 60 cycles 0.3 KVA. In excellent condition. \$35.00. W8JVJ, L. P. Atwell, 535 Capistrano, Toledo, Ohio.

SELL: Brand new (2-meter) 1-126/ARC-5 transmitter. Price \$40.00. Spencer Miller III, W1VNN, 259 Longmeadow St., Longmeadow, Mass.

BESTATE of W31BT: QST, 1929 to date. Type 81.3 tubes, \$6.00 each; LM frequency meter with calibration book, \$40.00. Dynamotors, tubes, meters, prop-pitch motors dural, aircraft receivers, transmitters, BC-459A, Wilcox Type F-3, many other items. List available, J. A. Guida, 2904 Newcastle Ave., Silver Spring, Md.

PERSONALIZED calling cards and stationery with your call letters. Free samples. Craftsman Printing, 8301 North 28th Avc., Omaha, Nebr.

FOR Sale: Complete 1000-1250-1500 .500 mill voit power supply, nothing else to buy, \$37.50. Wired and mounted. Also complete power supply 1700-2000-2300 voit 300 mill, mounted and wired, nothing else to buy, \$37.50. Power supply for Colline ART13. Complete, with power cable and plug, \$65.00, or will buy ART13. K. C. Horne, Steeville, Missouri.

WANTED: AN/APR-4, APR-5A, ARC-1, ARC-3, ART-13, etc.; TS-12 and other "TS-", particularly Microwave equipment, even salvage: VHF frequency meters and signal generators; quantities of 723A/B, 3C22, etc., tubes: any Laboratory equipment. Top cash or swap, rushi For sale: 304TL tubes, 4 for \$20.00; factory reconditioned glass Watthour meters, 4 for \$10.00, 446A tubes, 10 for \$15.00; X400 mercury flashlamp, trigger transformer, in case, \$7.50; Fl.-6A filters, \$6.00; Fl.-5F filters, 2 for \$6.00. Engineering Associates, 435 Patterson Road, Dayton 9, Ohio.

SELL: 120 W-10 thru 80 phone-CW xmittr. Integral Clapp VFO 829B final, Class B modulators, heavy duty power supplies, voltage regulated where required. Pi output. De-TVI'd through 20 meter No bugs. \$150.00 delivered within 250 miles. W#RAK/4, 500 James town Rd., Williamaburg, Va.

FOR SALE: National HRO 50TS speaker, National Select-O-Ject. SOJ-3, National HRO-50-XCU-2 calibrator 100/1000 Kc; National NFM adapter for HROS0, all for \$40.00. WIDBS John Savonis, 11 Dwight Court, New Britain, Conn.

Dwight Court, New Britain, Conn.

BARGAINS: Extra special: Motorola P-69-13. Mobile receivers, \$29-59. Globe King \$313.00; HT-9, \$199.00; HRO-50, \$275.00; Lyace 600 8109.00; HRO-78 1899.00; Collina 75.41 4275.00; HRO-57, \$175.00; SX-71, \$169.00; SX-42 \$189.00; SX-43 \$129.00; HRO-57, \$175.00; SX-71, \$169.00; SX-42 \$189.00; SX-43 \$129.00; HRO-Scenior \$119.50, RME 2-11 899.50; RME-45 \$99.00; Meisamet Ro-Schifter \$59.00; S-40A or SX-16, \$69.50. VHF-152, \$99.00; HRO-50, \$109.00; Globe Trotter \$69.50, Meis1 mobile transmitters, \$10-20, \$370.00; Globe Trotter \$69.50, Meis1 mobile transmitters, \$17.50, \$100.00; Globe Trotter \$69.50, Meis1 mobile transmitters, \$17.50, \$100.00; Globe Trotter \$69.50, Meis1 mobile transmitters, \$17.50, \$100.00; Globe Trotter \$69.50, XB-10, \$14.95; Gonset 10-11 converter \$17.50, \$100.00; Globe Trotter \$69.50, XB-10, \$14.95; Gonset 10-11 converter \$17.50, \$100.00; Globe Trotter \$69.50, XB-10, \$14.95; Gonset 10-11 converter \$17.50, \$100.00; Globe Trotter \$69.50, XB-10, \$14.95; Gonset 10-11 converter \$17.50, \$100.00; Globe Trotter \$69.50, XB-10, \$14.95; Gonset 10-11 converter \$17.50, \$100.00; Globe Trotter \$69.50, XB-10, \$14.95; Gonset 10-11 converter \$17.50, \$100.00; Globe Trotter \$69.50, XB-10, \$14.95; Gonset 10-11 converter \$17.50, \$100.00; Globe Trotter \$100.00; Globe

BARGAINS: New and reconditioned Collins, Hollicrafters, National, Hammariund, Johnson, Elmac, Harvey-Wells, Babcock, Gonset, Morrow, RME, Millen, Meissner, Lyzo, Workahop, Hylite, others. Reconditioned S77 569.00; S408, 879.00; S76, 8129.00; SX71, 8149.00; SW54, 815.00; NCS7, 869.00; HS 899.00; NC125, 8129.00; NC173, 8149.00; NC183, 8199.00; HF-10-20, 849.00; VHF152A, 859.00; Greet Tri-band, 829.00; Collins 32V1, 8375.00; HQ129X, SP400X, SX43, SX42, SX62, Collins 375A1, Collins 75A2, 3V2V, Viking 1, many others. Shipped on trial. Terms. Write for free list, Henry Radio, Butler, Mo.

GONSET Triband, excellent condition, like new, includes 15 meter band instructions, schematic, \$33.00. W6JOM, 715 Mira Mar, Long Beach, Calif.

250TL's. New pair, \$25.00 postpaid. W4SOR. SWAP Ohlsson "23" model engine for ham gear. Swap Q5'er and cash for 20-meter beam. W4QCW.

NEW VORK CITV and vicinity only, for sale: 2 mtr. T-23 VHF ARC-5 mnistr, \$25.00; Manter Mobile 2-mtr. coaxial dipole with 50 ft. coax, \$8.00; Ekidico grid dipore, \$18.00; Bc.453, \$15.00; Bc.455, \$7.00; beautiful 30-40 wat smittr in relay rack cabinet, AM phone, c.w. very stable VFO, final on 20 meters, can easily be put on 40. Completely TVI suppressed; low-pass filter, 3 meters, carcarley, etc., \$8.00; Ekidikori deli for i.F. alignment, band-edge marking, etc., \$8.00; Hi-fi F.M. tuner, amplifier, record-changer in beautiful modern cabinet, \$100.00, WZVT "Ernie" Palinkas, 335 E. 69th St., N. V. C. Phone Eves. TR 9-2120.

COMPLETE Motorola P69-18ARS receiver with noise clipper and Gonset Tri-band and FMT-30-DMS dual frequency FM-AM transmitter complete with all controls, cables, mike, genemotor, relays. Factory reconditioned and adjusted. BC-456E modulator. Carter Gene-motor (not surplus) 490 volts at 275 Ma, at 6.5 volt input (6 volt solenoid supplies). Gonset noise clipper. Best offer F.o.b. Wep17X, Robt. W. Shoemaker, I, Box 282, Anderson, Indiana.

BARGAIN: 125 watt xmitter 4-65A final, xtal mike, Budd VFO, 10-80, coils. \$125.00 F.o.b. No time for hamming. Dr. A. R. Watson, 1306 S. 27th St., Temple, Texas.

WANTED: AN/ARC-1 or AN/ARC-3 or components. Write to J. Durrant, 5526 Parkland Court, Apt. 202, Washington, D. C.

WILL pay cash for used receiver. Box 4, Kearney, Nebraska. WANTED: Collins 310 B-1 exciter, also for sale new, PE-103, \$30.00 F.o.b. W4GJS, Box 132, Goldsboro, N. C.

SELL: SCR-\$22, transmitter unmodified, receiver converted to tunable oscillator for two meters, \$27.50; BC-457 and BC-458 transmitters on dual rack, \$12.59; Electronics L450 rators power pack, output 12 outs DC, 10 amp, \$22.50. WSILJ, John A. Miller, Hebron Road, Route 5, Newark, Ohio.

TRADE: Omega enlarger 2½" x 2½" with 4.5-75mm Kodak lens. Interested in communication receiver. Philadelphia or vicinity preferred. J. Hudson, W3TMJ, 156 S. Easton Road, Glenside, Penns.

FOR Sale: Arc-4, tubes and dynamotor, \$30.00; BC-455-A 40 mtr reve, 113V power supply, \$22.50; BD-77-L dynamotor, cables, relays, filter, \$25.00; Broadcast band auto revy, mounts under dash, one piece unit luchudes spkr and vibrator, new, \$30.00. Walt McCoy, WgLZI, 433 Steephens, Wichita, Kansen,

FOR Sale! 32V-3, \$700; 75A-2, \$400. Both brand new. Or will trade either for clean 32V-1 and cash. Capt. James Craig, W5VRO/6, Box 6119, Mather A.F.B., California.

NC-183D receiver, new, less speaker: \$270 cash, Only one, W5WTV, Box 1054, NSC, Natchitoches, La.

V.F.O. Sonar C.F.C., \$29.50. Make good Novice transmitter and use in rig later when get General license. W5ALA, 4531 Fairway, Dallas 19, Texas.

SELL: BC-1006 Super-Pro, 550 kc. to 20 mc. In desk cabinet. Excellent shape, with power supply, \$175.00. Bill Orr, W6SAI, 555 Crestline Drive, Los Angeles 49, Calif.

FOR Sale: Complete station, includes HRO STAI rcvr, all band 390 watt phone, 750 watt c.w., TVI-suppressed transmitter, Melsauer VFO, dual beam antenna 3-element 10, 2 element 20 with commercial indicator and rotator, \$550. Photo on request. Al W. Speyers, W2C2A, 9 Lowell Avc., Summit, N. J.

SELL: National 240-D, rack-mounted, \$140. HT-18, \$65.00. Excellent condition. Al Raper, 3387 West 76, Denver, Colorado.

QSLS! Interesting samples, 10¢, Tooker Press, P.O. Box T, Lake-hurst, New Jersey.

10, 15 and 20 meter beams, aluminum tubing, etc. Perforated aluminum sheet for shielding. Radcliff's, 1720 No. Countyline St., Fostoria Ohio.

QSL samples. Dime, refunded. Roy Gale, W1BD, Waterford, Con SELSYNS or synchros wanted: Navy or Army ordnance 60 cycle types. Will pay \$15.00 each for IDG, IDF, ICT, IG, IF; \$25.00 each for IDG, GC, GC, GC, GDG, or sizes 7. Subject to inspection. Other types advise. Also want: Autosyns, Servo Control motors, PM motors, inverters, tubes and other electronic components. Electro Sales Co., Inc. 58 Eastern Ave., Dept. Q, Boston 13, Mass.

HAMFEST June 7, 1953. Come to Camp Ki-Shau-Wau where the Starved Rock Radio Club will again hold their annual Hamfest. Games, contests and entertainment for all. Awards for Novice-built equipment. Ham trading post and other features, including free coffee and doughnuts at 10 AM. Follow the Hamfest signs south from Junction of Illinois Routes 178 and 71 near Starved Rock State Park, or East on blacktop road from Route 51 at Tonica, Illinois. Registration, One Dollar prior to May 25th; One-fifty at the Hamfest. For additional information, write W9MKS, Starved Rock Radio Club, Inc., Box 22-A, Utica, Illinois.

FOR Sale: Type 90600, Complete set 3Mc to 140 Mc Millen absorp-tion frequency meters in wood case, like new, \$15.00, W8VLB, Glenn F. Markley.

SELL: Precision signal generator, #E-400, new, \$85.00, f21A teletype midget printer, \$50. Fieletype tape transmitter, \$35.00; #12 teletype per per transmitter, \$35.00; #12 teletype page printer, receiving distributor, polar relay, table, \$125. Want: ART-13, DY-12, GN-58, APR-4, Tom Howard, W1AFN, Box 19, Boston 1, Mass. Richmond 2-49816

EARLY OSTs, in good condition, unbound. 25 copies 1916-1921; complete, March 1922-December 1927, \$175.00 takes all 95 copies, plus two 1928s. Fred Dye, 210 Murphy Building, Detroit, Michigan.

COLLINS 10 meter mobile power supply, Gonset 10-11 converter and noise clipper, complete, except antenna, \$80.00 F.o.b, Orville Braaten, W@NYI, 1131 Park Avenue, Morris, Minn.

SELL: 300w modulator with power supply, tubes, meters; 60w modulator with 125w modulation transformer, speech amplifier, tubes; 150w transmitter with low voltage power supply, tubes. R. H. Beers, 33 Sterling Drive, Livingston, N. J.

FOR Sale: SP-400-SX Super Pro in excellent condition, to the highest bidder. J. A. Hagen, 1315 South 29th St., Birmingham, Ala.

FOR Sale: Collins 75A-1, less speaker. Antenna trimmer added and revised as per W6SAi article. Recently aligned. \$250.00. Gordon Nordstrom, W9ICQ, 1651-11th St., N.W., Cedar Rapids, Iowa.

SELL: HQ-120X for rack mounting, excellent, \$75.00, W4HLO.

FOR Sale: Three Motorola mobile transmitters, Model 69-20A, one Harvey all complete with cables, control box, Tri-band converter. J. R. Lorraine, Chatham, Mass.

JOHNSON Viking II trans., \$270.00, Used 2 months, Also SX-25, Make me an offer, W8HCC, 628 Jackson St., Sandusky, Ohio.

BC-522A, new, never in a/c, wth TM meter; BC-1303 control unit, transmitter original, receiver tuneable, three crystals, a/c power supply, all \$125.00, J36 bitopolex new, \$10.00; Model \$256 Triplett frequency meter, perfect. \$12.00; Alliance Tenna-Rotor, new, original carton, dfr., \$20.00. WoN]F, Box 1265, Sacramento, Calli.

FOR Sale: Navy ATD aircraft transmitter complete, \$50.00. Chicago-Webster wire recorder, Model 78-1, wire-mite, etc. complete, \$3.00.0 Gonset 14 mc. mobile converter \$10, Kaar 1700 kc. mobile receiver with noise clipper, \$15. W. C. Plumb, 22 Winding Way, Morris Plains, N. J.

SELL: RME-45 with speaker, \$70.00; Hickok Model 177X signal generator, \$35.00; BC453, \$10.00; BC454, \$5.00; BC453, \$5.00 Bruce Wood, 16 Bradley St., Warren, Penna.

FOR Sale: Harvey-Wella TBS50D transmitter with APS50 power supply, \$13,0.00; Gonset Tri-band converter, \$30,000; Gonset noise clipper, \$3,0.00; Master Mobile Mounts and center loaded antenna, \$10,000; FE103A converter, base and cables, \$23,00; Astatic dynamic pair of 304TLS final, \$400,00 (parts alone worth \$700,00). No shipping, Send 25¢ for pictures and data. Small stable VFO and voltage regulated power supply, 5 watts 80 and 40, National ACN dial, \$25,00. Consider Viking II transmitter and VFO in trade. C. W. Cook WSMB BE, En. ineer, City Hall, Alexandria, Louisiana.

SURPLUS Miesaner 150-B xmtr, 813, 811 s mod. 250 w. unmodified, excellent, \$240.00; HRO-507, 7 colis, xtal calib., speaker, excellent, \$270.00; two 5G selyans, \$25,00; Triplett 666-H multimeter, \$10; rack dolly, \$5.00; two 50-HLa, \$5.00 ea, GL-64: \$20.00; AVA-126-A Vibrator power supply, new, \$25.00; Collins TCS, misc. perts. W20VY, Vadney, 1853-8th Ave., Watervilet, New York.

WANTED: R9er, 10 and 20 colls, reasonable, OK. Sell or trade for Alliance HIR Tennarotor, new Magalip (selsyn) precision xmitter, receiver, pair DPDT AC relays. J. P. Neil, 1567 College Ave., Paio Alto, Callf.

PE-103: Have two to sell. Used and with 5-prong power plug, \$33.00. Braud new, \$38.00. Both have bases and battery cables. W2RUK, Socci, 3½ Hulbert St., Auburn, N, Y.

Designed for Application



The No. 90281 **High Voltage Power Supply**

The No. 90281 high veitage power supply has a d.c. autput of 700 volts, with maximum current of 250 ms. In addition, AC filament power of 6.3 volts at 4 emperes is also available so that this power supply is an ideal unit for use with trensmitters, such as the Millen No. 90800, as well as general laboratory purposes.

The power supply uses two No. 816 rectifers and has a two section z filter with 10 henry General Electric chakes and a 2-2-10 and d. bank of 1000 volt General Electric Pyramol capacitors. The power is supplied to the property of the power is supplied to the section of the power is supplied to the power is power in the power is supplied to the power is power in the power in the power is power in the power in the power is the power in the power is the power in the power in the power is the power in the power is the power in the power in the power is the power in the power in the power is the power in the power in the power in the power is the power in the power in the power is the power in the power in the power is a power in the power in the power in the power is a power in the power in the power in the power is a power in the pow

JAMES MILLEN MFG. CO., INC.

MAIN OFFICE AND FACTORY MALDEN MASSACHUSETTS



Index of Advertisers

X

13

15

Akers Co., Dallas C. 118 Allied Radio Corporation. 117 American Lava Corporation. 101 American Radio Relay League, Inc.
Group Offer 137 QST 152 Ashe Radio Co., Waiter 133
Babcock Radio Engineering, Iuc. 111
Candler System Company 116 Centralab 151 Central Electronics, Inc. 124 C & G Radio Supply Co. 142 Chicago Transformer Company 92 Collins Radio Company 2 Concord Radio 110 Delco-Remy Division 88,89
Delco-Remy Division 88, 89 Dow-Key Company, Inc. 128 DX Radio Products 102
E/tel-McCullough, Inc. 93, 118 E/dico of New York, Inc. 86, 87 Engineering Associates. 139 Evans Radio. 145
Ft. Orange Radio Distributing Co
Gardiner & Company 126 General Electric Company 1 Gonget Company, The 142, 144 Gottam Hobby Co. 134, 140 Grayhill. 100
Hallicrafters Co.
Instructograph Company
Johnson Company, E. F
Lafayette Radio. 125 Lampkin Laboratories, Inc. 122 Lettine Radio Manufacturing Co. 130 Lysco Manufacturing Co. 140
Mallory & Co., P. R 95 Mass, Radio & Telegraph School 126 Merit Transformer Company 114 Midland Manufacturing Co., Inc. 103 Millen Manufacturing Co., Inc., The Jas. 150 Motorols, Inc. 132
National Co. Inc
Penta Laboratories, Inc. 126 Petersen Radio Company 7 Phico (TechRep Div.) 145 Ploneer Tool Company 130 Port Arthur College 124 Precision Apparatus Company 98 Premax Products Company 143
Radio Corporation of America Cov. IV Radio Shack Corporation, The 131 Raytheon Manufacturing Co. 100 RCA Institutes, Inc. 139 Rider Publisher, Inc., John F. 139
Sonar Radio Corporation 107 Steinberg's, Inc. 123 Sun Parta Distributors 136 Sylvan Electronics Laboratories, Inc. 134
Telex, Inc. 147 Tele-Vue Towers, Inc. 136 Turner Company, The. 143
U.H.F. Resonator Company
Valparaiso Technical Institute 147 Variety Electric Company 122 Vesto Co., Inc. 105 Vibroplex Co., The 147
Valparaiso Technical Institute. 147 Variety Electric Company. 122 Vesto Co., Inc. 105 Vibropies Co., The. 147 Weston Laboratories, Inc. 120 Wind Turbine Company. 128 World Radio Laboratories, Inc. 127

Look! New small size Adashaft Radiohms!



See your Centralab distributor for these new guaranteed controls that are right for your rig

N OW — you can select the new Centralab "Adashafts" from a completely new line, All new Adashafts are in the popular new smaller size — 15½e" in diameter. What is more, you will find there are 43 additional values never before included in the line. Yes, and there are 10 new dual-tap models.

If you want to keep up-to-the-minute and build better rigs, Centralab's new, smaller Adashafts are the answer. Their patented design allows you to easily attach any of nine types of shafts to a basic control. The control unit has a patented stub shaft which permits instant, positive locking. You get a solid, well aligned unit every time.

Shafts range from \(\frac{4}{n} \) to 10" in length, and include auto types, insulating nylon and many others. In addition, you can convert these units to a switch type by using the new Centralab "Fastatch" type KB line switches.

Make your Centralab Distributor headquarters for exact electronic replacement

Centralab

A Division of Globe-Union inc. • Milwaukee 1, Wis. In Canada, 635 Queen Street East, Torente, Ontario

Centralab Adashaft Radiohms are among the more than 470 new items listed in Centralab's new Catalog No. 28. Get your copy of this new 32-page index to the latest developments in the fastchanging electronic field. See your distributor, or use the coupon.



CENTRALAB, A Division of Globe-Union Inc. 912D E Keefe Ave., Milwaukee 1, Wisconsin

Please send me my copy of the new Centralab Catalog 28 at once and without charge,

Name Position Positio

In Case You Don't Happen to Know



(Somewhat Enlarged)

... this is a "Twig Pruner"

An interesting looking insect, it performs one of Nature's important tasks in our forests: removing healthsapping twigs and other undesirable side growths from flourishing, developing trees.

Its job is to keep you up-to-date on all phases of the flourishing, developing art of amateur radio, but not to use valuable space in your magazine for articles and stories about the side growths.

QST's technical articles are accurate, its how-to-build-it directions are dependable, its operating news is the latest. Whether Novice or Old Timer you'll find something of interest in each copy of QST. CW and phone, automatic keying and SSB, contests and awards, DX and rag-chewing, 160 meters and VHF, TVI prescriptions and antenna designs, the manufacturers' newest equipment and the latest news from FCC, high-powered home stations and compact mobile rigs: all are covered.

J f you're in the U.S.A., \$4 buys you membership in ARRL for a year and brings *QST* to your mailbox once a month for twelve months; \$4.25 in Canada and \$5 elsewhere.

YOU'LL NEVER FIND A BETTER USE FOR YOUR MONEY!

The AMERICAN RADIO RELAY LEAGUE. Inc. West Hartford 7, CONN.



IN THE ROYALTY OF RADIO The HRO Jixty IS THE KING OF RECEIVERS





\$483.50" (less speaker) SLIGHTLY LESS THAN THE CROWN JEWELS!

National Company, Inc., Malden, Massachusetts

("slightly higher West of the Rockies.)

30 th edition • 1953

The radio amateur's handbook

THE STANDARD MANUAL OF AMATEUR

100% Beam Power

In the High-Frequency and VHF Transmitter chapters of the new 1953 Radio Amateur's Handbook, all of the 30 transmitting type tubes illustrated in rf applications are beam power types.

Why beam power?

Beam power tubes . . . an original RCA development . . . offer better results with fewer stages, tubes, and components. Beam power tubes require less driving power—enable you to work exciter circuits at lower power levels (a big step forward in TVI reduction). Beam power tubes have higher perveance—make it possible to get high plate input with lower plate voltage.

Take advantage of the features of beam power tubes when you design that new transmitter. Your RCA Tube Distributor carries a complete line of RCA Beam Power Tubes in stock.





RADIO CORPORATION OF AMERICA
ELECTRON TUBES HARRISON, N. J.